

# Laboratory 2

(Due date: October 11<sup>h</sup>)

## OBJECTIVES


- ✓ Design of a dedicated circuitry for trigonometric functions (CORDIC) in fixed-point arithmetic: FSM + Datapath
- ✓ Test of the CORDIC circuit using fixed-point inputs/outputs.

## VHDL CODING


- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a tutorial and a list of examples.
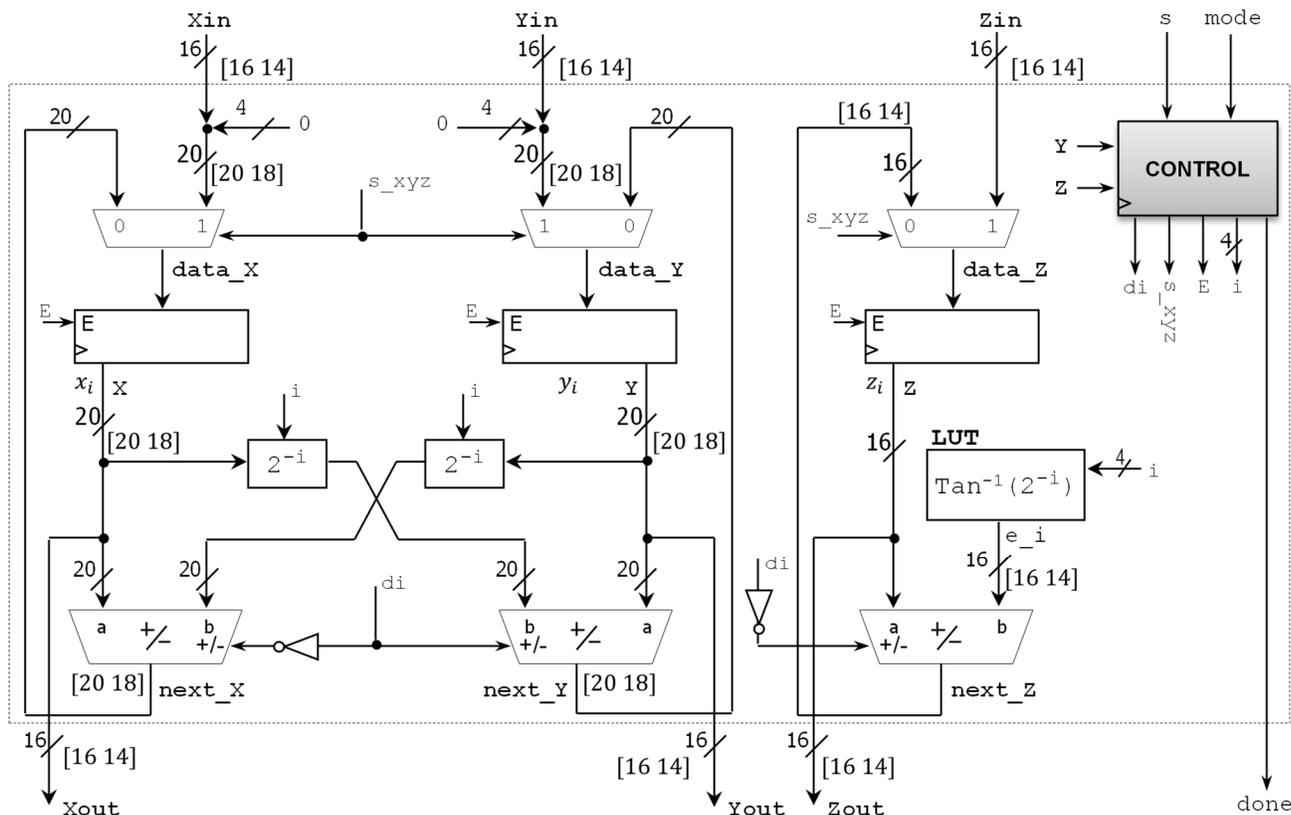
## FIRST ACTIVITY (100/100)

- Design the iterative Expanded Circular CORDIC FX architecture for  $i = 0, 0, 0, 1, 2, 3, \dots, 15$ .  $x_0, y_0, z_0$ : initial conditions.  $mode = '0' \rightarrow$  Rotation Mode.  $mode = '1' \rightarrow$  Vectoring Mode. Iteration  $i = 0$  is repeated two extra times in order to achieve convergence over the entire domain of  $\sin(x)$  and  $\cos(x)$ . This affects the value of  $A_n$ .  
MATLAB scripts (`cordic_circular_esp.m`, `testcordicesp.m`): They implement the expanded circular CORDIC algorithm.
- **Operation:** When  $s = 1$ ,  $x_{in}, y_{in}, z_{in}$ , and  $mode$  are captured. Data will then be processed iteratively. When data is ready ( $done = '1'$ ), output results appear in  $x_{out}, y_{out}, z_{out}$ .
- **Input/Intermediate/Output FX Format (signed):**
  - ✓ Input values:  $x_{in}, y_{in}, z_{in}$ : [16 14]. Output values:  $x_{out}, y_{out}, z_{out}$ : [16 14]
  - ✓ Intermediate values:  $z_i$ : [16 14].  $x_i, y_i$ : [20 18]. Here, we use 4 extra bits (add four 0's to the LSB) for extra precision.
  - ✓ We restrict the inputs  $x_0 = x_{in}, y_0 = y_{in}$  to  $[-1, 1)$ . Then, CORDIC operations need up to 2 integer bits (determined via MATLAB simulation). For consistency, we use 2 integer bits for all input/intermediate/output data.
- **Angles:** They are represented in the format [16 14]. Unit: radians.
- **Barrel shifters:** Use the VHDL code `mybarrelshifter.vhd` with `mode="ARITHMETIC"` (signed data), `N=20, SW=4, dir='1'`.
- Simulate it for the following cases. For each case verify that  $x_{16}, y_{16}, z_{16}$  reach the proper values.
  - ✓ Rotation Mode:  $x_0 = 0, y_0 = 1/A_n, z_0 = -\pi/2$ .
  - ✓ Rotation Mode:  $x_0 = 0, y_0 = 1/A_n, z_0 = -5\pi/8$ .
  - ✓ Rotation Mode:  $x_0 = 0, y_0 = 1/A_n, z_0 = -\pi/6$ .
  - ✓ Vectoring Mode:  $x_0 = y_0 = 0.3, z_0 = 0$
  - ✓ Vectoring Mode:  $x_0 = 0.1, y_0 = -0.3, z_0 = 0$
  - ✓ Vectoring Mode:  $x_0 = 0.3, y_0 = -0.1, z_0 = 0$



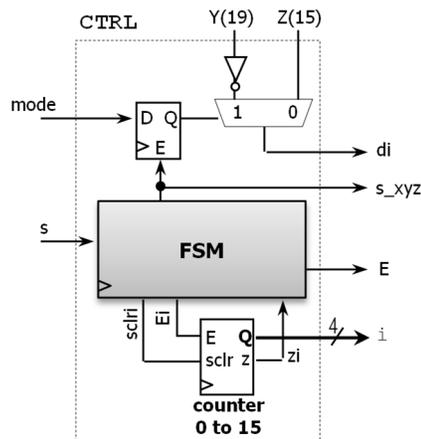- **Control:** This circuit controls the iteration index  $i$ , as well as the internal signals. The figure below is a suggested implementation.  
**FSM:** You need to design and implement a State Machine that controls the iteration index  $i$ , as well as the internal signals.



**XILINX ZYNQ SOC DESIGN FLOW:**

- ✓ Create a new Vivado Project. Select the **ZYNQ XC7Z010-1CLG400C** device.
  - ✓ Using the structural coding approach in VHDL: Instantiate the barrel shifter, multiplexors, LUT, FSM, and adder/subtractors into a top file. Synthesize your circuit (Run Synthesis).
  - ✓ Write the VHDL testbench to properly test the circuit.
  - ✓ Perform Functional Simulation (Run Simulation → Run Behavioral Simulation). **Demonstrate this to your instructor.**
- Submit (as a .zip file) the generated files: VHDL code, and VHDL testbench to Moodle (an assignment will be created). DO NOT submit the whole Vivado Project.

Instructor signature: \_\_\_\_\_

Date: \_\_\_\_\_