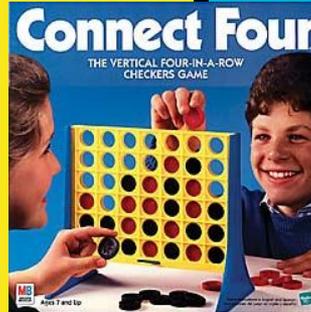


Connect Four


**Kyle Johannes
Diana Szeto
James Vankoevinger
Kevin Weinert**




**ECE 378 Winter 2016
Final Project
Instructor: Daniel Llamocca**

Gameplay

- Connect Four is a classic two-player game.
- The game board has 7 columns and 6 rows, allowing for 42 possible chip slot locations.
- Each player chooses one of two chip colors.
 - In our design, Player 1 is red while Player 2 is black.
- The players take turns dropping one chip into a column at a time.
- The objective of the game is to connect four of your own chips in a row before your opponent.
- The winning four-in-a-row can be vertical, horizontal, or diagonal.
- When a player wins, the board is cleared before beginning the next round.


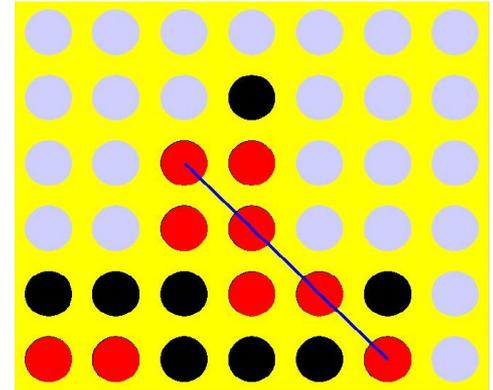


Top Level Design

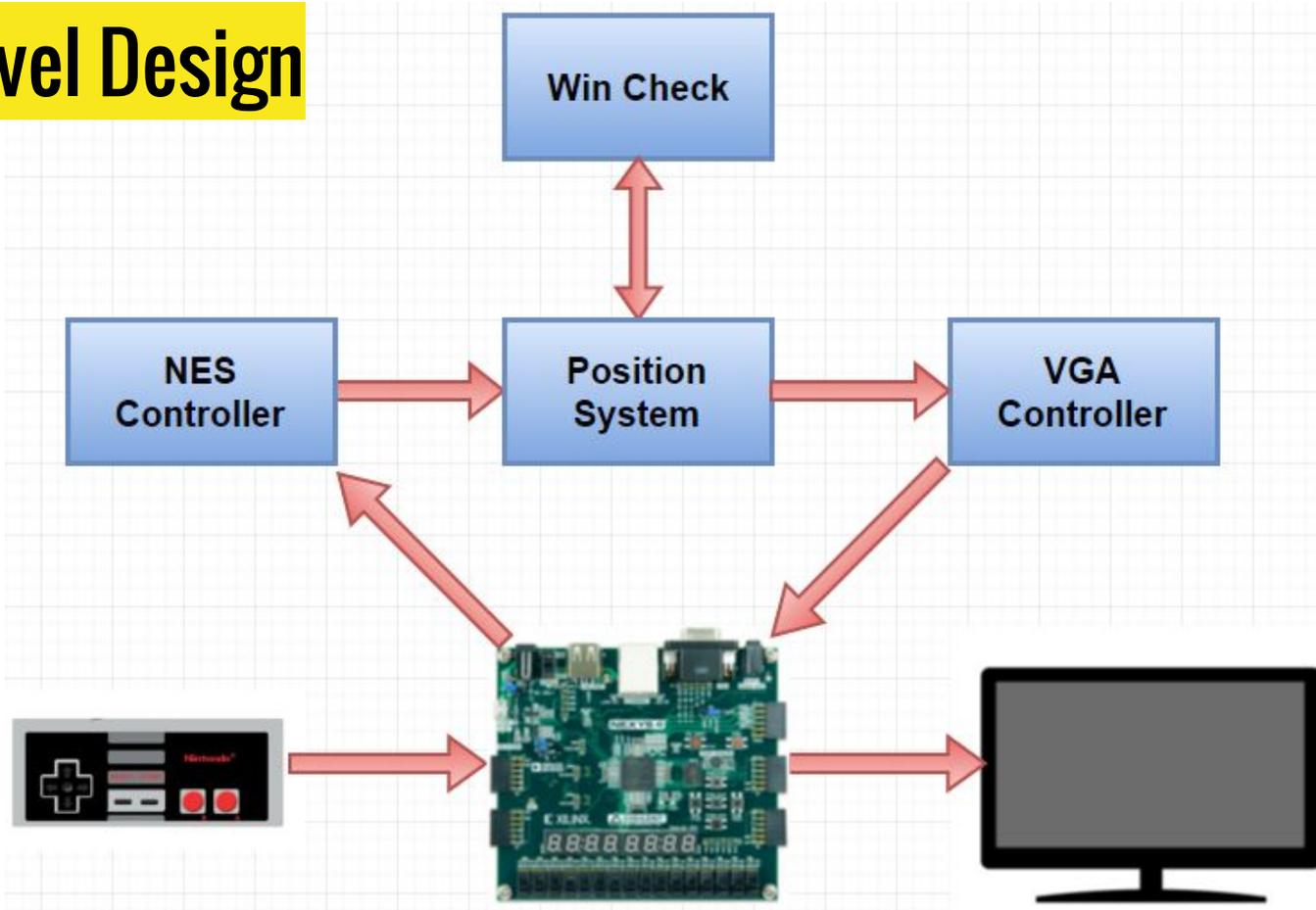

Position System


SN

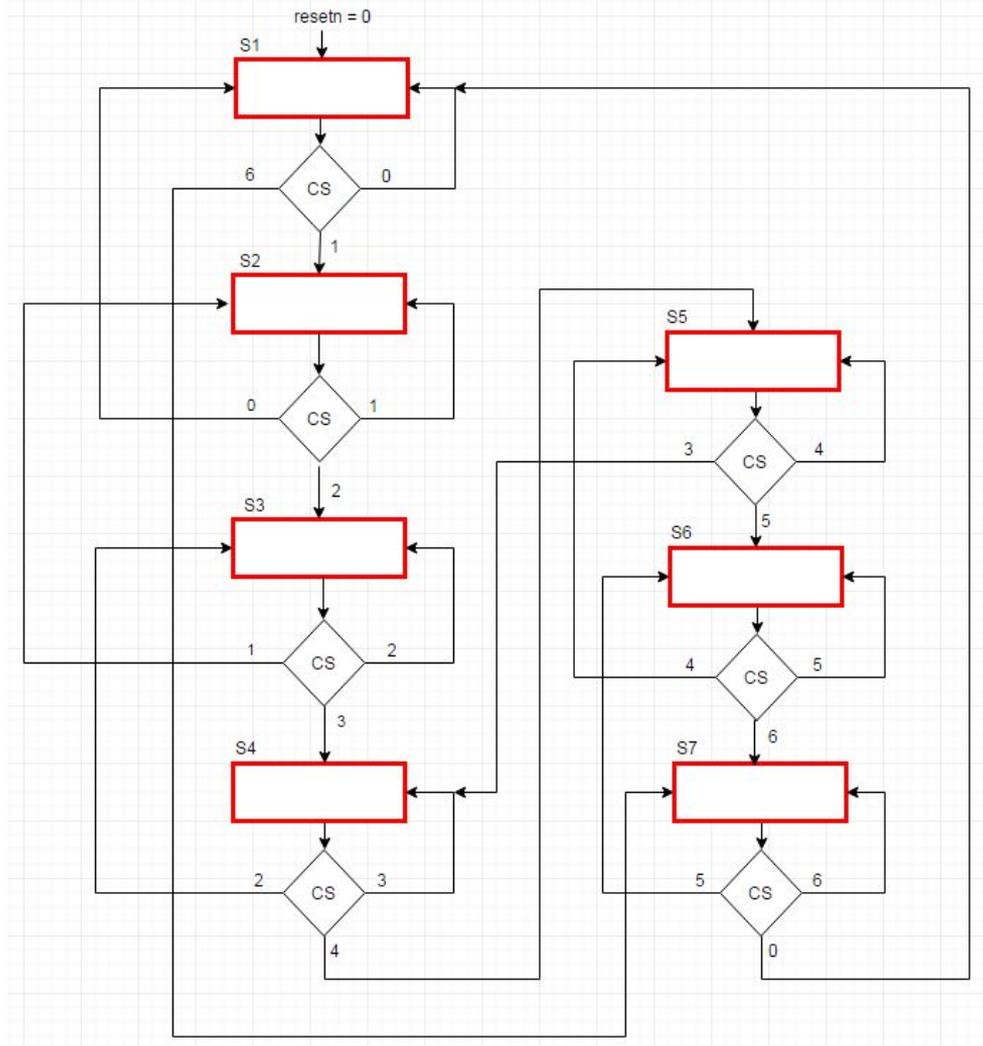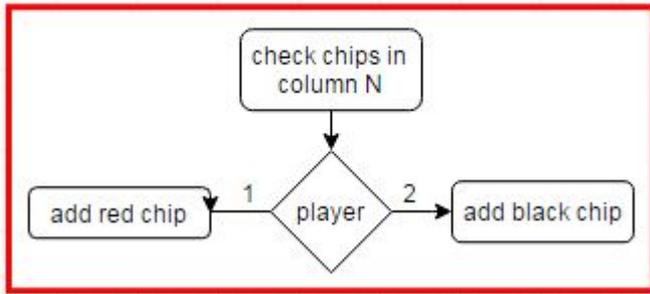



Win Check

- The Win Check system is made of three main components.
- `fullCheck.vhd` checks if four adjacent slots in the board are occupied. Outputs a signal that specifies which combinations of four adjacent slots are occupied.
- `gridCheck.vhd` checks if any four adjacent slots in the board are occupied by the same player's chip. Uses `singleCheck.vhd` to accomplish this. Takes input from the `fullCheck.vhd` as an enable for the `singleCheck.vhd`. Outputs a win signal if a player has won, by combining win signals from `singleCheck.vhd` components.
- `singleCheck.vhd` checks if the four specified input chips are of the same color. Enabled if four adjacent slots are occupied, the chips in those slots are input. Outputs a win signal if the four chips are the same color.


Win Check

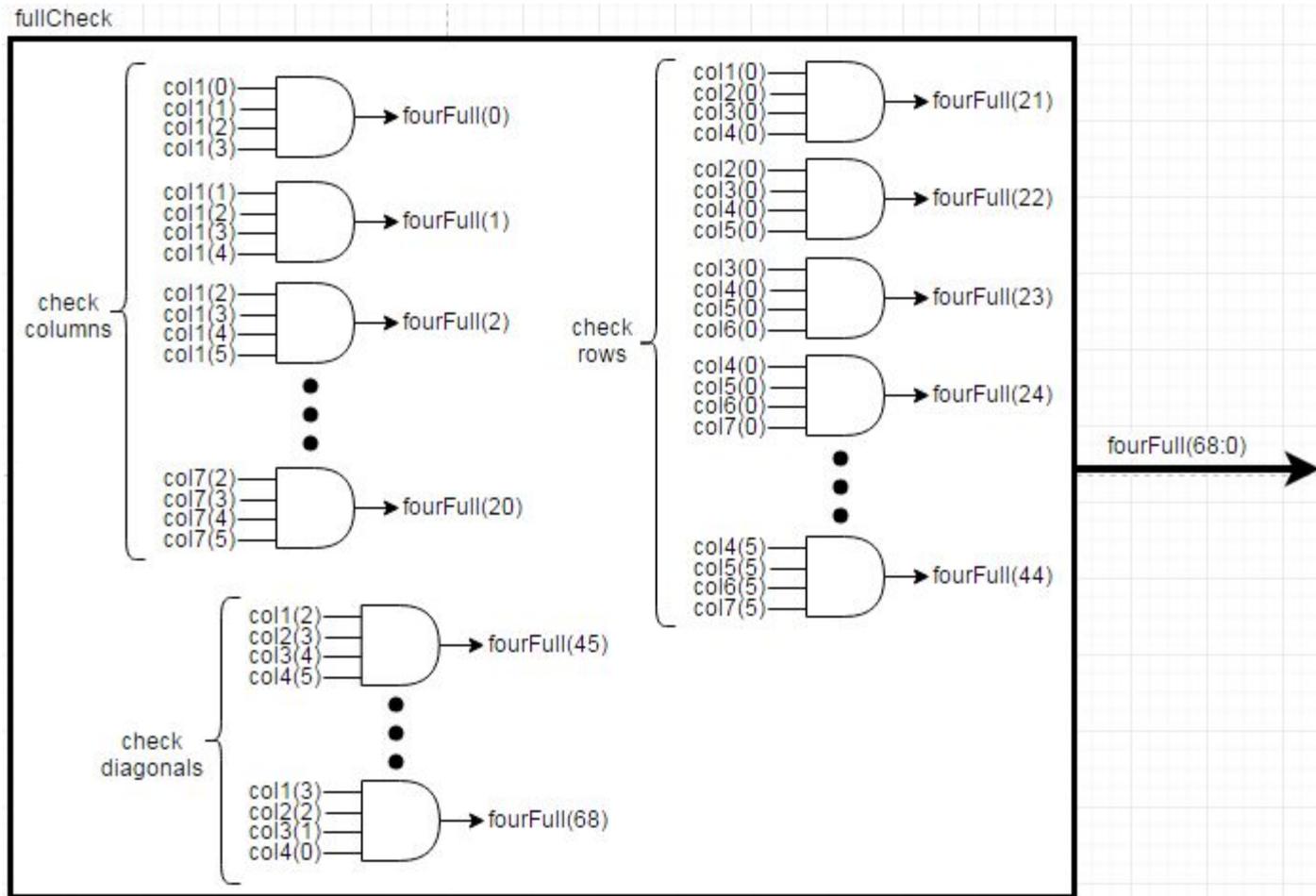

Win Check

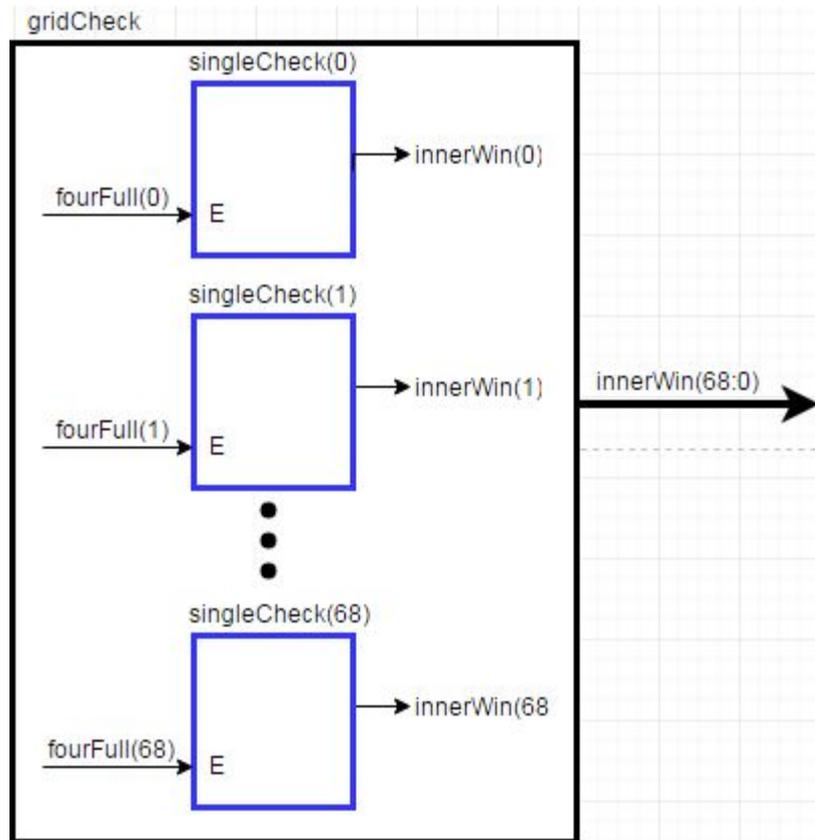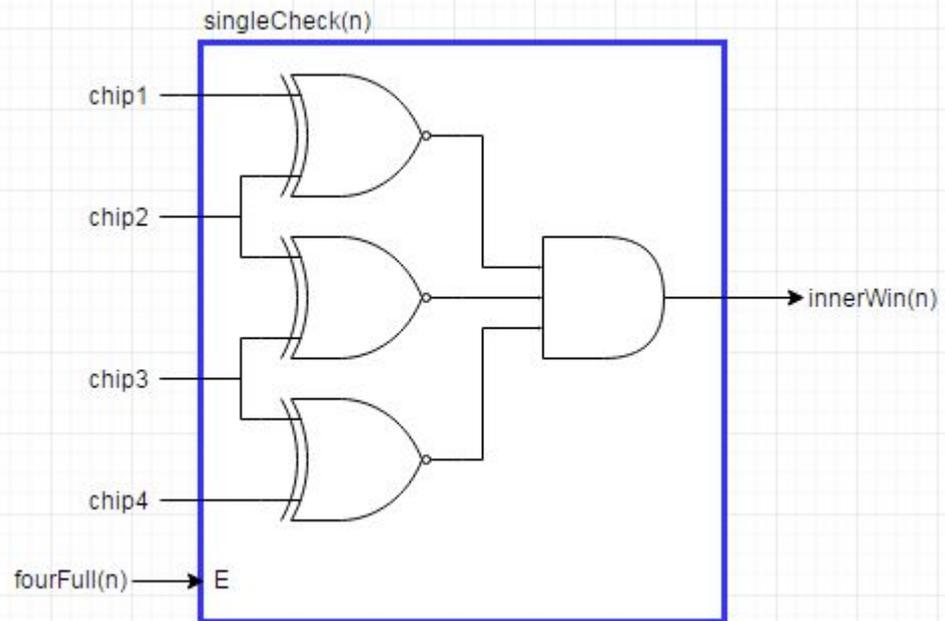

Win Check

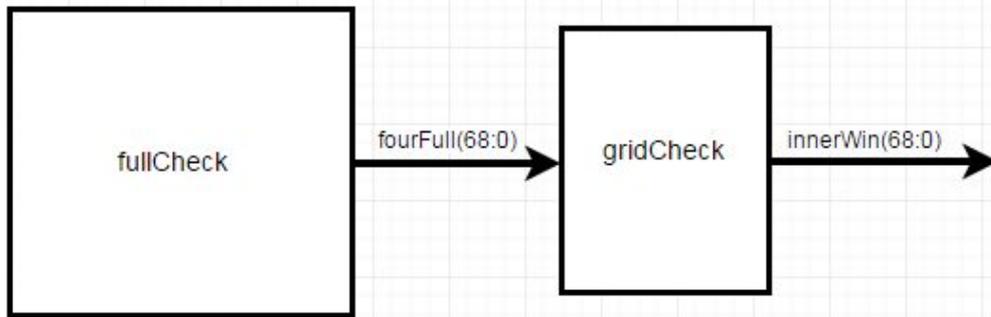

```
Check: process (clk, resetn, innerWin)
begin
  if resetn = '0' then win <= '0';
  elsif (clk'event and clk = '1') then
    if innerWin /= conv_std_logic_vector(0, 69) then
      win <= '1';
    else
      win <= '0';
    end if;
  end if;
end process;
```

NES Controller


Hardware:

CD4021 parallel to serial shift register

- buttons are pull-downs, register reads button state on latch
- shifts data out serially

3 data lines: latch, clock, and data out

- Latch loads parallel data in

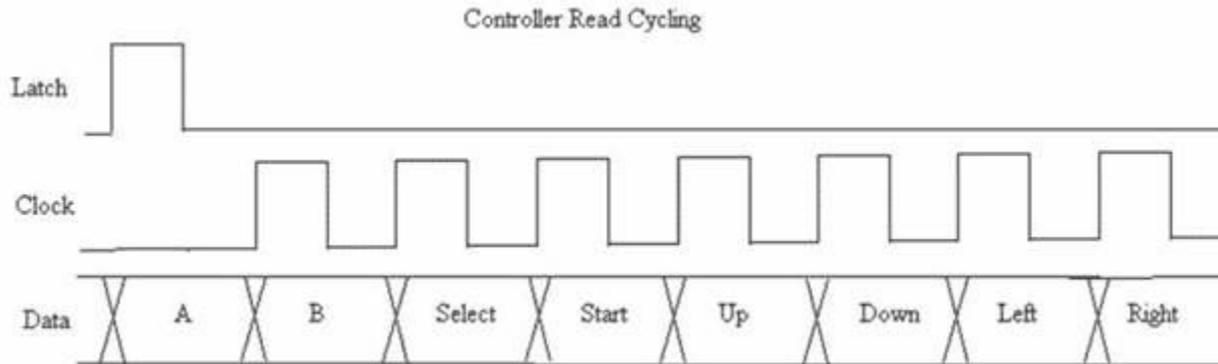


NES Controller

VHDL:

- Clock divider
 - Controller clock runs at 400 Hz, divided from 100MHz system clock
- Shift register
 - Receives serial data and reassembles as parallel
- Output register
 - Once data is shifted completely, the parallel output is stored in an output register until needed
- Timing state machine
 - Controller latch timing, output register latching
- “Button press” state machine
 - Looks for signal transitions, outputs based on button being pressed and released

NES Controller


Diagram:

 


VGA Controller

- VGA screen used to display game board to players.
- VGA controller and state machine code from Professor Llamocca was used.
- A circuit was added to choose the color to display based on the values of HC and VC.
- That circuit used a decoder and multiple MUX to select the input for a particular region on the screen.
- Colors of the chips, whether Red, Black, or Blank were also chosen by a smaller MUX.

VGA Controller

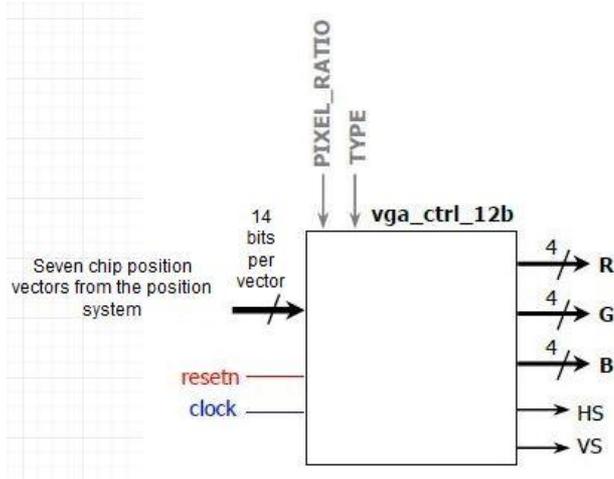


Top level of VGA controller

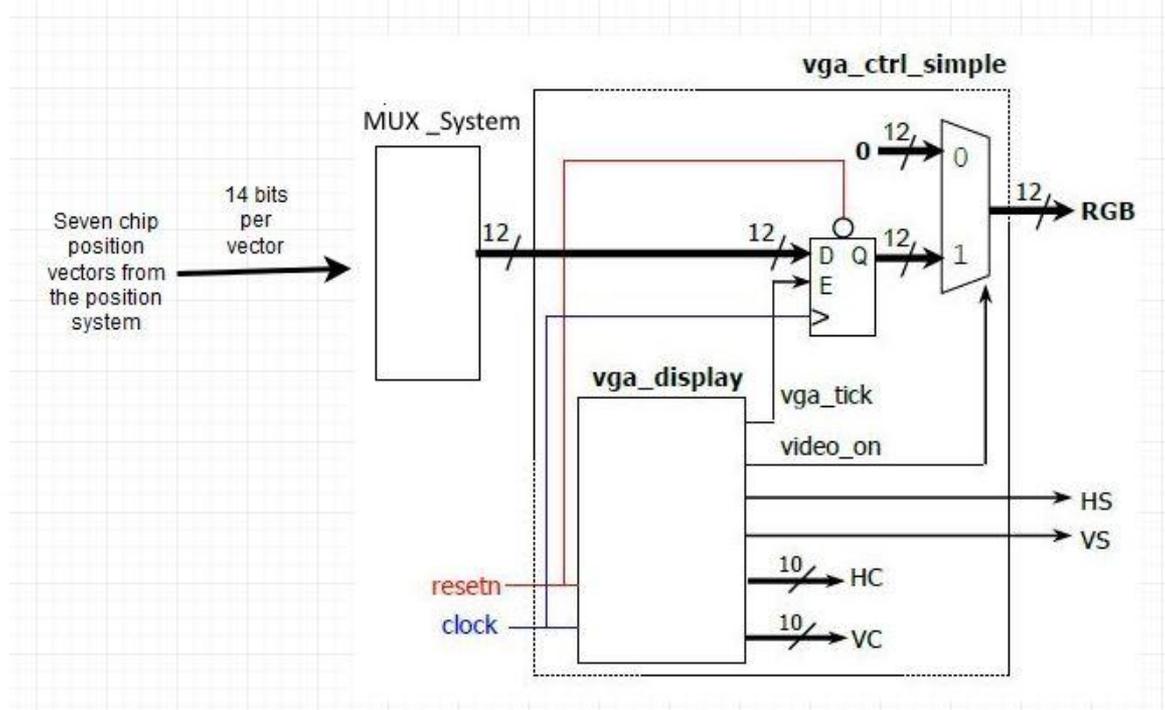

Internal circuits of the VGA controller


VGA Controller

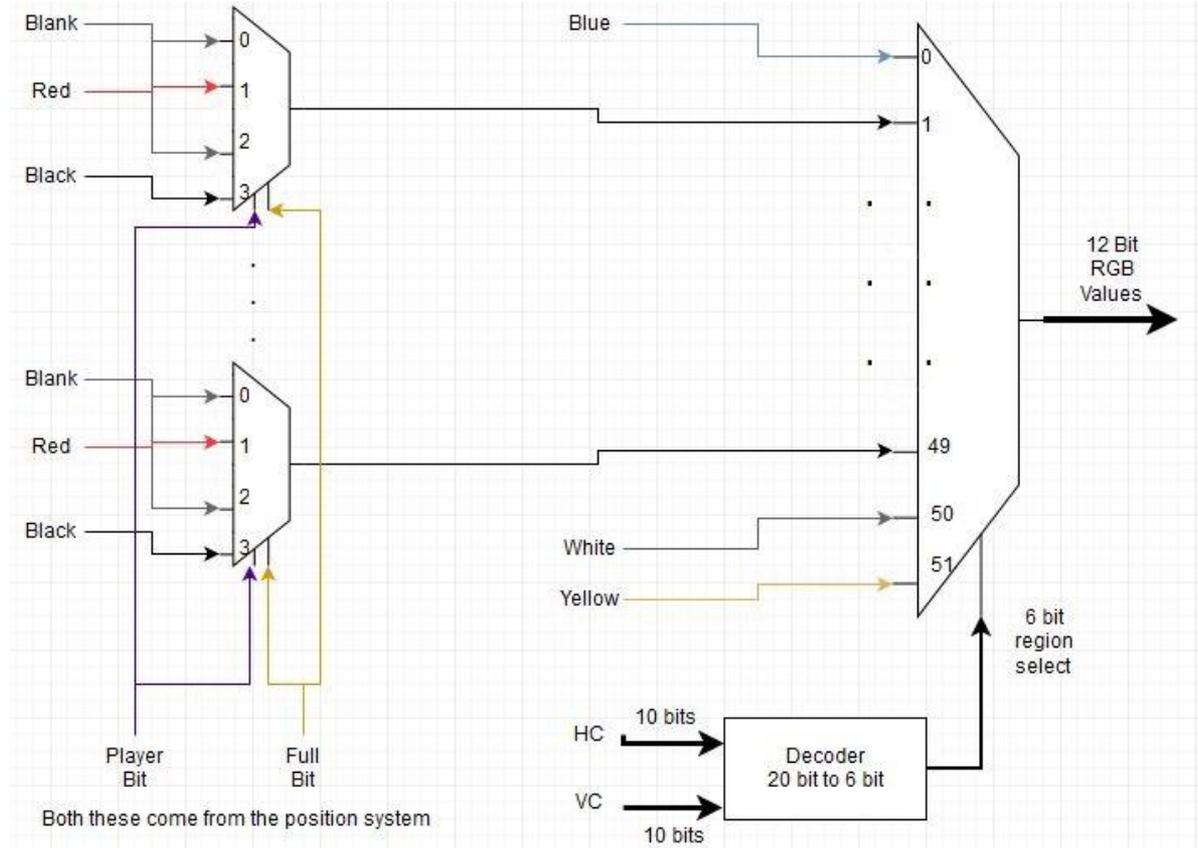Multiplexer system designed to determine which color the VGA needs to display based on the region of the display. Color names shown were encoded as standard logic vectors in the VHDL code. The blank chip space color was white.



Gameplay Pictures


1.

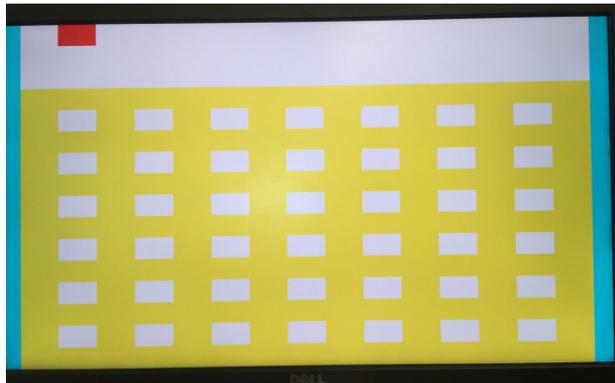

Game start.


Player 1's turn.

2.


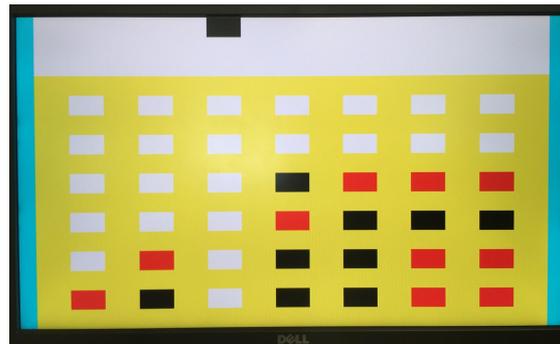


A few turns...

3.

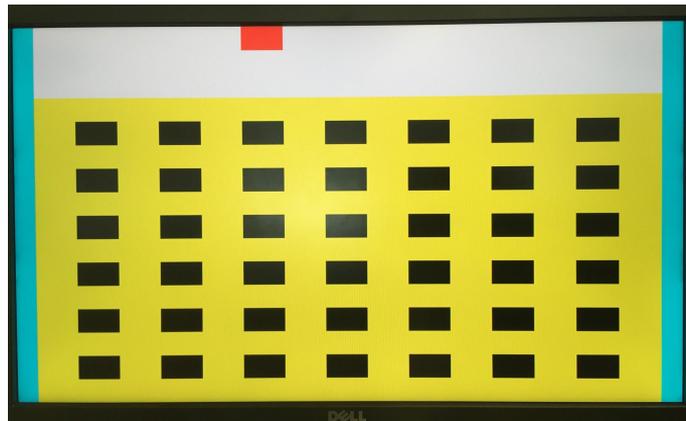

Player 2 wins!

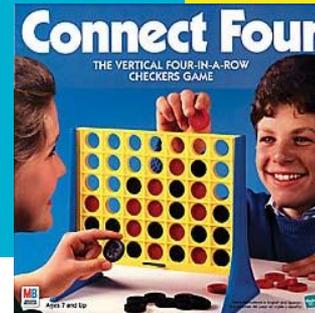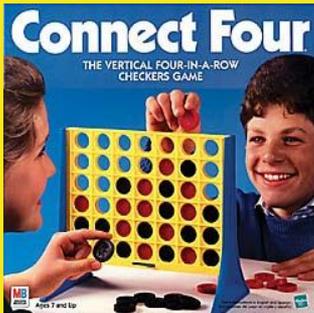

Wanna Play?

