


# Homework 3

(Due date: March 10<sup>th</sup> @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

## PROBLEM 1 (25 PTS)

 a) Complete the timing diagram of the circuit shown below. (5 pts)



b) Complete the timing diagram of the circuit whose VHDL description is shown below: (5 pts)

```

library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( prn, x, clk: in std_logic;
        q: out std_logic);
end circ;


architecture a of circ is
  signal qt: std_logic;

begin
  process (prn, clk, x)
  begin
    if prn = '0' then
      qt <= '1';
    
```



```

      elsif (clk'event and clk = '0') then
        if x = '1' then
          qt <= not(qt);
        end if;
      end if;
    end process;
    q <= qt;
end a;

```

 


  c) Complete the timing diagram of the circuits shown below: (15 pts)



 PROBLEM 2 (15 PTS)

- Complete the timing diagram of the circuit shown below: (8 pts)



- Complete the VHDL description of the synchronous sequential circuit whose truth table is shown below: (7 pts)

```

library ieee;
use ieee.std_logic_1164.all;

entity my_ff is
    port ( a, b, c: in std_logic;
          prn, clk: in std_logic;
          q: out std_logic);
end my_ff;


architecture a of my_ff is

begin
    -- ???
end a;
```

prn	clk	A	B	$Q_{t+1}$
1		0	0	$\overline{Q_t}$
1		0	1	$Q_t$
1		1	0	B
1		1	1	$\overline{C}$
0	X	X	X	1

 
PROBLEM 3 (20 PTS)

- Given the following circuit, complete the timing diagram (signals DO and DATA). The LUT 6-to-6 implements the following function:  $OLUT = \lceil ILUT^{0.95} \rceil$ . For example  $ILUT = 35 (100011_2) \rightarrow OLUT = \lceil 35^{0.95} \rceil = 30 (011110_2)$



 PROBLEM 4 (30 PTS)

- The following circuit is a 4-bit parallel/serial load shift register with enable input. Shifting operation:  $s\_1=0$ . Parallel load:  $s\_1=1$ . Note that  $Q = Q_3Q_2Q_1Q_0$ .  $D = D_3D_2D_1D_0$ 
  - Write a structural VHDL code. You MUST create a file for: i) flip flop, ii) MUX 2-to-1, and iii) top file (where you will interconnect the flip flops and MUXes). Provide a printout. (10 pts)
  - Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Timing Simulation). The clock frequency must be 50 MHz with 50% duty cycle. Provide a printout. (20 pts)



PROBLEM 5 (10 PTS)

- Attach a printout of your Initial Project Report (no more than a page). This report should contain the project title, the project description, and the current status of the project. Use the provided template (Final Project - Report Template.docx).