

Laboratory 3

(Due date: **002**: February 15th, **003**: February 16th, **004**: February 17th)

OBJECTIVES


- ✓ Use the Concurrent Description and the Structural Description in VHDL.
- ✓ Implement Combinational circuits on an FPGA.

VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.

FIRST ACTIVITY: (100/100)

- **SIMPLE 4-BIT ARITHMETIC LOGIC UNIT (ALU):** This circuit selects between arithmetic (absolute value, addition) and logical (XOR, AND) operations. Only one result (hexadecimal value) can be shown on the 7-segment display. This is selected by the input `sel(1..0)`.
- Input `EN`: If `EN=1` → result appears on the 7-segment display. If `EN=0` → all LEDs in the 7-segment display are off.
- Arithmetic operations: The 4-bit inputs `A` and `B` are treated as unsigned numbers.
 - ✓ `A+B`: If there is a carry out, ignore it.
 - ✓ `|A-B|`: 4-bit result, since $|A-B| \in [0,15]$.
Tip: zero-extend the inputs to 5 bits and implement `A-B` (5-bit signed result). Then, implement `|A-B|`, where the 5-bit signed result is always positive. Finally, use the magnitude (4 LSBs) as the unsigned output.
- Logic Operations (`A xnor B`, `A nand B`): These are bit-wise operations.
- **Nexys-4 DDR:** Each 7-segment display has active-low inputs (CA-CG) and an active-low enable. Make sure that only one 7-segment display is activated (e.g.: `AN0=0`, `AN1-AN7=1` to only use the right-most 7-segment display).

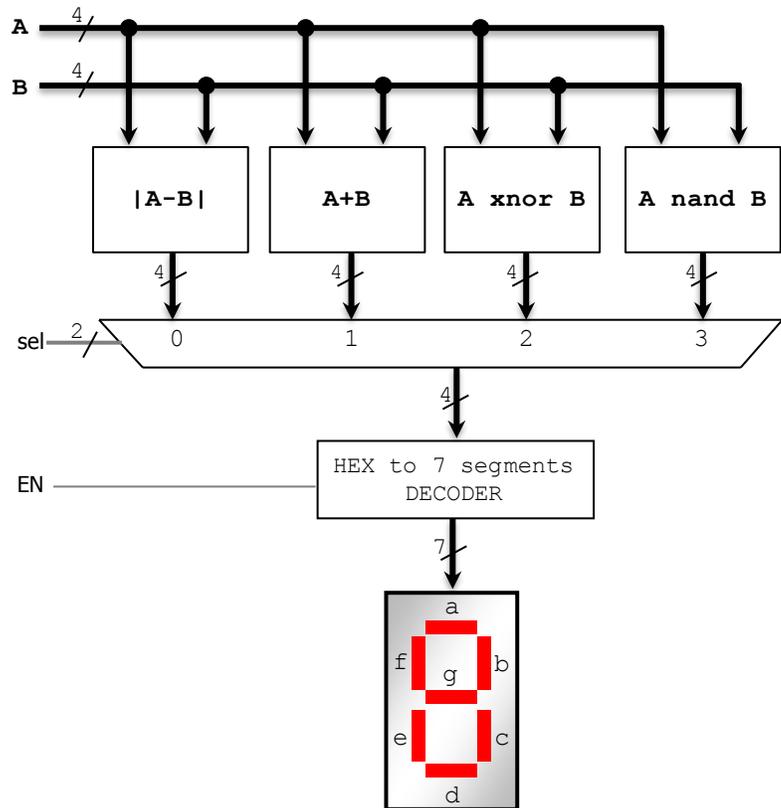

- ✓ Create a new ISE Project. Select the **XC7A100T-1CSG324 Artix-7 FPGA** device.
 - ✓ Write the VHDL code for the given circuit.
 - **IMPORTANT:** For `A+B` and `|A-B|` circuits, you must use full adders and logic gates (as in Lab 2).
 - To implement the Bus MUX and decoder, it is strongly advised that you use the VHDL concurrent statements. To implement the top file, use the **Structural Description**: Create a separate file for the Arithmetic and Logic circuits, the 4-to-1 Bus MUX, and the Hex to 7-segment decoder.
 - ✓ Write the VHDL testbench to test the circuit to test representative cases (or all cases).
 - ✓ Perform Functional Simulation and Timing Simulation of your design. **Demonstrate this to your TA.**
 - ✓ I/O Assignment: Create the UCF file. Nexys-4: Use SW0 to SW7 for the inputs `A` and `B`, SW8 to SW10 for the inputs `sel` and `EN`, and CA-CG (7-segment display signals) for the 7-bit output.
 - ✓ Generate and download the bitstream on the FPGA and test. **Demonstrate this to your TA.**
- Submit (as a .zip file) all the generated files: VHDL code files, VHDL testbench, and UCF file to Moodle (an assignment will be created). DO NOT submit the whole ISE Project.

TA signature: _____

Date: _____