

Laboratory 5

(Due date: **002:** March 21st, **003:** March 22nd, **004:** March 23rd)

OBJECTIVES


- ✓ Describe Finite State Machines (FSMs) in VHDL.
- ✓ Implement a Digital System: Control Unit and Datapath Unit.

VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.

ITERATIVE DIVIDER IMPLEMENTATION (100/100)

 - Given two unsigned numbers A and B , we want to design a circuit that produces the quotient Q and a remainder R . $A = B \times Q + R$. The algorithm that implements the traditional long-hand division is as follows:




ALGORITHM

```

R = 0
for i = n-1 downto 0
  left shift R (input = ai)
  if R ≥ B
    qi = 1, R ← R-B
  else
    qi = 0
  end
end
end
    
```

- An iterative architecture is depicted in the figure for A with 6 bits and B with 4 bits. The register R stores the remainder. A division operation is started when $E = 1$ (where A and B values are captured). Then, at every clock cycle, we either: i) shift in the next bit of A , or ii) shift in the next bit of A and subtract B . The signal $done$ is asserted to indicate that the operation has been completed and the result appears in Q and R .

 

- Modulo-6 counter: It includes: i) a synchronous input *sclr* that clears the count when $E = sclr = 1$, and ii) an output *zC* that is asserted when the count reaches 5.
- Left-shift register: Note that one of the shift registers includes a synchronous input *sclr* that clears the register outputs when $E = sclr = 1$.
- Each sequential component has *resetn* and *clock* inputs.

- The circuit is an example of a Digital System: It includes a Control Circuit (FSM) and a Datapath Circuit. The Datapath Circuit is made out of combinational and sequential components. The circuit is also called a Special-Purpose Processor. In this case, the special purpose is the unsigned division.
 - ✓ Create a new ISE Project. Select the **XC7A100T-1CSG324 Artix-7 FPGA** device.
 - ✓ Write the VHDL code for the given circuit. Suggestion: create a separate file for modulo-6 counter, shift Register, shift register with *sclr* input, register, adder, hex to 7-segments decoder, FSM, and top file.
 - ✓ Write the VHDL testbench (you must generate a 100 MHz input clock for your simulations) to test the following cases:
 - A = 011011 (27), B = 1001 (9)
 - A = 010100 (20), B = 0111 (7)
 - A = 101010 (42), B = 1111 (15)
 - A = 100101 (37), B = 0101 (5)
 - A = 001101 (13), B = 1100 (12)
 - A = 101111 (47), B = 0010 (2)
 - ✓ Perform Functional Simulation and Timing Simulation of your design. **Demonstrate this to your TA.**
 - ✓ I/O Assignment: Create the UCF file. Nexys-4-DDR: Use SW0 to SW10 for the inputs, CLK100MHZ for the input *clock*, CPU_RESET push-button for *resetn*, a LED for 'done', six LEDs for *Q*, and the 7-segment display for *R*.
 - ✓ Generate and download the bitstream on the FPGA and test. **Demonstrate this to your TA.**

- Submit (as a .zip file) all the generated files: VHDL code files, VHDL testbench, and UCF file to Moodle (an assignment will be created). DO NOT submit the whole ISE Project.

TA signature: _____

Date: _____