 


Notes - Unit 7


INTRODUCTION TO DIGITAL SYSTEM DESIGN

DIGITAL SYSTEM MODEL

- FSM + Datapath Circuit:



EXAMPLE: CAR LOT COUNTER

 

If A = 1 → No light received (car obstructing LED A)
If B = 1 → No light received (car obstructing LED B)


If car enters the lot, the following sequence (A|B) must be followed:
00 → 10 → 11 → 01 → 00

If car leaves the lot, the following sequence (A|B) must be followed:
00 → 01 → 11 → 10 → 00


A car might stay in a state for many cycles since the car speed is very large compared to that of the clock frequency.

DIGITAL SYSTEM (FSM + Datapath circuit)

 
- Usually, when 'resetrn' (asynchronous clear) and 'clock' are not drawn, they are implied.



▪ Finite State Machine (FSM):

 


▪ Algorithmic State Machine (ASM) chart:

 

 EXAMPLE: ACCUMULATOR


DIGITAL SYSTEM (FSM + Datapath circuit)

- sclr: Synchronous clear. If $E = '1'$ and $sclr = '1'$, then the output bits of the registers are set to zero.




Finite State Machine (FSM):

$E | restart | Ei | sclr$

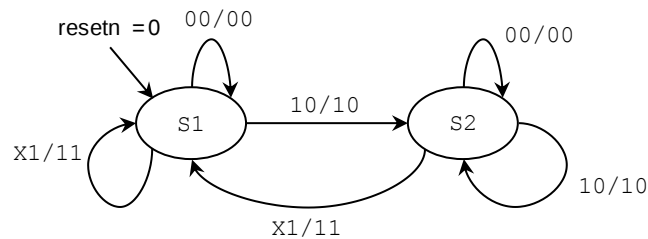


Algorithmic State Machine (ASM):

 

 
EXAMPLE: 7-SEGMENT SERIALIZER

DIGITAL SYSTEM (FSM + Datapath circuit)

- Most FPGA Development board have a number of 7-segment displays (e.g., 4, 8). However, only one can be used at a time.
- If we want to display four digits (inputs A, B, C, D), we can design a serializer that will only show one digit at a time on the 7-segment displays.
- Since only one 7-segment display can be used at a time, we need to serialize the four BCD outputs. In order for each digit to appear bright and continuously illuminated, each digit is illuminated for 1 ms every 4 ms (i.e. a digit is un-illuminated for 3 ms and illuminated for 1 ms). This is taken care of by feeding the output 'z' of the counter to 0.001 s to the enable input of the FSM. This way, state transitions only occur each 0.001 s.
- In the figure, the enable signals for the four 7-segment displays are active low (this is usually the case).



 - Algorithmic State Machine (ASM) chart:** This is a Moore-type FSM.



EXAMPLE: SERIAL MULTIPLIER

UNSIGNED MULTIPLICATION: SEQUENTIAL ALGORITHM

```

P ← 0, Load A,B
while B ≠ 0
  if b0 = 1 then
    P ← P + A
  end if
  left shift A
  right shift B
end while

```


Example:

$$\begin{array}{r}
 1111 \times \\
 \underline{1101} \\
 1111 \rightarrow P \leftarrow 0 + 1111 \\
 0000 \rightarrow P \leftarrow 1111 \\
 1111 \rightarrow P \leftarrow 1111 + 111100 = 1001011 \\
 1111 \rightarrow P \leftarrow 1001011 + 1111000 = 11000011 \\
 \hline
 11000011
 \end{array}$$


$P \leftarrow 0, A \leftarrow 1111, B \leftarrow 1101$
 $b_0=1 \Rightarrow P \leftarrow P + A = 1111. \quad A \leftarrow 11110, B \leftarrow 110$
 $b_0=0 \Rightarrow P \leftarrow P = 1111. \quad A \leftarrow 111100, B \leftarrow 11$
 $b_0=1 \Rightarrow P \leftarrow P + A = 1111 + 111100 = 1001011. \quad A \leftarrow 1111000, B \leftarrow 1$
 $b_0=1 \Rightarrow P \leftarrow P + A = 1001011 + 1111000 = \mathbf{11000011}. \quad A \leftarrow 11110000, B \leftarrow 0$

DIGITAL SYSTEM (FSM + Datapath circuit)

 
- Iterative Multiplier Architecture: *sclr*: synchronous clear. In this case, if *sclr* = 1 and *E* = 1, the register contents are initialized to 0. The solution is computed in at most $N + 1$ cycles.



Algorithmic State Machine (ASM) chart:

 



▪ **Example** (timing diagram):

 

  EXAMPLE: SERIAL DATA TRANSMISSION WITH UART

UART Interface



- This interface transfers data asynchronously (clock is not transmitted, transmitter and receiver use their own clocks).
- Data communication: RXD (receive pin), TXD transmit pin). The FT2232 chip inside the Nexys-4 board is in charge of handling the USB communication with a computer.
- Format of a Frame: Start bit ('0'), 8 to 9 data bits (LSB transmitted first), optional parity bit, and a stop bit ('1').
- Transmitter: Simple design that transmit the data frame at the Baud rate (or bit rate in bps).
- Receiver: It uses a clock signal whose frequency is a multiple (usually 16) of the incoming data rate.



DIGITAL SYSTEM (FSM + Datapath circuit)

For a baud rate of 9600 bps, the Baud rate clock is 9600 Hz.

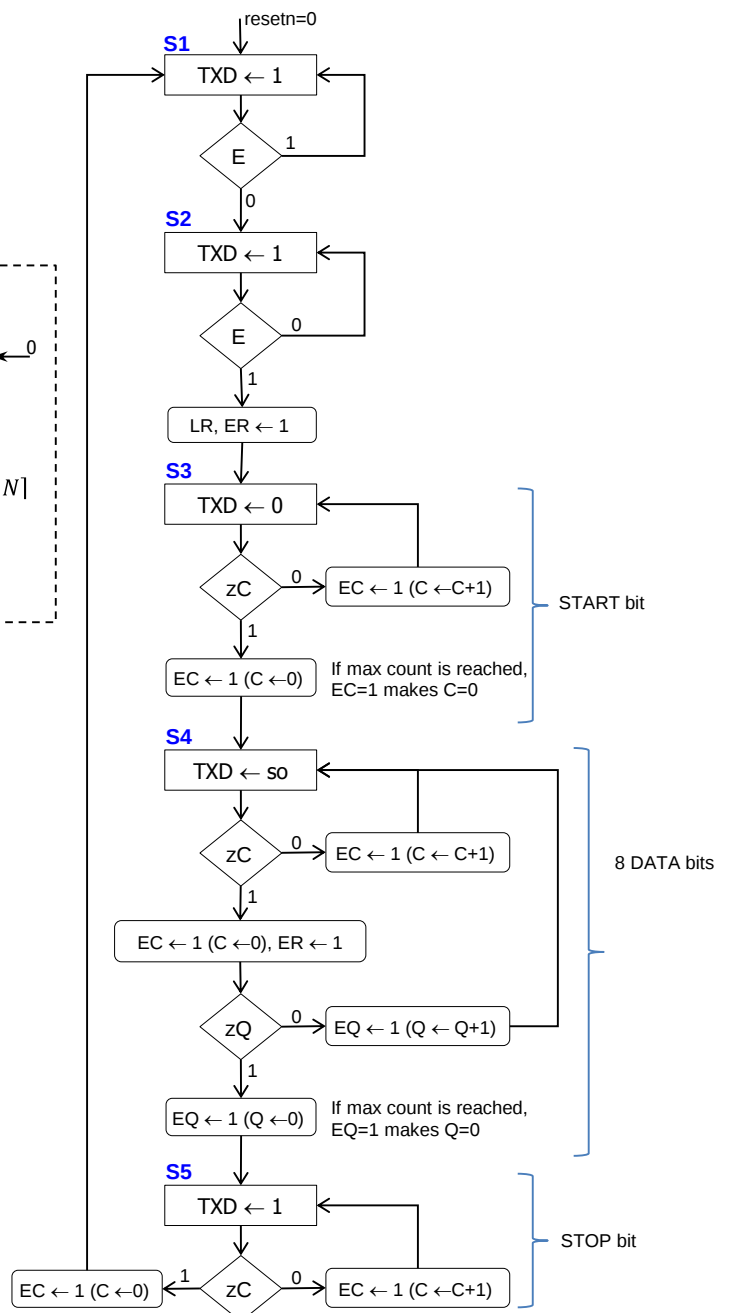 $N = \frac{1}{\frac{1}{9600} \cdot 10 \text{ ns}} = 10416$. This number changes according to the desired baud rate.



EXAMPLE: BIT-COUNTING CIRCUIT


SEQUENTIAL ALGORITHM

```


C ← 0
while A ≠ 0
  if a0 = 1 then
    C ← C + 1
  end if
  right shift A
end while
    
```

DIGITAL SYSTEM (FSM + Datapath circuit)

 - sclr: Synchronous clear. In this case, if sclr = '1', the count is initialized to zero (here, we do not need EC to be 1).




Algorithmic State Machine (ASM) chart:

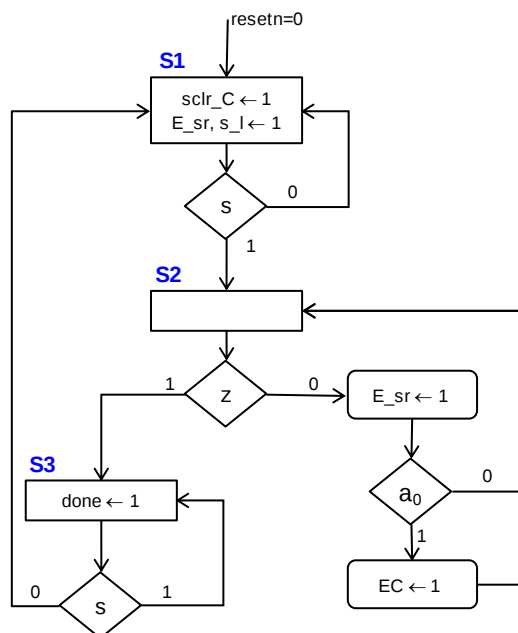

EXAMPLE: SIMPLE PROCESSOR


DIGITAL SYSTEM (FSM + Datapath circuit)

 


- Operation: Every time $w = '1'$, we grab the instruction from fun and execute it:
- $funq = |f_2|f_1|f_0|ry_1|ry_0|rx_1|rx_0|$

f	Operation	Function
000	Load Rx , Data	$Rx \leftarrow Data$
001	Move Rx , Ry	$Rx \leftarrow Ry$
010	Add Rx , Ry	$Rx \leftarrow Rx + Ry$
011	Sub Rx , Ry	$Rx \leftarrow Rx - Ry$
100	Not Rx	$Rx \leftarrow NOT (Rx)$
101	And Rx , Ry	$Rx \leftarrow Rx AND Ry$
110	Or Rx , Ry	$Rx \leftarrow Rx OR Ry$
111	Xor Rx , Ry	$Rx \leftarrow Rx XOR Ry$

▪ **Control Circuit:**

 


$$\text{funq} = |f_2|f_1|f_0|RY_1|RY_0|Rx_1|Rx_0|$$

 

▪ **Arithmetic-Logic Unit (ALU):**

op	Operation	Function	Unit
0000	y <= A	Transfer 'A'	Arithmetic
0001	y <= A + 1	Increment 'A'	
0010	y <= A - 1	Decrement 'A'	
0011	y <= B	Transfer 'B'	
0100	y <= B + 1	Increment 'B'	
0101	y <= B - 1	Decrement 'B'	
0110	y <= A + B	Add 'A' and 'B'	
0111	y <= A - B	Subtract 'B' from 'A'	
1000	y <= not A	Complement 'A'	Logic
1001	y <= not B	Complement 'B'	
1010	y <= A AND B	AND	
1011	y <= A OR B	OR	
1100	y <= A NAND B	NAND	
1101	y <= A NOR B	NOR	
1110	y <= A XOR B	XOR	
1111	y <= A XNOR B	XNOR	


▪ Algorithmic State Machine (ASM):

 

 
EXAMPLE: ARBITER CIRCUIT

DIGITAL SYSTEM (FSM + Datapath circuit)

- Three devices can request access to a certain resource at any time (example: access to a bus made of tri-state buffers, only one tri-state buffer can be enabled at a time). The FSM can only grant access to one device at a time. There should be a priority level among devices.
- If the FSM grants access to one device, one must wait until the request signal to that device is deasserted (i.e. set to zero) before granting access to a different device.




Algorithmic State Machine (ASM) chart:

 


 EXAMPLE: DISPLAYING PATTERNS ON 7-SEGMENT DISPLAYS


- Different patterns are shown based on the selector 'sel' signal. Two 7-segment displays are used.
- 'stop' input: If it is asserted (stop = 1), the lights' pattern freezes.
- The input 'x' selects the rate of change (every 1.5, 1.0, 0.5, or 0.25 seconds).



DIGITAL SYSTEM (FSM + Datapath circuit)

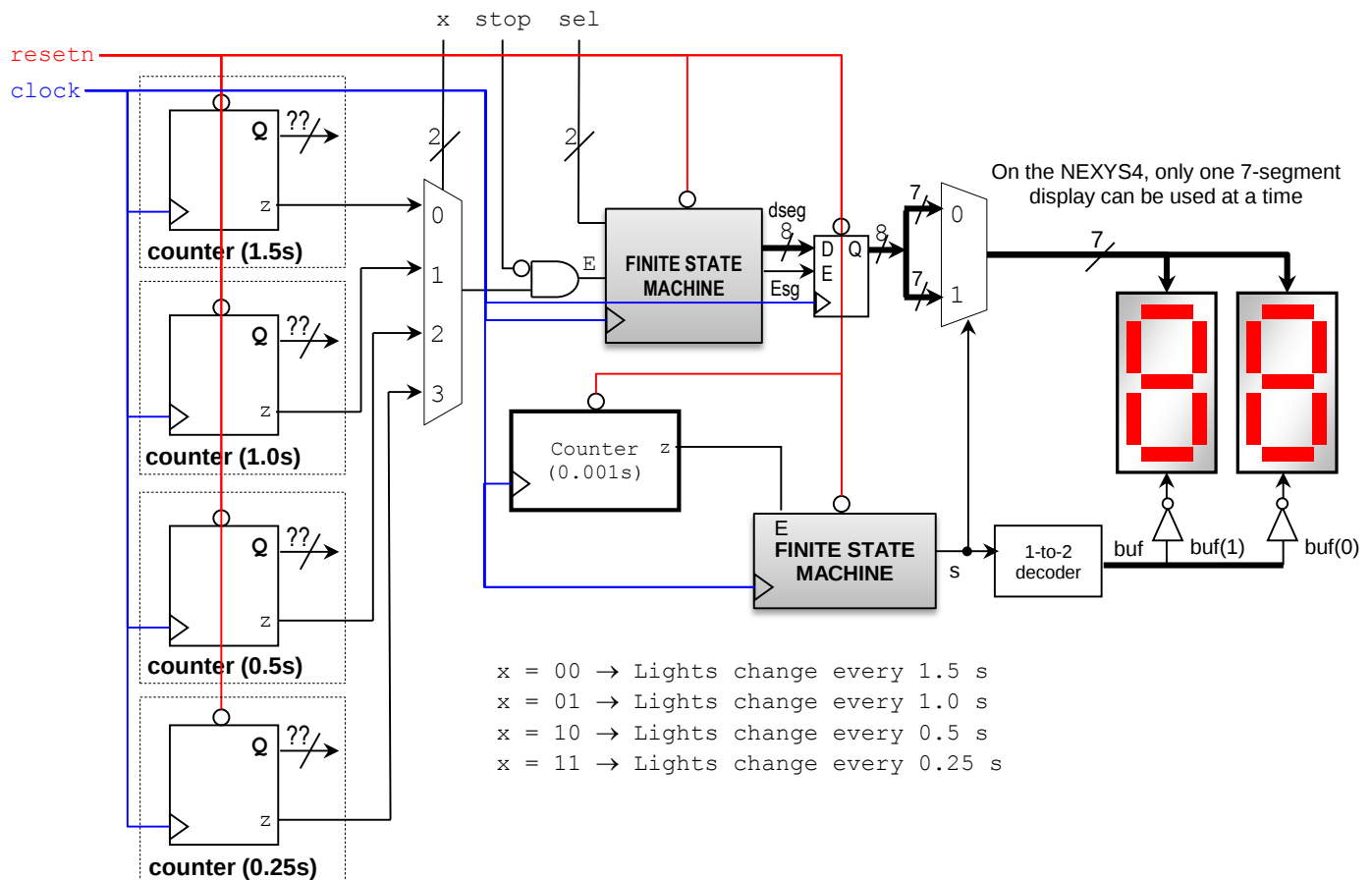

 ▪ **Algorithmic State Machine (ASM) chart:**



▪ **Algorithmic State Machine (ASM) chart:** This is the FSM that controls the output MUX

