

# Quiz 2

(February 9<sup>th</sup> @ 5:30 pm)

## PROBLEM 1 (35 PTS)

- Complete the following table. Use the fewest number of bits in each case:

REPRESENTATION			
Decimal	Sign-and-magnitude	1's complement	2's complement
			101100
	0100101		
		101111	
-32			

- Convert the following decimal number to its 2's complement representation: -16.625 (5 pts)

## PROBLEM 2 (30 PTS)

- Implement the following function using ONLY 2-to-1 MUXs (AND, OR, NOT gates are not allowed):

$$f(x, y, z) = x \oplus y \oplus z$$

## PROBLEM 3 (35 PTS)

- Complete the timing diagram of the circuit shown below:

