

# Quiz 3

(March 15<sup>th</sup> @ 5:30 pm)

## PROBLEM 1 (30 PTS)


- Complete the timing diagram of the circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( rstn, a, b, x, clk: in std_logic;
        q: out std_logic);
end circ;
```



```
architecture xst of circ is
  signal qt, f: std_logic;
begin
  f <= a xor b;

   process (rstn, clk, a, b, x)
  begin
    if rstn = '0' then
      qt <= '0';
    elsif (clk'event and clk = '1') then
      if x = '0' then
        qt <= qt or f;
      end if;
    end if;
  end process;
  q <= qt;
end xst;
```


  
## PROBLEM 2 (30 PTS)

- Complete the timing diagram of the following state machine:



## PROBLEM 3 (40 PTS)

- Complete the timing diagram of the following circuit.  $Q = Q_3Q_2Q_1Q_0$

