

# Solutions - Homework 1

(Due date: January 21<sup>st</sup> @ 5:30 pm)

Presentation and clarity are very important!

## PROBLEM 1 (25 PTS)

a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (12 pts)


✓  $F = A(\overline{B \oplus C}) + \overline{B}$

✓  $F = (\overline{C} + \overline{B})(C + A)(\overline{B} + A) + CA$


✓  $F(X, Y, Z) = \prod(M_1, M_3, M_6, M_7)$

✓  $F = \overline{(X + Z)}Y + X\overline{Y}Z$

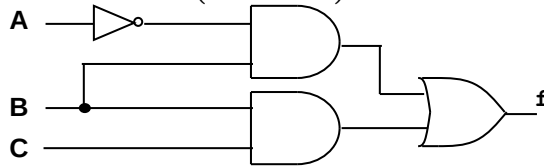
✓  $F = \overline{A(\overline{B \oplus C})} + \overline{B} = \overline{A(\overline{B \oplus C})} \cdot B = (\overline{A} + (\overline{B \oplus C})) \cdot B = (\overline{A} + BC + \overline{B}\overline{C}) \cdot B = \overline{A}B + BC + B\overline{B}\overline{C} = \overline{A}B + BC$



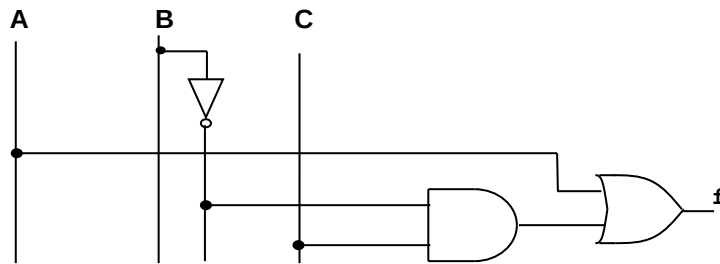
✓  $F = (C + A)(\overline{C} + \overline{B})(A + \overline{B}) + CA = (C + A)(\overline{C} + \overline{B}) + CA$   
 $(C + A)(\overline{C} + \overline{B}) + CA = \overline{C}\overline{B} + \overline{C}A + \overline{B}C + \overline{B}A + CA = \overline{C}\overline{B} + \overline{C}A + CA = \overline{C}\overline{B} + A$



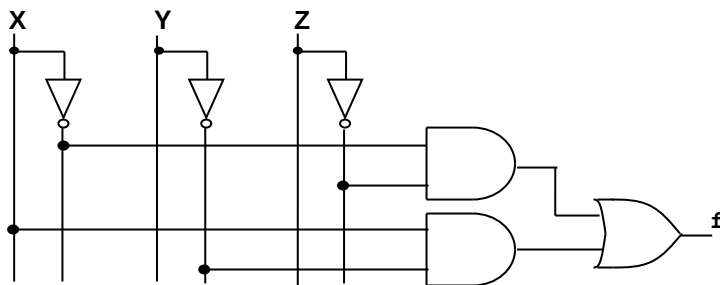✓  $F(X, Y, Z) = \prod(M_1, M_3, M_6, M_7) = \sum(m_0, m_2, m_4, m_5) = \overline{X}\overline{Y}\overline{Z} + \overline{X}Y\overline{Z} + X\overline{Y}\overline{Z} + X\overline{Y}Z = \overline{X}\overline{Z} + X\overline{Y}$



✓  $F = \overline{(X + Z)}Y + X\overline{Y}Z = (\overline{X} + \overline{Z})Y \cdot \overline{X}\overline{Y}Z = (X + \overline{Y} + Z)(\overline{X} + Y + \overline{Z})$   
 $F = X\overline{X} + X\overline{Y} + X\overline{Z} + Z\overline{X} + ZY + Z\overline{Z} + \overline{Y}\overline{X} + \overline{Y}Y + \overline{Y}\overline{Z} = XY + X\overline{Z} + Z\overline{X} + ZY + \overline{Y}\overline{X} + \overline{Y}\overline{Z}$   
 $F = \overline{X}\overline{Z} + \overline{X}Y + \overline{Y}\overline{Z} + XY + Z\overline{X} + ZY = X\overline{Z} + \overline{X}\overline{Y} + XY + Z\overline{X} + ZY$   
 $F = X\overline{Z} + XY + \overline{Y}Z + \overline{Y}\overline{X} + \overline{X}Z = X\overline{Z} + XY + YZ + \overline{Y}\overline{X} = \overline{Y}Z + \overline{Z}X + \overline{Y}\overline{X}$

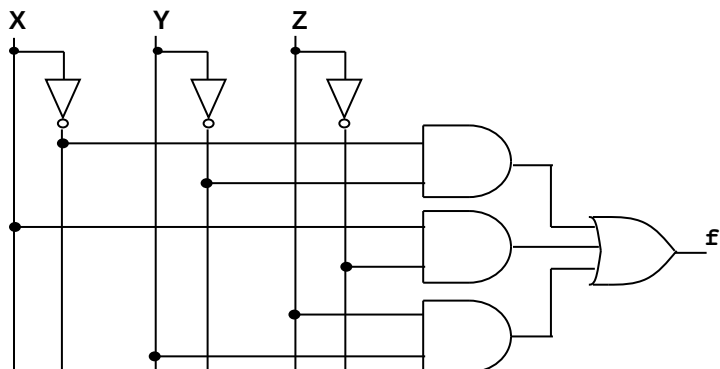

- b) Based on the formula  $x \oplus y = x\bar{y} + \bar{x}y$ , demonstrate that  $(a \oplus b) \oplus c = a \oplus (b \oplus c) = b \oplus (a \oplus c)$ . You can express each function using the canonical sum of products, or complete the truth table for each function. (5 pts)

.....

$$(a \oplus b) \oplus c = (a\bar{b} + \bar{a}b) \oplus c = (\overline{a\bar{b} + \bar{a}b})c + (a\bar{b} + \bar{a}b)\bar{c} = (ab + \bar{a}\bar{b})c + (a\bar{b} + \bar{a}b)\bar{c} = abc + \bar{a}\bar{b}c + a\bar{b}\bar{c} + \bar{a}b\bar{c} = \sum m(7,1,4,2).$$

$$a \oplus (b \oplus c) = a \oplus (b\bar{c} + \bar{b}c) = a(b\bar{c} + \bar{b}c) + \bar{a}(b\bar{c} + \bar{b}c) = abc + \bar{a}\bar{b}\bar{c} + \bar{a}b\bar{c} + \bar{a}\bar{b}c = \sum m(7,4,2,1).$$

$$b \oplus (a \oplus c) = (a \oplus c) \oplus b = (a\bar{c} + \bar{a}c) \oplus b = (ac + \bar{a}\bar{c})b + (a\bar{c} + \bar{a}c)\bar{b} = acb + \bar{a}\bar{c}b + a\bar{c}\bar{b} + \bar{a}c\bar{b} = \sum m(7,2,4,1).$$

\* Note that  $x \oplus y = y \oplus x$

- c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums.

| x | y | z | f <sub>1</sub> | f <sub>2</sub> |
|---|---|---|----------------|----------------|
| 0 | 0 | 0 | 0              | 1              |
| 0 | 0 | 1 | 1              | 0              |
| 0 | 1 | 0 | 1              | 1              |
| 0 | 1 | 1 | 0              | 1              |
| 1 | 0 | 0 | 1              | 0              |
| 1 | 0 | 1 | 0              | 0              |
| 1 | 1 | 0 | 0              | 0              |
| 1 | 1 | 1 | 1              | 0              |

**Sum of Products**

$$f_1 = \bar{X}\bar{Y}Z + \bar{X}Y\bar{Z} + X\bar{Y}\bar{Z} + XYZ$$

$$f_2 = \bar{X}\bar{Y}\bar{Z} + \bar{X}Y\bar{Z} + \bar{X}YZ$$

**Product of Sums**



$$f_1 = (X + Y + Z)(X + \bar{Y} + \bar{Z})(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + Z)$$

$$f_2 = (X + Y + \bar{Z})(\bar{X} + Y + Z)(\bar{X} + Y + \bar{Z})(\bar{X} + \bar{Y} + Z)(\bar{X} + \bar{Y} + \bar{Z})$$

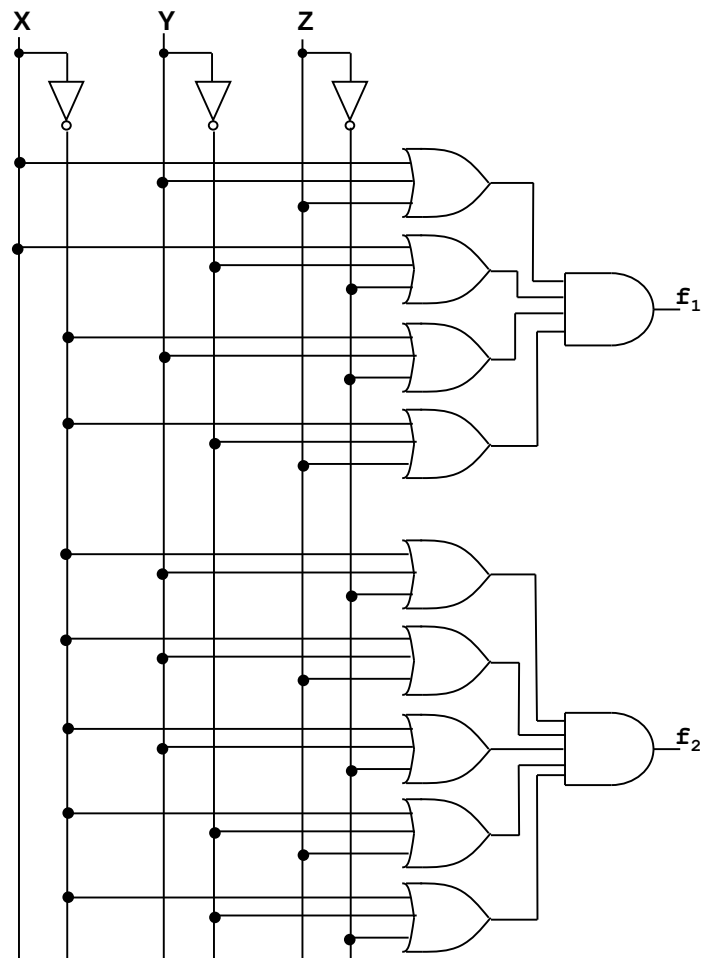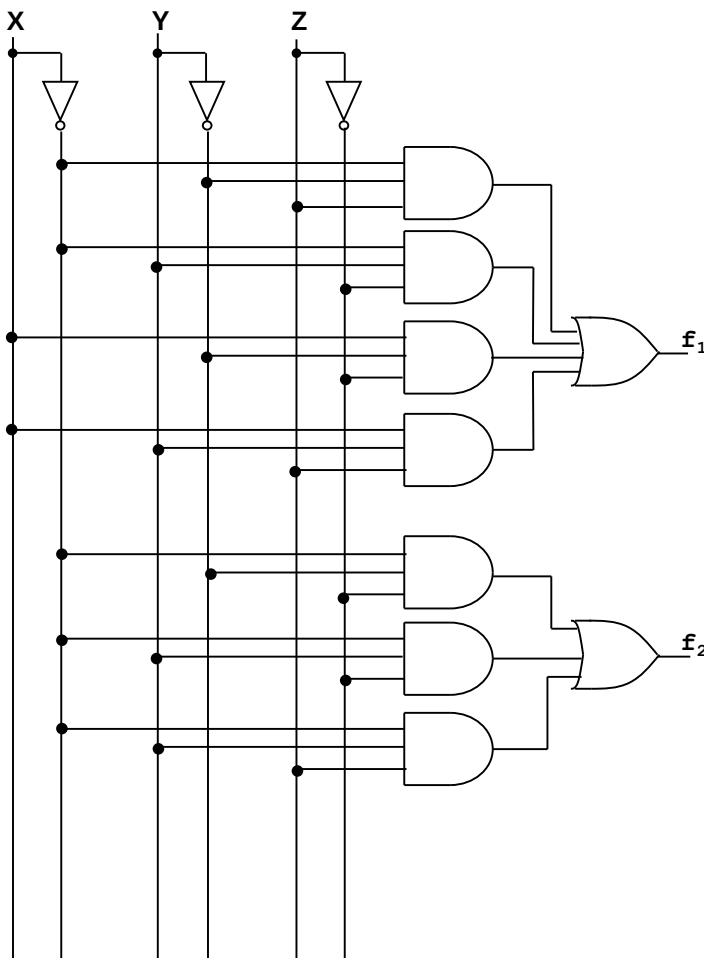**Minterms and maxterms:**


$$f_1 = \sum(m_1, m_2, m_4, m_7) = \prod(M_0, M_3, M_5, M_6).$$

$$f_2 = \sum(m_0, m_2, m_3) = \prod(M_1, M_4, M_5, M_6, M_7).$$



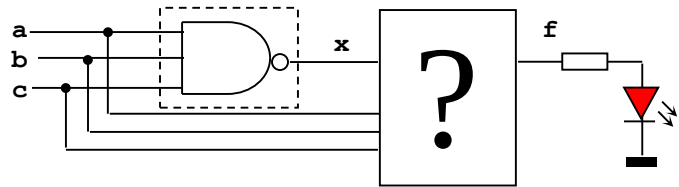
## PROBLEM 2 (10 PTS)

- Design a circuit (simplify your circuit) that verifies the logical operation of a 3-input NAND gate.  $f = '1'$  (LED ON) if the NAND gate does NOT work properly. Assumption: when the NAND gate is not working, it generates 1's instead of 0's and vice versa.



| x | a | b | c | f |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 1 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 1 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 1 |
| 0 | 1 | 1 | 0 | 1 |
| 0 | 1 | 1 | 1 | 0 |
| 1 | 0 | 0 | 0 | 0 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 0 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 0 |
| 1 | 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 | 1 |

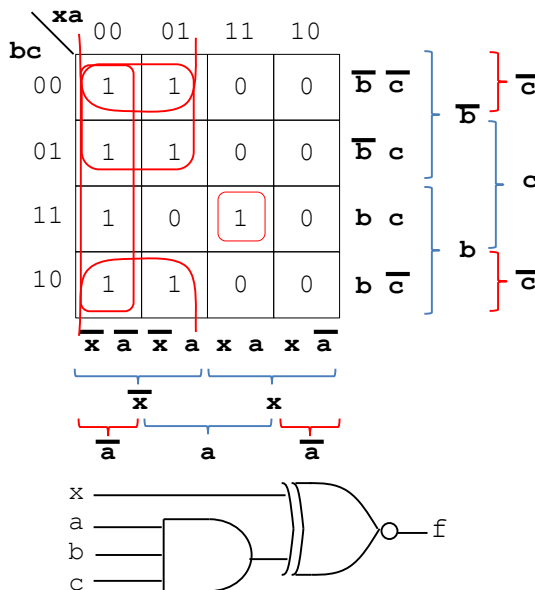

$$f = \bar{b}\bar{x} + \bar{x}\bar{c} + \bar{x}\bar{a} + xabc$$


$$f = \bar{x}(\bar{b} + \bar{c} + \bar{a}) + xabc$$

$$f = \bar{x}(\overline{bca}) + xabc = \bar{x} \oplus abc$$

## PROBLEM 3 (15 PTS)

- Complete the truth table for a circuit with 4 inputs  $x, y, z, w$  that activates an output ( $f = 1$ ) when the number of 1's in the inputs is odd. For example: If  $xyzw = 1100 \rightarrow f = 0$ . If  $xyzw = 1011 \rightarrow f = 1$ .
- Provide the Boolean function using the minterm representation.
- Sketch the logic circuit using ONLY 2-input NAND gates. Tip: try to simplify the function using XOR gates.

| x | y | z | w | f |
|---|---|---|---|---|
| 0 | 0 | 0 | 0 | 0 |
| 0 | 0 | 0 | 1 | 1 |
| 0 | 0 | 1 | 0 | 1 |
| 0 | 0 | 1 | 1 | 0 |
| 0 | 1 | 0 | 0 | 1 |
| 0 | 1 | 0 | 1 | 0 |
| 0 | 1 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 | 1 |
| 1 | 0 | 0 | 1 | 0 |
| 1 | 0 | 1 | 0 | 0 |
| 1 | 0 | 1 | 1 | 1 |
| 1 | 1 | 0 | 0 | 0 |
| 1 | 1 | 0 | 1 | 1 |
| 1 | 1 | 1 | 0 | 1 |
| 1 | 1 | 1 | 1 | 0 |

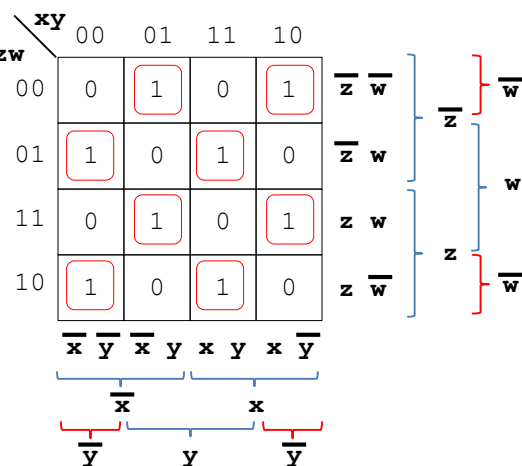

$$f = \bar{x}\bar{y}\bar{z}w + \bar{x}\bar{y}z\bar{w} + \bar{x}y\bar{z}\bar{w} + \bar{x}yzw + x\bar{y}\bar{z}\bar{w} + x\bar{y}z\bar{w} + x\bar{y}\bar{z}w + x\bar{y}zw$$



$$f = \bar{x}\bar{y}(z \oplus w) + \bar{x}y(\overline{z \oplus w}) + xy(z \oplus w) + x\bar{y}(\overline{z \oplus w})$$


$$f = (\bar{x} \oplus y)(z \oplus w) + (x \oplus y)(\overline{z \oplus w})$$

$$f = (x \oplus y) \oplus (z \oplus w) = (x \oplus y \oplus z \oplus w)$$

$$g = \bar{x}\bar{y} + x\bar{y}$$

III

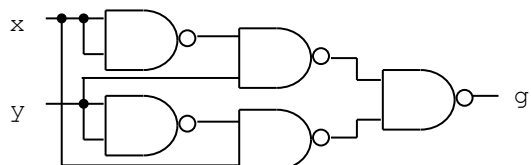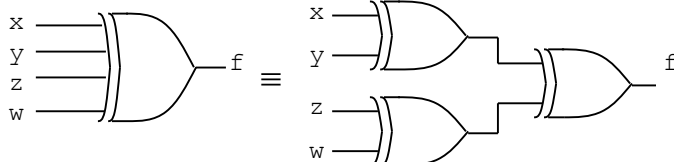

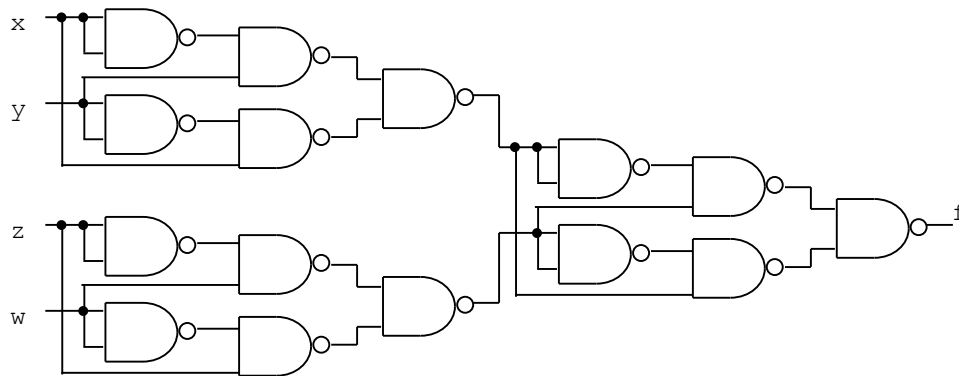


### PROBLEM 4 (20 PTS)

a) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (5 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( a, b, c: in std_logic;
          f: out std_logic);
end circ;

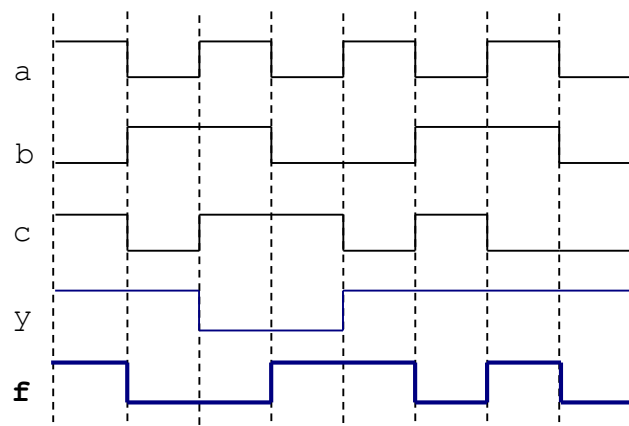architecture st of circ is
    signal x, y: std_logic;
begin
    x <= not(a xor b);
    y <= x nand c;
    f <= y xor (not a);
end st;
```




b) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (10 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity wav is
    port ( a, b, c: in std_logic;
          f: out std_logic);
end wav;

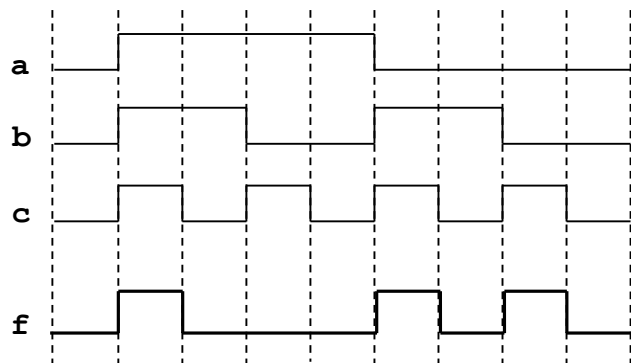
architecture st of wav is
begin
    f <= (not(a) and c) or (b and c);
end st;
```





| a | b | c | f |
|---|---|---|---|
| 0 | 0 | 0 | 0 |
| 0 | 0 | 1 | 1 |
| 0 | 1 | 0 | 0 |
| 0 | 1 | 1 | 1 |
| 1 | 0 | 0 | 0 |
| 1 | 0 | 1 | 0 |
| 1 | 1 | 0 | 0 |
| 1 | 1 | 1 | 1 |

| c | ab |    |    |    |
|---|----|----|----|----|
|   | 00 | 01 | 11 | 10 |
| 0 | 0  | 0  | 0  | 0  |
| 1 | 1  | 1  | 1  | 0  |

$$f = \bar{a}c + bc$$

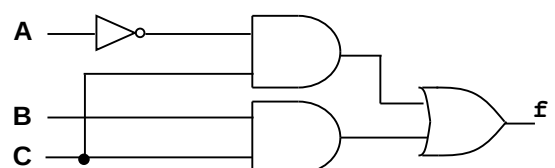


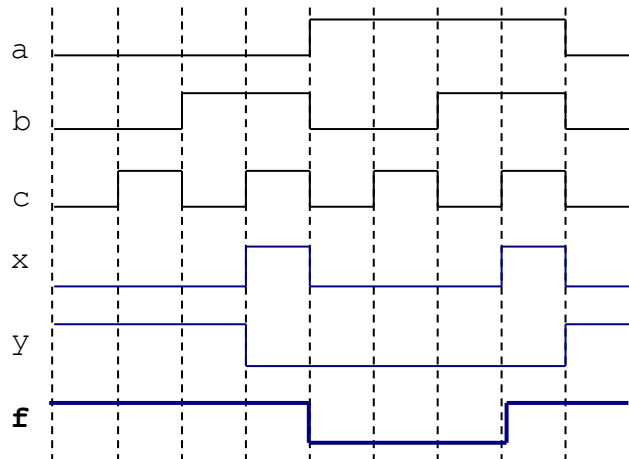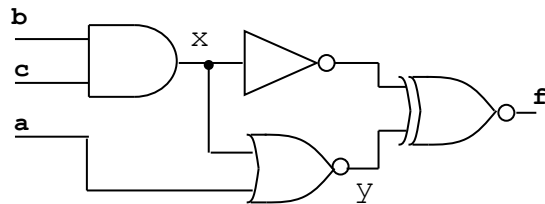c) Complete the timing diagram of the following circuit: (5 pts)



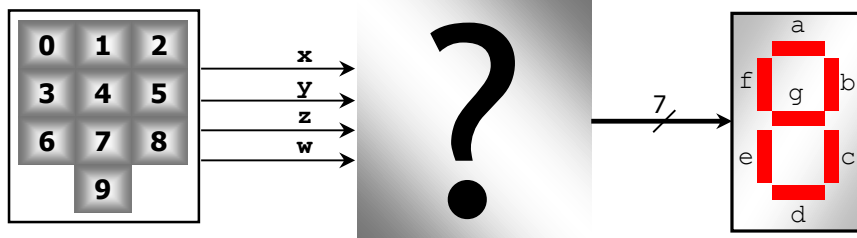
### PROBLEM 5 (30 PTS)

- A numeric keypad produces a 4-bit code as shown below. We want to design a logic circuit that converts each 4-bit code to a 7-segment code, where each segment is an LED: A LED is ON if it is given a logic '1'. A LED is OFF if it is given a logic '0'.
- Complete the truth table for each output ( $a, b, c, d, e, f, g$ ).
- Provide the simplified expression for each output ( $a, b, c, d, e, f, g$ ). Use Karnaugh maps for  $a, b, c, d, e$  and the Quine-McCluskey algorithm for  $f, g$ . Note it is safe to assume that the codes 1010 to 1111 will not be produced by the keypad.



| Value | X | Y | Z | W | a | b | c | d | e | f | g |
|-------|---|---|---|---|---|---|---|---|---|---|---|
| 0     | 0 | 0 | 0 | 0 |   |   |   |   |   |   |   |
| 1     | 0 | 0 | 0 | 1 |   |   |   |   |   |   |   |
| 2     | 0 | 0 | 1 | 0 |   |   |   |   |   |   |   |
| 3     | 0 | 0 | 1 | 1 |   |   |   |   |   |   |   |
| 4     | 0 | 1 | 0 | 0 |   |   |   |   |   |   |   |
| 5     | 0 | 1 | 0 | 1 |   |   |   |   |   |   |   |
| 6     | 0 | 1 | 1 | 0 |   |   |   |   |   |   |   |
| 7     | 0 | 1 | 1 | 1 |   |   |   |   |   |   |   |
| 8     | 1 | 0 | 0 | 0 |   |   |   |   |   |   |   |
| 9     | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
|       |   |   |   |   |   |   |   |   |   |   |   |
|       |   |   |   |   |   |   |   |   |   |   |   |
|       |   |   |   |   |   |   |   |   |   |   |   |
|       |   |   |   |   |   |   |   |   |   |   |   |
|       |   |   |   |   |   |   |   |   |   |   |   |
|       |   |   |   |   |   |   |   |   |   |   |   |
|       |   |   |   |   |   |   |   |   |   |   |   |
|       |   |   |   |   |   |   |   |   |   |   |   |
|       |   |   |   |   |   |   |   |   |   |   |   |

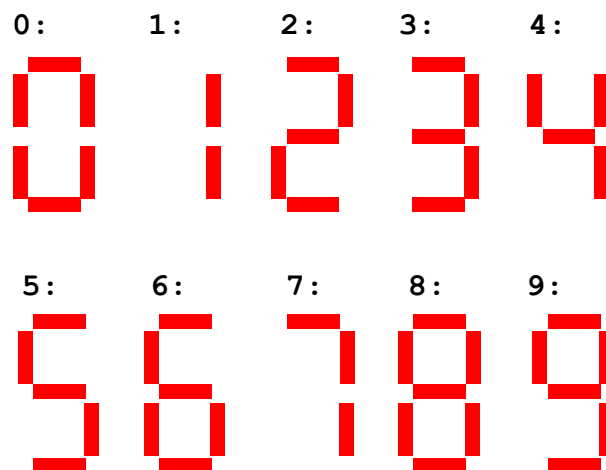

| Value | x | y | z | w | a | b | c | d | e | f | g |
|-------|---|---|---|---|---|---|---|---|---|---|---|
| 0     | 0 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 |
| 1     | 0 | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 0 | 0 | 0 |
| 2     | 0 | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 |
| 3     | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 1 |
| 4     | 0 | 1 | 0 | 0 | 0 | 1 | 1 | 0 | 0 | 1 | 1 |
| 5     | 0 | 1 | 0 | 1 | 1 | 0 | 1 | 1 | 0 | 1 | 1 |
| 6     | 0 | 1 | 1 | 0 | 1 | 0 | 1 | 1 | 1 | 1 | 1 |
| 7     | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 0 | 0 | 0 | 0 |
| 8     | 1 | 0 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 1 | 1 |
| 9     | 1 | 0 | 0 | 1 | 1 | 1 | 1 | 1 | 0 | 1 | 1 |
|       | 1 | 0 | 1 | 0 | X | X | X | X | X | X | X |
|       | 1 | 0 | 1 | 1 | X | X | X | X | X | X | X |
|       | 1 | 1 | 0 | 0 | X | X | X | X | X | X | X |
|       | 1 | 1 | 0 | 1 | X | X | X | X | X | X | X |
|       | 1 | 1 | 1 | 0 | X | X | X | X | X | X | X |
|       | 1 | 1 | 1 | 1 | X | X | X | X | X | X | X |

$$a = \bar{y}\bar{w} + wy + x + z$$

$$b = \bar{y} + \bar{z}\bar{w} + zw$$

$$c = y + \bar{z} + w$$

$$d = x + z\bar{w} + \bar{y}z + \bar{w}\bar{y} + \bar{z}wy$$

$$e = \bar{w}\bar{y} + z\bar{w}$$

a

| xy \ zw | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 0  | X  | 1  |
| 01      | 0  | 1  | X  | 1  |
| 11      | 1  | 1  | X  | X  |
| 10      | 1  | 1  | X  | X  |

b

| xy \ zw | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 1  | X  | 1  |
| 01      | 1  | 0  | X  | 1  |
| 11      | 1  | 1  | X  | X  |
| 10      | 1  | 0  | X  | X  |

c

| xy \ zw | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 1  | X  | 1  |
| 01      | 1  | 1  | X  | 1  |
| 11      | 1  | 1  | X  | X  |
| 10      | 0  | 1  | X  | X  |

d

| xy \ zw | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 0  | X  | 1  |
| 01      | 0  | 1  | X  | 1  |
| 11      | 1  | 0  | X  | X  |
| 10      | 1  | 1  | X  | X  |

e

| xy \ zw | 00 | 01 | 11 | 10 |
|---------|----|----|----|----|
| 00      | 1  | 0  | X  | 1  |
| 01      | 0  | 0  | X  | 0  |
| 11      | 0  | 0  | X  | X  |
| 10      | 1  | 1  | X  | X  |

$$f = \sum m(0,4,5,6,8,9) + \sum d(10,11,12,13,14,15).$$

| Number of ones | 4-literal implicants                                                                         | 3-literal implicants                                                                                                                                                                     | 2-literal implicants                                                                                                                                                                                                                                                                                                                                                                                                               | 1-literal implicants |
|----------------|----------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------------|----------------------|
| 0              | $m_0 = 0000$ ✓                                                                               | $m_{0,4} = 0-00$ ✓<br>$m_{0,8} = -000$ ✓                                                                                                                                                 | $m_{0,4,8,12} = --00$<br><del><math>m_{0,8,4,12} = --00</math></del>                                                                                                                                                                                                                                                                                                                                                               |                      |
| 1              | $m_4 = 0100$ ✓<br>$m_8 = 1000$ ✓                                                             | $m_{4,5} = 010-$ ✓<br>$m_{4,6} = 01-0$ ✓<br>$m_{4,12} = -100$ ✓<br>$m_{8,9} = 100-$ ✓<br>$m_{8,10} = 10-0$ ✓<br>$m_{8,12} = 1-00$ ✓                                                      | <del><math>m_{4,5,12,13} = -10-</math></del><br><del><math>m_{4,12,5,13} = -10-</math></del><br><del><math>m_{4,6,12,14} = -1-0</math></del><br><del><math>m_{4,12,6,14} = -1-0</math></del><br>$m_{8,9,10,11} = 10--$ ✓<br><del><math>m_{8,10,9,11} = 10--</math></del><br>$m_{8,9,12,13} = 1-0-$ ✓<br><del><math>m_{8,12,9,13} = 1-0-</math></del><br>$m_{8,10,12,14} = 1--0$ ✓<br><del><math>m_{8,12,10,14} = 1--0</math></del> |                      |
| 2              | $m_5 = 0101$ ✓<br>$m_6 = 0110$ ✓<br>$m_9 = 1001$ ✓<br>$m_{10} = 1010$ ✓<br>$m_{12} = 1100$ ✓ | $m_{5,13} = -101$ ✓<br>$m_{6,14} = -110$ ✓<br>$m_{9,11} = 10-1$ ✓<br>$m_{9,13} = 1-01$ ✓<br>$m_{10,11} = 101-$ ✓<br>$m_{10,14} = 1-10$ ✓<br>$m_{12,13} = 110-$ ✓<br>$m_{12,14} = 11-0$ ✓ | $m_{9,13,11,15} = 1--1$ ✓<br>$m_{10,14,11,15} = 1-1-$ ✓                                                                                                                                                                                                                                                                                                                                                                            |                      |
| 3              | $m_{11} = 1011$ ✓<br>$m_{13} = 1101$ ✓<br>$m_{14} = 1110$ ✓                                  | $m_{11,15} = 1-11$ ✓                                                                                                                                                                     |                                                                                                                                                                                                                                                                                                                                                                                                                                    |                      |
| 4              | $m_{15} = 1111$ ✓                                                                            |                                                                                                                                                                                          |                                                                                                                                                                                                                                                                                                                                                                                                                                    |                      |

$$f = \bar{z}\bar{w} + y\bar{z} + y\bar{w} + x\bar{y} + x$$

| Prime Implicants            |                  | Minterms |   |          |          |   |          |
|-----------------------------|------------------|----------|---|----------|----------|---|----------|
|                             |                  | 0        | 4 | 5        | 6        | 8 | 9        |
| $m_{0,4,8,12}$              | $\bar{z}\bar{w}$ | <b>X</b> | X |          |          | X |          |
| $m_{4,5,12,13}$             | $y\bar{z}$       |          | X | <b>X</b> |          |   |          |
| $m_{4,6,12,14}$             | $y\bar{w}$       |          | X |          | <b>X</b> |   |          |
| $m_{8,9,10,11}$             | $x\bar{y}$       |          |   |          |          | X | <b>X</b> |
| $m_{8,10,12,14,9,13,11,15}$ | $x$              |          |   |          |          | X | <b>X</b> |

$$f = \bar{z}\bar{w} + y\bar{z} + y\bar{w} + x$$

- $g = \sum m(2,3,4,5,6,8,9) + \sum d(10,11,12,13,14,15)$ .  
Too many minterms. We better optimize:  $\bar{g} = \sum m(0,1,7) + \sum d(10,11,12,13,14,15)$

| Number of ones | 4-literal implicants                                                          | 3-literal implicants                                                                         | 2-literal implicants                                                                                                                                      | 1-literal implicants |
|----------------|-------------------------------------------------------------------------------|----------------------------------------------------------------------------------------------|-----------------------------------------------------------------------------------------------------------------------------------------------------------|----------------------|
| 0              | $m_0 = 0000$ ✓                                                                | $m_{0,1} = 000-$                                                                             |                                                                                                                                                           |                      |
| 1              | $m_1 = 0001$                                                                  |                                                                                              |                                                                                                                                                           |                      |
| 2              | $m_{10} = 1010$ ✓<br>$m_{12} = 1100$ ✓                                        | $m_{10,11} = 101-$ ✓<br>$m_{10,14} = 1-10$ ✓<br>$m_{12,13} = 110-$ ✓<br>$m_{12,14} = 11-0$ ✓ | $m_{10,14,11,15} = 1-1-$<br><del><math>m_{10,11,14,15} = 1-1</math></del> ✓<br>$m_{12,14,13,15} = 11--$<br><del><math>m_{12,13,14,15} = 11</math></del> ✓ |                      |
| 3              | $m_7 = 0111$ ✓<br>$m_{11} = 1011$ ✓<br>$m_{13} = 1101$ ✓<br>$m_{14} = 1110$ ✓ | $m_{7,15} = -111$<br>$m_{11,15} = 1-11$ ✓<br>$m_{13,15} = 11-1$ ✓<br>$m_{14,15} = 111-$ ✓    |                                                                                                                                                           |                      |
| 4              | $m_{15} = 1111$ ✓                                                             |                                                                                              |                                                                                                                                                           |                      |

$$\bar{g} = \bar{x}\bar{y}\bar{z}w + \bar{x}\bar{y}z + yzw + xz + xy$$

| Prime Implicants  |                          | Minterms |   |          |
|-------------------|--------------------------|----------|---|----------|
|                   |                          | 0        | 1 | 7        |
| $m_1$             | $\bar{x}\bar{y}\bar{z}w$ |          | X |          |
| $m_{0,1}$         | $\bar{x}\bar{y}z$        | <b>X</b> | X |          |
| $m_{7,15}$        | $yzw$                    |          |   | <b>X</b> |
| $m_{10,14,11,15}$ | $xz$                     |          |   |          |
| $m_{12,14,13,15}$ | $xy$                     |          |   |          |

$$\bar{g} = \bar{x}\bar{y}z + yzw \quad \Rightarrow \quad g = (x + y + z)(\bar{y} + \bar{z} + \bar{w})$$