

# Solutions - Homework 4

(Due date: March 31<sup>st</sup> @ 5:30 pm)


Presentation and clarity are very important! Show your procedure!

## PROBLEM 1 (20 PTS)

- Design a counter using a Finite State Machine (FSM):


*Counter features:*

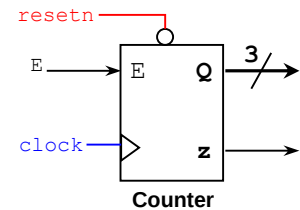- ✓ Count: **000**, 010, 111, 011, 110, 100, 001, 101, **000**, 010, 111, ...
- ✓ *resetn*: Asynchronous active-low input signal. It initializes the count to "000"
- ✓ Input *E*: Synchronous input that increases the count when it is set to '1'.
- ✓ output *z*: It becomes '1' when the count is 101.



- Provide the State Diagram (any representation), State Table, and the Excitation Table. Is this a Mealy or a Moore machine? Why? (10 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (5 pts)

- State Diagram and State Table:*

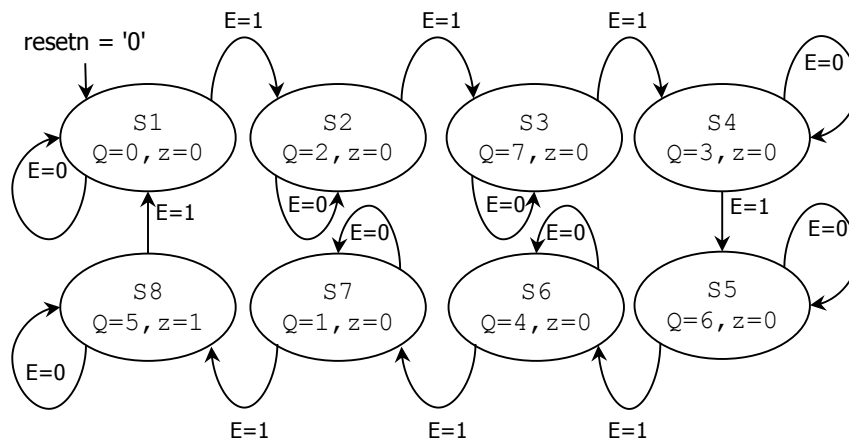

| E | PRESENT STATE | NEXT STATE | z |
|---|---------------|------------|---|
|   |               |            |   |
| 0 | S1            | S1         | 0 |
| 0 | S2            | S2         | 0 |
| 0 | S3            | S3         | 0 |
| 0 | S4            | S4         | 0 |
| 0 | S5            | S5         | 0 |
| 0 | S6            | S6         | 0 |
| 0 | S7            | S7         | 0 |
| 0 | S8            | S8         | 1 |
| 1 | S1            | S2         | 0 |
| 1 | S2            | S3         | 0 |
| 1 | S3            | S4         | 0 |
| 1 | S4            | S5         | 0 |
| 1 | S5            | S6         | 0 |
| 1 | S6            | S7         | 0 |
| 1 | S7            | S8         | 0 |
| 1 | S8            | S1         | 1 |

The output 'z' only depends on the present state  $\Rightarrow$  Moore FSM.

- State Assignment and Excitation Table:*

- ✓ S1: Q = 000
- ✓ S2: Q = 010
- ✓ S3: Q = 111
- ✓ S4: Q = 011
- ✓ S5: Q = 110
- ✓ S6: Q = 100
- ✓ S7: Q = 001
- ✓ S8: Q = 101

| E | PRESENT STATE |       |       | NEXT STATE |       |       | z |
|---|---------------|-------|-------|------------|-------|-------|---|
|   | $Q_2$         | $Q_1$ | $Q_0$ | $Q_2$      | $Q_1$ | $Q_0$ |   |
|   | $(t)$         |       |       | $(t+1)$    |       |       |   |
| 0 | 0             | 0     | 0     | 0          | 0     | 0     | 0 |
| 0 | 0             | 0     | 1     | 0          | 1     | 0     | 0 |
| 0 | 0             | 1     | 1     | 1          | 1     | 1     | 0 |
| 0 | 0             | 0     | 1     | 0          | 1     | 1     | 0 |
| 0 | 0             | 1     | 1     | 1          | 1     | 0     | 0 |
| 0 | 0             | 1     | 0     | 1          | 0     | 0     | 0 |
| 0 | 0             | 0     | 1     | 0          | 0     | 1     | 0 |
| 0 | 0             | 1     | 0     | 1          | 0     | 1     | 1 |
| 1 | 0             | 0     | 0     | 0          | 1     | 0     | 0 |
| 1 | 0             | 1     | 0     | 1          | 1     | 1     | 0 |
| 1 | 1             | 1     | 1     | 0          | 1     | 1     | 0 |
| 1 | 1             | 0     | 1     | 1          | 1     | 0     | 0 |
| 1 | 1             | 1     | 1     | 1          | 0     | 0     | 0 |
| 1 | 1             | 1     | 0     | 0          | 0     | 1     | 0 |
| 1 | 0             | 0     | 1     | 1          | 0     | 1     | 0 |
| 1 | 1             | 0     | 1     | 0          | 0     | 0     | 1 |

Excitation equations and minimization:

$$Q_2(t+1) = \bar{E}Q_2 + E\bar{Q}_2Q_0 + EQ_1\bar{Q}_0$$

$$Q_1(t+1) = Q_1Q_0 + \bar{E}Q_1 + EQ_2\bar{Q}_0$$

$$Q_0(t+1) = \bar{E}Q_0 + Q_0(\bar{Q}_1 \oplus \bar{Q}_2) + E\bar{Q}_0(Q_1 \oplus Q_2)$$

$$z = Q_2\bar{Q}_1Q_0$$

$$Q_2(t+1)$$

| $EQ_2$   | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| $Q_1Q_0$ |    |    |    |    |
| 00       | 0  | 1  | 0  | 0  |
| 01       | 0  | 1  | 0  | 1  |
| 11       | 0  | 1  | 0  | 1  |
| 10       | 0  | 1  | 1  | 1  |

$$Q_1(t+1)$$

| $EQ_2$   | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| $Q_1Q_0$ |    |    |    |    |
| 00       | 0  | 0  | 0  | 1  |
| 01       | 0  | 0  | 0  | 0  |
| 11       | 1  | 1  | 1  | 1  |
| 10       | 1  | 1  | 0  | 1  |


$$Q_0(t+1)$$

| $EQ_2$   | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| $Q_1Q_0$ |    |    |    |    |
| 00       | 0  | 0  | 1  | 0  |
| 01       | 1  | 1  | 0  | 1  |
| 11       | 1  | 1  | 1  | 0  |
| 10       | 0  | 0  | 0  | 1  |

$$z$$


| $EQ_2$   | 00 | 01 | 11 | 10 |
|----------|----|----|----|----|
| $Q_1Q_0$ |    |    |    |    |
| 00       | 0  | 0  | 0  | 0  |
| 01       | 0  | 1  | 1  | 0  |
| 11       | 0  | 0  | 0  | 0  |
| 10       | 0  | 0  | 0  | 0  |

Circuit Implementation:

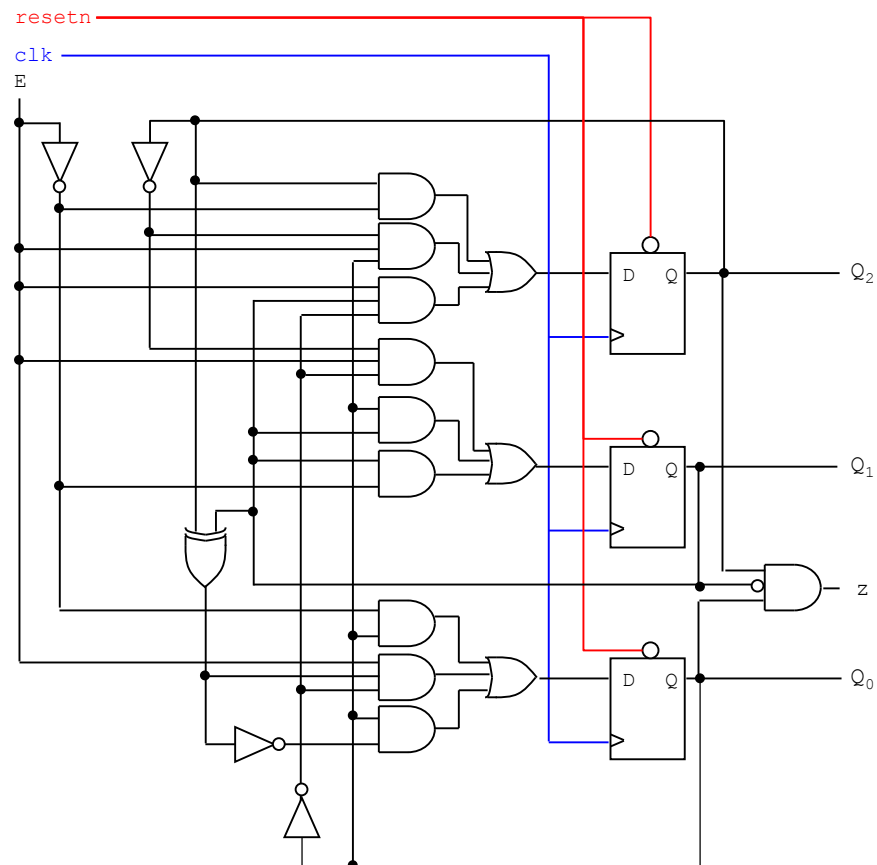


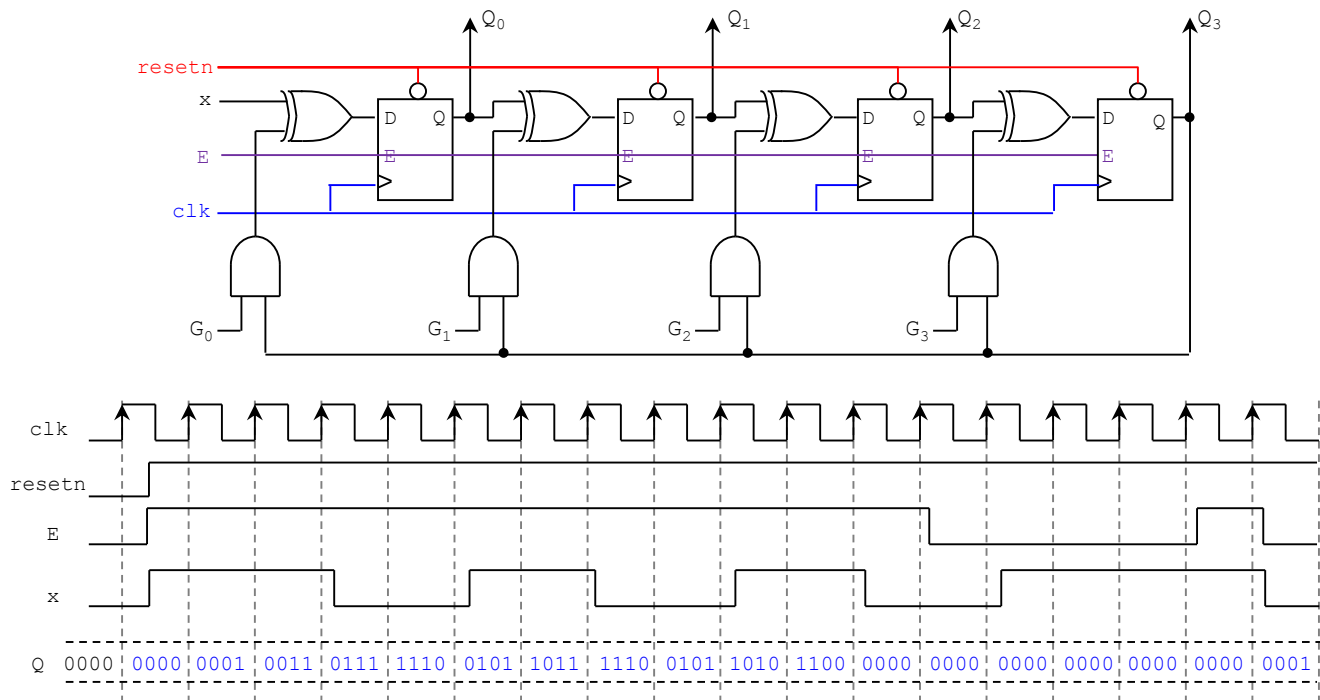
## PROBLEM 2 (15 PTS)

- Complete the timing diagram of the following circuit.  $G = G_3G_2G_1G_0 = 1001$ ,  $Q = Q_3Q_2Q_1Q_0$



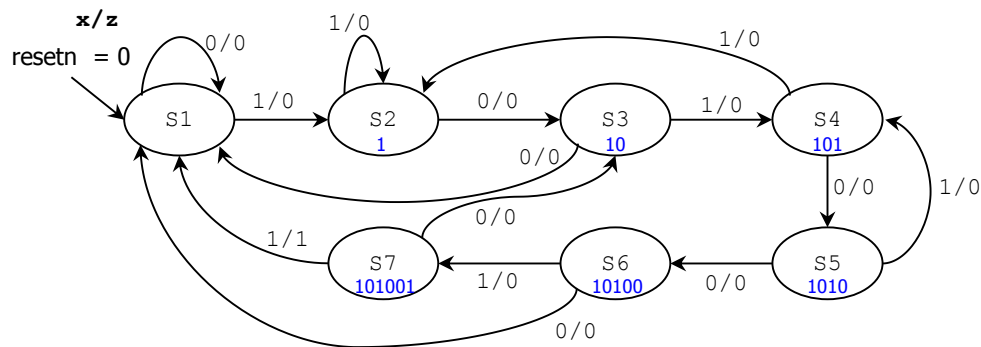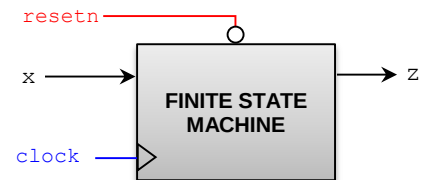
## PROBLEM 3 (30 PTS)


- Sequence detector (with overlap): (10 pts)  
Draw the state diagram (any representation) of a circuit (with an input  $x$ ) that detects the following sequence: 1010011. The detector must assert an output  $z$  when the sequence is detected.



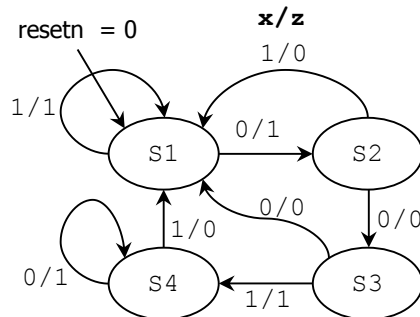- Complete the timing diagram of the following FSM. Is this a Mealy or a Moore machine? Why? (5 pts)



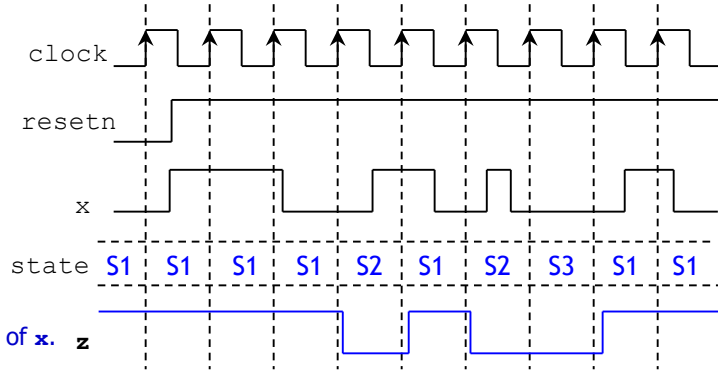
On S4 and S3, the output  $z$  depends on the value of  $x$ . Thus, it is a Mealy machine.



- Provide the state diagram (in ASM form) and complete the timing diagram of the FSM whose VHDL description is listed below. (15 pts)

```
library ieee;
use ieee.std_logic_1164.all;

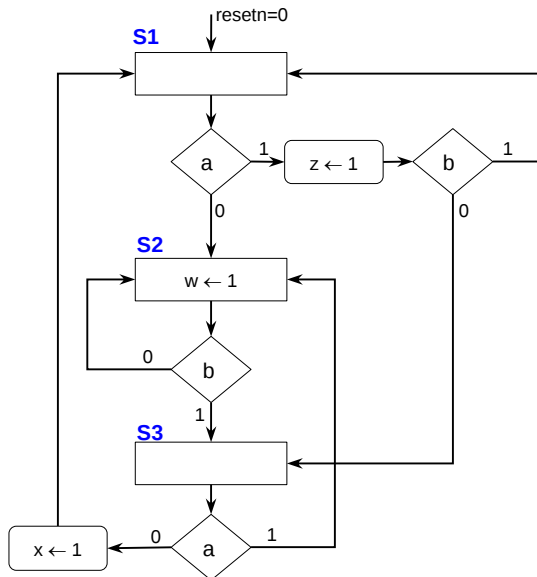entity circ is
    port ( clk, resetn: in std_logic;
          a, b: in std_logic;
          x, w, z: out std_logic);
end circ;
```



```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, a, b)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if a = '1' then
                        if b = '0' then y <= S3; else y <= S1; end if;
                    else
                        y <= S2;
                    end if;
                when S2 =>
                    if b = '1' then y <= S3; else y <= S2; end if;
                when S3 =>
                    if a = '1' then y <= S2; else y <= S1; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, a, b)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if a = '1' then z <= '1'; end if;
            when S2 => w <= '1';
            when S3 => if a = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```

