

# Homework 1

(Due date: January 24<sup>th</sup> @ 5:30 pm)  
 Presentation and clarity are very important!

## PROBLEM 1 (25 PTS)

a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (9 pts)

$$✓ F = A(C + \bar{B}) + \bar{A}$$

$$✓ F = (Y + Z)(\bar{Y} + X)$$


$$✓ F(X, Y, Z) = \prod(M_0, M_1, M_4, M_5)$$

b) For the following Truth table: (6 pts)

- Provide the Boolean function using the Canonical Sum of Products (SOP), and Product of Sums (POS).
- Express the Boolean function using the minterms and maxterms representations.
- Sketch the logic circuit as Canonical Sum of Products and Product of Sums.

x	y	z	f
0	0	0	0
0	0	1	1
0	1	0	0
0	1	1	1
1	0	0	1
1	0	1	0
1	1	0	1
1	1	1	1

 c) Complete the truth table for a circuit (active high inputs, active high outputs) that activates an output ( $f=1$ ) when the decimal value of the 4 inputs is equal to 0, 3, 5, 6, 9, 12, or 13. Then, simplify the function using Karnaugh maps. (10 pts)




## PROBLEM 2 (15 PTS)

a) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (5 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( a, b, c: in std_logic;
          f: out std_logic);
end circ;

 architecture st of circ is
    signal x, y: std_logic;
begin
    x <= a and b;
    y <= x nand c;
    f <= y xor (not b);
end st;
```




b) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the logic circuit that generates this waveform. Then, complete the VHDL code. (10 pts)

```
library ieee;
use ieee.std_logic_1164.all;



entity circ is
    port ( a, b, c: in std_logic;
          f: out std_logic);
end circ;

 architecture st of circ is
-- ???
begin
-- ???
end st;
```



  
**PROBLEM 3 (10 PTS)**

- For the following 4-bit bidirectional port, complete the timing diagram (signals *DO* and *DATA*):



 
**PROBLEM 4 (10 PTS)**

- A 24-bit address line in a  $\mu$ processor handles up to  $2^{24} = 16\text{ MB}$  of addresses, each address containing one-byte of information. We want to connect four 4MB memory chips to the  $\mu$ processor.
- Sketch the circuit that: i) addresses the memory chips, and ii) enables only one memory chip (via CE: chip enable) when the address falls in the corresponding range. Example: if  $address = 0x5FFFFFF$ ,  $\rightarrow$  only memory chip 2 is enabled (CE=1). If  $address = 0xD00FA0$ ,  $\rightarrow$  only memory chip 4 is enabled.
- Complete the number of bits '??' required for each 4MB memory chip.



 **PROBLEM 5 (15 PTS)**

- Complete the timing diagram of the circuit shown below:



**PROBLEM 6 (15 PTS)**

- In these problems, you MUST show your conversion procedure.
  - a) Convert the following unsigned integer numbers to their binary and hexadecimal representation. (4 pts)  
 124, 115, 128, 255.
  - b) What is the minimum number of bits required to represent: (3 pts)
    - ✓ 50,000 colors?
    - ✓ 32679 symbols?
    - ✓ 65536 memory addresses in a computer?
  - c) A microprocessor can handle addresses from 0x0000 to 0x1FFF. How many bits do we need to represent those addresses? (2 pts).
  - d) Complete the following table. (6 pts)

Decimal	BCD	Binary number	Reflective Gray Code
128			
		10101011	
	0100 1001		
			10001001
		1110010	
	0110 0011 0001		

**PROBLEM 7 (10 PTS)**

- Complete the timing diagram of the digital circuit shown in the figure below. You must consider the propagation delays. Assume that the propagation delay of every gate is 5 ns. The initial values of the signals are specified in the figure.

