

Laboratory 1

(Due date : **002**: January 25th, **003**: January 26th)

OBJECTIVES

- ✓ Introduce VHDL Coding for FPGAs: Circuit description and testbench generation.
- ✓ Learn the Xilinx FPGA Design Flow with Vivado HL Webpack: Synthesis, Simulation, and Bitstream Generation.
- ✓ Learn how to assign FPGA I/O pins and download the bitstream onto the Nexys™-4 DDR Artix-7 FPGA Board.

VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.


NEXYS™-4 DDR ARTIX-7 FPGA BOARD SETUP

- The Nexys-4 DDR Board can receive power from the Digilent USB-JTAG Port (J6). Connect your Board to a computer via the USB cable. If it does not turn on, connect the power supply of the Board.
- Nexys-4 DDR documentation: Available in [class website](#).

FIRST ACTIVITY (100/100)


- **RGB LED Control:** A color can be represented by a combination of red (R), green (G), and blue (B) intensities, hence RGB color. An RGB LED includes a red LED, a green LED, and a blue LED, which are controlled independently.

R	G	B	Color
0	0	0	Black
1	0	0	Red
0	1	0	Green
0	0	1	Blue
1	1	0	Yellow
1	0	1	Magenta
0	1	1	Cyan
1	1	1	White

 

- In this experiment, we control the maximum intensities of each LED using '1' as the brightest color, and '0' as the darkest color. This produces eight colors.

 - Colors are produced via six push-buttons, as shown. Pressing on a button generates a particular color. If no button is pressed, we get Black. If more than one button is pressed, we get White. The circuit '?' generates three output signals (RLED, GLED, BLED) based on the six push-buttons.



- **VIVADO DESIGN FLOW FOR FPGAs (follow this order strictly):**

- ✓ Create a new Vivado Project. Select the **XC7A100T-1CSG324 Artix-7 FPGA** device.
- ✓ Write the VHDL code for the circuit '?' (use logic gates or *with-select* description). Synthesize your circuit (Run Synthesis).
- ✓ Write the VHDL testbench to test the circuit: the circuit must generate the eight given colors (via RLED, GLED, BLED).
- ✓ Perform Functional Simulation (Run Simulation → Run Behavioral Simulation). **Demonstrate this to your TA.**
- ✓ I/O Assignment: Create the XDC file.
Nexys-4 DDR Board: Use BTNU, BTNL, BTNC, BTNR, BTND, CPU RESET as inputs, and the red, green, and blue LEDs of the LD17 component (RGB LED) as outputs. All I/Os are active high, except for CPU RESET which is active low.
- ✓ Implement your design (Run Implementation).
- ✓ Do Timing Simulation (Run Simulation → Run Post-Implementation Timing Simulation). **Demonstrate this to your TA.**
- ✓ Generate the bitstream file (Generate Bitstream).
- ✓ Download the bitstream on the FPGA (Open Hardware Manager) and test. **Demonstrate this to your TA.**

- Submit (as a .zip file) the generated files: VHDL code, VHDL testbench, and XDC file to Moodle (an assignment will be created). DO NOT submit the whole Vivado Project.

TA signature: _____

Date: _____