

Multiplier Implementation

UNSIGNED MULTIPLICATION

ITERATIVE MULTIPLIER

Sequential algorithm:

```

P ← 0, Load A,B
while B ≠ 0
  if b0 = 1 then
    P ← P + A
  end if
  left shift A
  right shift B
end while

```

Example:

```

  1 1 1 1 x
  1 1 0 1
  -----
    1 1 1 1 → P ← 0 + 1111
    0 0 0 0 → P ← 1111
    1 1 1 1 → P ← 1111 + 111100 = 1001011
    1 1 1 1 → P ← 1001011 + 1111000 = 11000011
  -----
  1 1 0 0 0 1 1

```

P ← 0, A ← 1111, B ← 1101

b₀=1 ⇒ P ← P + A = 1111. A ← 11110, B ← 110


b₀=0 ⇒ P ← P = 1111. A ← 111100, B ← 11

b₀=1 ⇒ P ← P + A = 1111 + 111100 = 1001011. A ← 1111000, B ← 1


b₀=1 ⇒ P ← P + A = 1001011 + 1111000 = 11000011. A ← 11110000, B ← 0

Iterative Multiplier Architecture: FSM + Datapath circuit.

 sclr: synchronous clear. In this case, if *sclr* = 1 and *E* = 1, the register contents are initialized to 0. The solution is computed in *M* + 1 cycles (worst-case scenario)




Example (timing diagram):

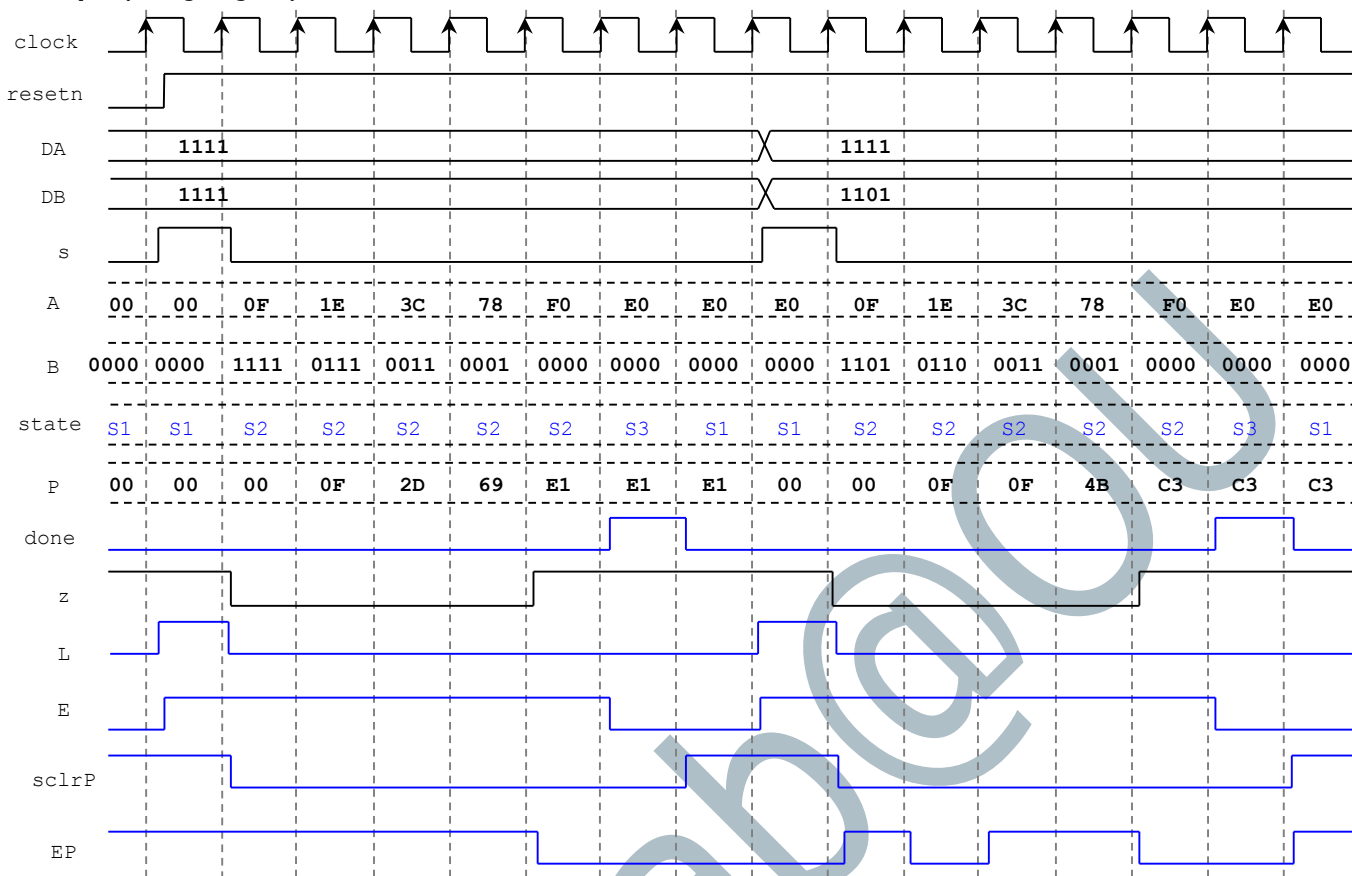

COMBINATIONAL ARRAY MULTIPLIER

 - In this unfolded version (purely combinational), we have a different hardware for every summation of two rows.



PIPELINED ARRAY MULTIPLIER

- To increase the frequency of operation, we place registers at every stage. We also include an enable and a valid output.

