


Homework 4

(Due date: November 17th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

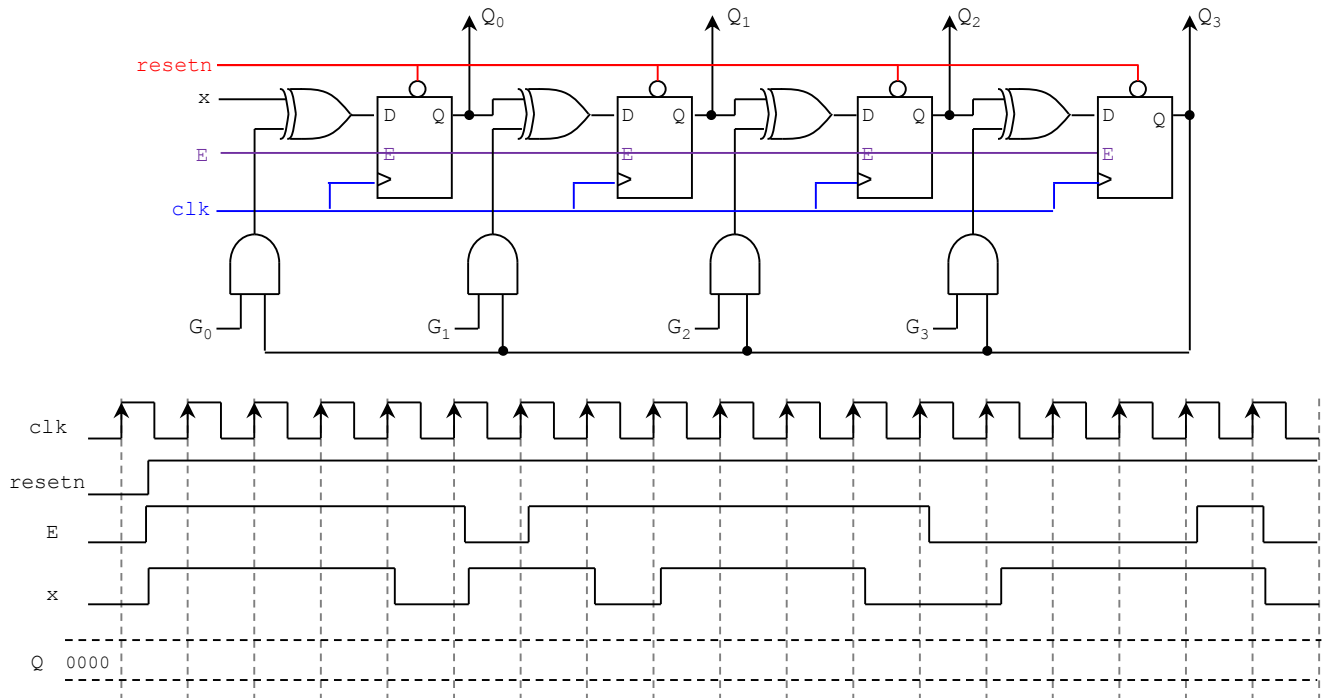PROBLEM 1 (15 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1101$, $Q = Q_3Q_2Q_1Q_0$




PROBLEM 2 (20 PTS)

- Design a counter using a Finite State Machine (FSM):

Counter features:

 
- Count: **000**, 010, 100, 110, 001, 011, 101, 111, **000**, 010, 100, ...
- resetn: Asynchronous active-low input signal. It initializes the count to '000'.
- Input E: Synchronous input that increases the count when it is set to '1'.
- output z: It becomes '1' when the count is 111.





- Provide the State Diagram (any representation), State Table, and the Excitation Table. Is this a Mealy or a Moore machine? Why? (10 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (5 pts)

 PROBLEM 3 (30 PTS)

- Sequence detector: Provide the State Diagram (any representation) and the Excitation Table of a circuit with an input x and output z . The machine has to generate $z = 1$ when it detects the sequence 0110101. Right after the sequence is detected, the circuit looks for a new sequence. (10 pts).
The signal E is an input enable: It validates the input x , i.e., if $E = 1$, x is valid, otherwise x is not valid. The figure below illustrates the behavior for a certain input stream.



  - Complete the timing diagram of the following FSM. Is this a Mealy or a Moore machine? Why? (5 pts)



- Provide the state diagram (in ASM form) and complete the timing diagram of the FSM whose VHDL description is listed below. (15 pts)

```


library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( clk, resetn: in std_logic;
        a, b: in std_logic;
        x,w,z: out std_logic);
end circ;
  
```

```


architecture behavioral of circ is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (resetn, clk, a, b)
  begin
    if resetn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if a = '1' then
            if b = '1' then y <= S3; else y <= S1; end if;
          else
            y <= S2;
          end if;
        when S2 =>
          if b = '1' then y <= S3; else y <= S2; end if;
        when S3 =>
          if a = b then y <= S3; else y <= S1; end if;
        end case;
      end if;
    end process;

   Outputs: process (y, a, b)
  begin
    x <= '0'; w <= '0'; z <= '0';
    case y is
      when S1 => if a = '1' then x <= '1'; end if;
      when S2 => w <= '1';
      when S3 => if a = b then z <= '1'; end if;
    end case;
  end process;
end behavioral;
  
```



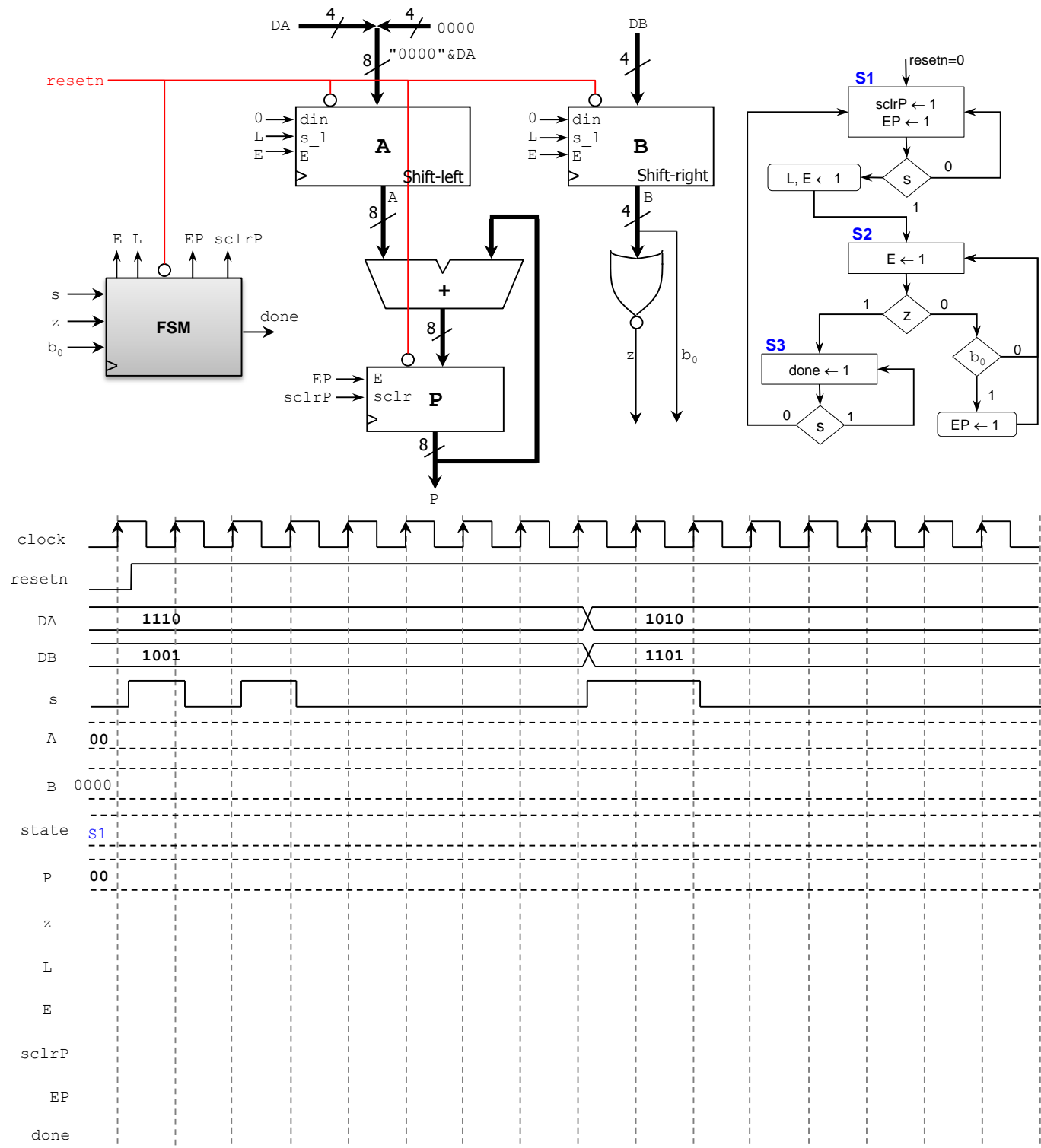PROBLEM 4 (20 PTS)

- Complete the following timing diagram (A and P are specified as hexadecimals) of the following Iterative unsigned multiplier. The circuit includes an FSM (in ASM form) and a datapath circuit.
Register (for P): *sclr*: synchronous clear. Here, if *sclr* = *E* = 1, the register contents are initialized to 0.
Parallel access shift registers (for A and B): If *E* = 1: *s_l* = 1 → Load, *s_l* = 0 → Shift



PROBLEM 5 (15 PTS)

- Attach a printout of your Project Status Report (no more than two pages, single-spaced, 2 columns). This report should contain the current status of the project. You **MUST** use the provided template (Final Project - Report Template.docx).