

Quiz 3

(November 1st @ 5:30 pm)


PROBLEM 1 (30 PTS)

- Complete the timing diagram of the circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;
```



```
entity circ is
  port ( rstn, a,b, x, clk: in std_logic;
        q: out std_logic);
end circ;
```
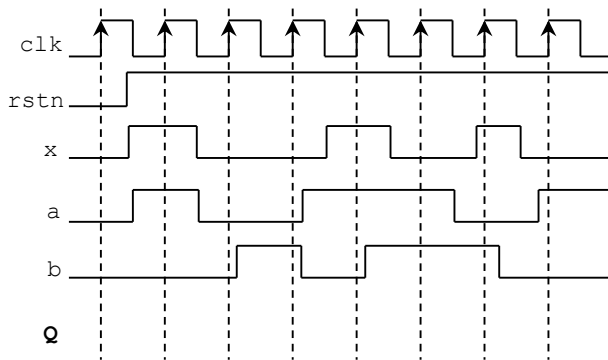
```
architecture xst of circ is
  signal qt: std_logic;
begin
  process (rstn, clk, a, b, x)
  begin
    if rstn = '0' then
      qt <= '0';
    elsif (clk'event and clk = '1') then
      if x = '0' then
        qt <= a xnor b;
      end if;
    end if;
  end process;
  q <= qt;
end xst;
```



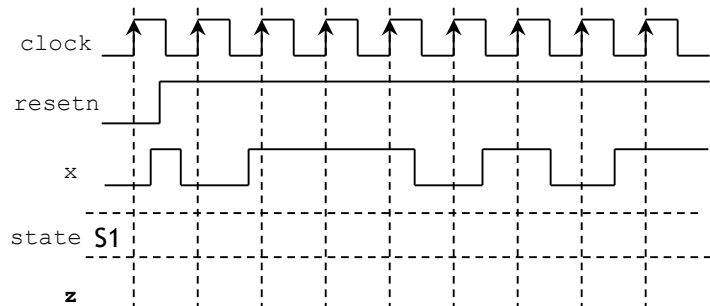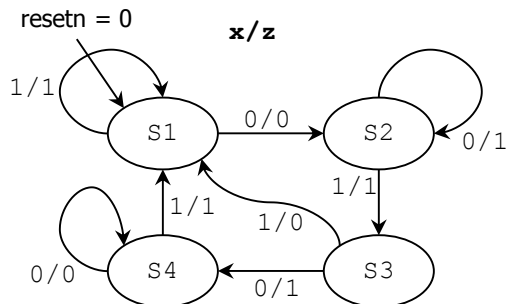PROBLEM 2 (30 PTS)

- Complete the timing diagram of the following state machine:



PROBLEM 3 (40 PTS)

- Complete the timing diagram of the following circuit:

