


# Final Exam

(December 10<sup>th</sup> @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

 
## PROBLEM 1 (12 PTS)

- Given the following circuit, complete the timing diagram.  
The LUT 6-to-6 implements the following function:  $OLUT = \lceil \sqrt{ILUT} \rceil$ , where  $ILUT$  is a 6-bit unsigned number.  
For example  $ILUT = 35 (100011_2) \rightarrow OLUT = \lceil \sqrt{35} \rceil = 6 (000110_2)$



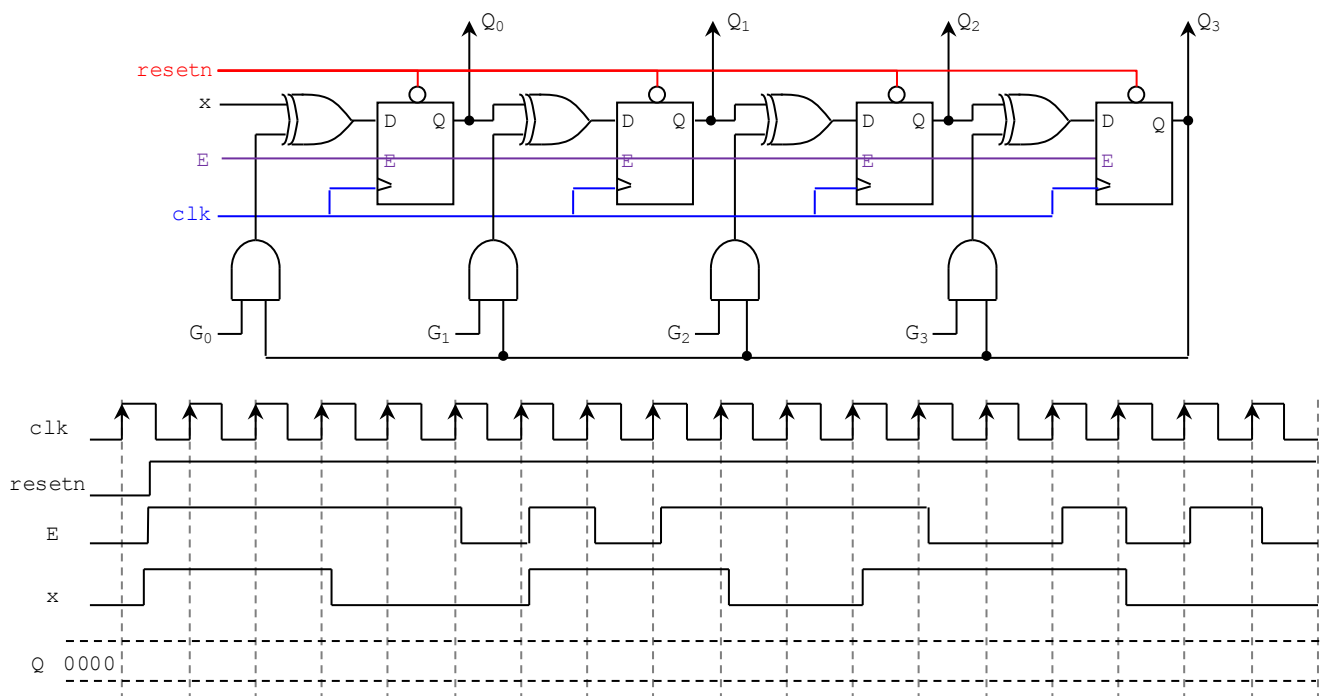
## PROBLEM 2 (12 PTS)

- Complete the timing diagram of the following circuit.  $G = G_3G_2G_1G_0 = 1001$ ,  $Q = Q_3Q_2Q_1Q_0$


 
### PROBLEM 3 (22 PTS)


- Sequence detector: The machine has to generate  $z = 1$  when it detects the sequence 1001. Once the sequence is detected, the circuit looks for a new sequence.
- The signal  $E$  is an input enable: It validates the input  $x$ , i.e., if  $E = 1$ ,  $x$  is valid, otherwise  $x$  is not valid.




- Draw the State Diagram (any representation), State Table, and the Excitation Table of this circuit with inputs  $E$  and  $x$  and output  $z$ . Is this a Mealy or a Moore machine? Why? (15 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (4 pts)
- Sketch the circuit. (3 pts)
 
### PROBLEM 4 (21 PTS)

- Given the following State Machine Diagram: (10 pts)
  - ✓ Provide the State Table and the Excitation Table.
  - ✓ Get the excitation equations and the Boolean equation for  $z$ .  
Use S1 (Q=00), S2 (Q=01), S3 (Q=10), S4 (Q=11) to encode the states.
  - ✓ Sketch the Finite State Machine circuit.



 - Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following Finite State Machine: (11 pts)



### PROBLEM 5 (15 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( clk, resetn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end circ;
```

```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p, q)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '0' then
                        y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;


                when S2 =>
                    if q = '1' then y <= S1; else y <= S3; end if;

                when S3 =>
                    if p = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '1' then
                            w <= '1';
                        if p = '0' then
                            x <= '1';
                        end if;
                    end if;

            when S2 => if p = '1' then x <= '1'; end if;
                       if q = '0' then z <= '1'; end if;

             when S3 => if p = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```



## PROBLEM 6 (18 PTS)

- Complete the timing diagram of the following digital circuit that includes an FSM (in ASM form) and a datapath circuit.

