

GIA	
□ 1 7 	
K [3	
JJ E	
H <u>II</u>	
GM C, EL	
	With VGA Output and Al Single Player
	With VGA Output and Al Single Player
	A Final Project for ECE 2700, Fall 2019
	Designers: Matthew Button, Chris Lair, Kacper Wojtowicz
	 (1) (2) (2)
FUB	

GAME DEMO: Features

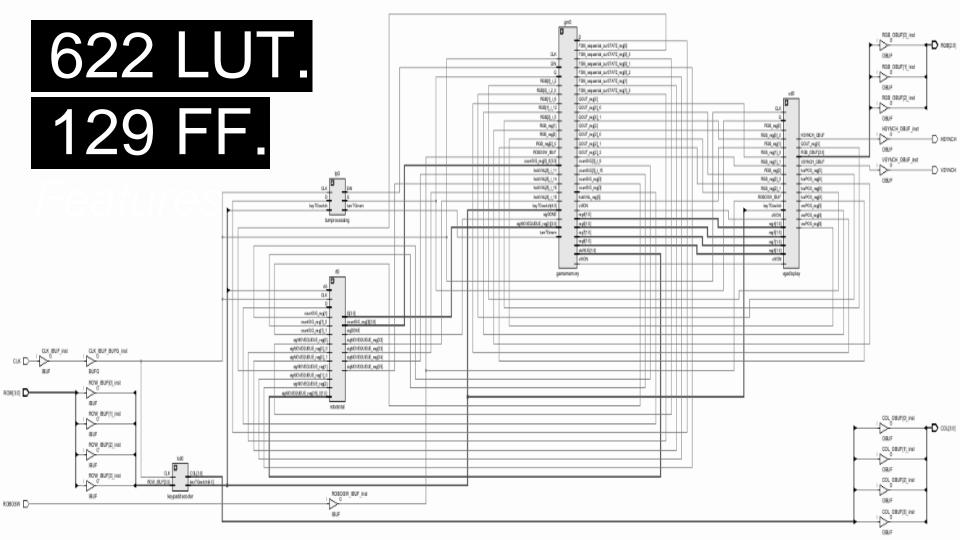- Two Player Mode Tic-Tac-Toe Game Play
- Double Move Protection
- > Win and Tie Notification
- Single Player Mode with Strategic AI
- ➤ Blazing 3-Bit Color in 640X480 Resolution at 60HZ



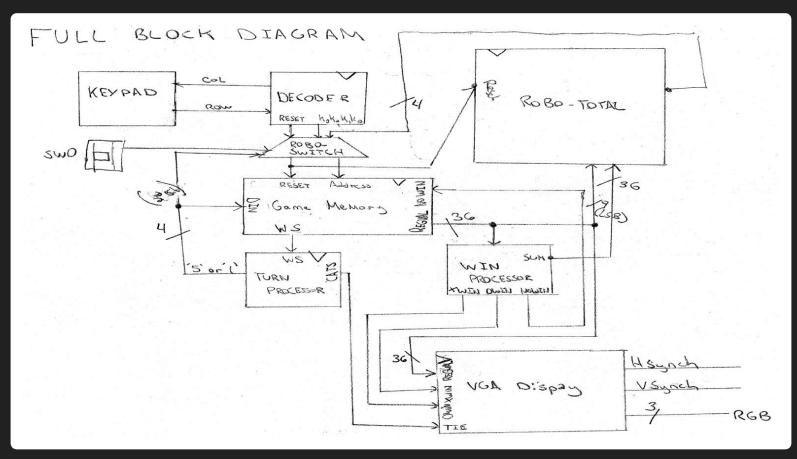

Palatable Full Block Diagram


INPUTS & OUTPUTS:

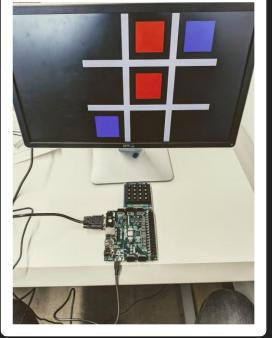Keys 1-9Switch 0D Key ResetFor One Player











VGA Plug for Output to Any Monitor

MAIN COMPONENTS: GAME MEMORY

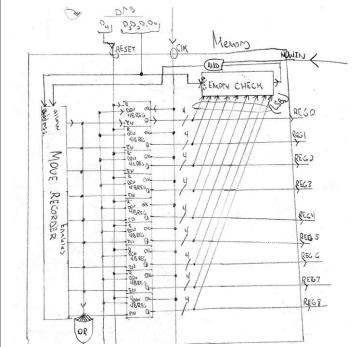- \succ Consists of 8 4-Bit
 - Registers
- Checks if Cell Empty before
 Allowing Play
- \succ Disallows Play After a Win
- Successful Memory Write Changes Turns



MAIN COMPONENTS: Turn Processor

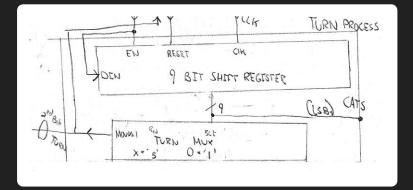


A 9-Bit Shift Register and LUT


- Shifts '1' to Vector when
 Memory Written
- Outputs '1' for X Turn '5' for
 'O' Turn (Even/Odd)


 \succ Outputs Tie if All 9 Bits '1'

MAIN COMPONENTS: VGA Display

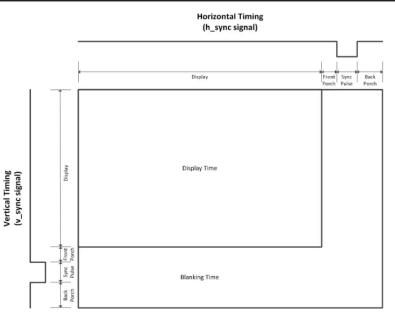

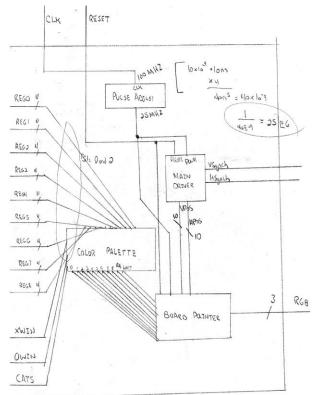Shifts Horizontal and Vertical Pixel Position ➤ Generates V-Synch & H-Synch from Positions Turns Display on In Monitor Space ➤ Defines Shapes, and Colors



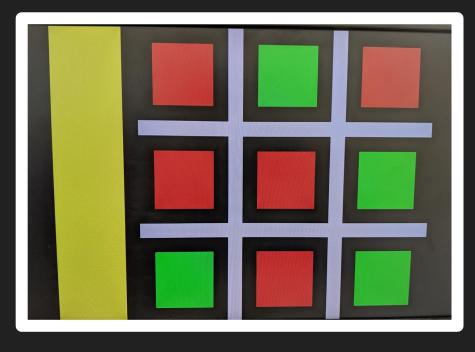


VGA Display Бюск Diagram Output



MAIN COMPONENTS: Win Processor MUJ OLI Sums Memory Values for Win Combinations (3 RW, 3 COL, 2 DIAG) \succ If sum is 15, X wins, if 3 O Wins, Otherwise No Win


Two 4-Bit Adders and Two Comparators

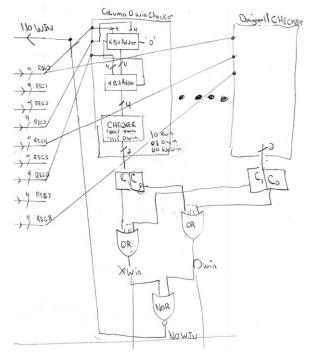

MAIN COMPONENTS: Single Player Al


- Evaluates Each Cell, Assigns Values
- ➤ Finds Lowest Value, State Machine
 - Puts Lowest Cells into Queue
- Counter Considers Choices, Selects Strategic Move
- \succ Tries to win, tries to block win, only

then employs strategic move

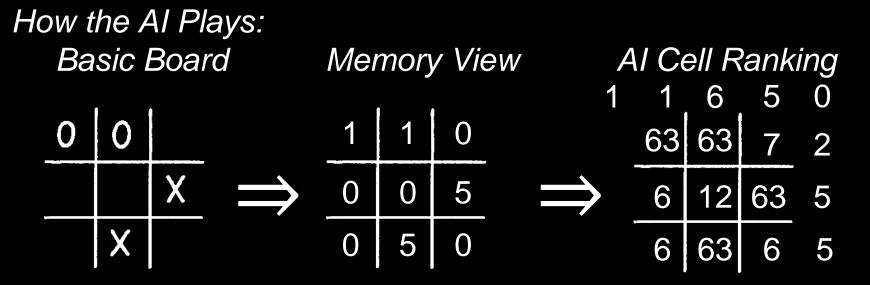


Cell Labels012345678

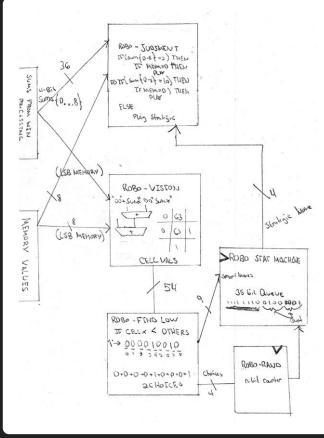Cells 3, 6, and 8 share the lowest value of '6' they are the optimal moves. '63' Represents an occupied space. Border values are win sums. Row 0 = '2' so O can win this turn.



AI Block Diagram

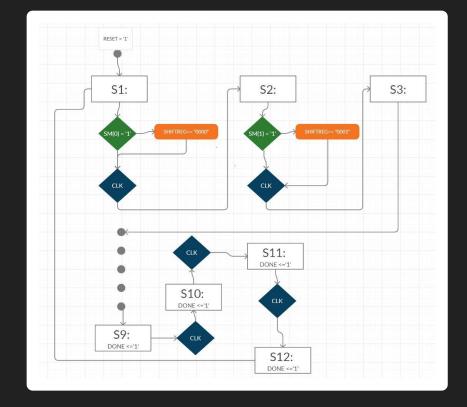

State Diagram for Robo-FSM

