

ECE 2700 Final Project

2x2 Matrix Multiplier


By: Brendan Zarycky, Dmytro Melnikov, Alec Hill, and
Eric Niezabytowski

Introduction



$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} \times \begin{pmatrix} E & F \\ G & H \end{pmatrix} = \begin{pmatrix} AE+BG & AF+BH \\ CE+DG & CF+DH \end{pmatrix}$$

Matrix Multiplier Block Diagram

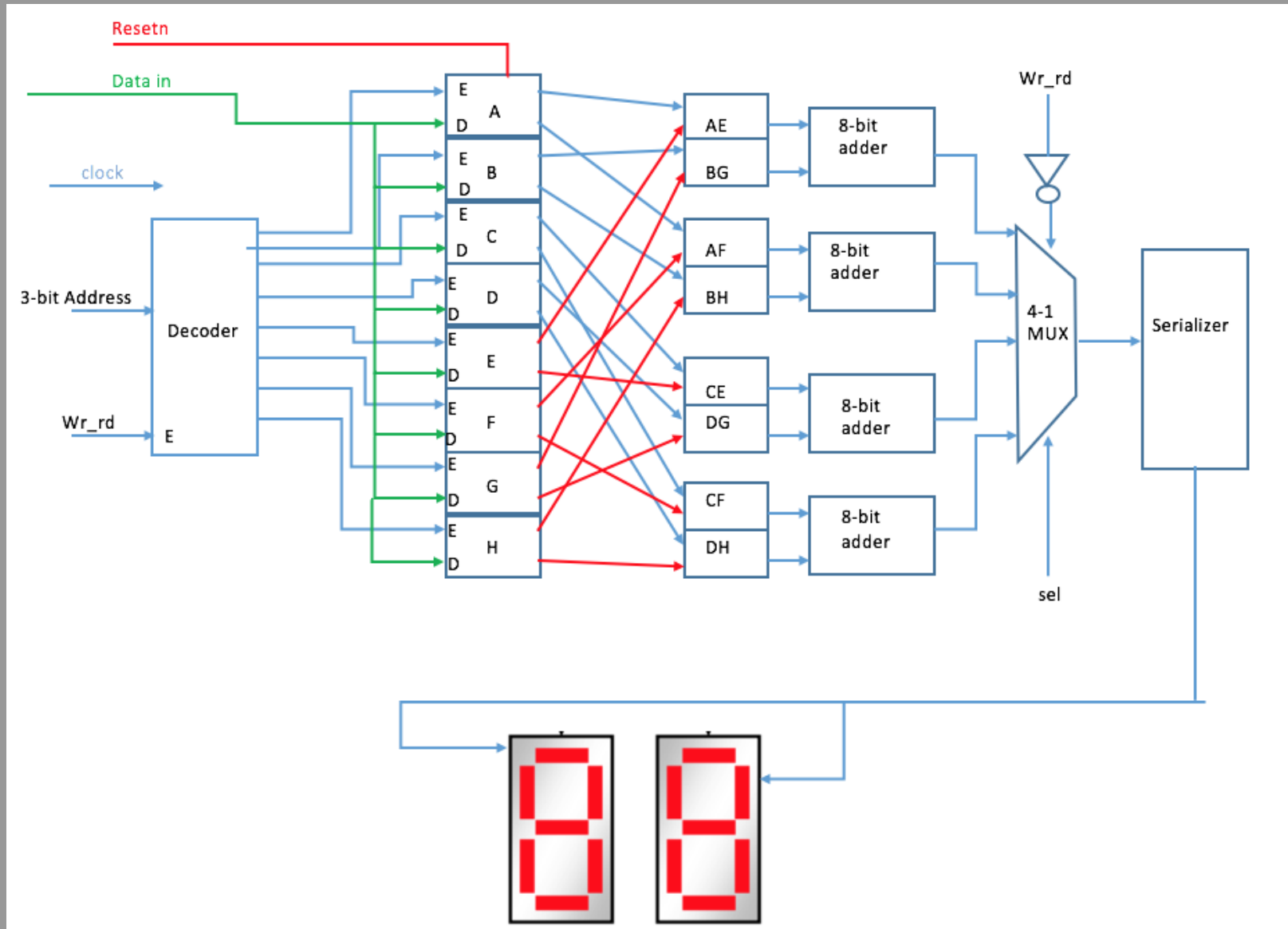


Inputting the values

Address position

Data Input Value

1	2	X	5	6
3	4		7	8

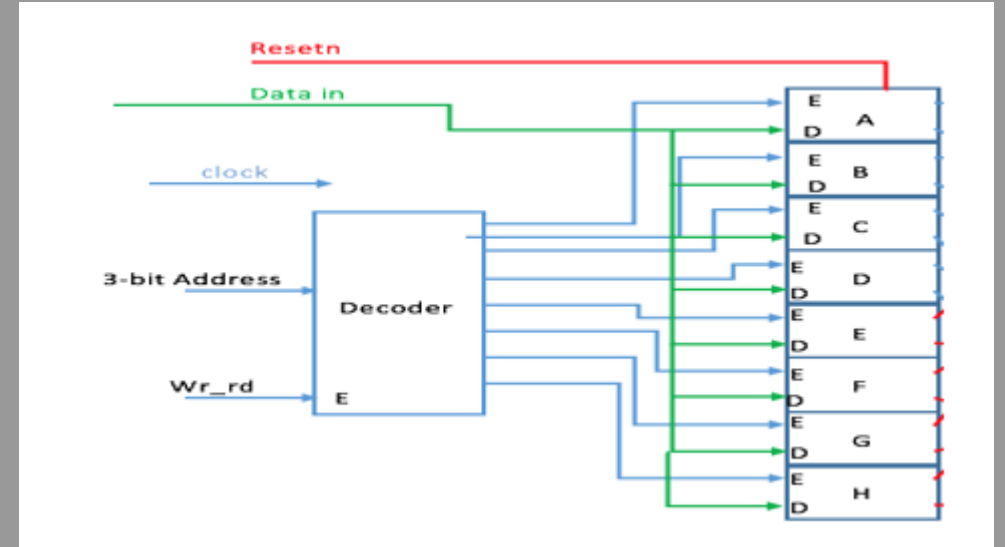

$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} \times \begin{pmatrix} E & F \\ G & H \end{pmatrix} = \begin{pmatrix} AE+BG & AF+BH \\ CE+DG & CF+DH \end{pmatrix}$$


Multiplying the inputs

1	2		5	6
3	4	X	7	8

Address value 000
with a Data input 1

Address value 100
with a Data input 5
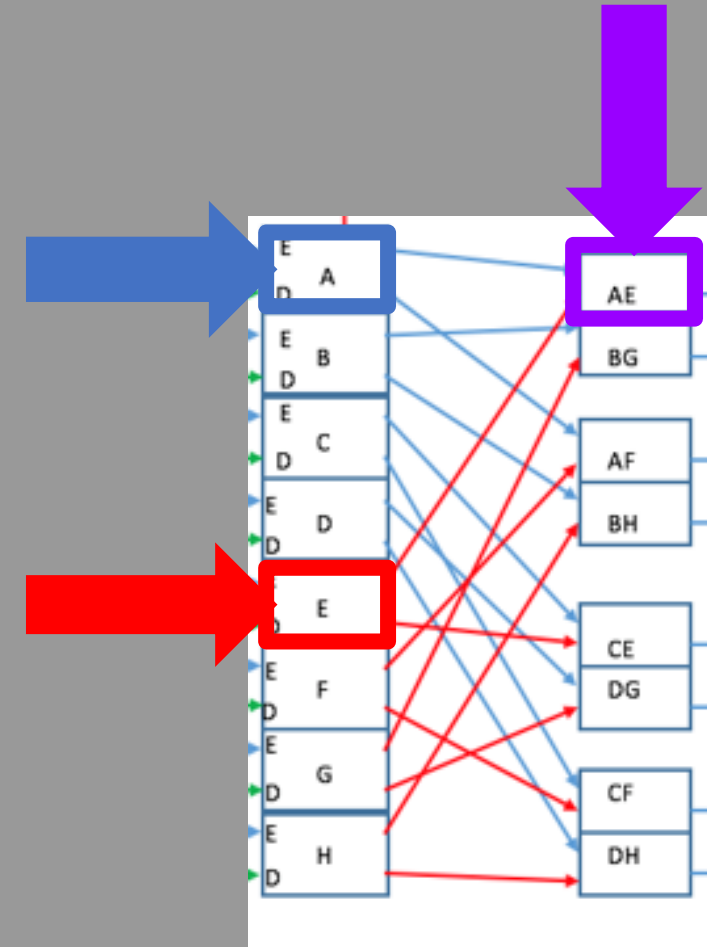
$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} \times \begin{pmatrix} E & F \\ G & H \end{pmatrix} = \begin{pmatrix} AE+BG & AF+BH \\ CE+DG & CF+DH \end{pmatrix}$$




Getting the solutions for the Matrices


$$= \begin{vmatrix} 1 \times 5 + 2 \times 7 & 1 \times 6 + 2 \times 8 \\ 3 \times 5 + 4 \times 7 & 3 \times 6 + 4 \times 8 \end{vmatrix}$$

$$= \begin{vmatrix} 19 & 22 \\ 43 & 50 \end{vmatrix}$$

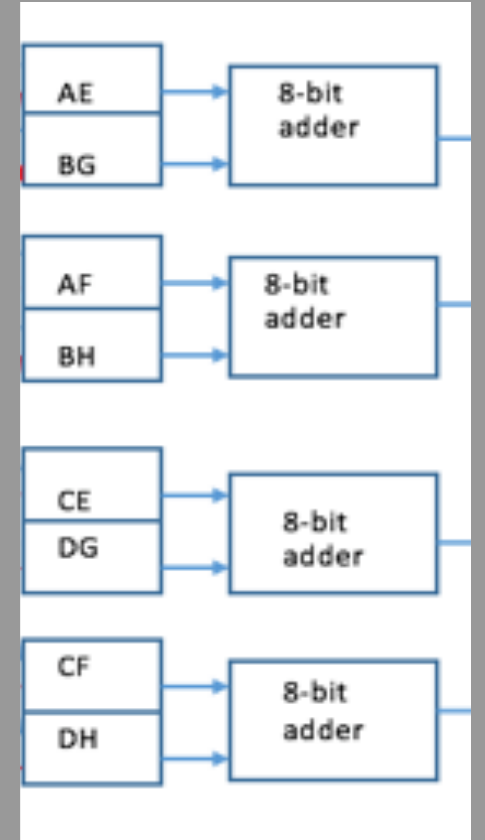
$$\begin{pmatrix} A & B \\ C & D \end{pmatrix} \times \begin{pmatrix} E & F \\ G & H \end{pmatrix} = \begin{pmatrix} AE+BG & AF+BH \\ CE+DG & CF+DH \end{pmatrix}$$



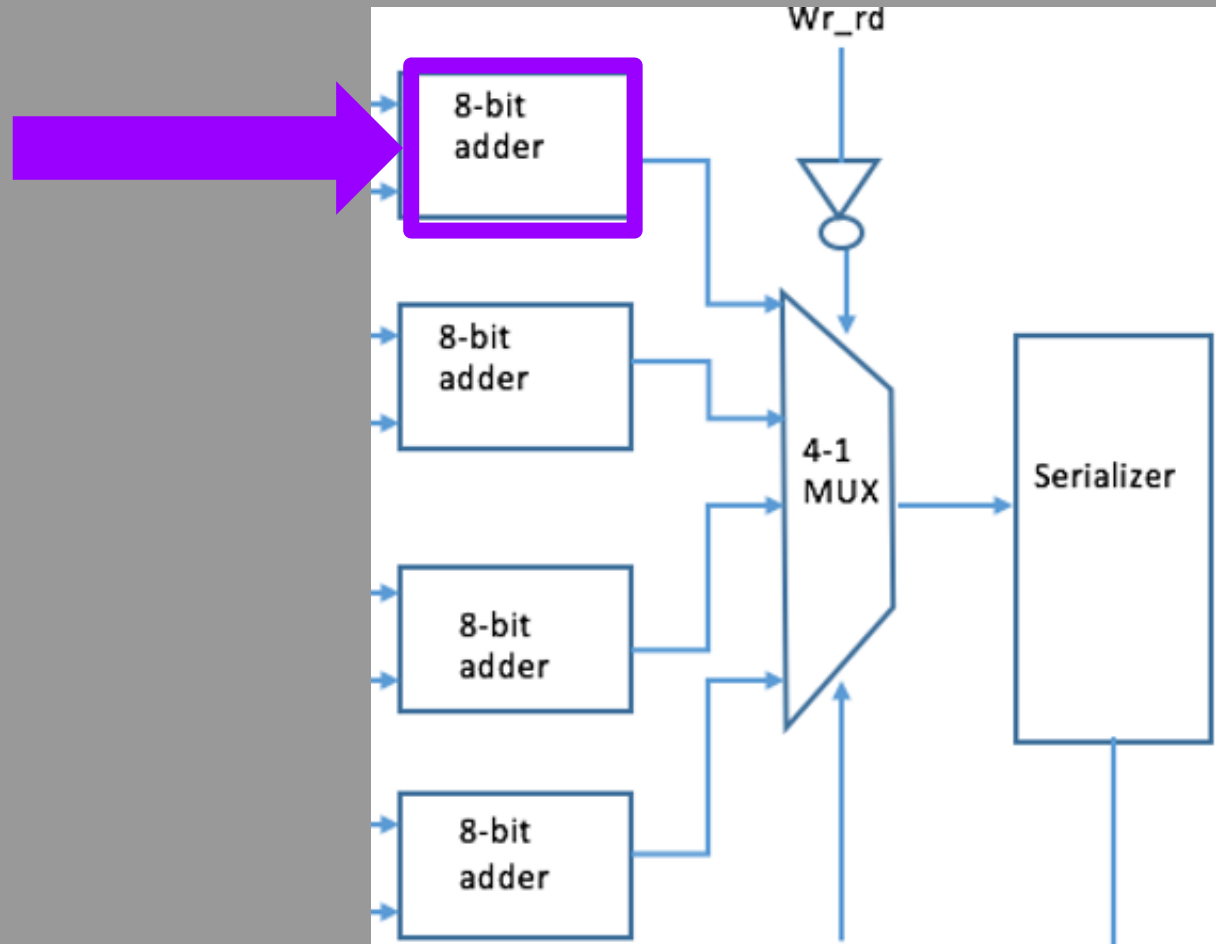
Address value "00"
with a Data input of
the 1st 8-bit adder is
then sent to the
serializer



FSM diagram

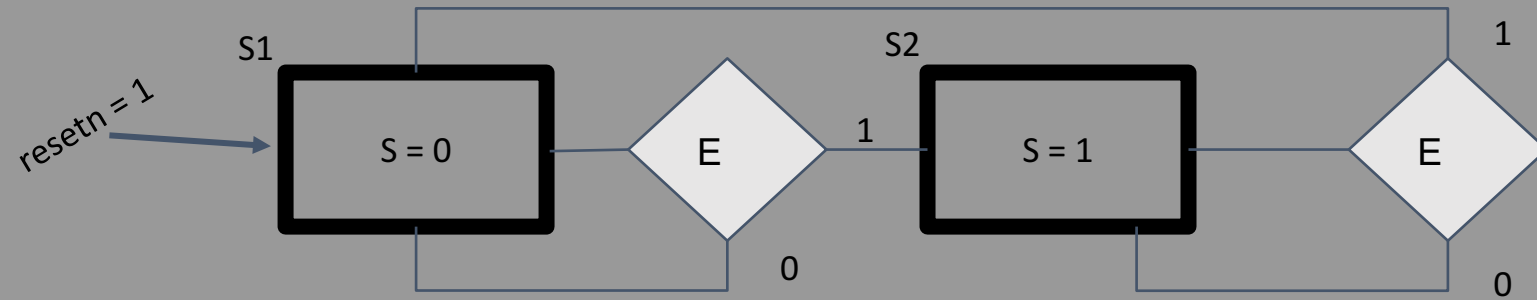


4 bit address being
sent (XXXX, ----)

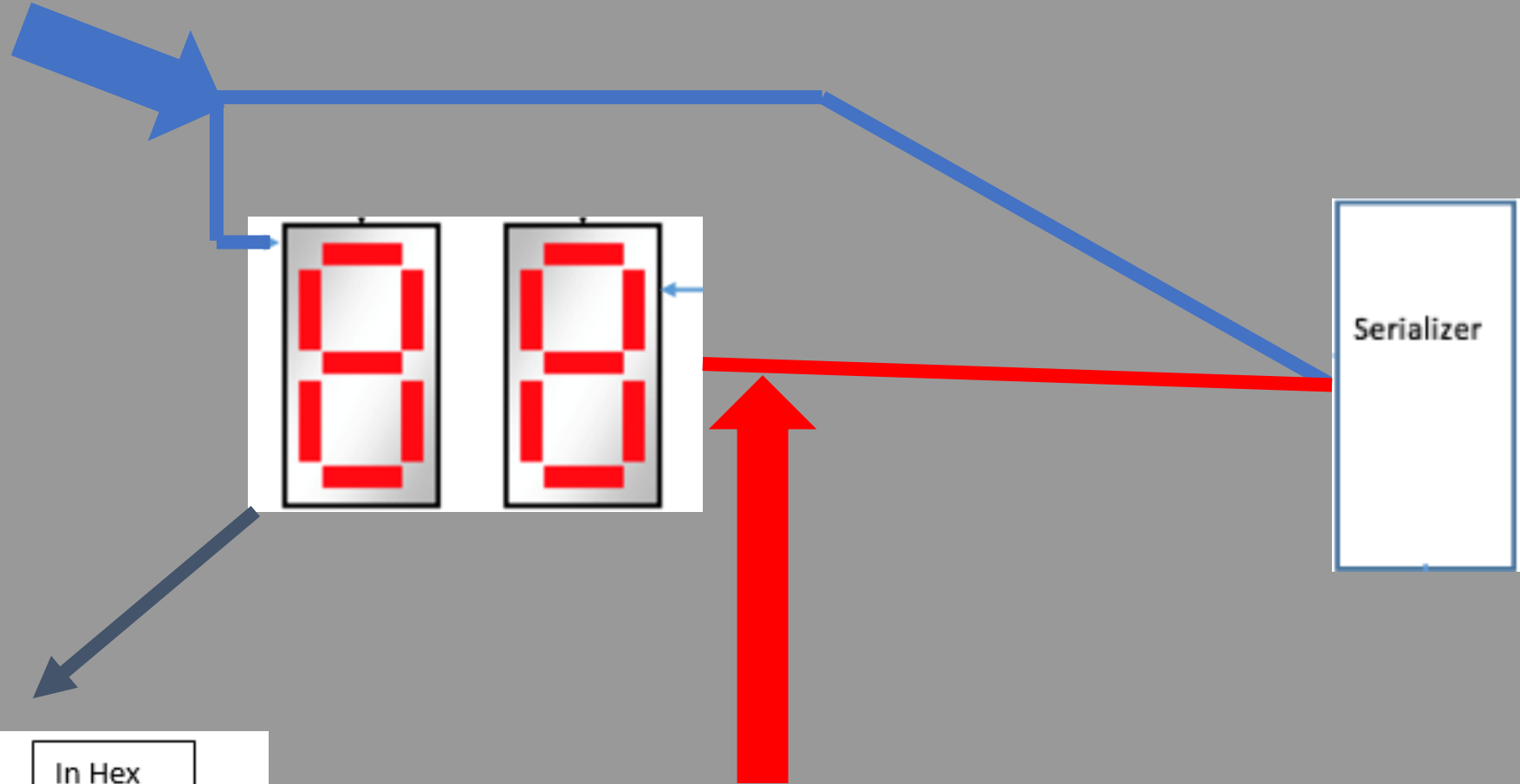

4 bit address being
sent (----,XXXX)

		In Hex									
=	<table><tr><td>19</td><td>22</td></tr><tr><td>43</td><td>50</td></tr></table>	19	22	43	50	=	<table><tr><td>13</td><td>16</td></tr><tr><td>2b</td><td>32</td></tr></table>	13	16	2b	32
19	22										
43	50										
13	16										
2b	32										

Layout of the Nexys a7-50t board

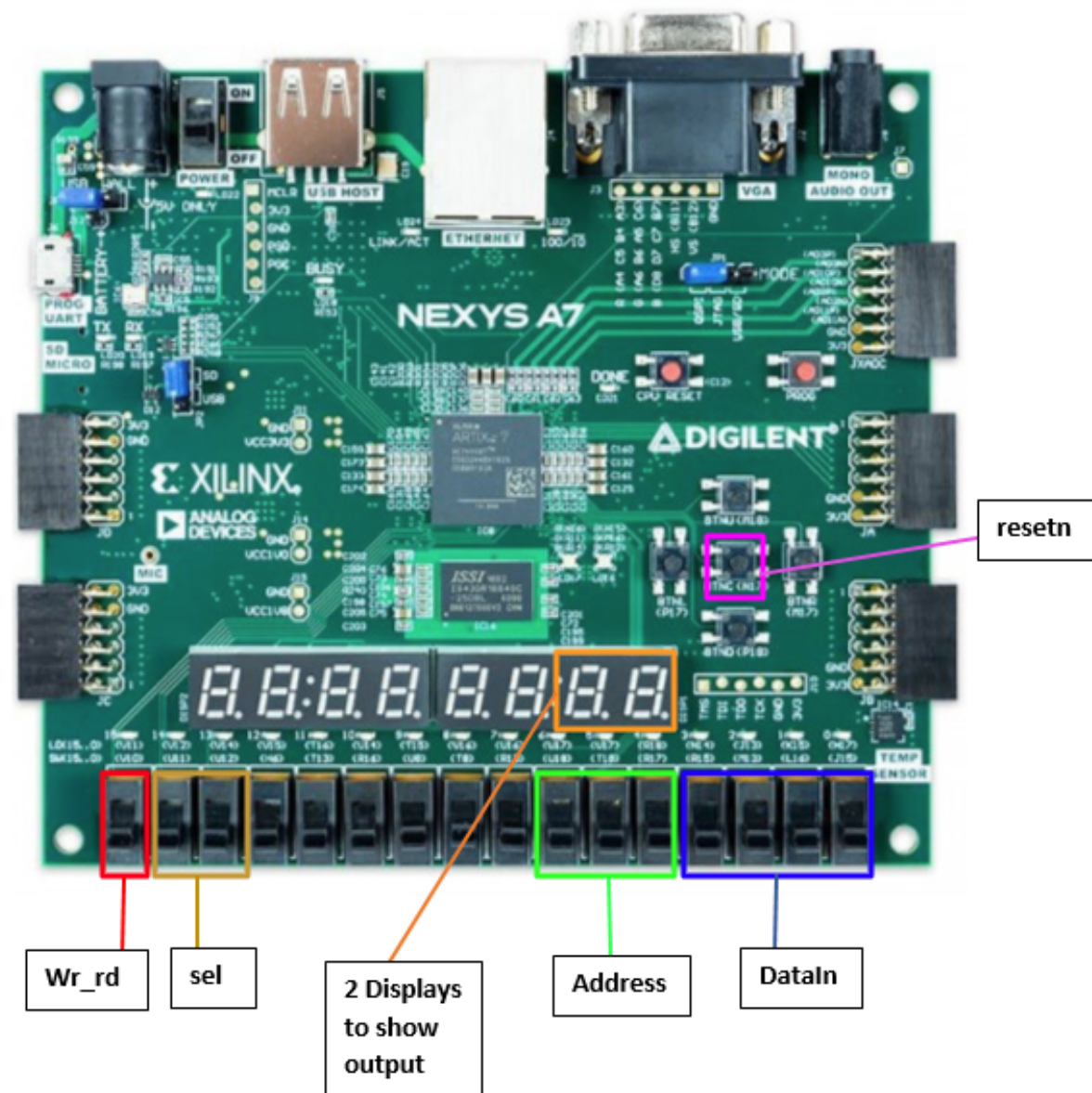

Time to Demonstrate