

Quiz 3


(November 4th @ 5:30 pm)

PROBLEM 1 (35 PTS)

- Complete the timing diagram of the circuit whose VHDL description is shown below (30 pts):

```
library ieee;
use ieee.std_logic_1164.all;
```
 
```
entity circ is
port ( rstn, a, b, x, clk: in std_logic;
      q: out std_logic);
end circ;
```





```
architecture xst of circ is
signal qt, f: std_logic;
begin
process (rstn, clk, a, b, x)
begin
if rstn = '0' then
qt <= '0';
elsif (clk'event and clk = '1') then
if x = '0' then
qt <= a xnor b;
end if;
end if;
end process;
q <= qt;
end xst;
```

- Get the excitation equation for q . (5 pts)

  PROBLEM 2 (30 PTS)

- Complete the timing diagram of the following state machine:



PROBLEM 3 (35 PTS)

- Complete the timing diagram of the following circuit. $Q = Q_3Q_2Q_1Q_0$

