

## Quiz 4

(November 25<sup>th</sup> @ 5:30 pm)

### PROBLEM 1 (30 PTS)

- Draw the state diagram (in ASM form) of the FSM whose VHDL description is listed below:

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( clk, rstn: in std_logic;
          r, p, q: in std_logic;
          x, w, z: out std_logic);
end circ;
```

```

architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (rstn, clk, r, p, q)
    begin
        if rstn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '1' then y <= S2;
                    else if p = '1' then y <= S3; else y <= S1; end if;
                    end if;

                when S2 =>
                    if p = '1' then y <= S1; else y <= S3; end if;

                when S3 =>
                    if q = '1' then y <= S3; else y <= S2; end if;


            end case;
        end if;
    end process;

    Outputs: process (y, r, p, q)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '0' then x <= '1'; end if;
            when S2 => if q = '0' then w <= '1'; end if;
                        if p = '0' then z <= '1'; end if;
            when S3 => if q = '0' then w <= '1'; end if;
        end case;
    end process;
end behavioral;

```
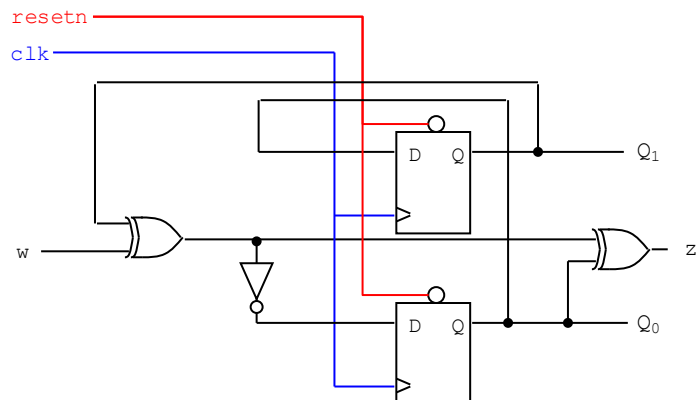
### PROBLEM 2 (40 PTS)

- Provide the excitation equations (including the Boolean equation for  $z$ ) and the Excitation Table for the following FSM:



- Is this a Mealy or a Moore FSM? Why? (5 pts)

### PROBLEM 3 (30 PTS)

- **Sequence detector:** Draw the state diagram (any representation) of an FSM with input  $x$  and output  $z$ . The detector asserts  $z = 1$  when the sequence 0110 is detected. Right after the sequence is detected, the circuit looks for a new sequence.