

BCD TO BINARY CONVERTER




BY: COLSTON EL-HAYEK,
ROBERT KAYFISH,
ANDREW PICKLO,
KYLE AL-ATTAR


Overview

- PS/2 Keyboard connected to FPGA board via USB
- 12 bit typed BCD keyboard input
- Decimal representation shown on three 7-segment displays
- VHDL code converts the input from BCD to Unsigned Binary
- Binary representation shown on LEDs



Main Block Diagram

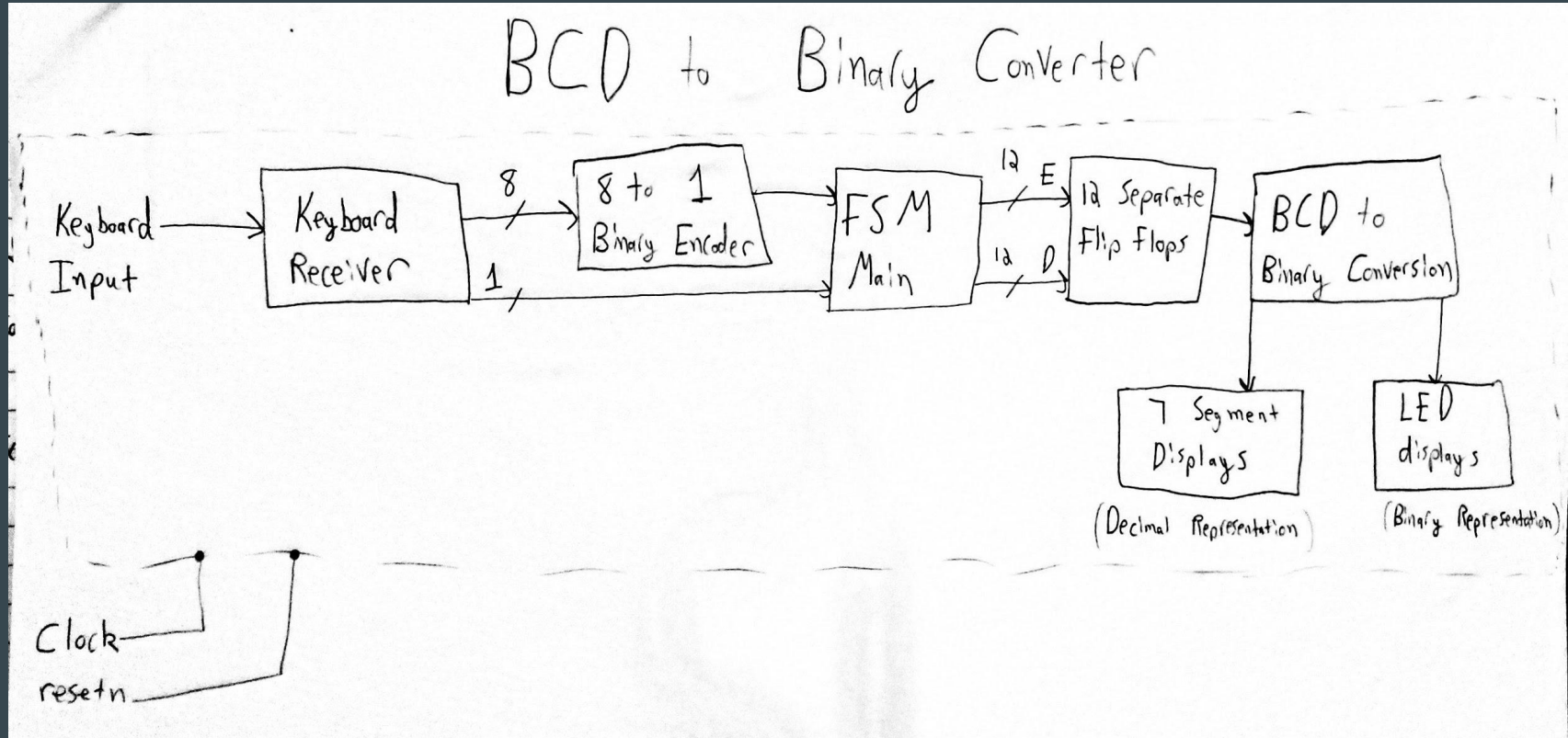


PS2 Keyboard

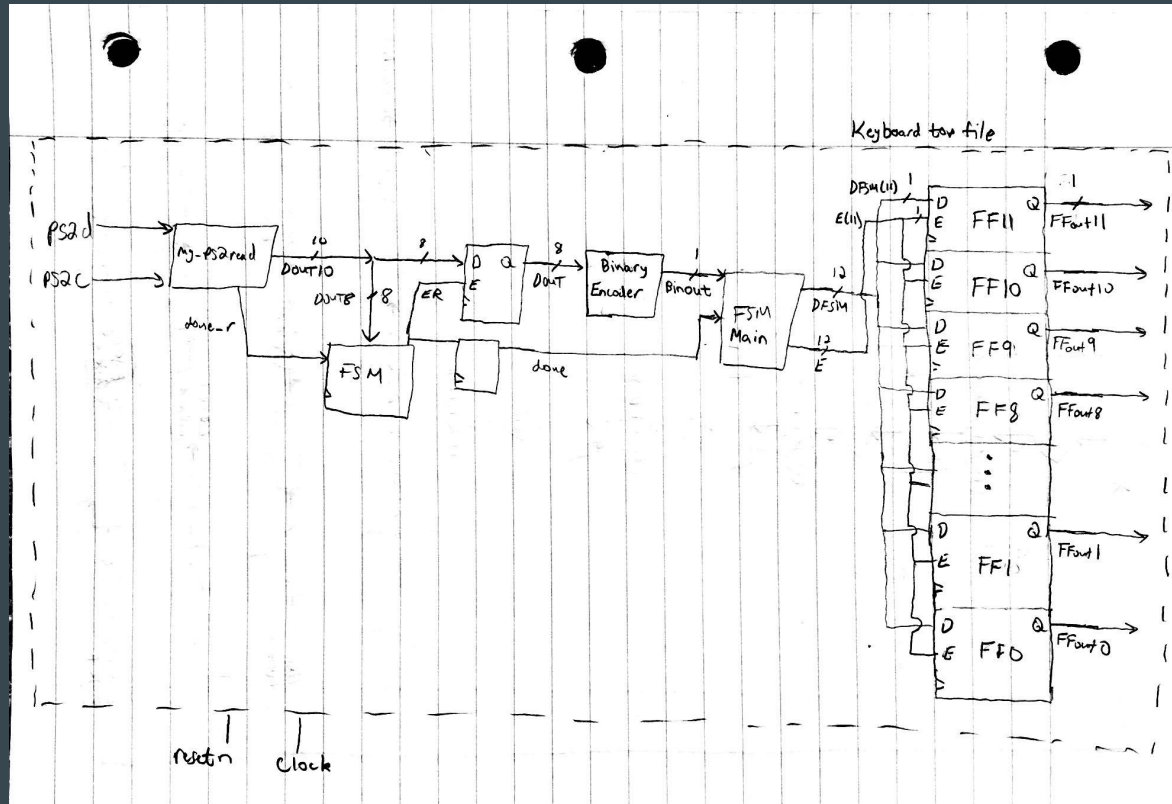


FSM Main

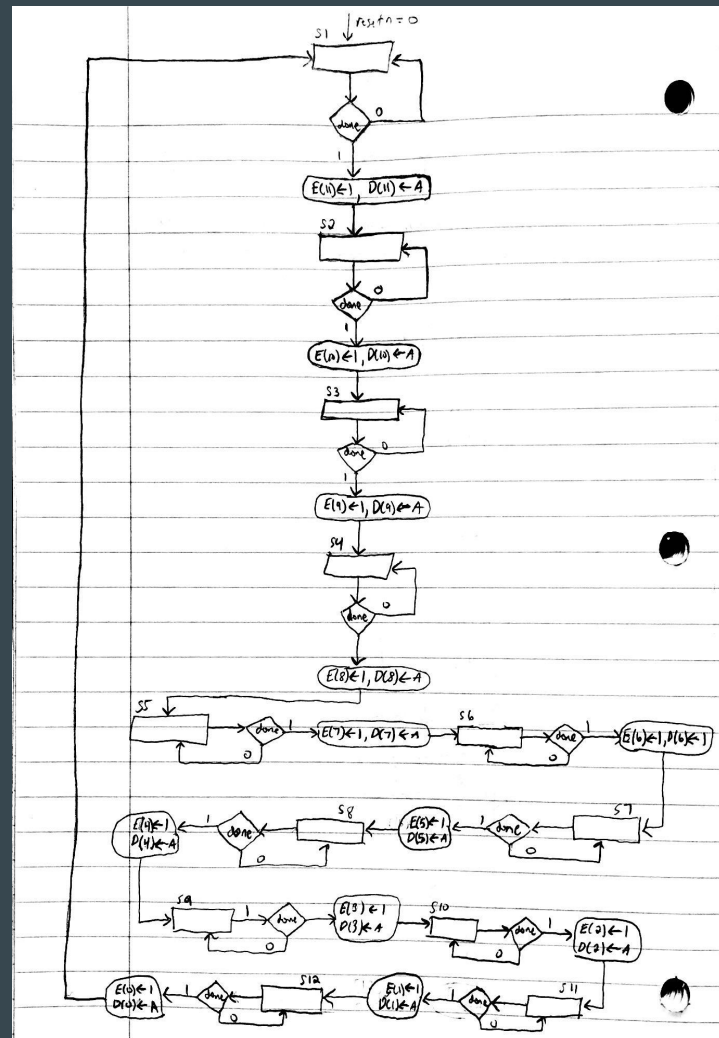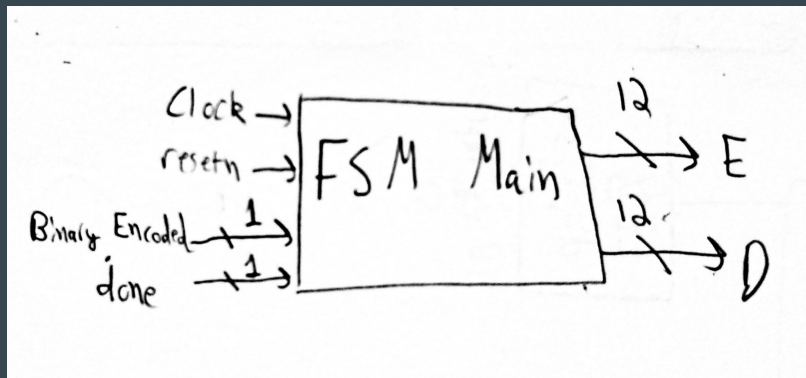


7 Segment Displays

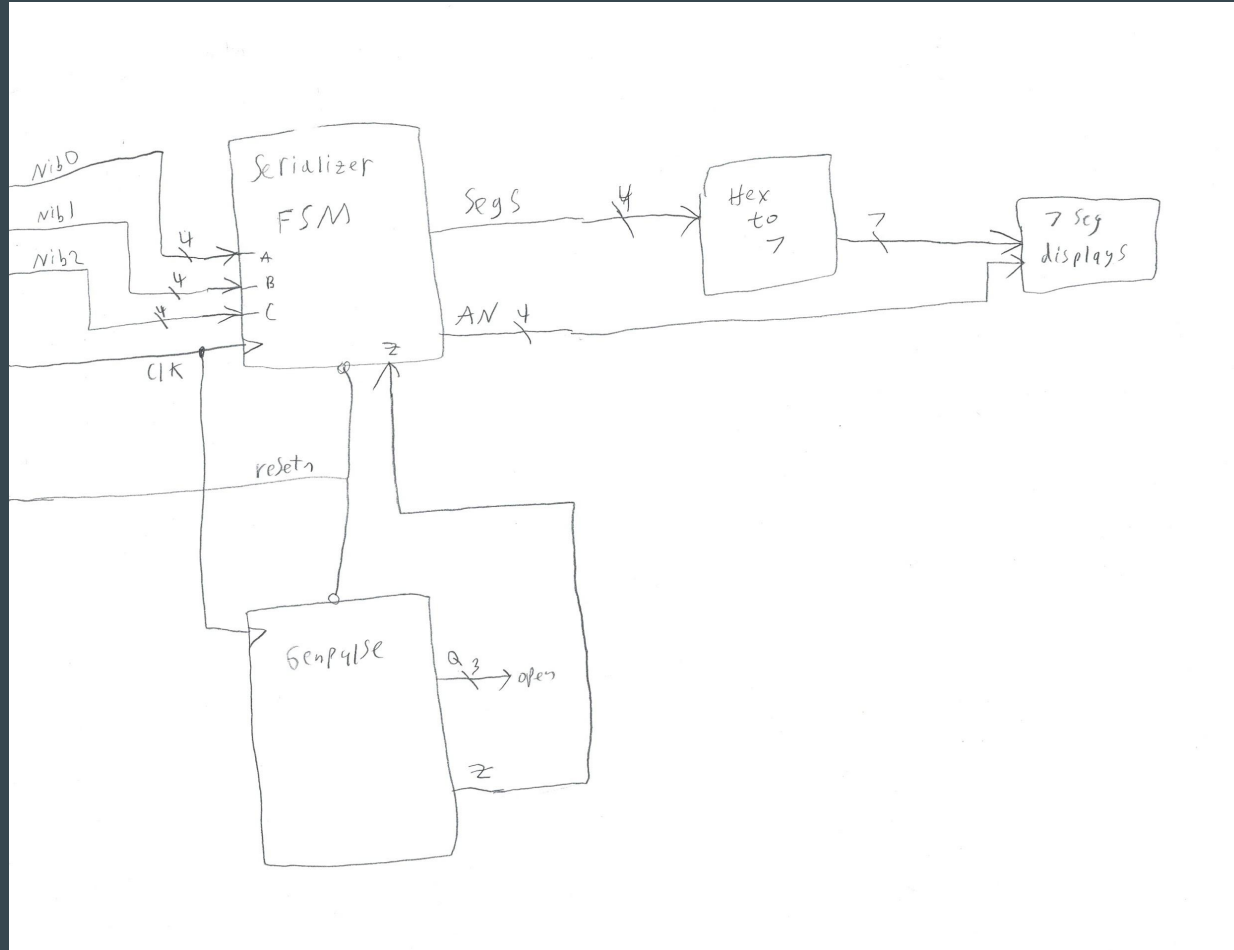

BCD Converter

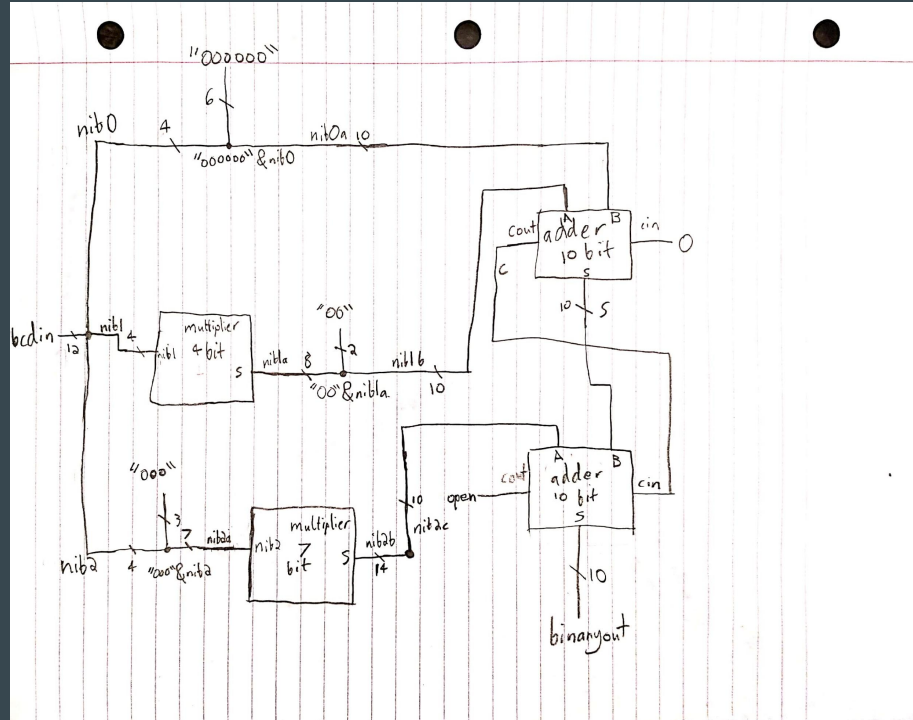

Timing Diagram

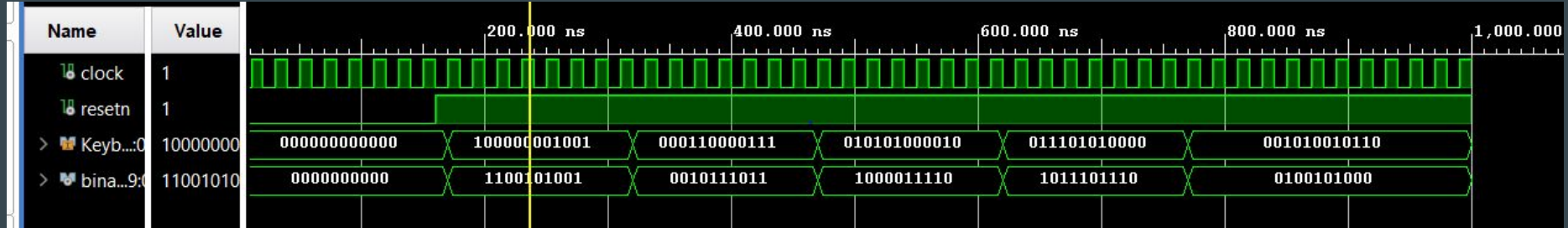

Testing Setup

Trial #	BCD Keyboard Input	Decimal Output	Binary Output
1	1000-0000-1001	809	1100101001
2	0001-1000-0111	187	0010111011
3	0101-0100-0010	542	1000011110
4	0111-0101-0000	750	1011101110
5	0010-1001-0110	296	0100101000

Backup Video Demonstration

(https://drive.google.com/file/d/1vA4av1TpVnwTqaM3dTbfXN0yEs8A_fmB/view?usp=sharing)

Conclusion

- Project successfully completed fully within our initial expectations
- Keyboard
- FSM
- VHDL libraries
- Utilization of generic map function
- Learned how to work as a group and delegate work
- Changes can be made to make full output displayed at once