


Solutions - Homework 3

(Due date: November 3rd @ 5:30 pm)


Presentation and clarity are very important! Show your procedure!

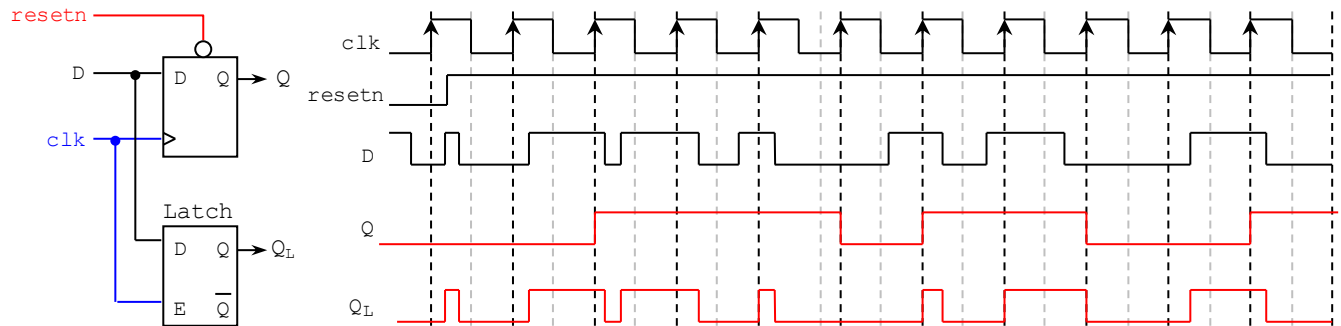PROBLEM 1 (10 PTS)

- Complete the timing diagram for the flip flop and the latch shown below: (6 pts)



 
- Complete the timing diagram of the circuit shown below. (4 pts)




$$Q_{t+1} \leftarrow T \oplus Q_t$$

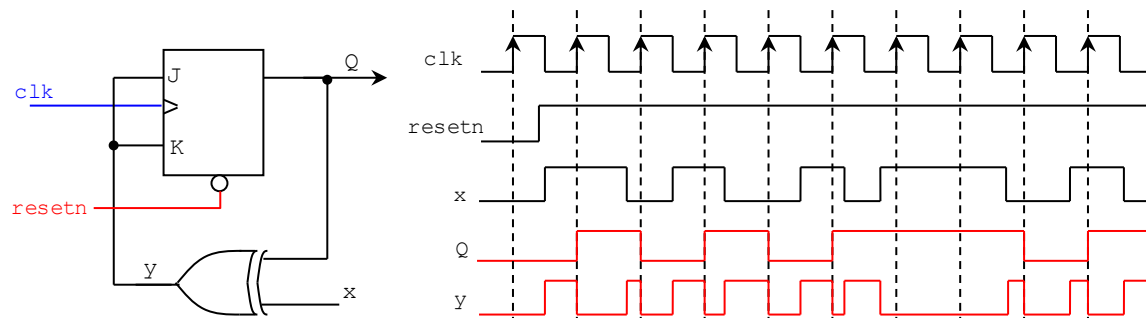PROBLEM 2 (23 PTS)

- Complete the timing diagram of the circuit shown below: (7 pts)




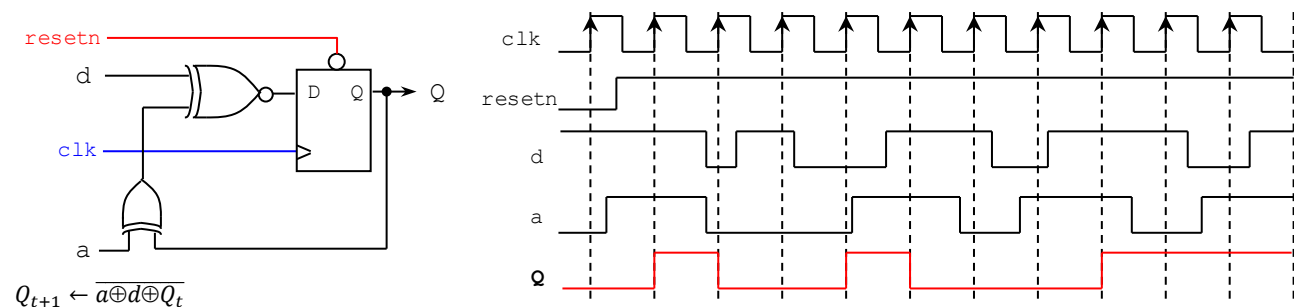- Complete the timing diagram of the circuit shown below: (6 pts)



$$Q_{t+1} \leftarrow a \oplus d \oplus Q_t$$

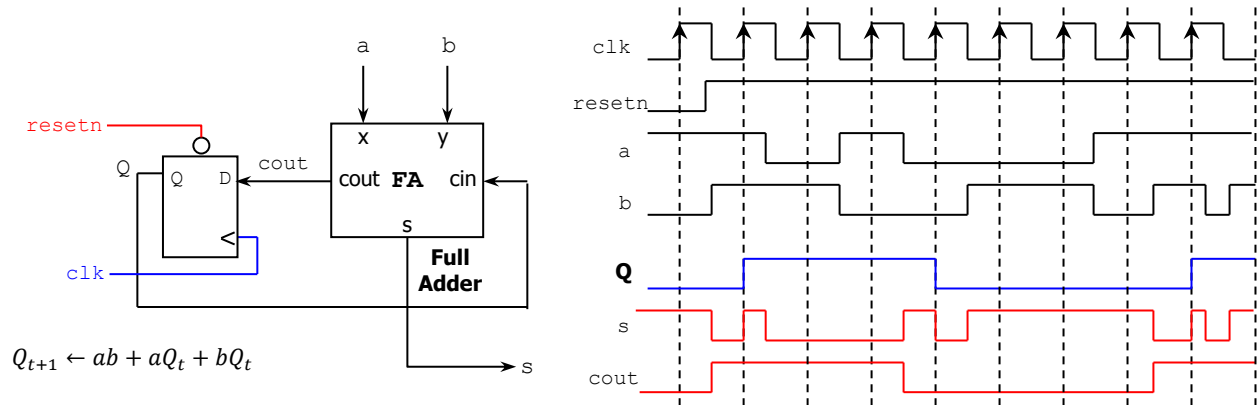
- Complete the timing diagram of the circuit shown below: (10 pts)



 PROBLEM 3 (17 PTS)


- With a D flip flop and logic gates, sketch the circuit whose excitation equation is given by (4 pts):

✓ $Q(t+1) \leftarrow x\overline{Q}(t) + (y \oplus \overline{Q}(t))$



- Given the following circuit: (8 pts)

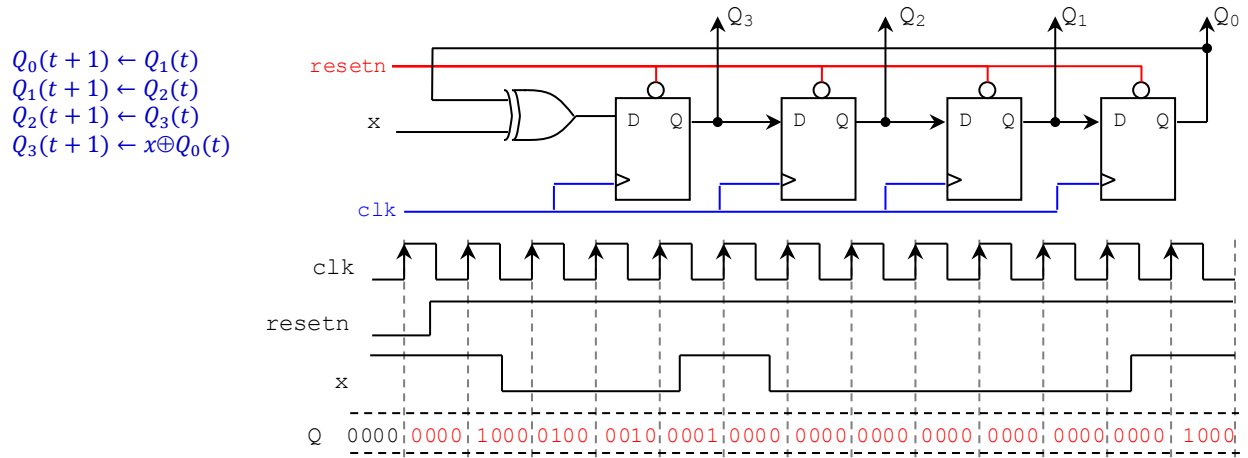- ✓ Get the excitation equations for each flip flop output.
- ✓ Complete the timing diagram of the circuit. $Q = Q_3Q_2Q_1Q_0$.



- Complete the timing diagram of the circuit whose VHDL description is shown below. Also, get the excitation equation for q.

```
library ieee;
use ieee.std_logic_1164.all;


entity circ is
    port ( prn, a,x,clk: in std_logic;
          q: out std_logic);
end circ;

architecture t of circ is
    signal qt: std_logic;

begin
    process (prn, clk, a, x)
    begin
        if prn = '0' then
            qt <= '1';
        else
            qt <= qt xor not(a);
        end if;
    end process;
    q <= qt;
end t;
```


$q(t+1) \leftarrow \bar{x}(\bar{a} \oplus q(t)) + xq(t)$
 
```
elsif (clk'event and clk = '0') then
    if x = '0' then
        qt <= qt xor not(a);
    end if;
end if;
end process;
q <= qt;
end t;
```



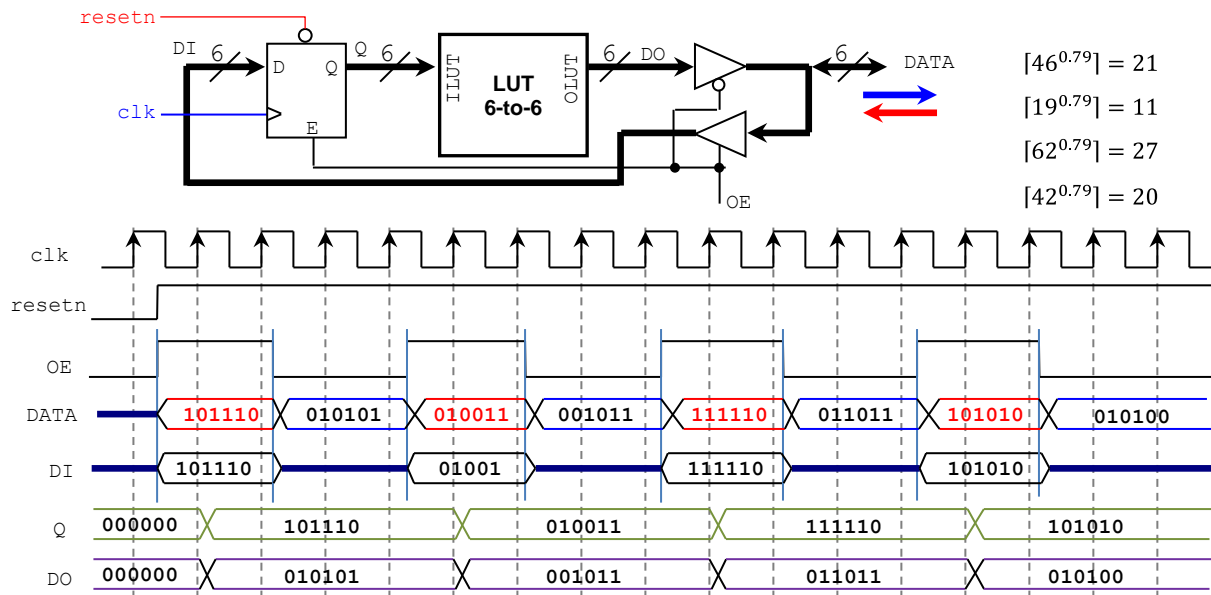PROBLEM 4 (14 PTS)

- Given the following circuit, complete the timing diagram (signals DO , Q , and $DATA$).
The LUT 6-to-6 implements the following function: $OLUT = [ILUT^{0.79}]$, where $ILUT$ is a 6-bit unsigned number.
For example: $ILUT = 35 (100011_2) \rightarrow OLUT = [35^{0.79}] = 17 (010001_2)$



PROBLEM 5 (20 PTS)

- For the following circuit (4-bit parallel/serial load shift register with enable input) we have: $Q = Q_3Q_2Q_1Q_0$. $D = D_3D_2D_1D_0$.
When $E=1$: If $s_l=0$ (shifting operation). If $s_l=1$ (parallel load).s
 - ✓ Write a structural VHDL code. You MUST create a file for: i) flip flop, ii) MUX 2-to-1, and iii) top file (where you will interconnect the flip flops and MUXes). (10 pts)
 - ✓ Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Behavioral Simulation). The clock frequency must be 100 MHz with 50% duty cycle. (10 pts)
- Upload (as a .zip file) the following files to Moodle (an assignment will be created):
 - ✓ VHDL code files and testbench
 - ✓ A screenshot of your simulation showing the results for Q (this is on top of you completing the timing diagram below).

VHDL Code: Top File

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity my_st_shiftreg is
    generic (N: INTEGER:= 4;
            DIR: STRING:= "RIGHT"); -- RIGHT/LEFT
    port (D: in std_logic_vector (N-1 downto 0);
          resetn, clock, din, E, s_l: in std_logic;
          Q: out std_logic_vector (N-1 downto 0));
end my_st_shiftreg;

architecture structure of my_st_shiftreg is
    component dffe
        port ( d : in  STD_LOGIC;
              clrn, prn, clk, ena: in std_logic;
              q : out STD_LOGIC);
    end component;

    component mux2to1
        port (a,b, sel : in std_logic;
              y : out std_logic);
    end component;

    signal ds, md, Qt: std_logic_vector (N-1 downto 0);
begin

```

```

a0: assert (DIR = "LEFT" or DIR = "RIGHT")
    report "DIR can only be LEFT or RIGHT"
    severity error;

rr: if DIR = "RIGHT" generate
    ds(N-1) <= din;
    ds(N-2 downto 0) <= Qt(N-1 downto 1);
end generate;

rl: if DIR = "LEFT" generate
    ds(0) <= din;
    ds(N-1 downto 1) <= Qt(N-2 downto 0);
end generate;

ti: for i in N-1 downto 0 generate
    fi: dffe port map (d => md(i), clrn => resetn, prn => '1', clk => clock, ena => E, q => Qt(i));
    mi: mux2to1 port map (a => ds(i), b => D(i), sel => s_1, y => md(i));
end generate;

    Q <= Qt;
end structure;

```

VHDL Code: D-Type flip flop

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;
use IEEE.STD_LOGIC_UNSIGNED.ALL;

entity dffe is
    port ( d : in  STD_LOGIC;
          clrn, prn, clk, ena: in std_logic;
          q : out  STD_LOGIC);
end dffe;

architecture behaviour of dffe is
begin
    process (clk, ena, prn, clrn)
    begin
        if clrn = '0' then q <= '0';
        elsif prn = '0' then q <= '1';
        elsif (clk'event and clk='1') then
            if ena = '1' then q <= d; end if;
        end if;
    end process;
end behaviour;

```

VHDL Tesbench:

```

LIBRARY ieee;
USE ieee.std_logic_1164.ALL;

ENTITY tb_my_st_shiftreg IS
    generic (N: INTEGER:= 4);
END tb_my_st_shiftreg;

ARCHITECTURE behavior OF tb_my_st_shiftreg IS
    COMPONENT my_st_shiftreg
        PORT( D : IN  std_logic_vector(N-1 downto 0);
              resetn, clock, din : IN  std_logic;
              E, s_1 : IN  std_logic;
              Q : OUT std_logic_vector(N-1 downto 0));
    END COMPONENT;

    --Inputs
    signal D : std_logic_vector(N-1 downto 0) := (others => '0');
    signal resetn : std_logic := '0';
    signal clock : std_logic := '0';
    signal din : std_logic := '0';
    signal E : std_logic := '0';
    signal s_1 : std_logic := '0';

    --Outputs
    signal Q : std_logic_vector(N-1 downto 0);

    -- Clock period definitions

```

VHDL Code: MUX 2-to-1

```

library IEEE;
use IEEE.STD_LOGIC_1164.ALL;

entity mux2to1 is
    port (a,b, sel: in std_logic;
          y : out std_logic);
end mux2to1;

architecture structure of mux2to1 is
begin
    with sel select
        y <= a when '0',
            b when others;
end structure;

```

```


constant T : time := 10 ns;

BEGIN
  -- Instantiate the Unit Under Test (UUT)
  uut: my_st_shiftreg PORT MAP (D => D, resetn => resetn, clock => clock, din => din,
                                E => E, s_l => s_l, Q => Q);

  -- Clock process definitions
  clock_process: process
  begin
    clock <= '0'; wait for T/2;
    clock <= '1'; wait for T/2;
  end process;



  -- Stimulus process
  stim_proc: process
  begin
    resetn <= '0'; wait for 100 ns;
    D <= "1000"; din <= '1'; E <= '0'; s_l <= '1'; wait for T;
    resetn <= '1';
    D <= "1000"; din <= '1'; E <= '1'; s_l <= '1'; wait for T;
    D <= "1000"; din <= '0'; E <= '1'; s_l <= '0'; wait for T;
    D <= "1010"; din <= '0'; E <= '1'; s_l <= '1'; wait for T;
    D <= "1010"; din <= '1'; E <= '1'; s_l <= '1'; wait for T;
    D <= "1010"; din <= '1'; E <= '1'; s_l <= '1'; wait for T;
    D <= "1010"; din <= '0'; E <= '0'; s_l <= '1'; wait for T;
    D <= "1101"; din <= '1'; E <= '0'; s_l <= '0'; wait for T;
    D <= "1101"; din <= '0'; E <= '1'; s_l <= '0'; wait for T;
    D <= "1101"; din <= '0'; E <= '1'; s_l <= '1'; wait for T;
    D <= "1110"; din <= '0'; E <= '1'; s_l <= '1'; wait for T;
    D <= "1110"; din <= '1'; E <= '1'; s_l <= '0'; wait for T;
    D <= "1110"; din <= '1'; E <= '1'; s_l <= '1'; wait for T;
    D <= "1110"; din <= '0'; E <= '0'; s_l <= '1'; wait for T;
    D <= "1011"; din <= '0'; E <= '1'; s_l <= '1'; wait for T;
    D <= "1011"; din <= '1'; E <= '1'; s_l <= '0'; wait for T;
    D <= "1011"; din <= '0'; E <= '1'; s_l <= '1'; wait for T;
    wait;
  end process;
END;

```

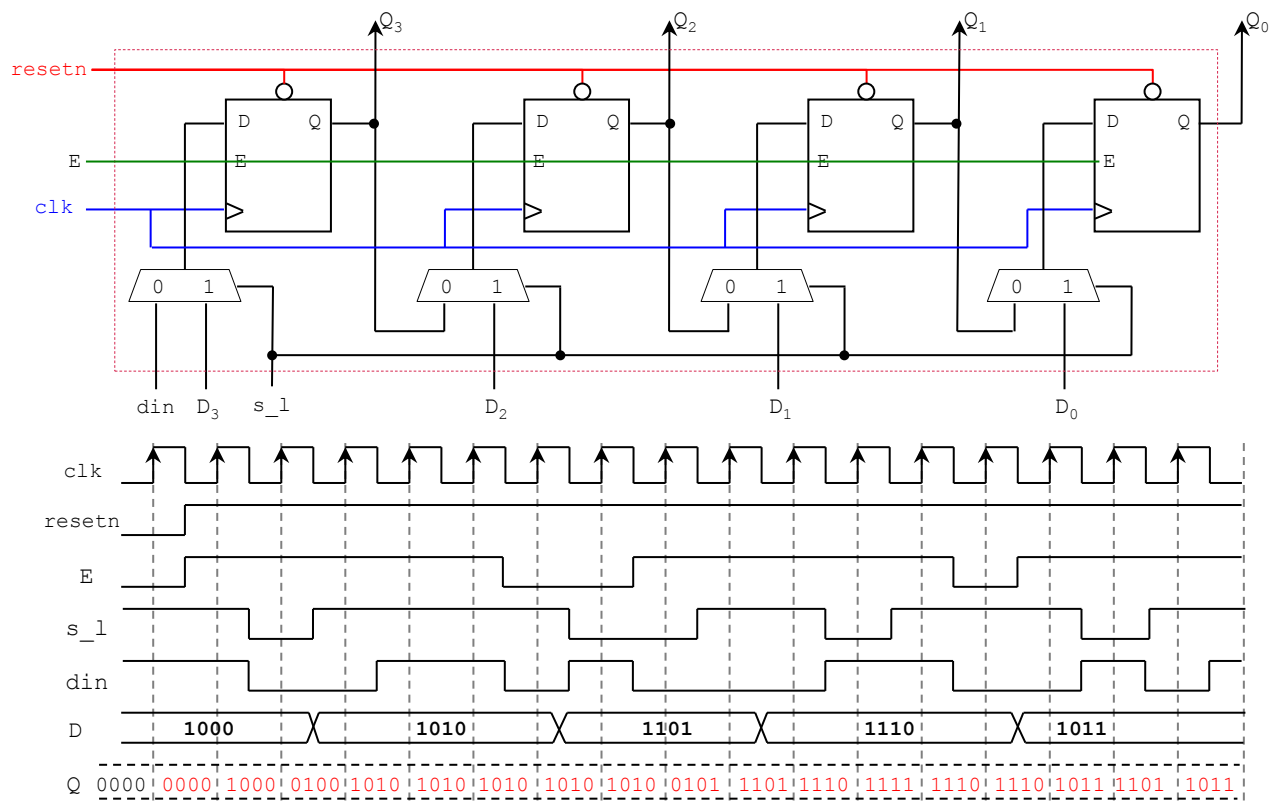

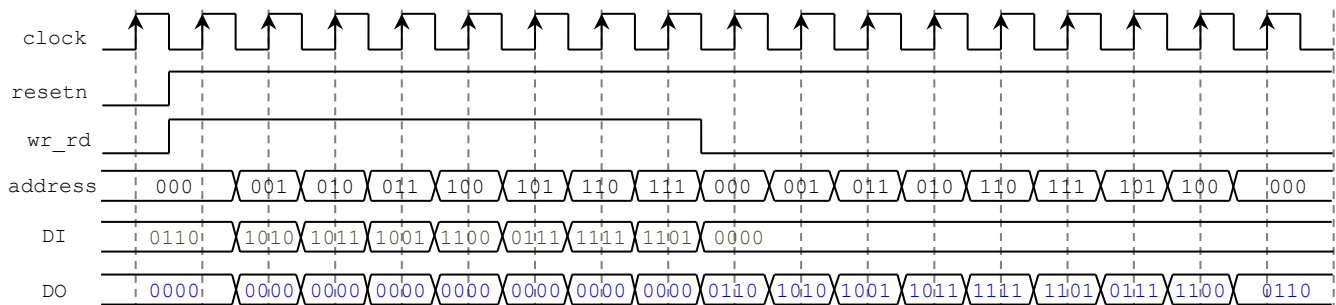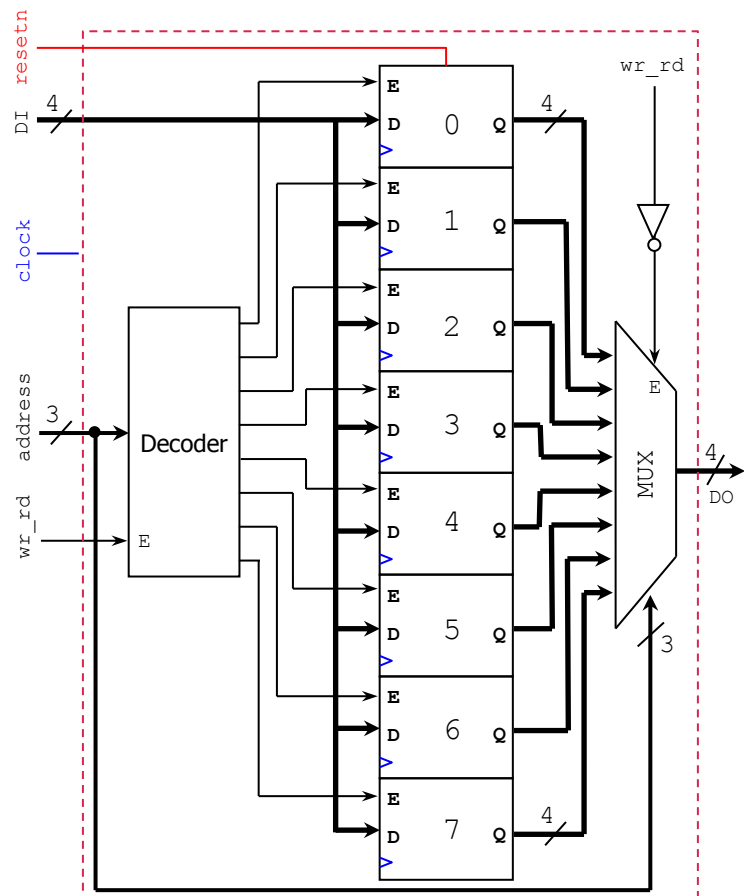PROBLEM 6 (8 PTS)

- Complete the timing diagram (output DO) of the following Random Memory Access (RAM) Emulator.
- RAM Emulator: It has 8 addresses, where each address holds a 4-bit data. The memory positions are implemented by 4-bit registers. The *resetn* and *clock* signals are shared by all the registers. Data is written or read onto/from one of the registers (selected by the signal address).
- Operations:
 - Writing onto memory (*wr_rd*=1): The 4-bit input data (DI) is written into one of the 8 registers. The address signal selects which register is to be written.
 - For example: if address = "101", then the value of DI is written into register 5.
 - Note that because the BusMUX 8-to-1 includes an enable input, if *wr_rd*=1, then the BusMUX outputs are 0's.
 - Reading from memory (*wr_rd*=0): The address signal selects the register from which data is read. This data appears on the BusMUX output.
 - For example: If address = "010", then data from register 2 appears on BusMUX output.



PROBLEM 7 (8 PTS)

- Attach your Project Status Report (no more than 1 page, single-spaced, 2 columns, only one submission per group). This report should contain the initial status of your project. For formatting, use the provided template (Final Project - Report Template.docx). The sections included in the template are the ones required in your Final Report. At this stage, you are only required to:
 - Include a (draft) project description and title.
 - Include a draft Block Diagram of your hardware architecture.
- As a guideline, the figure shows a simple Block Diagram. There are input and output signals, as well as internal components along with their interconnection.
 - At this stage, only a rough draft is required. There is no need to go into details: it is enough to show the tentative top-level components that would constitute your system as well as the tentative inputs and outputs.
- Only student is needed to attach the report (make sure to indicate all the team members).

