

Signed calculator

Fady Sto, Karam Matti, Jason Wend, Manuel Muresan

Signed calculator

For the final project we have created a simple signed calculator. Our calculator is able to add, subtract, divide, and multiply. As a signed calculator it uses positive and negative numbers. The results are in BCD and our inputs are 6 bits in sign and magnitude binary form.



The design:





Adder

- One of the five bit adders from the subtractor (see subtractor a=on next slide)
- These five bit adders contain 5 full adders



Subtractor

- Uses two five bit adders and various other logic to compute the absolute value of input 1 minus input 2.
- Subtractor: There are two inputs that are 4 bits and one output that is 5 bits

Multiplier:



• A component that takes advantage of full adders.

 uses two 4-bit inputs and saves them as an 8-bit output (Lab 3)



Division:

- Unlike our previous asynchronous operations, the division operation was controlled by a clock since it used various shift registers, a counter, and an FSM (See Lab 6)
- Two of our inputs are vectors and three of our outputs are vectors.

Basic 4-to-1 MUX:



• main component of the output function of the calculator

• Receives the answer of all four operations and outputs only the desired answer.

7-Segment Decoder:

• Receives answer as a 16-bit Binary number.

• Converts to a 16-bit signed BCD and then segmented into four 4-bit numbers.

• Each display is turned on by a counter and state machine, which also updates the information once every millisecond.



Problems Faced:

• Organizing Files: When all the files were combined, they needed to be organized into groups of similar files that each member had created.

- Using several 7-segment displays at once
- Code that operates properly when used separately but not when combined
- Division being a synchronous process
- Did not have enough time to use a keyboard instead of the switches from the FPGA board



Thank you

Any Questions?

