

Quiz 3


(November 2nd @ 3:30 pm)

PROBLEM 1 (30 PTS)

- Complete the timing diagram of the circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;


 
entity circ is
  port ( rstn, a, b, x, clk: in std_logic;
        q: out std_logic);
end circ;
```



```
architecture xst of circ is
  signal qt, f: std_logic;
begin
  process (rstn, clk, a, b, x)
  begin
    if rstn = '0' then
      qt <= '0';
    elsif (clk'event and clk = '1') then
      if x = '0' then
        qt <= qt xor (a or b);
      end if;
    end if;
    q <= qt;
  end process;
end xst;
```

  PROBLEM 2 (35 PTS)


- Complete the timing diagram of the following state machine: (30 pts.)



- For the given FSM diagram, circle or mark the correct FSM type: (Mealy) (Moore)

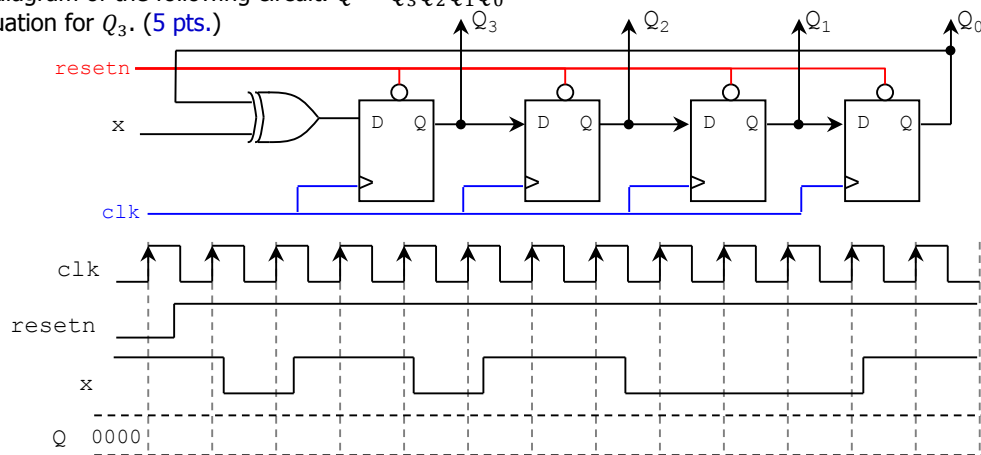PROBLEM 3 (35 PTS)

- Complete the timing diagram of the following circuit. $Q = Q_3Q_2Q_1Q_0$
- Get the excitation equation for Q_3 . (5 pts.)



$$Q_3(t+1) \leftarrow$$