

Quiz 4

(November 16th @ 3:30 pm)

PROBLEM 1 (30 PTS)

- Draw the state diagram (in ASM form) of the FSM whose VHDL description is listed below:

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
    port ( clk, rstn: in std_logic;
          a, b: in std_logic;
          x,w,z: out std_logic);
end circ;
```


```
architecture behavioral of circ is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (rstn, clk, a, b)
    begin
        if rstn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if a = '1' then y <= S2; else y <= S3; end if;
                when S2 =>
                    if b = '1' then y <= S3; else y <= S1; end if;
                when S3 =>
                    if a = '1' then y <= S3; else y <= S1; end if;
            end case;
        end if;
    end process;

    Outputs: process (y,a)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if a = '1' then z <= '1'; end if;
            when S2 => x <= '1';
            when S3 => w <= '1';
        end case;
    end process;
end behavioral;
```

- Circle or mark the correct FSM type:
(Mealy) (Moore)

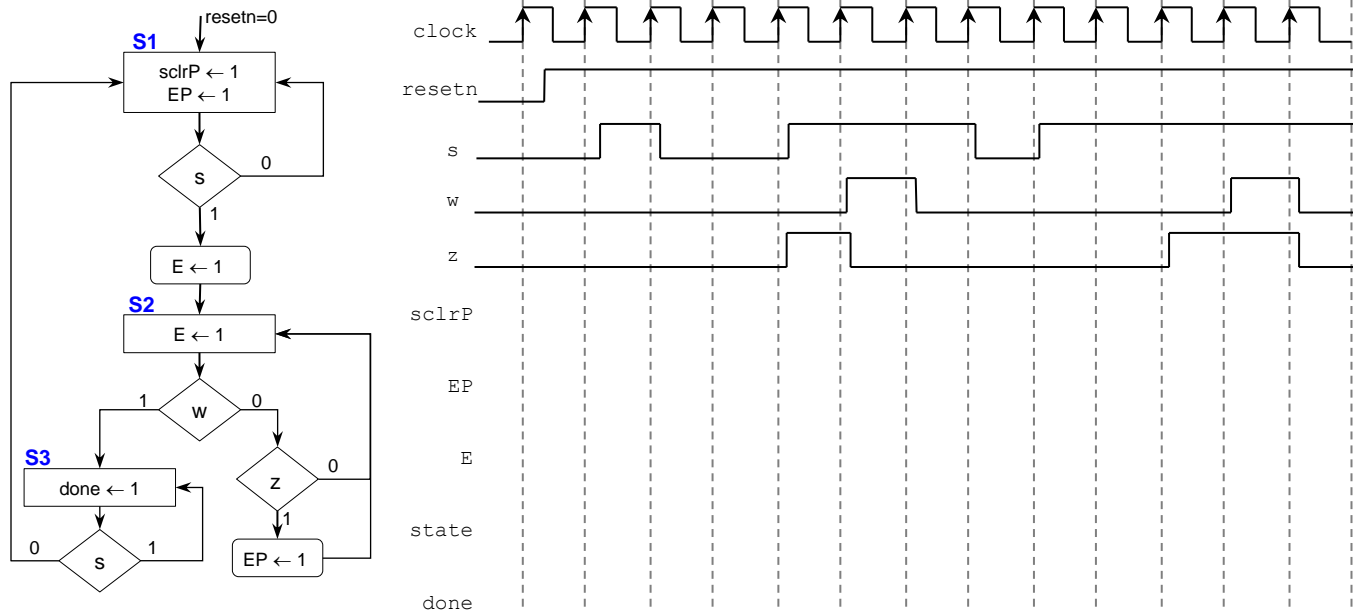PROBLEM 2 (40 PTS)

- Complete the timing diagram of the following FSM (represented in ASM form):



PROBLEM 3 (30 PTS)

- Sequence detector: Draw the state diagram (any representation) of an FSM with input x and output z . The detector asserts $z = 1$ when the sequence 01101 is detected. Right after the sequence is detected, the circuit looks for a new sequence.