

# Laboratory 3

(Due date: **011**: October 8<sup>th</sup>, **005**: October 9<sup>th</sup>, **007**: October 10<sup>th</sup>)

## OBJECTIVES

- ✓ Use the Structural Description on VHDL.
- ✓ Test arithmetic circuits on an FPGA.


## VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a list of examples.

## FIRST ACTIVITY (100/100)
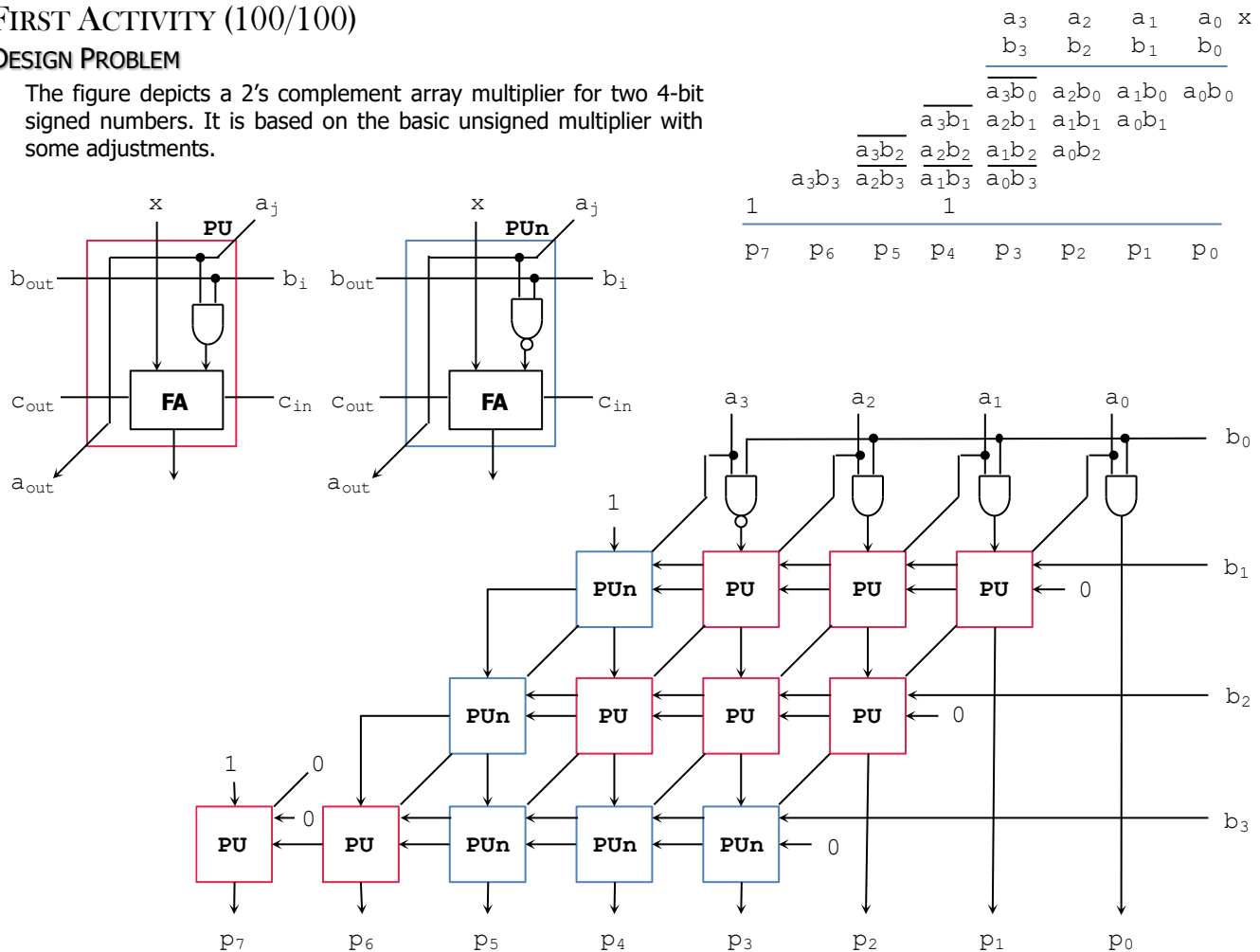
### DESIGN PROBLEM

- The figure depicts a 2's complement array multiplier for two 4-bit signed numbers. It is based on the basic unsigned multiplier with some adjustments.



## PROCEDURE

- **Vivado: Complete the following steps:**
  - ✓ Create a new Vivado Project. Select the corresponding Artix-7 FPGA device (e.g.: the XC7A50T-1CSG324 FPGA device for the Nexys A7-50T).
  - ✓ Write the VHDL code for this signed array multiplier. Synthesize your code.
    - Use the **Structural Description**: Create a separate .vhd file for the Full Adder, the Processing Unit (PU), the flipped Processing Unit (PUn) and the top file (Array Multiplier).
  - ✓ Write the VHDL testbench to test the circuit for all possible cases (256 cases). Use 'for loop'.
  - ✓ Perform Functional Simulation and Timing Simulation of your design. **Demonstrate this to your TA.**
    - Your simulation might need more time than Vivado Simulator's default (1 us). For example, to add 5 us, you can go to the TCL console and type: `run 5 us`.
    - Note that you can represent your data as signed (2C) integers (use Radix → Signed Decimal).

- ✓ I/O Assignment: Generate the XDC file associated with your board.


- Suggestion:

Board pin names	SW7	SW6	SW5	SW4	SW3	SW2	SW1	SW0	LED7	LED6	LED5	LED4	LED3	LED2	LED1	LED0
Signal names in code	A <sub>3</sub>	A <sub>2</sub>	A <sub>1</sub>	A <sub>0</sub>	B <sub>3</sub>	B <sub>2</sub>	B <sub>1</sub>	B <sub>0</sub>	P <sub>7</sub>	P <sub>6</sub>	P <sub>5</sub>	P <sub>4</sub>	P <sub>3</sub>	P <sub>2</sub>	P <sub>1</sub>	P <sub>0</sub>

- The board pin names are used by all the listed boards (Nexys A7-50T/A7-100T, Basys 3, Nexys 4/DDR). The I/Os listed here are all active high.
- ✓ Generate and download the bitstream on the FPGA and perform testing: use a sample of representative cases (e.g.: 8 cases) from your testbench. **Demonstrate this to your TA.**
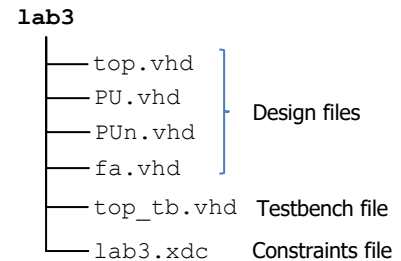
## SUBMISSION

- Submit to Moodle (an assignment will be created):
  - ✓ The lab sheet ([as a .pdf](#)) signed off by the TA (or instructor).
  - ✓ ([As a .zip file](#)) the six generated files: VHDL code (4 files), VHDL testbench, and XDC file. **DO NOT submit the whole Vivado Project.**
    - Your .zip file should only include one folder. Do not include subdirectories.
    - It is strongly recommended that all your design files, testbench, and constraints file be located in a single directory. This will allow for a smooth experience with Vivado.
    - You should only submit your source files AFTER you have demoed your work. Submission of work files without demoing will be assigned NO CREDIT.



TA signature: \_\_\_\_\_

Date: \_\_\_\_\_