

# Midterm Exam

(October 15<sup>th</sup> @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

## PROBLEM 1 (22 PTS)

- a) Complete the following table. The decimal numbers are unsigned: (3 pts.)

Decimal	BCD	Binary	Reflective Gray Code
			101011
	000100101000		

- b) Complete the following table. The decimal numbers are signed. Use the fewest number of bits in each case: (15 pts.)

REPRESENTATION			
Decimal	Sign-and-magnitude	1's complement	2's complement
	110001		
			10000
			1111
		0101001	
		1011010	

- c) Convert the following decimal numbers to their 2's complement representations. (4 pts)

✓ -9.25

✓ 8.75


## PROBLEM 2 (10 PTS)

- Sketch the circuit that computes  $|A - B|$ , where  $A, B$  are 4-bit signed (2C) numbers. For example,  $A = 0101, B = 1101 \rightarrow |A - B| = |5 - (-3)| = 8$ . You can only use full adders (or multi-bit adders) and logic gates. Your circuit must avoid overflow: design your circuit so that the result and intermediate operations have the proper number of bits.
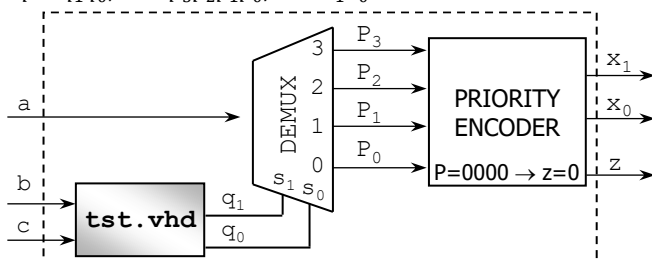
## PROBLEM 3 (15 PTS)

- Complete the timing diagram of the following circuit. The VHDL code (tst.vhd) corresponds to the shaded circuit.

$$q = q_1q_0, P = p_3p_2p_1p_0, x = x_1x_0$$



```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity tst is
  port (b, c : in std_logic;
        q: out std_logic_vector(1 downto 0));
end tst;
```


architecture bhv of tst is

signal t: std\_logic;

begin

```
t <= b xor c;
process (b,c,t)
begin
  q <= b & c;
  if t = '0' then
    q <= c & b;
  end if;
end process;
```

end bhv;

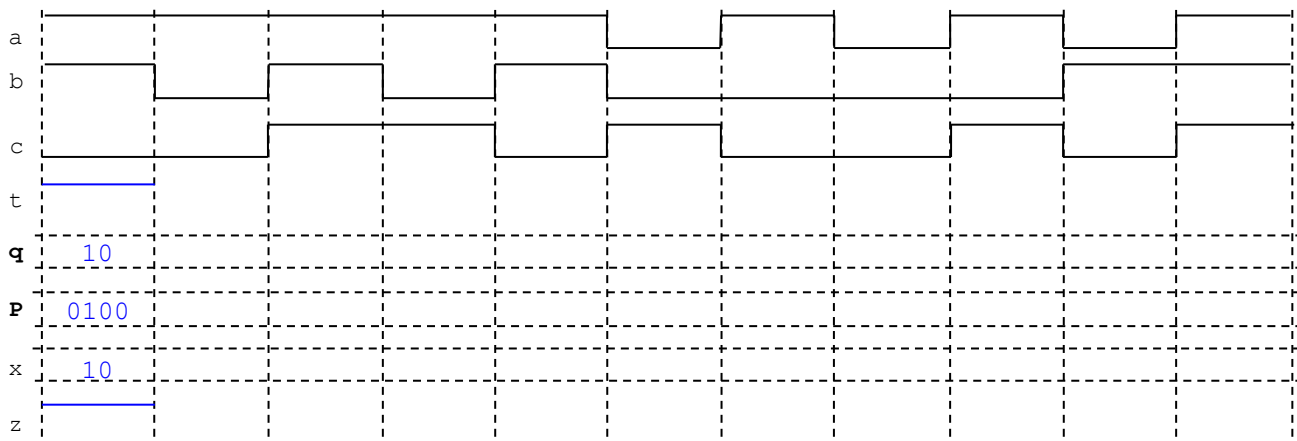


### PROBLEM 4 (11 PTS)

- Complete the timing diagram (signals *DO* and *DATA*) of the following circuit. The circuit in the blue box computes the signed operation *T-7*, with the result having 5 bits. *T* is a 4-bit signed (2C) number.

✓ Example: if  $T=1010$ :

$DO = 1010 - 0111 = 11010 + 11001$


$DO = 10011$

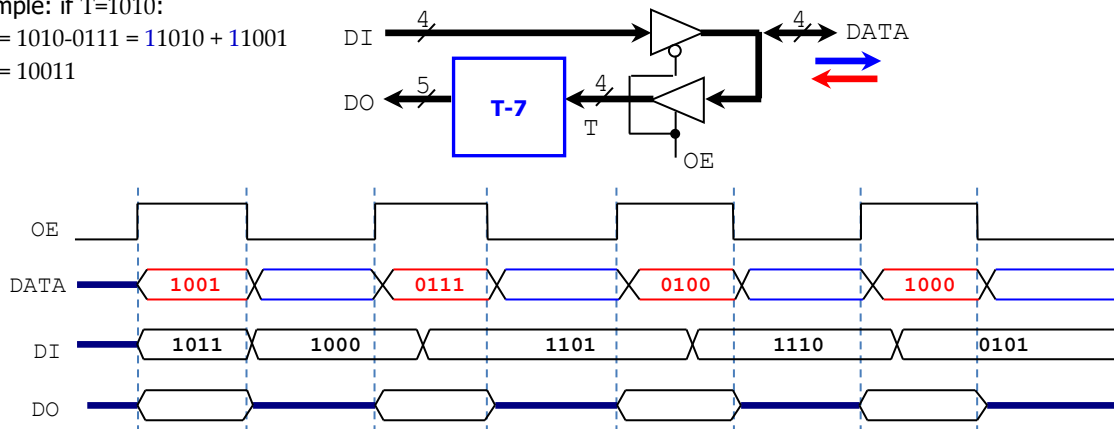
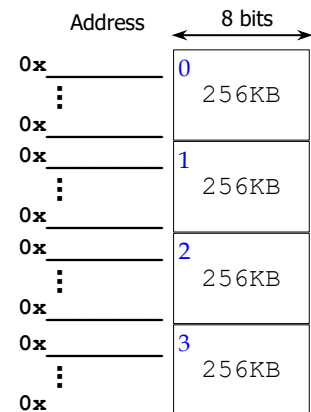
### PROBLEM 5 (10 PTS)

- A microprocessor has a memory space of 1 MB. Each memory address occupies one byte.  $1KB = 2^{10}$  bytes,  $1MB = 2^{20}$  bytes,  $1GB = 2^{30}$  bytes.

- What is the address bus size (number of bits of the address) of the microprocessor?
- What is the range (lowest to highest, in hexadecimal) of the memory space for this microprocessor? (1 pt.)
- The figure to the right shows four memory chips that are placed in the given positions:
  - Complete the address ranges (lowest to highest, in hexadecimal) for each of the memory chips. (8 pts)



### PROBLEM 6 (15 PTS)

- Perform the following additions and subtractions of the following unsigned integers. Use the fewest number of bits *n* to represent both operators. Indicate every carry (or borrow) from  $c_0$  to  $c_n$  (or  $b_0$  to  $b_n$ ). For the addition, determine whether there is an overflow. For the subtraction, determine whether we need to keep borrowing from a higher bit. (6 pts)

✓  $37 + 41$


✓  $37 - 41$

- For the decimal numbers in the figure, perform the signed (2C) 8-bit addition. The operands must be represented in 2's complement arithmetic with 8 bits. Also, complete all the carries and summation bits. Indicate the corresponding decimal number of the 8-bit result.

Does this 8-bit operation incur in overflow? Yes No

Value of the overflow bit: \_\_\_\_\_

Value of carry out bit: \_\_\_\_\_

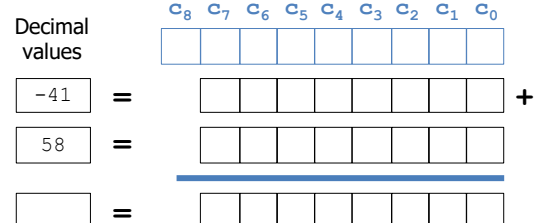

- Perform binary multiplication of the following numbers (they must be represented in 2's complement arithmetic). (3 pts)

✓  $-7 \times 9$

### PROBLEM 7 (17 PTS)

- Given the circuit in the figure:
  - Implement  $s_0$  using ONLY an 8-to-1 MUX. (5 pts.)
  - Implement  $c_1$  using ONLY 2-to-1 MUXs (AND, OR, NOT, XOR gates are not allowed). (12 pts)

