

Solutions - Homework 1

(Due date: September 19th @ 11:59 pm)

Presentation and clarity are very important! Show your procedure!

PROBLEM 1 (25 PTS)


- a) Simplify the following functions using ONLY Boolean Algebra Theorems. For each resulting simplified function, sketch the logic circuit using AND, OR, XOR, and NOT gates. (15 pts)

$$\checkmark F = \overline{\overline{x}(\overline{y \oplus z})} + y$$

$$\checkmark F = (A + \overline{B} + \overline{C})(\overline{A}B + \overline{C})$$


$$\checkmark F(x, y, z) = \prod(M_2, M_3, M_6, M_7)$$
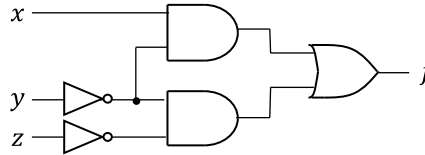
$$\checkmark F = \overline{\overline{x}(\overline{y \oplus z})} + y = \overline{\overline{x}(y \oplus z)} \cdot \overline{y} = (x + \overline{y \oplus z})\overline{y} = (x + yz + \overline{y} \cdot \overline{z})\overline{y} = x\overline{y} + \overline{y} \cdot \overline{z}$$




$$\checkmark F = (A + \overline{B} + \overline{C})(\overline{A}B + \overline{C}) = (X + \overline{C})(\overline{X} + \overline{C}) = X\overline{C} + \overline{X}\overline{C}, \quad X = A + \overline{B}$$
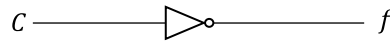
$$= (X + \overline{X})\overline{C} = \overline{C}$$



$$\checkmark F(x, y, z) = \prod(M_2, M_3, M_6, M_7) = \sum(m_0, m_1, m_4, m_5) = \overline{X}\overline{Y}\overline{Z} + \overline{X}\overline{Y}Z + X\overline{Y}\overline{Z} + X\overline{Y}Z = \overline{X}\overline{Y}(\overline{Z} + Z) + X\overline{Y}(\overline{Z} + Z)$$
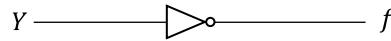
$$= \overline{X}\overline{Y} + X\overline{Y} = \overline{Y}$$



- b) Determine whether or not the following expression is valid, i.e., whether the left- and right-hand sides represent the same function. Suggestion: complete the truth tables for both sides: (5 pts)

$$\overline{x_1}x_2 + x_1x_3 + \overline{x_2}\overline{x_3} = \overline{x_1}\overline{x_3} + x_2x_3 + x_1\overline{x_2}$$

Left-hand side:

$$\overline{x_1}x_2(x_3 + \overline{x_3}) + x_1(\overline{x_2} + x_2)x_3 + (x_1 + \overline{x_1})\overline{x_2}\overline{x_3} = \overline{x_1}x_2x_3 + \overline{x_1}x_2\overline{x_3} + x_1x_2x_3 + x_1\overline{x_2}x_3 + x_1\overline{x_2}\overline{x_3} + \overline{x_1}\overline{x_2}\overline{x_3}$$

$$= \sum m(0, 2, 3, 4, 5, 7)$$

Right-hand side:

$$\overline{x_1}(x_2 + \overline{x_2})\overline{x_3} + (x_1 + \overline{x_1})x_2x_3 + x_1\overline{x_2}(x_3 + \overline{x_3}) = \overline{x_1}x_2\overline{x_3} + \overline{x_1}\overline{x_2}\overline{x_3} + x_1x_2x_3 + \overline{x_1}x_2x_3 + x_1\overline{x_2}x_3 + x_1\overline{x_2}\overline{x_3}$$

$$= \sum m(0, 2, 3, 4, 5, 7)$$

Both left-hand and right-hand equations represent the same Boolean function.

c) For the following Truth table with two outputs: (8 pts)

- Provide the Boolean functions using the Canonical Sum of Products (SOP), and Product of Sums (POS). (4 pts)
- Express the Boolean functions using the minterms and maxterms representations.
- Sketch the logic circuits as Canonical Sum of Products and Product of Sums. (3 pts)

x	y	z	f ₁	f ₂
0	0	0	0	0
0	0	1	1	1
0	1	0	0	1
0	1	1	0	0
1	0	0	0	1
1	0	1	0	0
1	1	0	1	1
1	1	1	1	0

Sum of Products

$$f_1 = \bar{x}\bar{y}z + xy\bar{z} + xyz$$

$$f_2 = \bar{x}\bar{y}z + \bar{x}y\bar{z} + x\bar{y}\bar{z} + xy\bar{z}$$

Product of Sums



$$f_1 = (x + y + z)(x + \bar{y} + \bar{z})(\bar{x} + y + z)(\bar{x} + y + \bar{z})$$

$$f_2 = (x + y + z)(x + \bar{y} + \bar{z})(\bar{x} + y + \bar{z})(\bar{x} + \bar{y} + \bar{z})$$

Minterms and maxterms:

$$f_1 = \sum(m_1, m_6, m_7) = \prod(M_0, M_2, M_3, M_4, M_5).$$
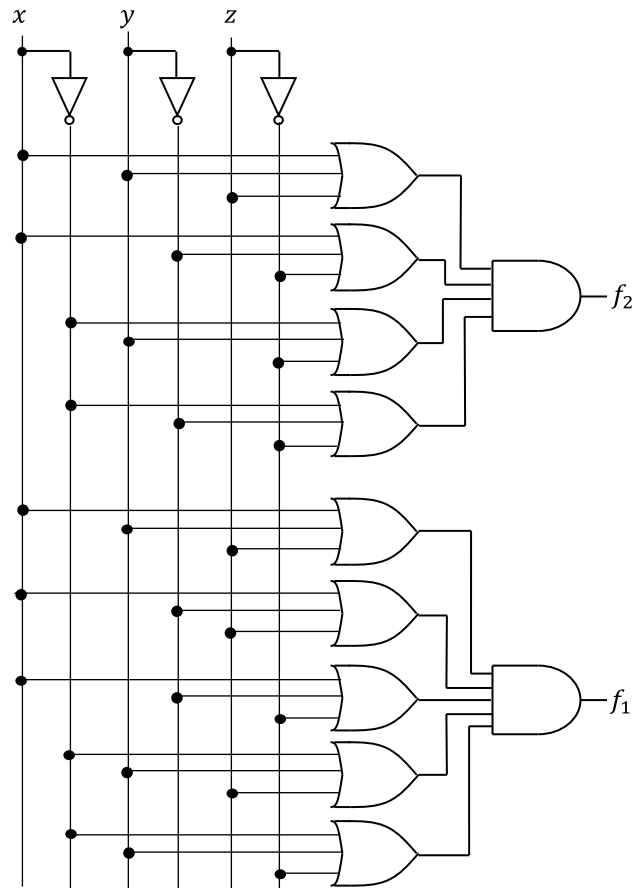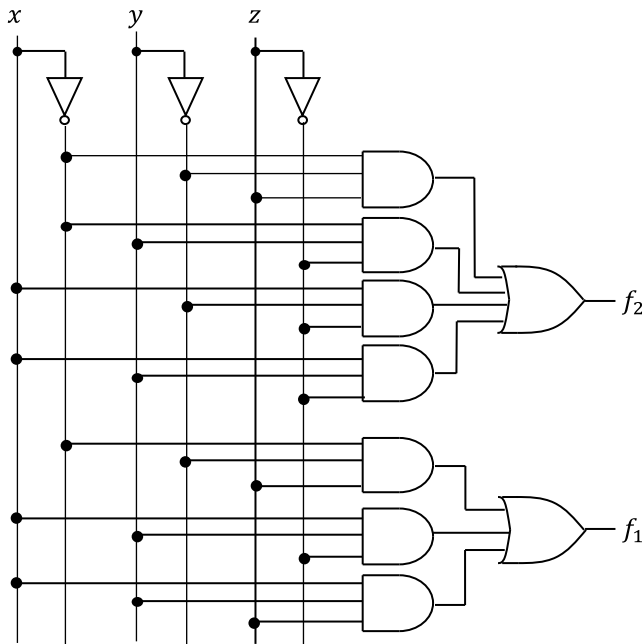
$$f_2 = \sum(m_1, m_2, m_4, m_6) = \prod(M_0, M_3, M_5, M_7).$$



PROBLEM 2 (10 PTS)

- The following is a truth table for logic functions f_1 and f_2 . Note that an 'X' on the input means that the logical value can be either '0' or '1'. So, if the input $xyzw$ is 01XX, it means that for the output f_1 to be 1, we only need $x = 0$ and $y = 1$.

- Provide the simplified Boolean expressions for f_1 and f_2 .

x	y	z	w	f ₁	f ₂
1	X	X	X	1	1
0	1	X	X	0	1
0	0	1	X	1	0
all others				0	0

$$f_1 = x \cdot f(y, z, w) + \bar{x}\bar{y}z \cdot h(w)$$

$$f_2 = x \cdot f(y, z, w) + \bar{x}y \cdot g(z, w)$$

$$f(y, z, w) = \sum m(0, 1, 2, 3, 4, 5, 6, 7) = 1, g(z, w) = \sum m(0, 1, 2, 3) = 1, h(w) = w + \bar{w} = 1$$



Then:

$$f_1 = x + \bar{x}\bar{y}z = x + \bar{y}z$$

$$f_2 = x + \bar{x}y = x + y$$

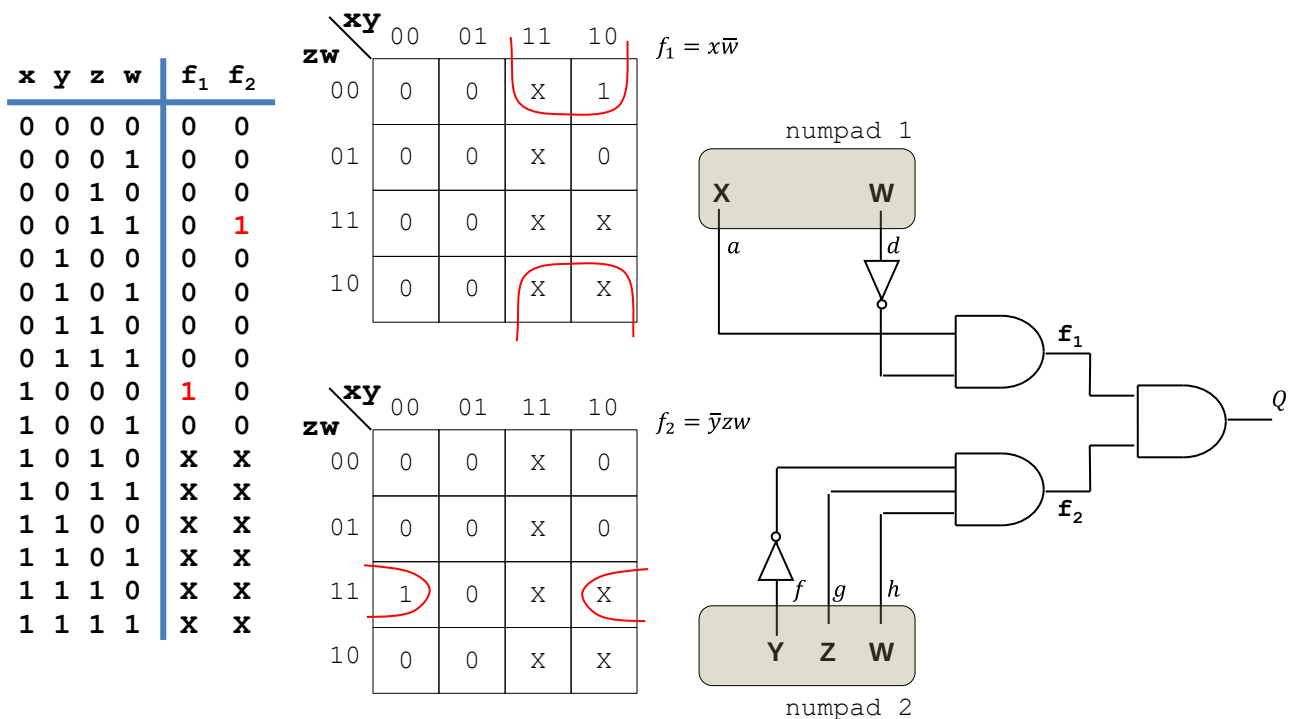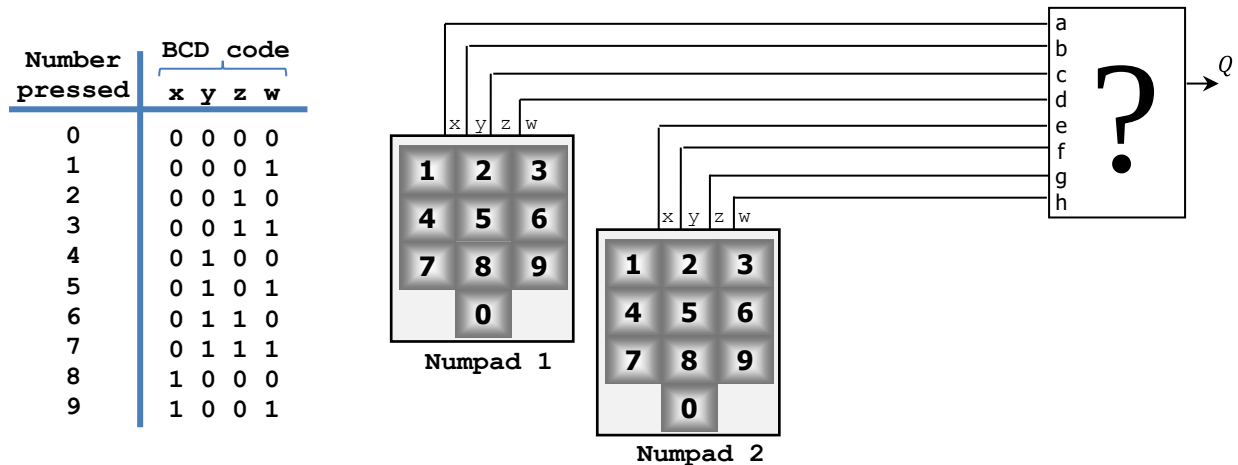PROBLEM 3 (11 PTS)



- We want to design a logic circuit that opens a lock ($Q = 1$) whenever the user presses the correct number on each numpad (numpad 1: **8**, numpad 2: **3**). The numpad encodes each decimal number using BCD encoding (see figure). We expect that the 4-bit groups generated by each numpad be in the range from 0000 to 1001. Note that the values from 1010 to 1111 are assumed not to occur.
- Provide the simplified expression for $Q(a, b, c, d, e, f, g, h)$ and sketch the logic circuit.
Suggestion: Create two circuits: one that verifies the first number (**8**), and another that verifies the second number (**3**). Then perform the AND operation on the two outputs. This avoids creating a truth table with 8 inputs.



$$Q = a\bar{d}\bar{f}gh = (a\bar{d})(\bar{f}g)h$$

PROBLEM 4 (26 PTS)

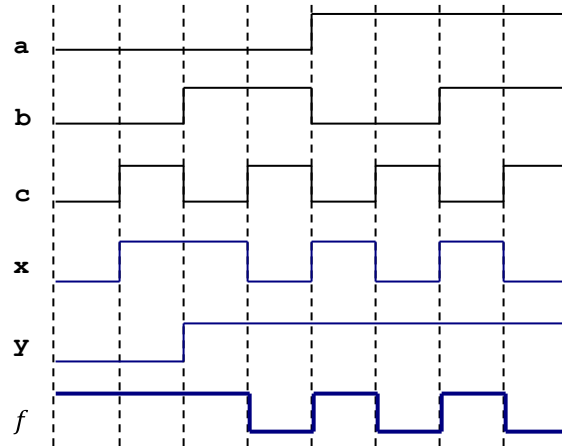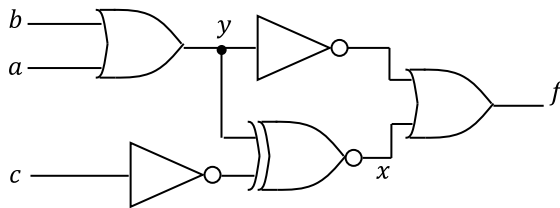a) Complete the timing diagram of the following circuit: (5 pts)




b) Complete the timing diagram of the logic circuit whose VHDL description is shown below: (7 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end circ;

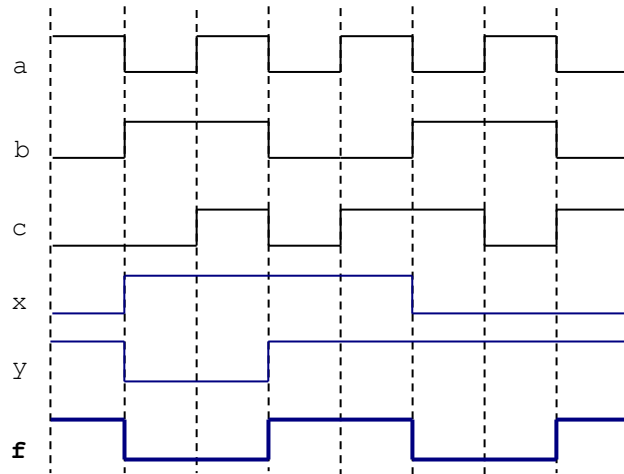architecture struct of circ is
  signal x, y: std_logic;
begin
  x <= a xor not(c);
  f <= y and (not b);
  y <= x nand b;
end struct;
```




c) The following is the timing diagram of a logic circuit with 3 inputs. Sketch the simplified logic circuit that generates this waveform. Then, complete the VHDL code. (8 pts)

```
library ieee;
use ieee.std_logic_1164.all;

entity wav is
  port ( a, b, c: in std_logic;
        f: out std_logic);
end wav;

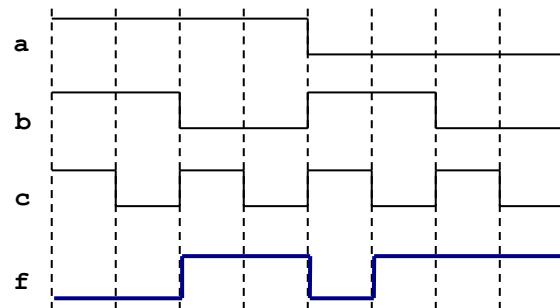
architecture struct of wav is
begin
  f <= not(b) or (a nor c)
end struct;
```




a	b	c	f
0	0	0	1
0	0	1	1
0	1	0	1
0	1	1	0
1	0	0	1
1	0	1	1
1	1	0	0
1	1	1	0

c	ab			
	00	01	11	10
0	1	1	0	1
1	1	0	0	1
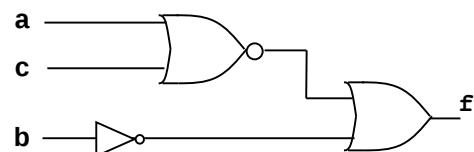
$$f = \bar{b} + \bar{a}c = \bar{b} + \overline{a+c}$$



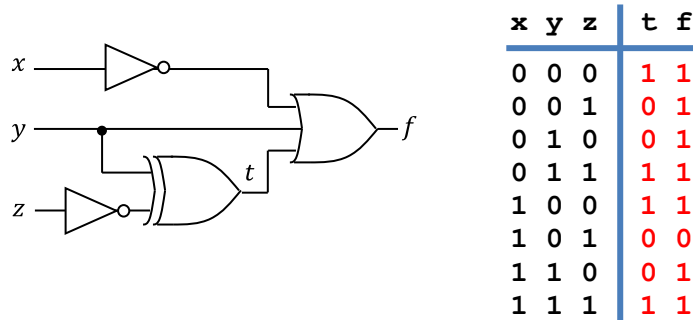
d) Construct the truth table describing the output of the following circuit and write the simplified Boolean equation (6 pts).



$$f = \bar{x} + y + \bar{z}$$

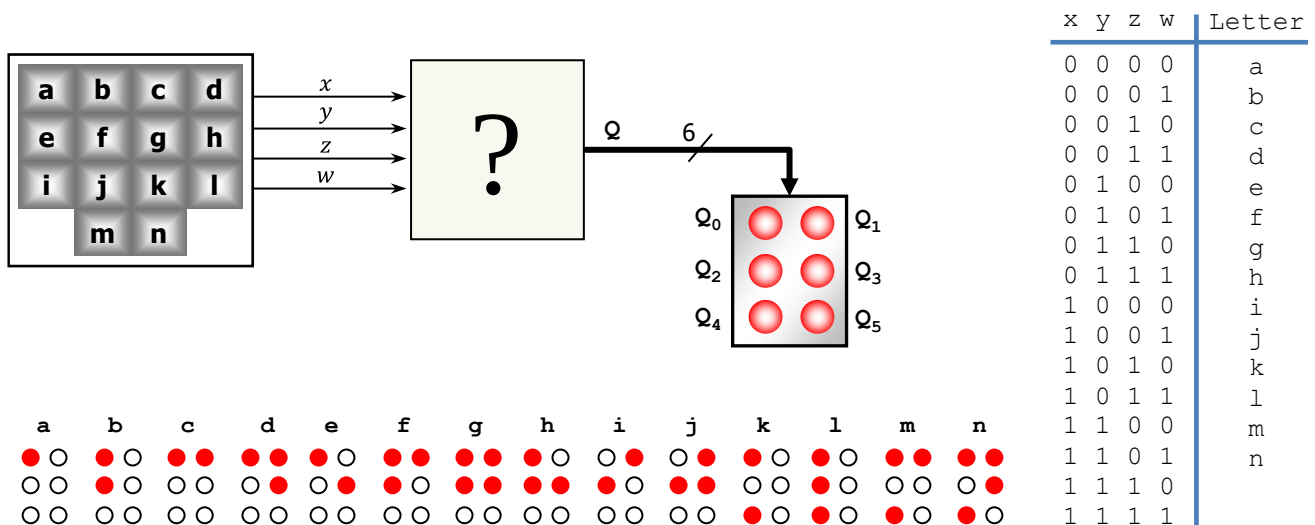PROBLEM 5 (25 PTS)

- A 14-letter keypad produces a 4-bit code as shown in the table. We want to design a logic circuit that converts those 4-bit codes to Braille code, where the 6 dots are represented by LEDs. A raised (or embossed) dot is represented by an LED ON (logic value of '1'). A missing dot is represented by a LED off (logic value of '0').
- Complete the truth table for each output (Q_0 - Q_5). (4 pts)
- Provide the simplified expression for each output (Q_0 - Q_5). Use Karnaugh maps for Q_5, Q_4, Q_1, Q_0 and the Quine-McCluskey algorithm for Q_3 - Q_2 . Note it is safe to assume that the codes 1110 and 1111 will not be produced by the keypad.



x	y	z	w	Q ₅	Q ₄	Q ₃	Q ₂	Q ₁	Q ₀	Letter
0	0	0	0	0	0	0	0	0	1	a
0	0	0	1	0	0	0	1	0	1	b
0	0	1	0	0	0	0	0	1	1	c
0	0	1	1	0	0	1	0	1	1	d
0	1	0	0	0	0	1	0	0	1	e
0	1	0	1	0	0	0	1	1	1	f
0	1	1	0	0	0	1	1	1	1	g
0	1	1	1	0	0	1	1	0	1	h
1	0	0	0	0	0	0	1	1	0	i
1	0	0	1	0	0	1	1	1	0	j
1	0	1	0	0	1	0	0	0	1	k
1	0	1	1	0	1	0	1	0	1	l
1	1	0	0	0	1	0	0	1	1	m
1	1	0	1	0	1	1	0	1	1	n
1	1	1	0	X	X	X	X	X	X	
1	1	1	1	X	X	X	X	X	X	

Q₅ = 0

Q₄ = xz + xy

Q₃ = x̄ȳw + x̄zw + xz̄w

Q₂ = yz + x̄z̄w + x̄ȳz̄ + x̄ȳw

Q₁ = x̄ȳz + yz̄w + x̄z̄w + xz̄

Q₀ = x̄ + y + z

- $Q_3 = \sum m(3,4,6,7,9,13) + \sum d(14,15)$.

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
1	$m_4 = 0100$ ✓	$m_{4,6} = 01-0$	$m_{6,14,7,15} = -11-$ $m_{6,7,14,15} = -11-$	We can't combine any further, so we stop here
2	$m_3 = 0011$ ✓ $m_6 = 0110$ ✓ $m_9 = 1001$ ✓	$m_{3,7} = 0-11$ ✓ $m_{6,7} = 011-$ ✓ $m_{6,14} = -110$ ✓ $m_{9,13} = 1-01$		
3	$m_7 = 0111$ ✓ $m_{13} = 1101$ ✓ $m_{14} = 1110$ ✓	$m_{7,15} = -111$ ✓ $m_{13,15} = 11-1$ $m_{14,15} = 111-$ ✓		
4	$m_{15} = 1111$ ✓			

Prime Implicants		Minterms					
		3	4	6	7	9	13
$m_{4,6}$	$\bar{x}y\bar{w}$		X	X			
$m_{3,7}$	$\bar{x}zw$	X			X		
$m_{9,13}$	$x\bar{z}w$					X	X
$m_{13,15}$	$x\bar{y}w$						X
$m_{6,14,7,15}$	yz			X	X		

$$\rightarrow Q_3 = \bar{x}y\bar{w} + \bar{x}zw + x\bar{z}w$$

- $Q_2 = \sum m(1,5,6,7,8,9,11) + \sum d(14,15)$.

Number of ones	4-literal implicants	3-literal implicants	2-literal implicants	1-literal implicants
1	$m_1 = 0001$ ✓ $m_8 = 1000$ ✓	$m_{1,5} = 0-01$ $m_{1,9} = -001$ $m_{8,9} = 100-$	$m_{6,7,14,15} = -11-$ $m_{6,7,14,15} = -11-$	We can't combine any further, so we stop here
2	$m_5 = 0101$ ✓ $m_6 = 0110$ ✓ $m_9 = 1001$ ✓	$m_{5,7} = 01-1$ $m_{6,7} = 011-$ ✓ $m_{6,14} = -110$ ✓ $m_{9,11} = 10-1$		
3	$m_7 = 0111$ ✓ $m_{11} = 1011$ ✓ $m_{14} = 1110$ ✓	$m_{7,15} = -111$ ✓ $m_{11,15} = 1-11$ $m_{14,15} = 111-$ ✓		
4	$m_{15} = 1111$ ✓			

Prime Implicants		Minterms						
		1	5	6	7	8	9	11
$m_{1,5}$	$\bar{x}\bar{z}w$	X	X					
$m_{1,9}$	$\bar{y}\bar{z}w$	X					X	
$m_{8,9}$	$x\bar{y}\bar{z}$					X	X	
$m_{5,7}$	$\bar{x}yw$		X		X			
$m_{9,11}$	$x\bar{y}w$						X	X
$m_{11,15}$	xzw							X
$m_{6,7,14,15}$	yz			X	X			

$$\rightarrow Q_2 = yz + \bar{x}\bar{z}w + x\bar{y}\bar{z} + x\bar{y}w$$