

# Solutions - Midterm Exam

(October 15<sup>th</sup> @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

## PROBLEM 1 (22 PTS)

a) Complete the following table. The decimal numbers are unsigned: (3 pts.)

Decimal	BCD	Binary	Reflective Gray Code
50	01010000	110010	101011
128	000100101000	10000000	11000000

b) Complete the following table. The decimal numbers are signed. Use the fewest number of bits in each case: (15 pts.)

REPRESENTATION			
Decimal	Sign-and-magnitude	1's complement	2's complement
-17	110001	101110	101111
-16	110000	101111	10000
-1	11	10	1111
41	0101001	0101001	0101001
-37	1100101	1011010	1011011

c) Convert the following decimal numbers to their 2's complement representations. (4 pts)

✓ -9.25

+9.25 = 01001.01  $\Rightarrow$  -17.25 = 10110.11

✓ 8.75

+8.75 = 01000.11

## PROBLEM 2 (10 PTS)

- Sketch the circuit that computes  $|A - B|$ , where  $A, B$  are 4-bit signed (2C) numbers. For example,  $A = 0101, B = 1101 \rightarrow |A - B| = |5 - (-3)| = 8$ . You can only use full adders (or multi-bit adders) and logic gates. Your circuit must avoid overflow: design your circuit so that the result and intermediate operations have the proper number of bits.

$$A = a_3a_2a_1a_0, B = b_3b_2b_1b_0$$


 $A, B \in [-8, 7] \rightarrow A, B$  require 4 bits in 2C representation.

 ✓  $X = A - B \in [-15, 15]$  requires 5 bits in 2C. Thus, we need to zero-extend  $A$  and  $B$ .

 ✓  $|X| = |A - B| \in [0, 15]$  requires 5 bits in 2C. Thus, the second operation  $0 \pm X$  only requires 5 bits.

 ▫ If  $x_4 = 1 \rightarrow X < 0 \rightarrow$  we do  $0 - X$ .


 ▫ If  $x_4 = 0 \rightarrow X \geq 0 \rightarrow$  we do  $0 + X$ .

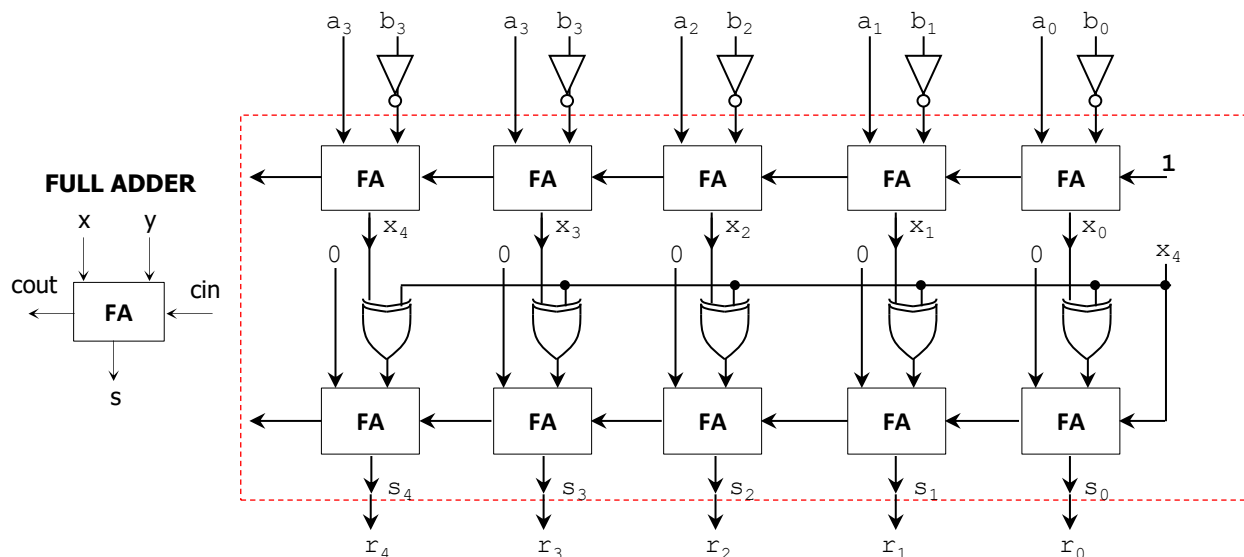 ✓  $R = |A - B| \in [0, 15]$  requires 5 bits in 2C. Note that the MSB is always 0.

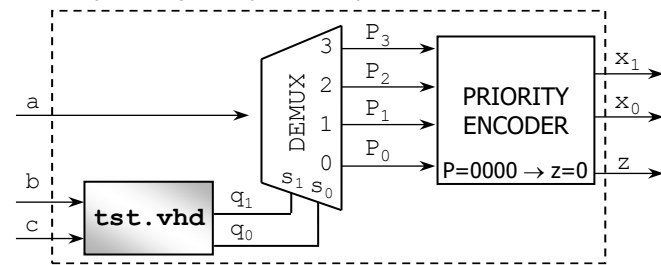
### PROBLEM 3 (15 PTS)

- Complete the timing diagram of the following circuit. The VHDL code (tst.vhd) corresponds to the shaded circuit.

$$q = q_1q_0, P = p_3p_2p_1p_0, x = x_1x_0$$



```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity tst is
  port (b, c : in std_logic;
        q: out std_logic_vector(1 downto 0));
end tst;
```


architecture bhv of tst is

```
  signal t: std_logic;
```

```
begin
```

```
  t <= b xor c;
  process (b,c,t)
  begin
    q <= b & c;
    if t = '0' then
      q <= c & b;
    end if;
  end process;
```

```
end bhv;
```

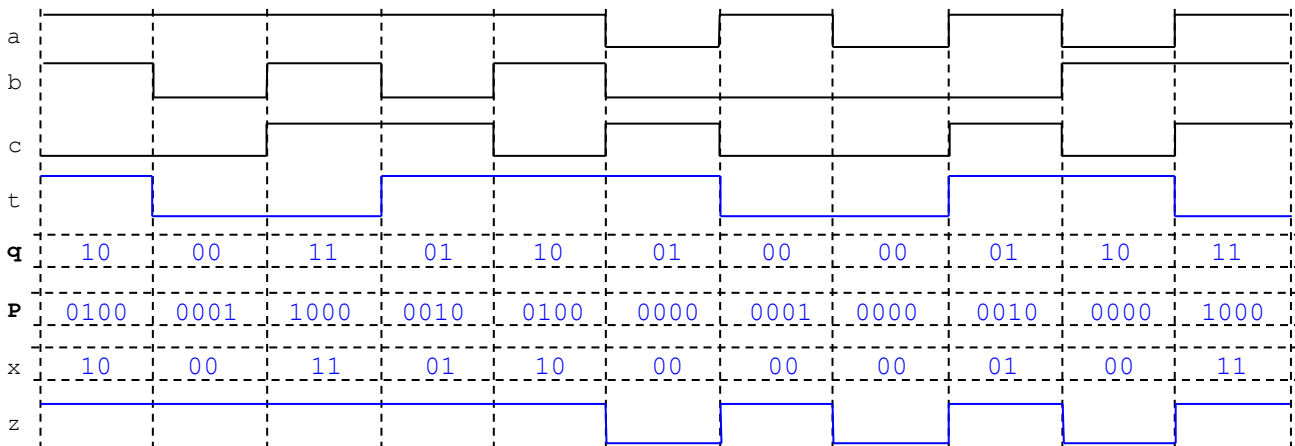



### PROBLEM 4 (11 PTS)

- Complete the timing diagram (signals DO and DATA) of the following circuit. The circuit in the blue box computes the signed operation T-7, with the result having 5 bits. T is a 4-bit signed (2C) number.

✓ Example: if T=1010:


$$DO = 1010 - 0111 = 11010 + 11001$$

$$DO = 10011$$

  
 
### PROBLEM 5 (10 PTS)

- A microprocessor has a memory space of 1 MB. Each memory address occupies one byte. 1KB =  $2^{10}$  bytes, 1MB =  $2^{20}$  bytes, 1GB =  $2^{30}$  bytes.
- a) What is the address bus size (number of bits of the address) of the microprocessor?  
Size of memory space: 1 MB =  $2^{20}$  bytes. Thus, we require 20 bits to address the memory space.
- b) What is the range (lowest to highest, in hexadecimal) of the memory space for this microprocessor? (1 pt.)  
With 20 bits, the address range is 0x00000 to 0xFFFFF.
- c) The figure to the right shows four memory chips that are placed in the given positions:
  - ✓ Complete the address ranges (lowest to highest, in hexadecimal) for each of the memory chips. (8 pts)



Address	8 bits
0000 0000 0000 0000 0000: 0x00000	0
0000 0000 0000 0000 0001: 0x00001	256KB
...	
0011 1111 1111 1111 1111: 0x3FFFF	
0100 0000 0000 0000 0000: 0x40000	1
0100 0000 0000 0000 0001: 0x40001	256KB
...	
0111 1111 1111 1111 1111: 0x7FFFF	
1000 0000 0000 0000 0000: 0x80000	2
1000 0000 0000 0000 0001: 0x80001	256KB
...	
1011 1111 1111 1111 1111: 0xBFFFF	
1100 0000 0000 0000 0000: 0xC0000	3
1100 0000 0000 0000 0001: 0xC0001	256KB
...	
1111 1111 1111 1111 1111: 0xFFFFF	

### PROBLEM 6 (15 PTS)

- a) Perform the following additions and subtractions of the following unsigned integers. Use the fewest number of bits  $n$  to represent both operators. Indicate every carry (or borrow) from  $c_0$  to  $c_n$  (or  $b_0$  to  $b_n$ ). For the addition, determine whether there is an overflow. For the subtraction, determine whether we need to keep borrowing from a higher bit. (6 pts)

✓ 37 + 41

$$\begin{array}{r}
 37 = 0x25 = 1\ 0\ 0\ 1\ 0\ 1\ + \\
 41 = 0x29 = 1\ 0\ 1\ 0\ 0\ 1 \\
 \hline
 \text{Overflow!} \rightarrow 1\ 0\ 0\ 1\ 1\ 1\ 0
 \end{array}$$

✓ 37 - 41

$$\begin{array}{r}
 37 = 0x25 = 1\ 0\ 0\ 1\ 0\ 1\ - \\
 41 = 0x29 = 1\ 0\ 1\ 0\ 0\ 1 \\
 \hline
 1\ 1\ 1\ 1\ 0\ 0
 \end{array}$$

- b) For the decimal numbers in the figure, perform the signed (2C) 8-bit addition. The operands must be represented in 2's complement arithmetic with 8 bits. Also, complete all the carries and summation bits. Indicate the corresponding decimal number of the 8-bit result.

Does this 8-bit operation incur in overflow? Yes ~~No~~

Value of the overflow bit:  $c_8 \oplus c_7 = 0$

Value of carry out bit:  $c_8 = 1$

Decimal values	$c_8$	$c_7$	$c_6$	$c_5$	$c_4$	$c_3$	$c_2$	$c_1$	$c_0$
-41	1	1	1	1	1	1	1	0	0
58	1	1	0	1	0	1	1	1	1
17	0	0	1	1	1	0	1	0	0

- c) Perform binary multiplication of the following numbers (they must be be represented in 2's complement arithmetic). (3 pts)

✓ -7 x 9



$$\begin{array}{r}
 1\ 0\ 0\ 1 \times 1\ 0\ 0\ 1 \\
 0\ 1\ 0\ 0\ 1 \times 0\ 1\ 1\ 1 \\
 \hline
 1\ 0\ 0\ 1 \\
 1\ 0\ 0\ 1 \\
 1\ 0\ 0\ 1 \\
 0\ 0\ 0\ 0 \\
 \hline
 0\ 1\ 1\ 1\ 1\ 1\ 1 \\
 \hline
 1\ 0\ 0\ 0\ 0\ 0\ 1
 \end{array}$$

### PROBLEM 7 (17 PTS)

- Given the circuit in the figure:
  - Implement  $s_0$  using ONLY an 8-to-1 MUX. (5 pts.)

$$s_0(x_0, y_0, c_0) = x_0 \oplus y_0 \oplus c_0$$

$x_0$	$y_0$	$c_0$	$c_1$	$s_0$
0	0	0	0	0
0	0	1	0	1
0	1	0	0	1
0	1	1	1	0
1	0	0	0	1
1	0	1	1	0
1	1	0	1	0
1	1	1	1	1

  

- Implement  $c_1$  using ONLY 2-to-1 MUXs (AND, OR, NOT, XOR gates are not allowed). (12 pts)

$$c_1(x_0, y_0, c_0) = x_0 y_0 + x_0 c_0 + y_0 c_0$$

$$c_1(x_0, y_0, c_0) = \overline{x_0}c_1(0, y_0, c_0) + x_0c_1(1, y_0, c_0) = \overline{x_0}(y_0c_0) + x_0(y_0 + c_0 + y_0c_0)$$

$$c_1(x_0, y_0, c_0) = \overline{x_0}g(y_0, c_0) + x_0h(y_0, c_0)$$

$$g(y_0, c_0) = \overline{y_0}g(0, c_0) + y_0g(1, c_0) = \overline{y_0}(0) + y_0(c_0)$$

$$h(y_0, c_0) = \overline{y_0}h(0, c_0) + y_0h(1, c_0) = \overline{y_0}(c_0) + y_0(1)$$

