

Solutions - Quiz 4


(November 19th @ 5:30 pm)

PROBLEM 1 (35 PTS)

- Draw the state diagram (in ASM form) of the FSM whose VHDL description is listed below:

```
library ieee;
use ieee.std_logic_1164.all;

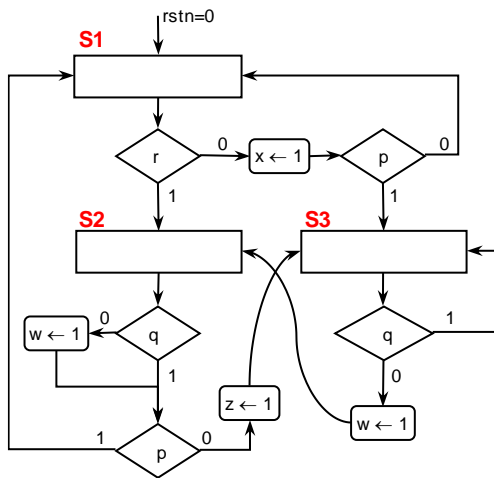entity circ is
  port ( clk, rstn: in std_logic;
        r, p, q: in std_logic;
        x, w, z: out std_logic);
end circ;
```



- Circle or mark the correct FSM type:
(Mealy) (Moore)

```
architecture behavioral of circ is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (rstn, clk, r, p, q)
  begin
    if rstn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if r = '1' then y <= S2;
          else if p = '1' then y <= S3; else y <= S1; end if;
          end if;
        when S2 =>
          if p = '1' then y <= S1; else y <= S3; end if;
        when S3 =>
          if q = '1' then y <= S3; else y <= S2; end if;
      end case;
    end if;
  end process;

  Outputs: process (y, r, p, q)
  begin
    x <= '0'; w <= '0'; z <= '0';
    case y is
      when S1 => if r = '0' then x <= '1'; end if;
      when S2 => if q = '0' then w <= '1'; end if;
                   if p = '0' then z <= '1'; end if;
      when S3 => if q = '0' then w <= '1'; end if;
    end case;
  end process;
end behavioral;
```

PROBLEM 2 (35 PTS)


- Given the following FSM circuit:
 - Provide the Excitation Table and the Excitation equations (including the Boolean equation for z).

$$Q_1(t+1) \leftarrow Q_0(t)$$

$$Q_0(t+1) \leftarrow Q_1(t) \oplus w$$

$$z = Q_1(t) \oplus Q_0(t) \oplus w$$

PRESENT STATE			NEXTSTATE	
w	Q ₁ Q ₀ (t)		Q ₁ Q ₀ (t+1)	z
0	0 0		0 1	0
0	0 1		1 1	1
0	1 0		0 0	1
0	1 1		1 0	0
1	0 0		0 0	1
1	0 1		1 0	0
1	1 0		0 1	0
1	1 1		1 1	1

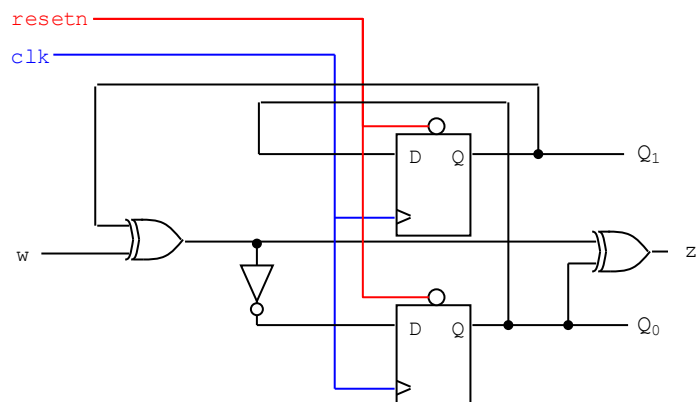

- Is this a Mealy or a Moore FSM? Why? (5 pts)
The output z depends on input w as well as on the present state. Thus, it is a Mealy FSM.

PROBLEM 3 (30 PTS)

- Sequence detector: Draw the state diagram (any representation) of an FSM with input x and output z . The detector asserts $z = 1$ when the sequence 0110 is detected. Right after the sequence is detected, the circuit looks for a new sequence.

