

# Banner on Seven Segment Displays


With Varying Speeds and Scrolling Messages

Arsha Ali, Drew Correll, Nina Luong, Bruce McCallister

# Overview

- Patterns
  - Forward pattern banner
  - Backward pattern banner
  - “HELLO” scrolling message
  - “ECE2700” scrolling message
- Switches
  - Stop
  - One of four speeds
  - One of four patterns

# Circuit Overview

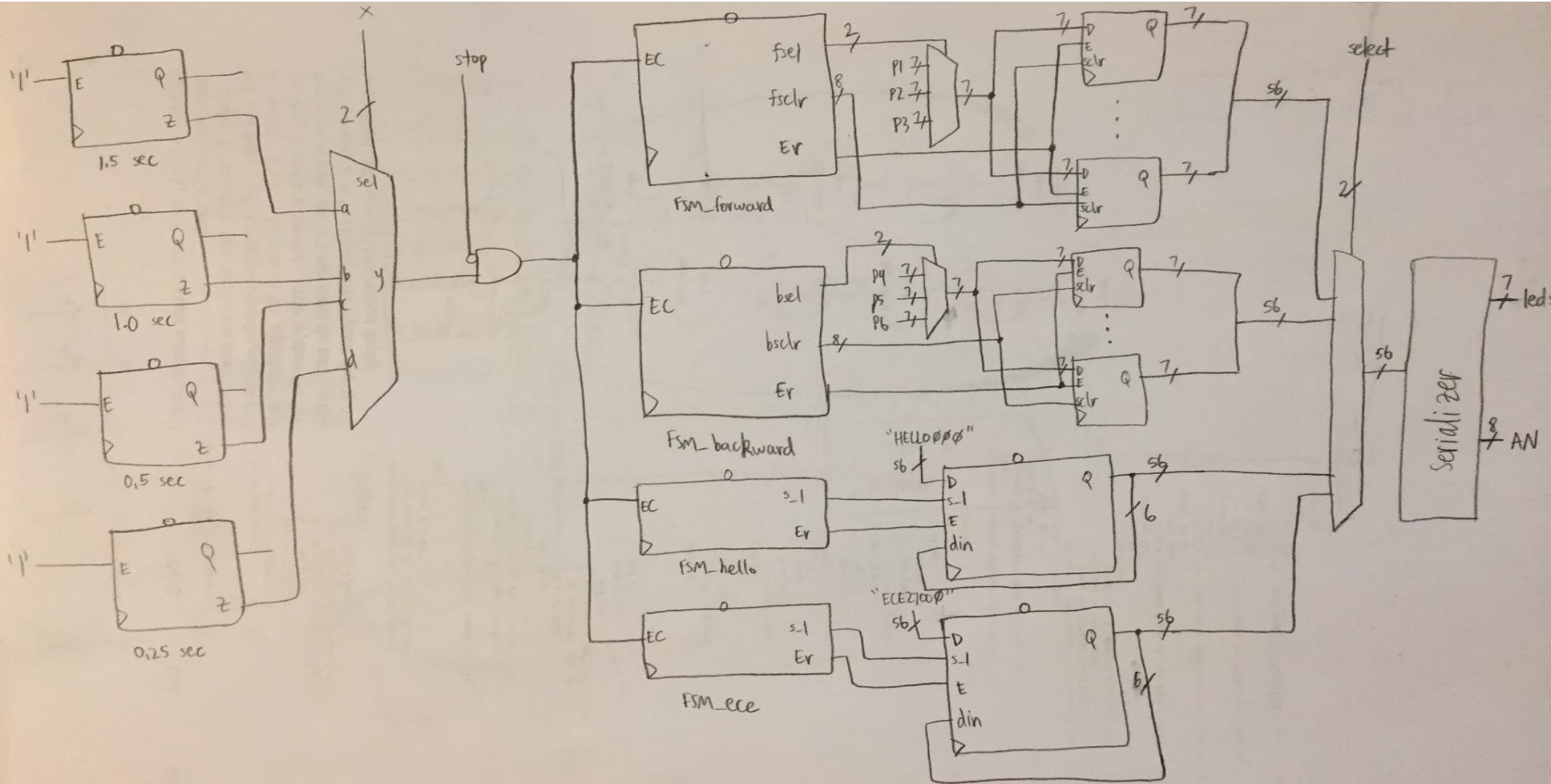

# FSM\_forward




For each of the eight seven segment displays, there are three different states that illuminate on each anode (active low).

**FSEL**

00  
01  
10

**LEDs**

0111001  
0011100  
0001111

 


# FSM\_backward




For each of the eight seven segment displays, there are three different states that illuminate on each anode (active low).

BSEL	LEDs
00	1000111
01	1100011
10	1110001

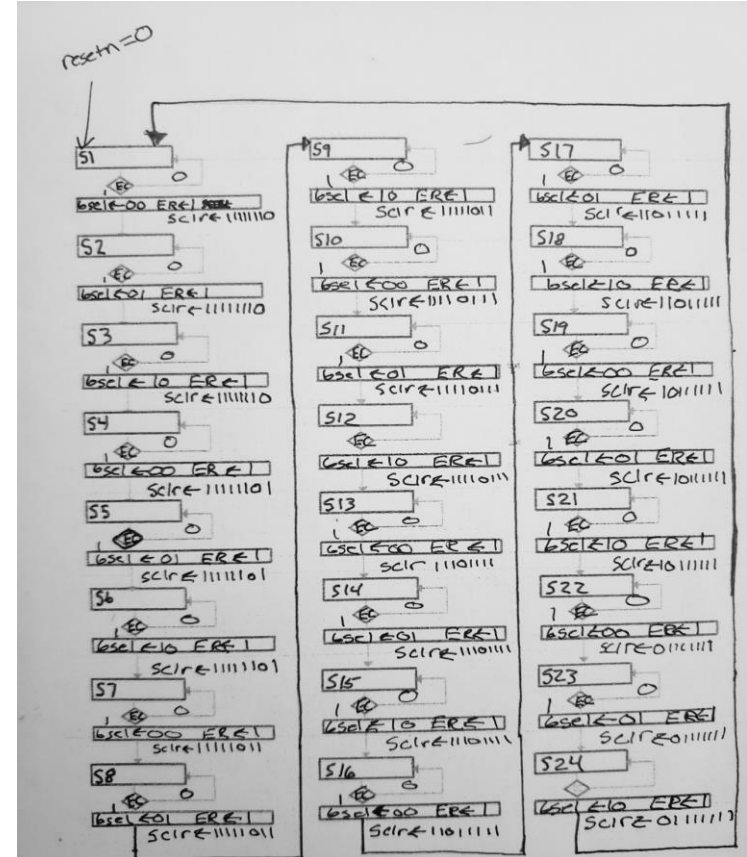
 
# FSM\_hello

FSM controls a parallel access right shift register to allow the “HELLO” message to flow from AN7 to AN0 and repeat.



# FSM\_ece2700

The FSM for “ECE2700” has the same state diagram as that of the FSM for “HELLO.” The transition and outputs processes are displayed.



```
architecture Behavioral of FSM_ece is
```

```
    type state is (S1, S2);
```

```
    signal y: state;
```

```
begin
```

```
    Transitions: process(clock, resetn, Ec, y)
```

```
    begin
```

```
        if resetn = '0' then y <= S1;
```

```
        elsif (clock'event and clock = '1') then
```

```
            case y is
```

```
                when S1 => y<=S2;
```

```
                when S2 => y <= S2;
```

```
            end case;
```

```
        end if;
```

```
    end process;
```

```
    Outputs: process (clock, resetn, Ec, y)
```

```
    begin
```

```
        s_1<= '1'; Er <= '0';--default values
```

```
        case y is
```

```
            when S1 => Er <= '1'; s_1 <= '1';
```

```
            when S2 =>
```

```
                if Ec = '1' then Er <= '1'; s_1 <= '0';
```

```
                end if;
```


```
            end case;
```

```
    end process;
```


```
end Behavioral;
```

# Demo

Name	Value
resetrn	1
clock	0
stop	0
x[1:0]	00
MasterSel[1:0]	00
leds[6:0]	7f
AN[7:0]	ef
T	10000 ps
serializerIn	1

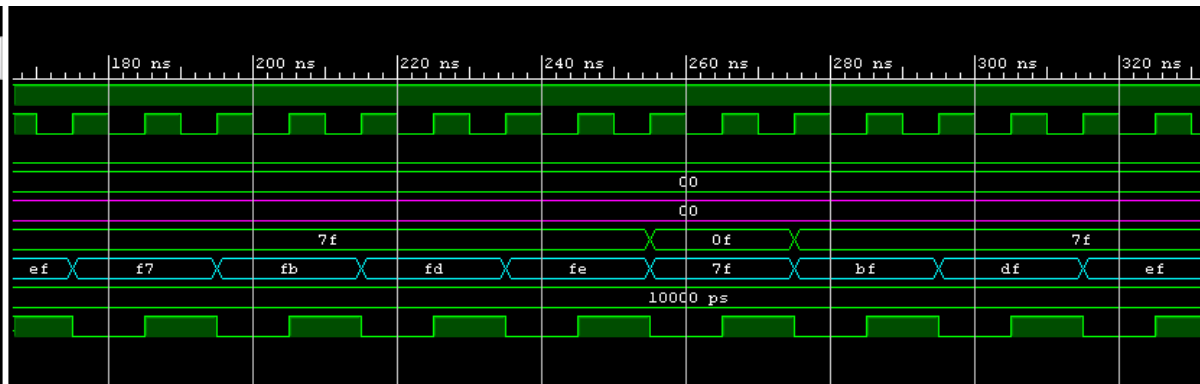

Name	Value
resetrn	1
clock	1
stop	0
x[1:0]	00
MasterSel[1:0]	10
leds[6:0]	0110000
AN[7:0]	fe
T	10000 ps
serializerIn	0
Q[55:0]	e3c40fffffe430

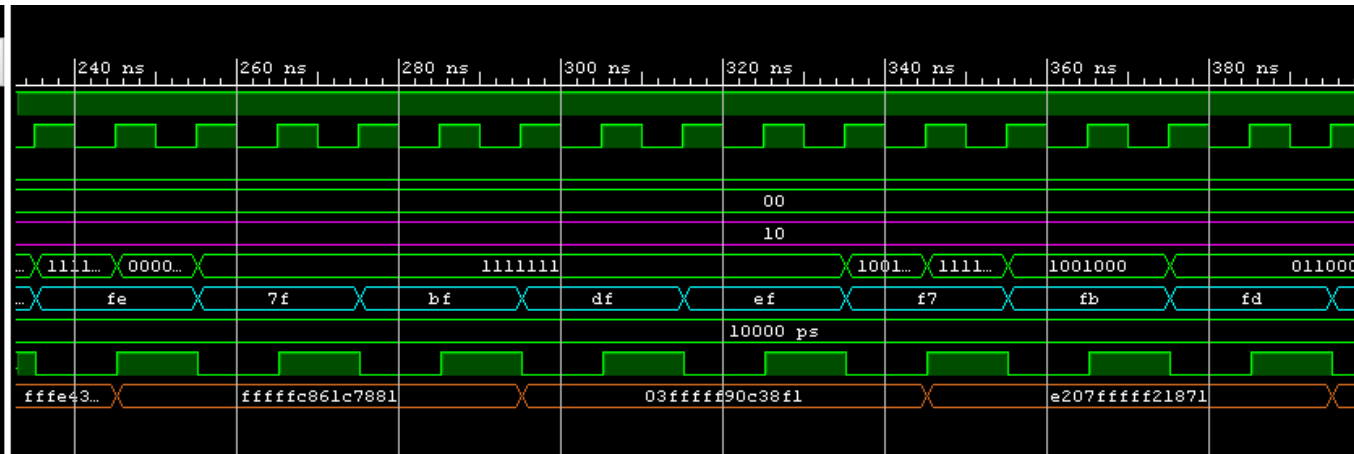



# Conclusions

- Four patterns and speed controlled by switches
- Total of 5 FSMs
- Datapath circuit
  - 7-bit registers
  - Shift registers
  - MUXs
  - NOT & AND gates
  - Serializer
    - FSM controlled by 1ms counter
    - Decoder
    - MUX

## References

Llamocca, Daniel. "Notes - Unit 7." *Introductions to Digital Systems Design*, Jan. 2018, pp.12–13., [moodle.oakland.edu/pluginfile.php/4385644/mod\\_resource/content/5/Notes%20-%20Unit%207.pdf](http://moodle.oakland.edu/pluginfile.php/4385644/mod_resource/content/5/Notes%20-%20Unit%207.pdf).

Llamocca, Daniel. "Unit 7: Digital System Design." *VHDL Coding for FPGAs*, slides6-7., <http://www.secs.oakland.edu/~llamocca/Tutorials/VHDLFPGA/Unit%207.pdf>

Llamocca, Daniel. "Serializer: Four 7-segment displays." *VHDL Projects (VHDL files, testbench)*, [http://www.secs.oakland.edu/~llamocca/Tutorials/VHDLFPGA/ISE/Unit\\_7/serializer.vhd](http://www.secs.oakland.edu/~llamocca/Tutorials/VHDLFPGA/ISE/Unit_7/serializer.vhd)