


Homework 3

(Due date: March 15th @ 5:30 pm)


Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (12 PTS)

- Complete the timing diagram of the circuit shown below. (5 pts)




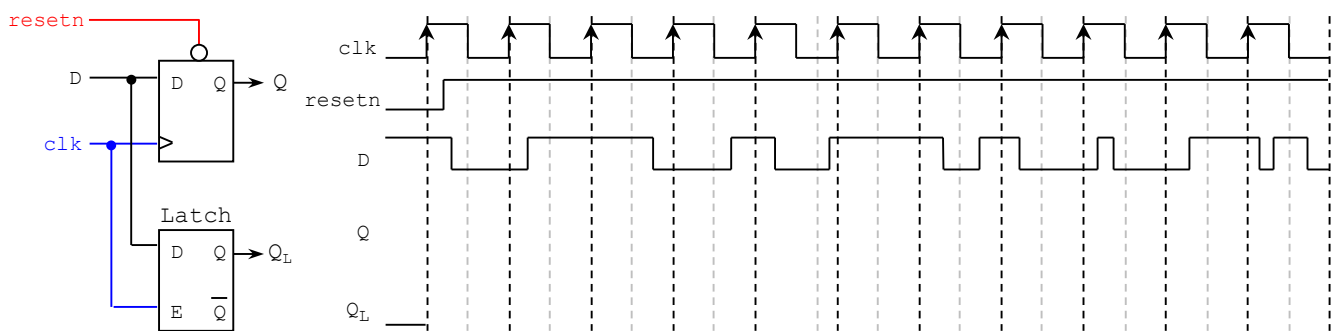- Complete the timing diagram of the circuits shown below: (7 pts)




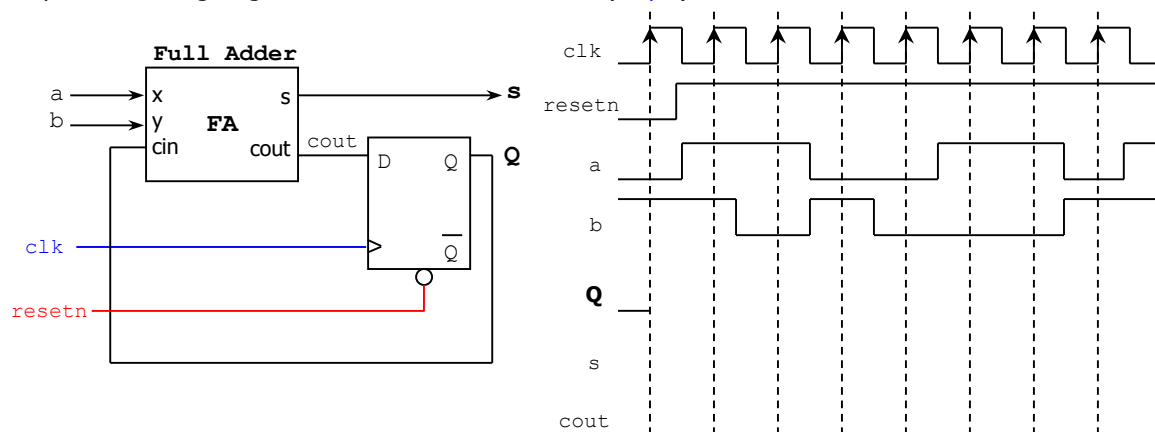PROBLEM 2 (33 PTS)

- Complete the timing diagram of the circuit shown below: (10 pts)



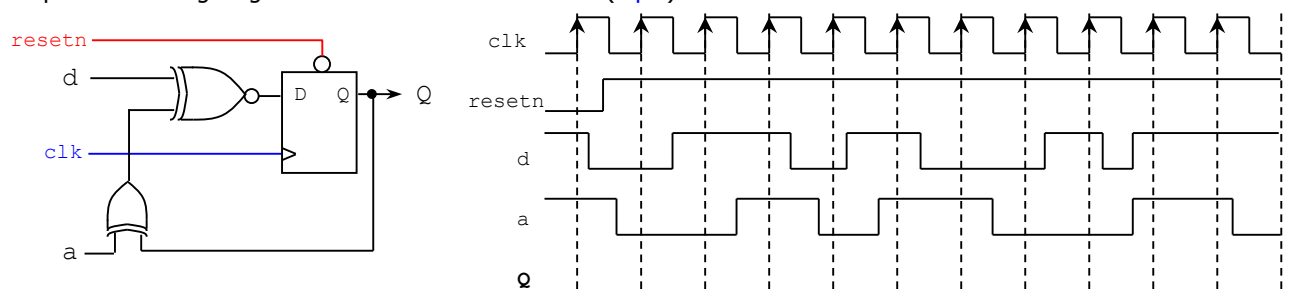- Complete the timing diagram of the circuit shown below: (7 pts)



- Complete the timing diagram of the circuit whose VHDL description is shown below: (6 pts)


```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
port ( prn, a , clk: in std_logic;
      q: out std_logic);
end circ;


architecture t of circ is
    signal qt: std_logic;

begin
    process (prn, clk, x, a)
    begin
        if prn = '0' then
            qt <= '1';
        end if;
    end process;
end t;
```
 
```
elsif (clk'event and clk = '1') then
    if x = '1' then
        qt <= a xnor qt;
    end if;
end process;
q <= qt;
end t;
```




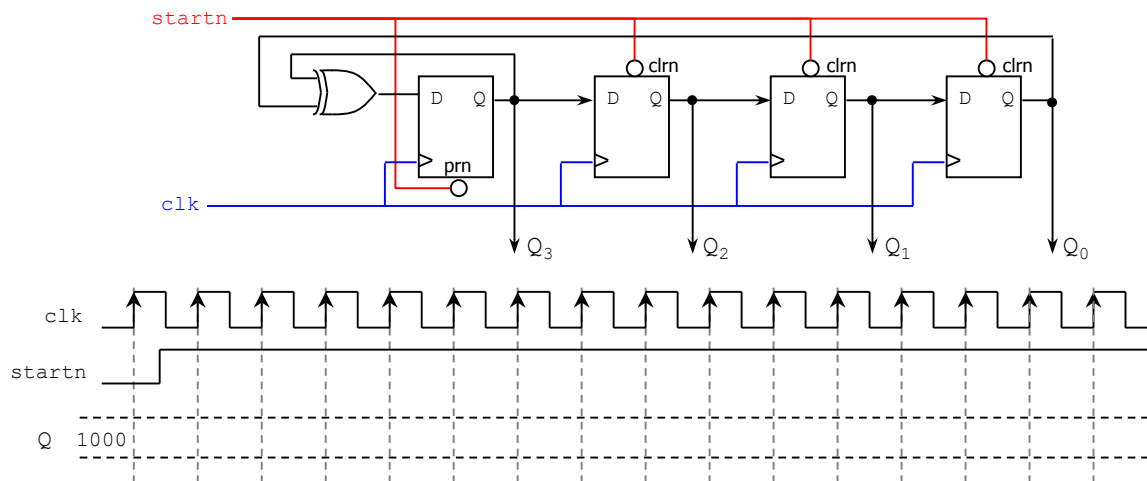- Complete the timing diagram of the following circuit: $Q = Q_3Q_2Q_1Q_0$ (10 pts)



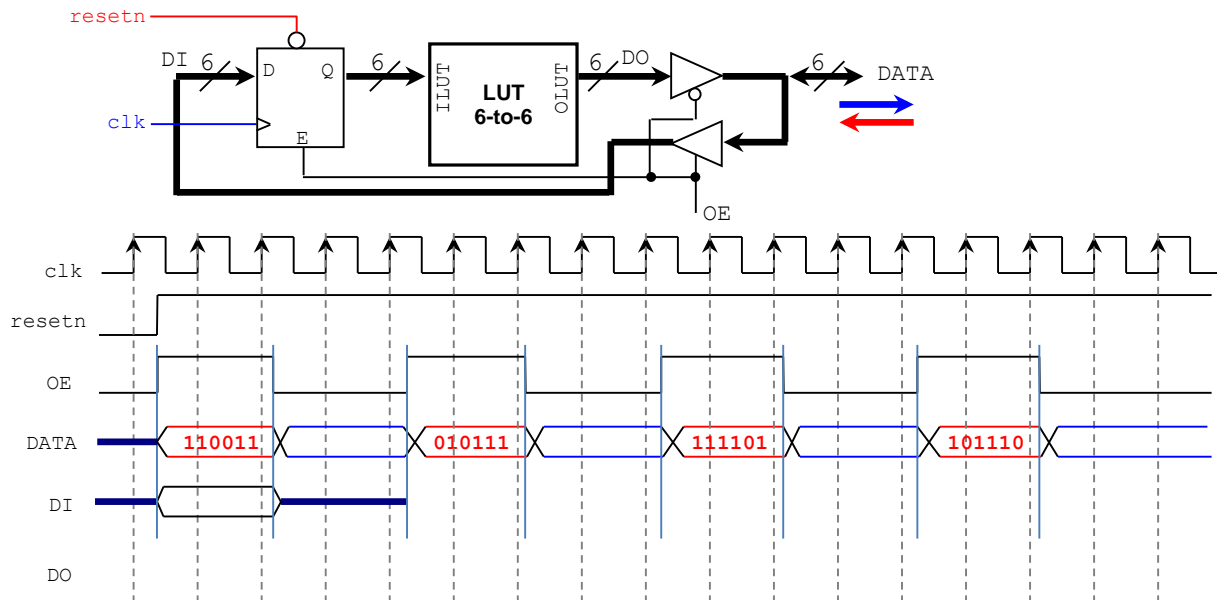
PROBLEM 3 (18 PTS)

- Given the following circuit, complete the timing diagram (signals *DO* and *DATA*).
The LUT 6-to-6 implements the following function: $OLUT = [ILUT^{0.75}]$, where *ILUT* is an unsigned number.
For example $ILUT = 35 (100011_2) \rightarrow OLUT = [35^{0.75}] = 14 (001110_2)$



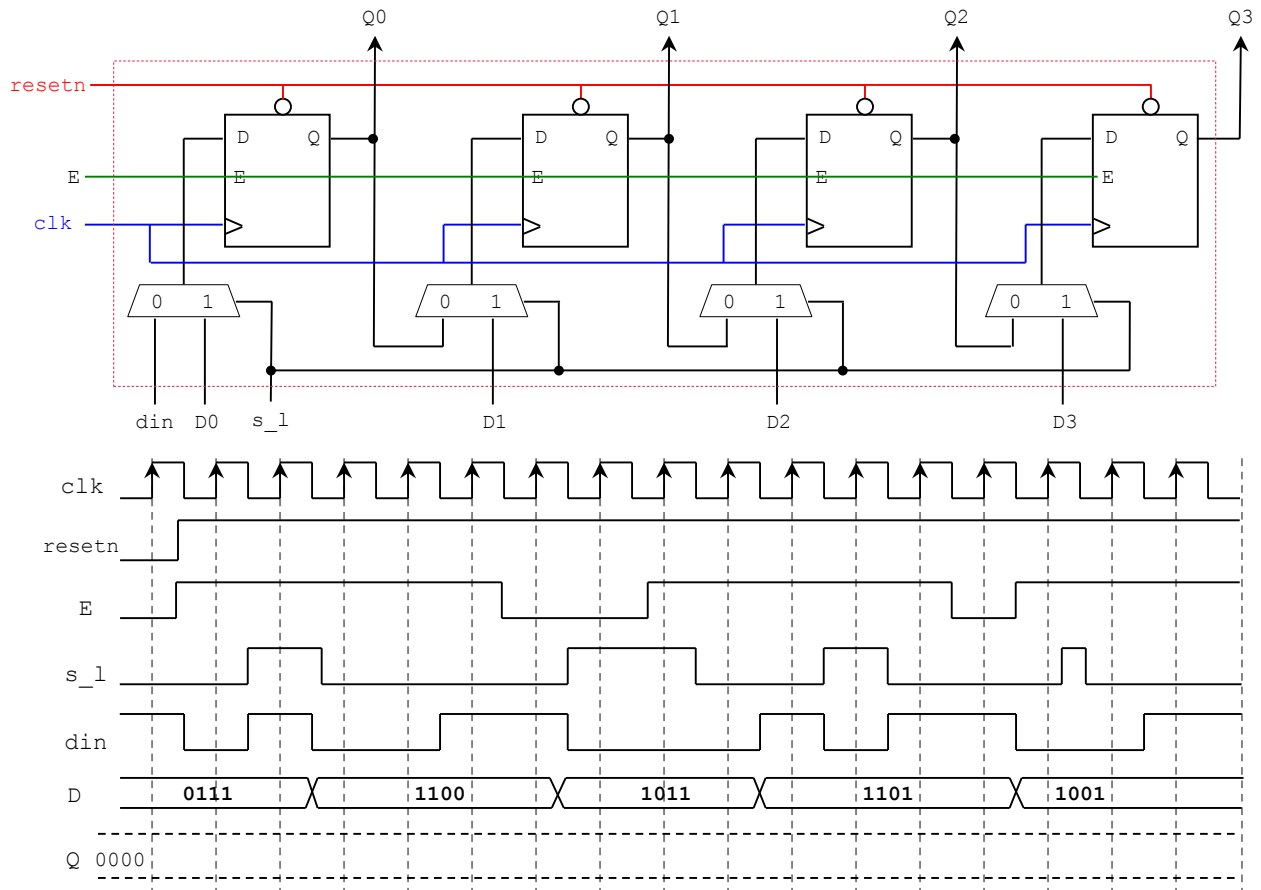PROBLEM 4 (12 PTS)

- Complete the timing diagram of the following 4-bit parallel access shift register with enable input. Shifting operation: $s_1=0$. Parallel load: $s_1=1$. Note that $Q = Q_3Q_2Q_1Q_0$. $D = D_3D_2D_1D_0$



PROBLEM 5 (25 PTS)

- The following circuit is a multiple-input compressor circuit (MIC), a component in Built-in Self-Test systems. $Q = Q_3Q_2Q_1Q_0$. $P = P_3P_2P_1P_0$
 - Write **structural** VHDL code. Create two files: i) flip flop, ii) top file (where you will interconnect the flip flops and the logic gates). Provide a printout. (10 pts)
 - Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Behavioral Simulation). The clock frequency must be 50 MHz with 50% duty cycle. Provide a printout. (15 pts)

