

Solutions - Quiz 3

(March 20th @ 5:30 pm)

PROBLEM 1 (30 PTS)

- Complete the timing diagram of the circuit whose VHDL description is shown below:

```
library ieee;
use ieee.std_logic_1164.all;
```

```
entity circ is
port ( rstn, a, b, x, clk: in std_logic;
      q: out std_logic);
end circ;
```

```
architecture xst of circ is
signal qt, f: std_logic;
```

```
begin
```

```
process (rstn, clk, a, b, x)
```

```
begin
```

```
if rstn = '0' then
```

```
qt <= '0';
```

```
elsif (clk'event and clk = '1') then
```

```
if x = '0' then
```

```
qt <= qt xor (a or b);
```


```
end if;
```

```
end if;
```

```
end process;
```



```
q <= qt;
```

```
end xst;
```

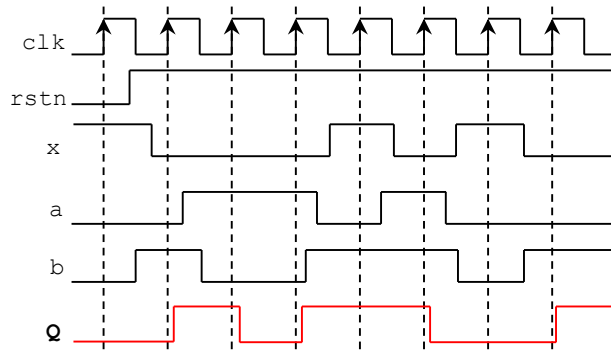

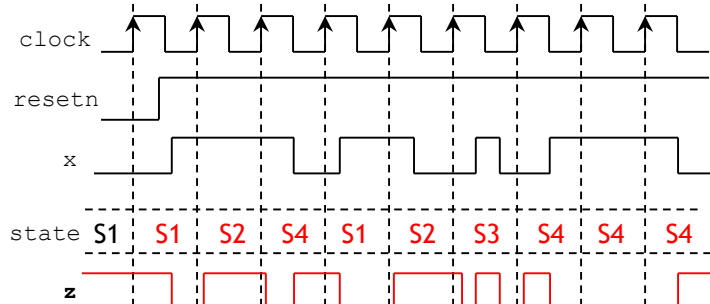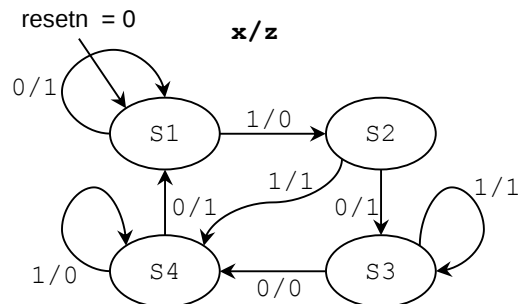PROBLEM 2 (35 PTS)

- Complete the timing diagram of the following state machine:



PROBLEM 3 (35 PTS)

- Complete the timing diagram of the following circuit. $Q = Q_3Q_2Q_1Q_0$

