



TRAFFIC LIGHT CONTROL

By: Jason Fisher, Melvin Pulianthuruthil, Merna Aziz, Joseph Yatooma


DIGITAL LOGIC DESIGN

Instructor: Dr. Llamocca

04/15/2019


INTRODUCTION

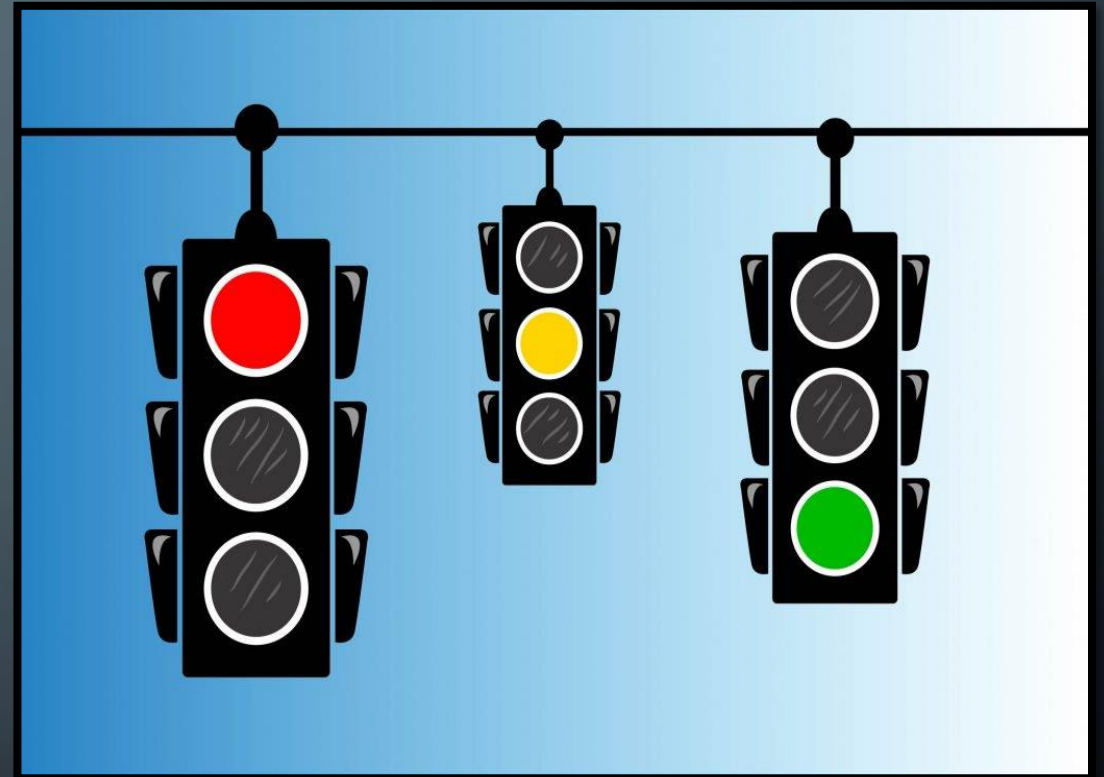- Two way intersection light system
 - 1- Day time / longer time needed for transitions.
 - 2- Night time / shorter time needed for transitions.
- Used Nexys A7 board to control the light during the day
- LED's, FSM, Clock Divider were used.
- 4s counter.
- Seven Segment Display.
- Switch to determine the mode.
- Stopwatch to communicate the time till the next transition.




WHAT WE USED TO BUILD THE TRAFFIC LIGHT

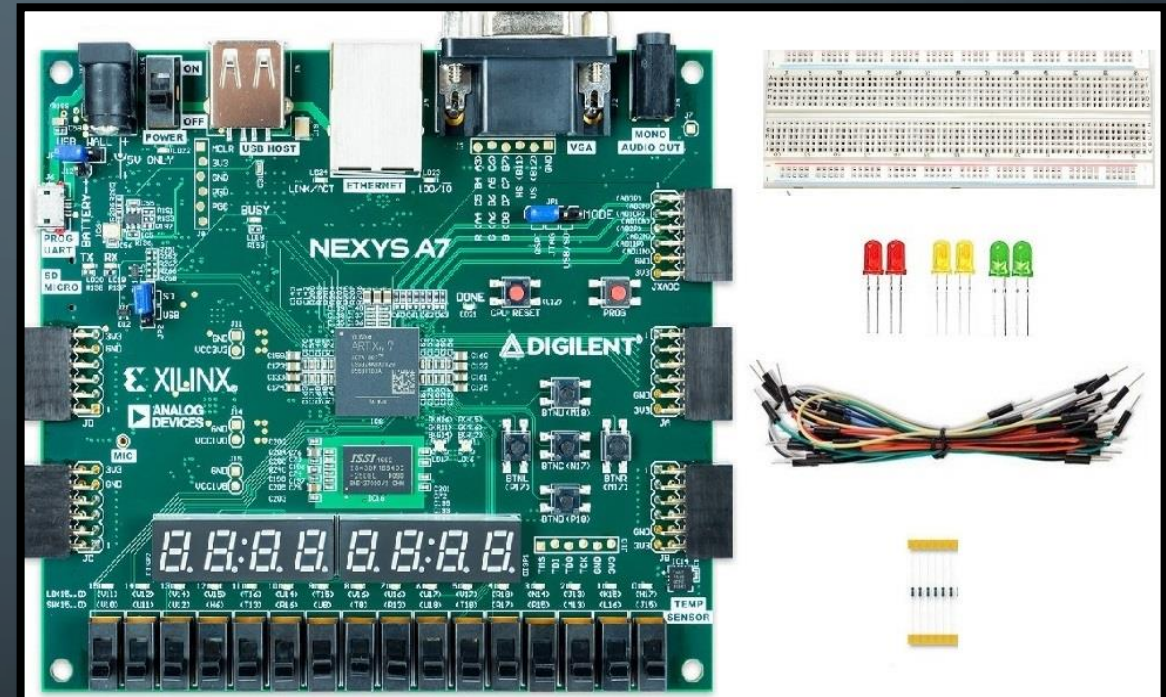- Breadboard.
- Resistors.
- Wires.
- 2X Red, 2X Yellow and 2X Green LED's.
- Nexys A7 board.
- Vivado code.
- Traffic light design.




HOW DOES IT WORK?

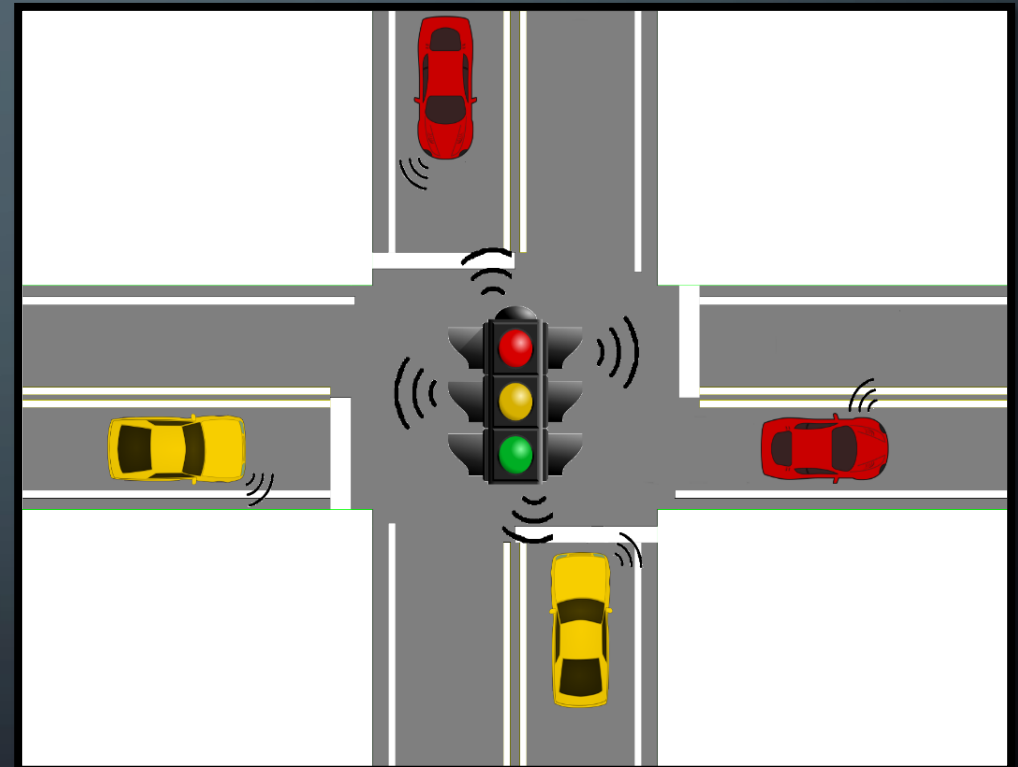- Create a traffic light control system by controlling the transition period of the lights during the day and the night.
- During the day the traffic light cycle lasts 24sec.
- During the night, the traffic light cycle lasts for 16sec.
- In when switching between modes the lights go yellow for 4sec.



TRAFFIC LIGHT CONTROL CIRCUIT

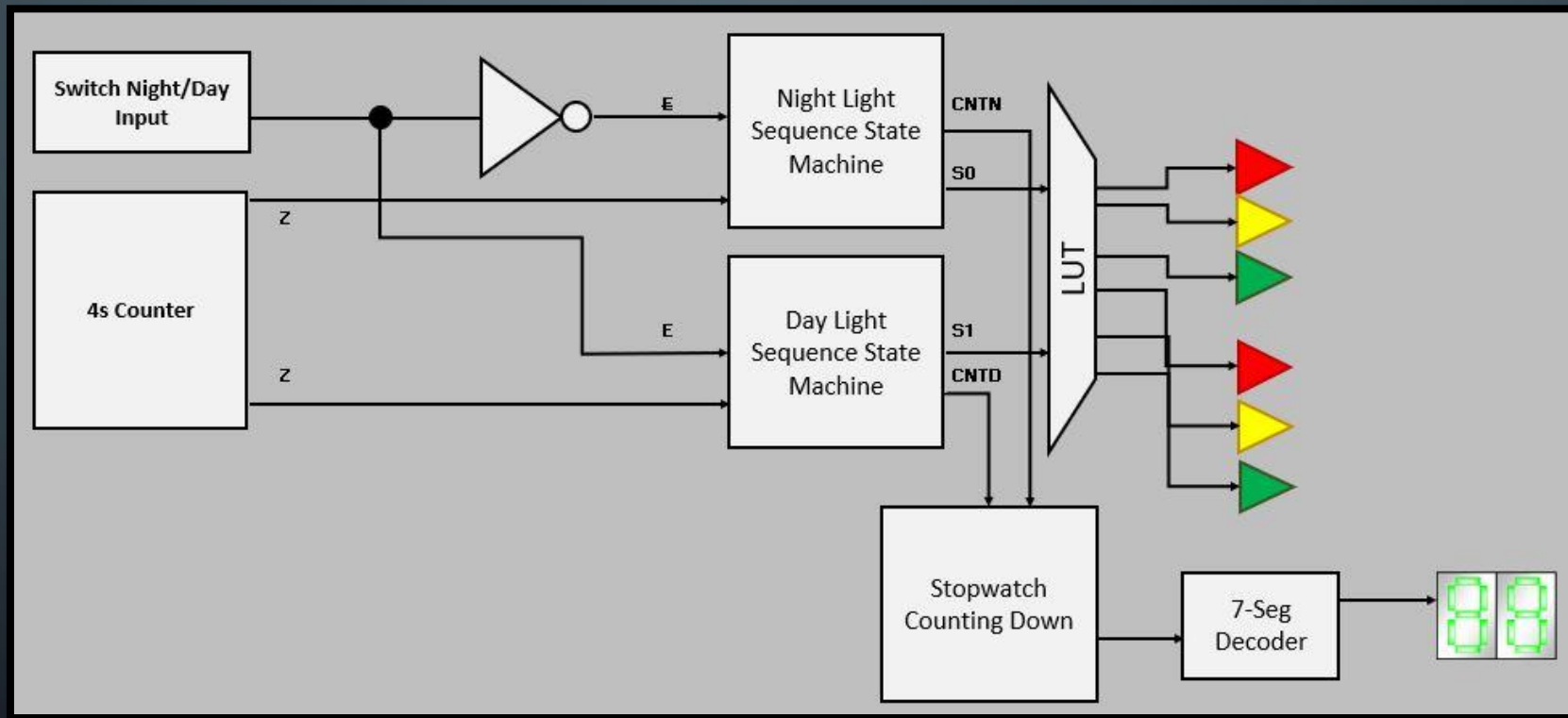



DAY STATE MACHINE STATES

		Day State Machine States												
		Current State		Inputs		Next State		Output 1		Output 2		Out 3	Out 4	
				E	Z			GREEN/YELLOW/RED	GREEN/YELLOW/RED	b	CNTD			
		0		0	X	0		010		010		0		11
		0		1	0	0		010		010		0		11
		0		1	1	1		010		010		0		11
		1		0	X	13		100		001		0		10
		1		1	0	1		100		001		0		10
		1		1	1	2		100		001		1		10
		2		0	X	13		100		001		0		10
		2		1	0	2		100		001		0		10
		2		1	1	3		100		001		1		10
		3		0	X	13		100		001		0		10
		3		1	0	3		100		001		0		10
		3		1	1	4		100		001		1		10
		4		0	X	13		100		001		0		10
		4		1	0	4		100		001		0		10
		4		1	1	5		100		001		1		10
		5		0	X	13		100		001		0		10
		5		1	0	5		100		001		0		10
		5		1	1	6		100		001		1		10
		6		0	X	13		010		001		0		10
		6		1	0	6		010		001		0		10
		6		1	1	7		010		001		1		10
		7		0	X	13		001		100		0		10
		7		1	0	7		001		100		0		10
		7		1	1	8		001		100		1		10
		8		0	X	13		001		100		0		10
		8		1	0	8		001		100		0		10
		8		1	1	9		001		100		1		10
		9		0	X	13		001		100		0		10
		9		1	0	9		001		100		0		10
		9		1	1	10		001		100		1		10
		10		0	X	13		001		100		0		10
		10		1	0	10		001		100		0		10
		10		1	1	11		001		100		1		10
		11		0	X	13		001		100		0		10
		11		1	0	11		001		100		0		10
		11		1	1	12		001		100		1		10
		12		0	X	13		001		010		0		10
		12		1	0	12		001		010		0		10
		12		1	1	1		001		010		1		10
		13		X	1	0		010		010		1		10
		13		X	0	13		010		010		1		10
		--		--	--	--		--		--		--		--

NIGHT STATE MACHINE STATES

[illegible]

TIMING SIMULATION

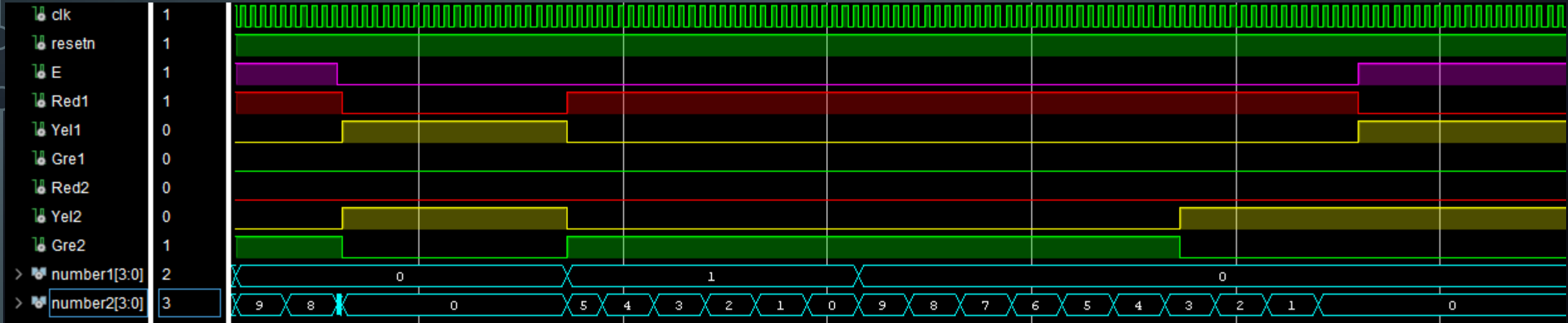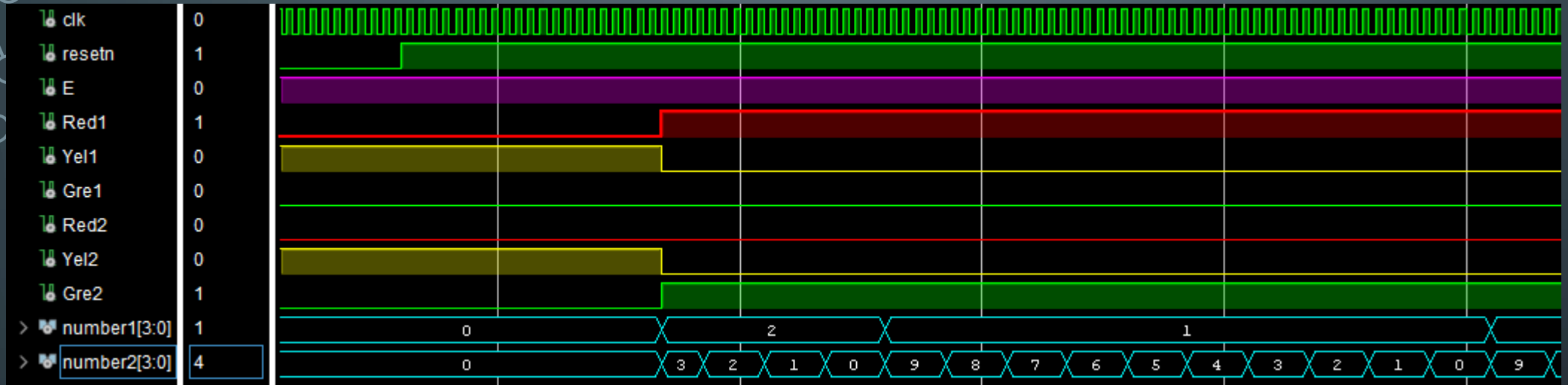

CHALLENGES!

- Running simulations of a real time system in Vivado had to convert back and forth from ns to sec.
- Determining the sequence to change between night and day mode.

DEMONSTRATION

- **Need a picture of our project here**