


# Homework 4

(Due date: March 28<sup>th</sup> @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!
 
## PROBLEM 1 (23 PTS)


- Sequence Detector: The machine has to generate  $z=1$  when it detects the sequence 1010011. Once the sequence is detected, the circuit looks for a new sequence.



- Draw the State Diagram (any representation), State Table, and Excitation Table. Is this a Mealy or a Moore machine? Why?
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (3 pts)
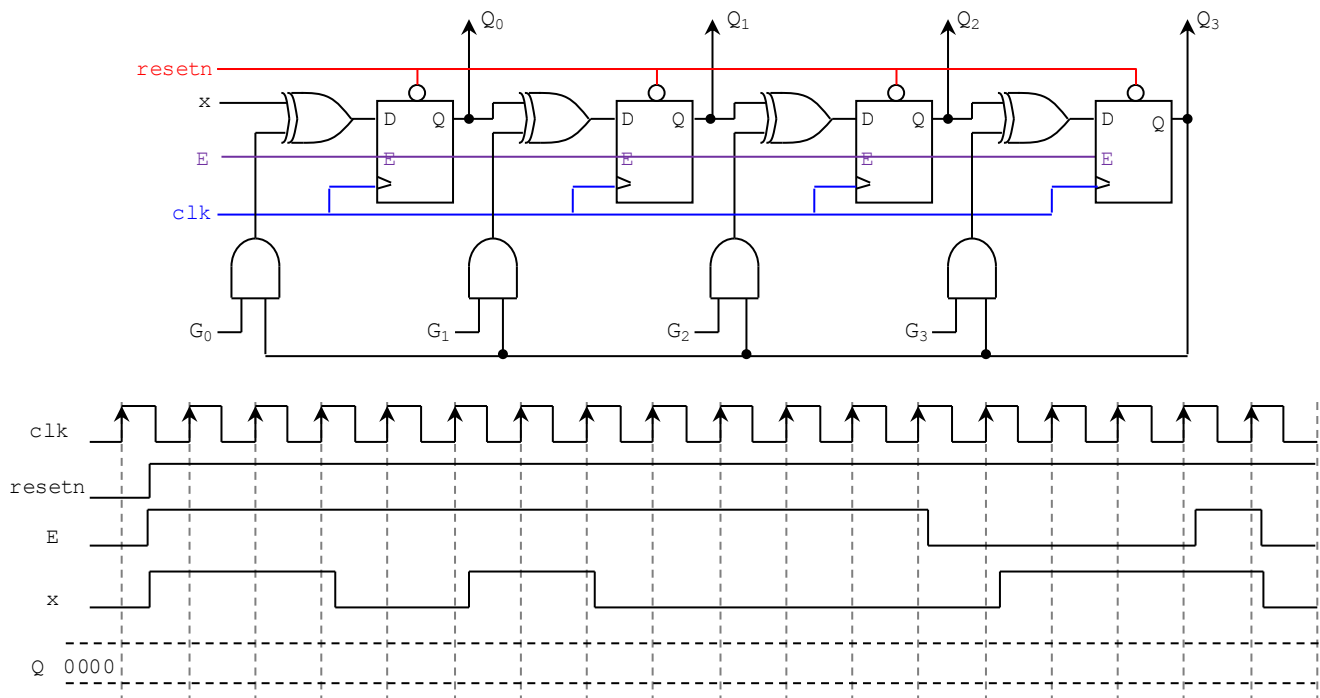
## PROBLEM 2 (15 PTS)


- Complete the timing diagram of the following circuit.  $G = G_3G_2G_1G_0 = 1001$ ,  $Q = Q_3Q_2Q_1Q_0$


 
## PROBLEM 3 (12 PTS)

- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following FSM.

$w$ : input,  $z$ : output,  $Q_1Q_0$ : state.



## PROBLEM 4 (17 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

entity myfsm is
    port ( clk, resetn: in std_logic;
          a, b, c: in std_logic;
          x, w, z: out std_logic);
end myfsm;
```

```
architecture behavior of myfsm is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, a, b, c)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if a = '1' then
                        y <= S2;
                    else
                        if b = '1' then y <= S3; else y <= S1; end if;
                    end if;

                when S2 =>
                    if b = '1' then y <= S1; else y <= S3; end if;


                when S3 =>
                    if c = '1' then y <= S3; else y <= S2; end if;

            end case;
        end if;
    end process;

    Outputs: process (y, a, b, c)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if a = '0' then
                            if b = '0' then
                                z <= '1'; x <= '1';
                            end if;
                        end if;

            when S2 => if c = '0' then x <= '1'; end if;
                       if b = '0' then w <= '1'; end if;

             when S3 => if c = '0' then x <= '1'; end if;
        end case;
    end process;
end behavior;
```





### PROBLEM 5 (18 PTS)

- “Counting 1’s” Circuit: It counts the number of bits in register A that has the value of ‘1’.  
The digital system is depicted below: FSM + Datapath. Example: For  $n = 8$ : if  $A = 00110110$ , then  $C = 0100$ .  
✓ m-bit counter: If  $E = sclr = 1$ , the count is initialized to zero. If  $E = 1, sclr = 0$ , the count is increased by 1.  
✓ Parallel access shift register: If  $E = 1: s_l = 1 \rightarrow \text{Load}, s_l = 0 \rightarrow \text{Shift}$ .
- Complete the timing diagram where  $n = 8, m = 4$ .

```

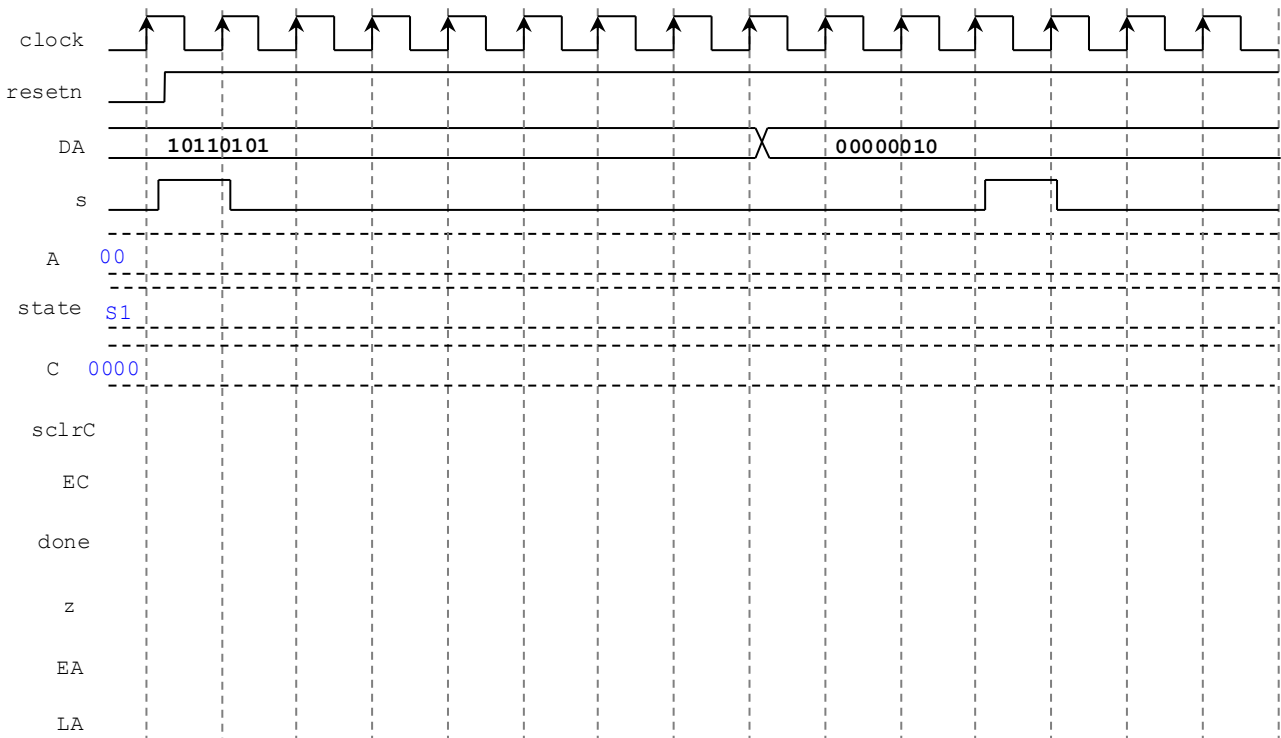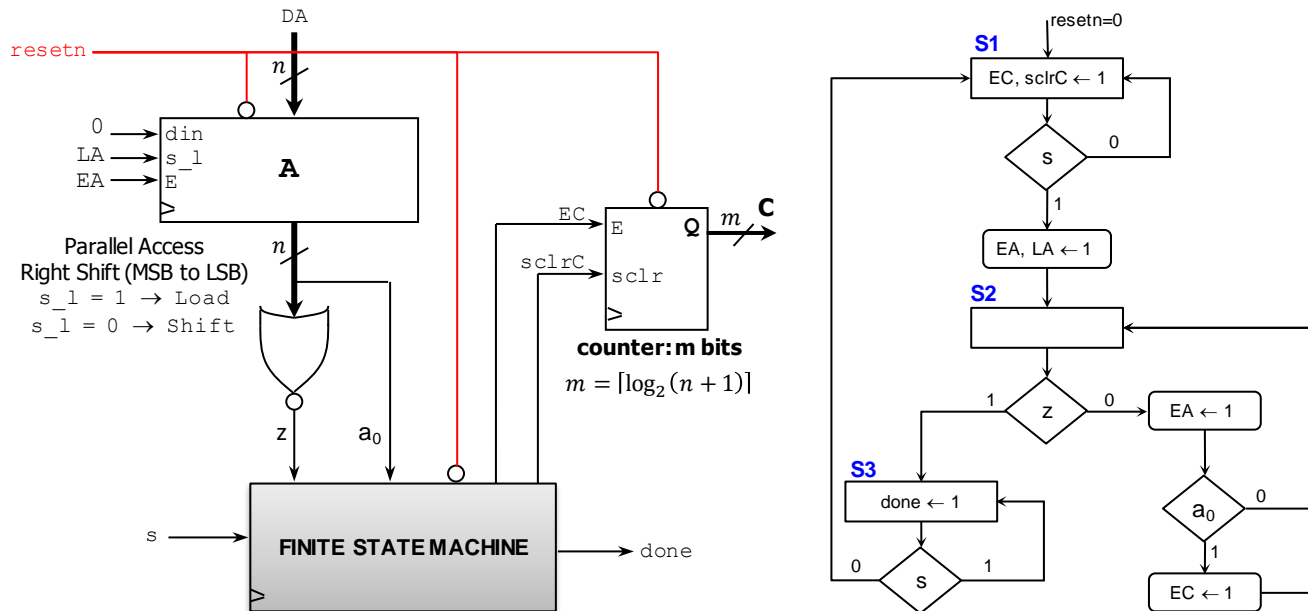C ← 0
while A ≠ 0
  if a0 = 1 then
    C ← C + 1
  end if
  right shift A
end while
    
```



### PROBLEM 6 (15 PTS)

- Attach a printout of your Project Status Report (no more than a page). This report should contain the current status of the project, including a block diagram of your system. You **MUST** use the provided template (Final Project - Report Template.docx).