


Solutions - Homework 4

(Due date: March 28th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (23 PTS)

- Sequence Detector: The machine has to generate $z=1$ when it detects the sequence 1010011. Once the sequence is detected, the circuit looks for a new sequence.




- Draw the State Diagram (any representation), State Table, and Excitation Table. Is this a Mealy or a Moore machine? Why?
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (3 pts)

- State Diagram, State Table, and Excitation Table:

State Assignment:

 S1: Q=000 S2: Q=001
 S3: Q=010 S4: Q=011
 S5: Q=100 S6: Q=101
 S7: Q=110



PRESENT STATE				NEXT STATE			
x	STATE	STATE	z	x	Q ₂ Q ₁ Q ₀ (t)	Q ₂ Q ₁ Q ₀ (t+1)	z
0	S1	S1	0	0	0 0 0 0	0 0 0 0	0
0	S2	S3	0	0	0 0 0 1	0 1 0 0	0
0	S3	S1	0	0	0 0 1 0	0 0 0 0	0
0	S4	S5	0	0	0 0 1 1	1 0 0 0	0
0	S5	S6	0	0	0 1 0 0	1 0 1 0	0
0	S6	S1	0	0	0 1 0 1	0 0 0 0	0
0	S7	S3	0	0	0 1 1 0	0 1 0 0	0
1	S1	S2	0	0	0 1 1 1	X X X	X
1	S2	S2	0	1	1 0 0 0	0 0 1 0	0
1	S3	S4	0	1	1 0 0 1	0 0 1 0	0
1	S4	S2	0	1	1 0 1 0	0 1 1 0	0
1	S5	S4	0	1	1 0 1 1	0 0 1 0	0
1	S6	S7	0	1	1 1 0 0	0 1 1 0	0
1	S7	S1	1	1	1 1 0 1	1 1 0 0	0
					1 1 1 0	0 0 0 0	1
					1 1 1 1	X X X	X

This is a Mealy FSM. The output 'z' depends on the input as well as on the present state.


- Excitation equations, minimization, and circuit implementation:

$$Q_2(t+1) = \bar{x}Q_2\bar{Q}_1\bar{Q}_0 + xQ_2Q_0 + \bar{x}Q_1Q_0$$

$$Q_1(t+1) = \bar{x}\bar{Q}_2\bar{Q}_1Q_0 + x\bar{Q}_2Q_1\bar{Q}_0 + xQ_2\bar{Q}_1 + \bar{x}Q_2Q_1 = \bar{x}\bar{Q}_2\bar{Q}_1Q_0 + x\bar{Q}_2Q_1\bar{Q}_0 + Q_2(x \oplus Q_1)$$


$$Q_0(t+1) = Q_2\bar{Q}_1\bar{Q}_0 + x\bar{Q}_2$$

$$z = xQ_2Q_1$$

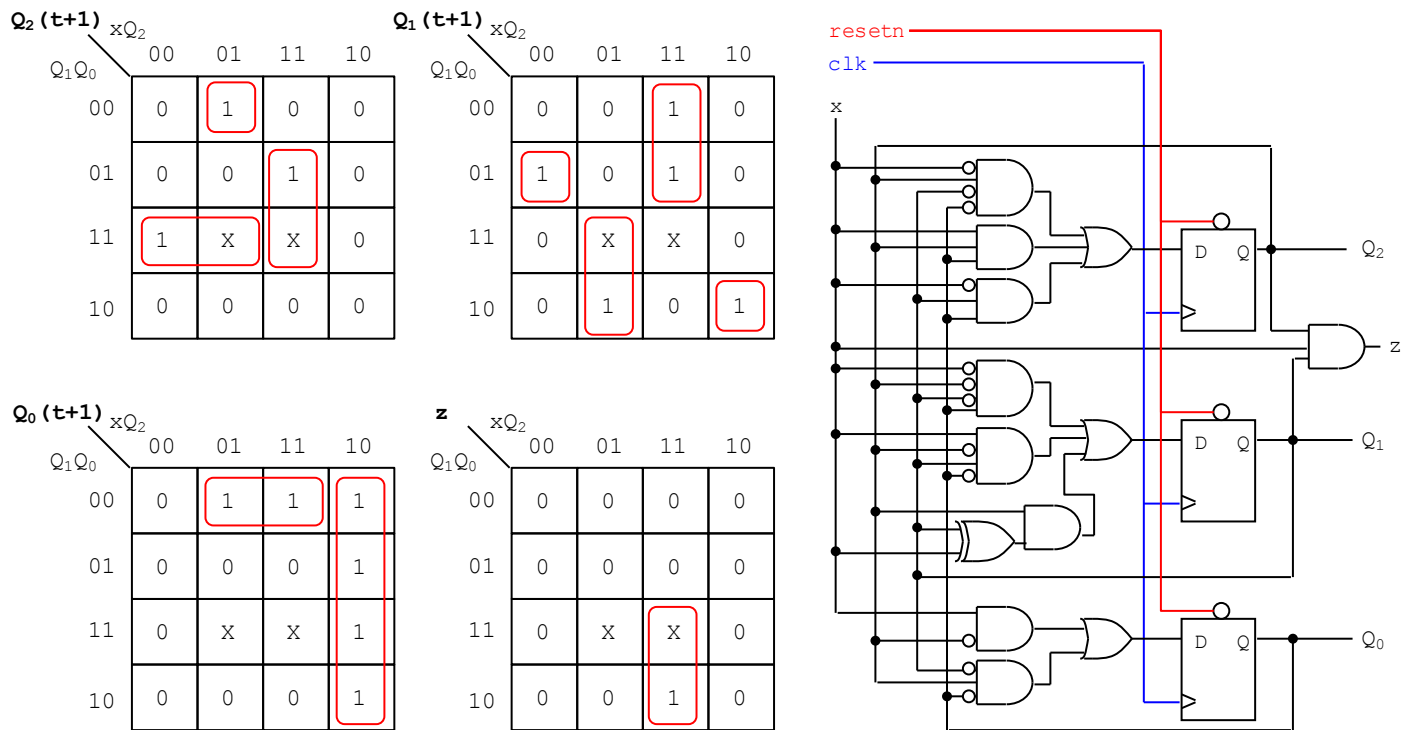

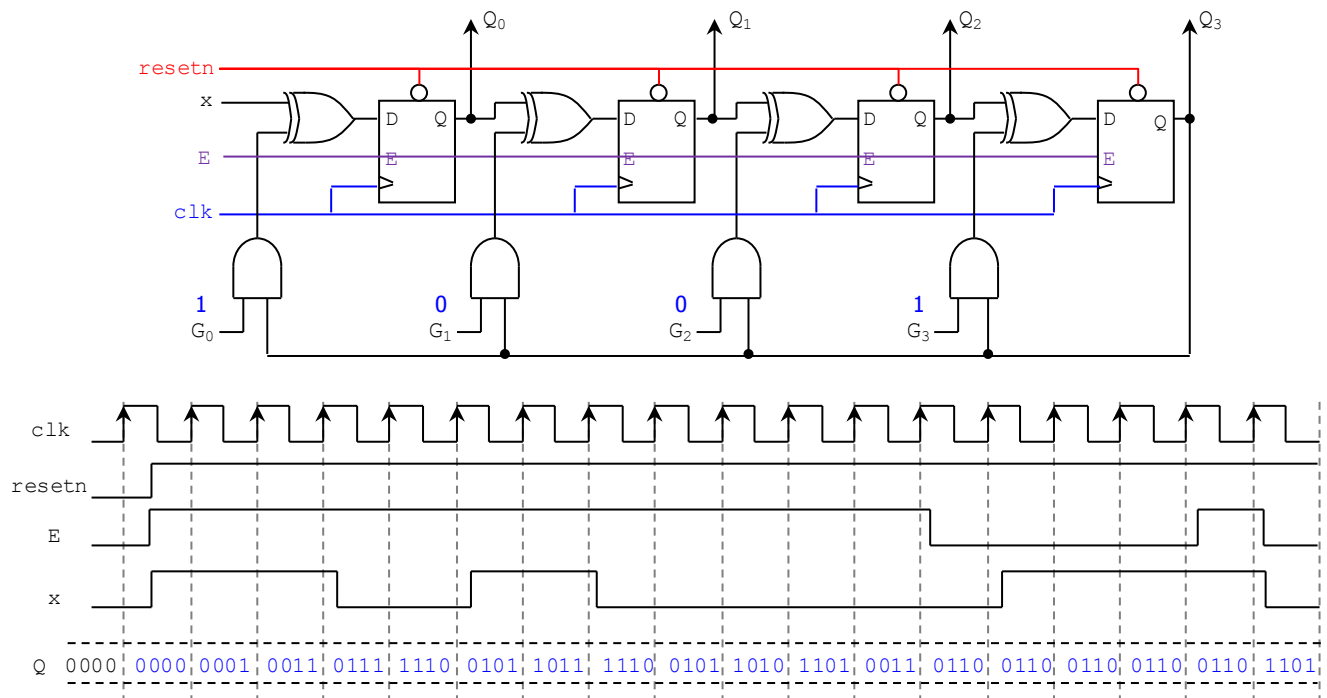PROBLEM 2 (15 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1001$, $Q = Q_3Q_2Q_1Q_0$



PROBLEM 3 (12 PTS)

- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following FSM.

w : input, z : output, Q_1Q_0 : state.


$$Q_1(t+1) = (Q_1 + Q_0)w$$

$$Q_0(t+1) = (\overline{Q_1}Q_0) \oplus w$$

$$z = Q_1 + Q_0$$

- State Assignment:**

 
- ✓ S1: $Q = 00$
- ✓ S2: $Q = 01$
- ✓ S3: $Q = 10$
- ✓ S4: $Q = 11$



PRESENT STATE			NEXTSTATE	
w	$Q_1Q_0(t)$		$Q_1Q_0(t+1)$	z
0	0 0	0	0 0	0
0	0 1	0	0 1	1
0	1 0	0	0 0	1
0	1 1	0	0 0	1
1	0 0	0	0 1	0
1	0 1	1	1 0	1
1	1 0	1	1 1	1
1	1 1	1	1 1	1



w	PRESENT STATE	NEXT STATE	z
0	S1	S1	0
0	S2	S2	1
0	S3	S1	1
0	S4	S1	1
1	S1	S2	0
1	S2	S3	1
1	S3	S4	1
1	S4	S4	1

 


PROBLEM 4 (17 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

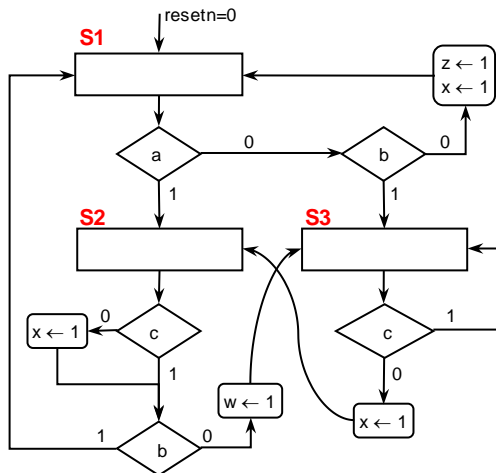entity myfsm is
    port ( clk, resetn: in std_logic;
          a, b, c: in std_logic;
          x, w, z: out std_logic);
end myfsm;
```



```
architecture behavior of myfsm is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, a, b, c)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if a = '1' then
                        y <= S2;
                    else
                        if b = '1' then y <= S3; else y <= S1; end if;
                    end if;

                when S2 =>
                    if b = '1' then y <= S1; else y <= S3; end if;


                when S3 =>
                    if c = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, a, b, c)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if a = '0' then
                            if b = '0' then
                                z <= '1'; x <= '1';
                            end if;
                        end if;

            when S2 => if c = '0' then x <= '1'; end if;
                       if b = '0' then w <= '1'; end if;

            when S3 => if c = '0' then x <= '1'; end if;
        end case;
    end process;
end behavior;
```

 This is a Mealy Machine. The outputs 'x,w,z' depend on the input as well as on the present state.





PROBLEM 5 (18 PTS)

- “Counting 1’s” Circuit: It counts the number of bits in register A that has the value of ‘1’.
The digital system is depicted below: FSM + Datapath. Example: For $n = 8$: if $A = 00110110$, then $C = 0100$.
✓ m-bit counter: If $E = sclr = 1$, the count is initialized to zero. If $E = 1, sclr = 0$, the count is increased by 1.
✓ Parallel access shift register: If $E = 1: s_l = 1 \rightarrow \text{Load}, s_l = 0 \rightarrow \text{Shift}$.
- Complete the timing diagram where $n = 8, m = 4$.

```

C ← 0
while A ≠ 0
  if a0 = 1 then
    C ← C + 1
  end if
  right shift A
end while

```

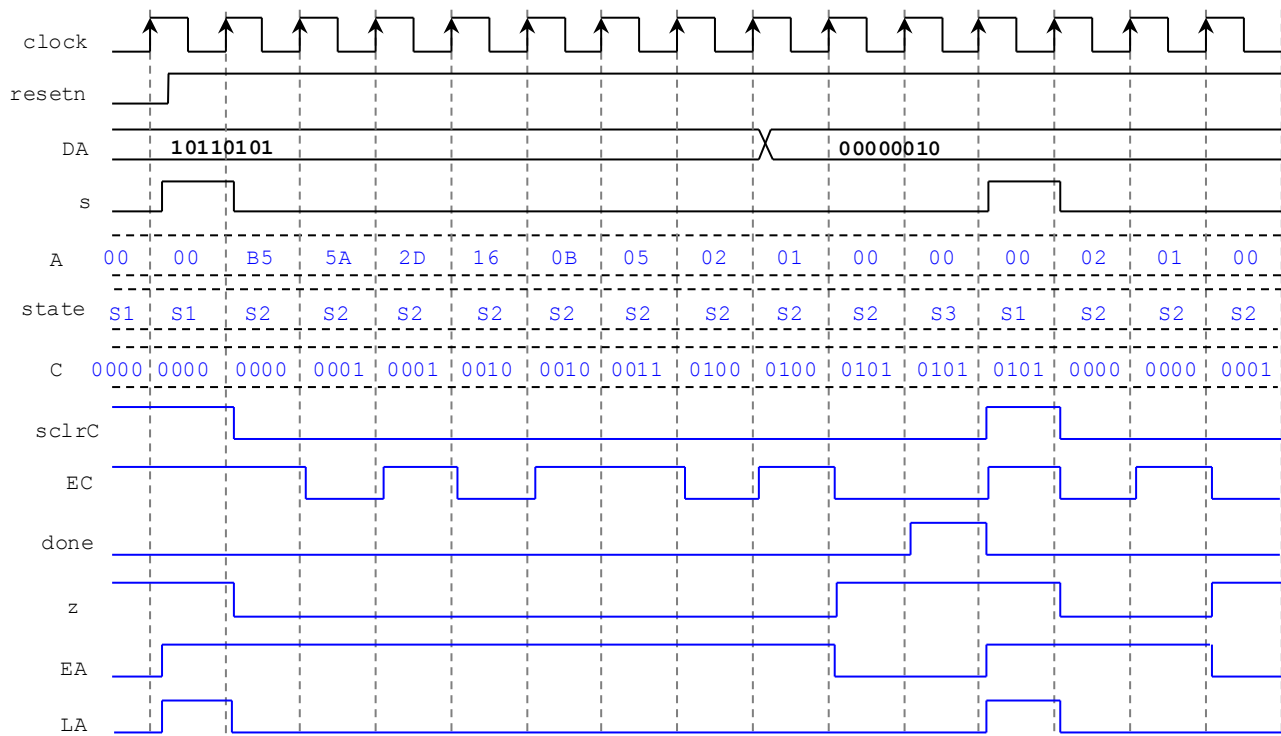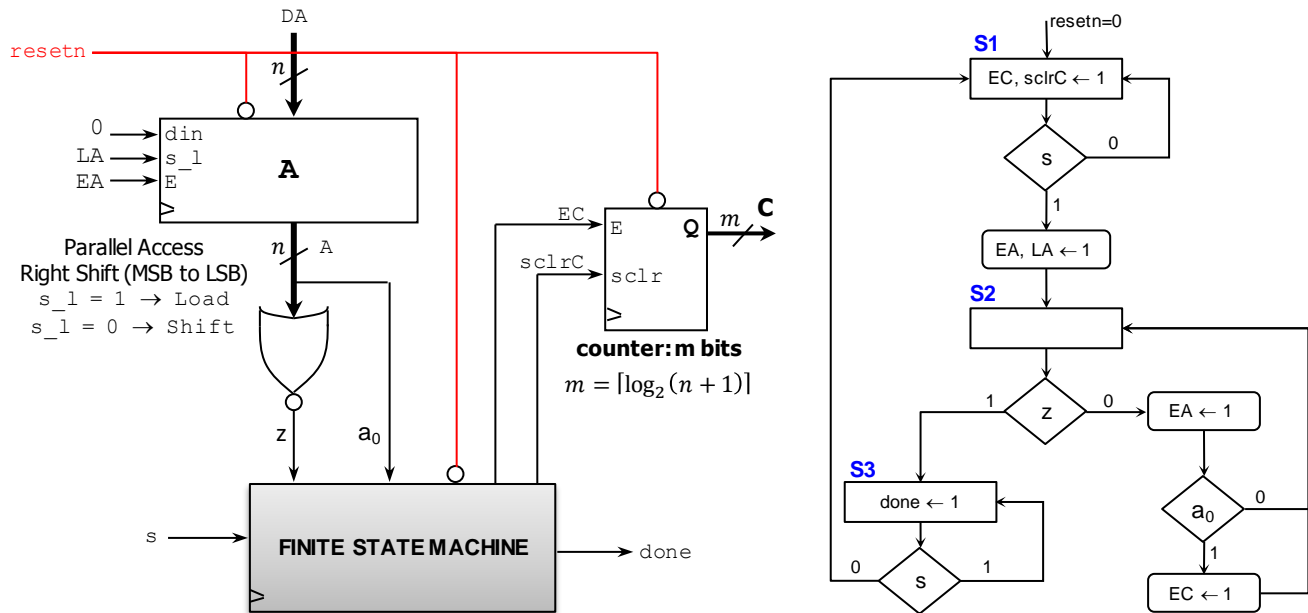

PROBLEM 6 (15 PTS)

- Attach a printout of your Project Status Report (no more than a page). This report should contain the current status of the project, including a block diagram of your system. You **MUST** use the provided template (Final Project - Report Template.docx).