


Homework 3

(Due date: March 19th @ 5:30 pm)


Presentation and clarity are very important! Show your procedure!

 PROBLEM 1 (12 PTS)

- Complete the timing diagram of the circuit shown below. (7 pts)




 - Complete the timing diagram of the circuit shown below: (5 pts)




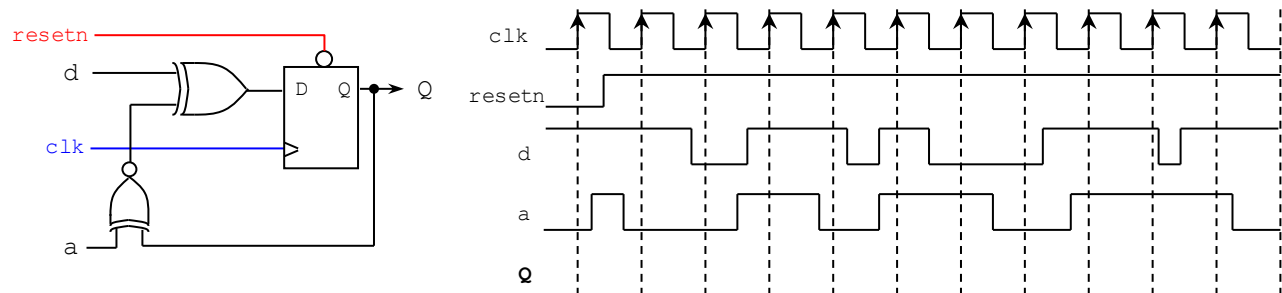PROBLEM 2 (17 PTS)

- Complete the timing diagram of the circuit shown below: (7 pts)



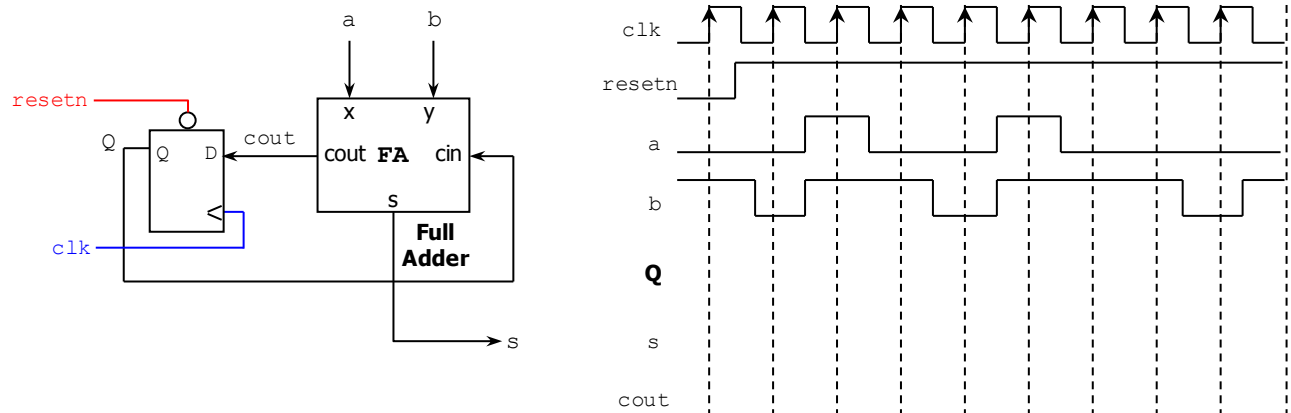
- Complete the timing diagram of the circuit shown below: (10 pts)



 PROBLEM 3 (16 PTS)

- With a D flip flop and logic gates, sketch the circuit whose excitation equation is given by:
✓ $Q(t+1) \leftarrow x\bar{y} + Q(t)(\bar{x} \oplus y)$ (4 pts)

- Given the following circuit, get the excitation equations for each flip flop output $Q = Q_3Q_2Q_1Q_0$ (6 pts)



- Complete the timing diagram of the circuit whose VHDL description is shown below. Also, get the excitation equation for q .


```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port (clrn, clk, a: in std_logic;
        q: out std_logic);
end circ;

architecture t of circ is
  signal qt: std_logic;

begin
  process (clrn, clk, x, a)
  begin
    if clrn = '0' then
      qt <= '0';
    else
      if (clk'event and clk = '1') then
        if x = '0' then
          qt <= not(a) xor not(qt);
        end if;
      end if;
    end process;
    q <= qt;
  end t;
```


 
```
elsif (clk'event and clk = '1') then
  if x = '0' then
    qt <= not(a) xor not(qt);
  end if;
end if;
end process;
q <= qt;
end t;
```



$$q(t+1) \leftarrow$$

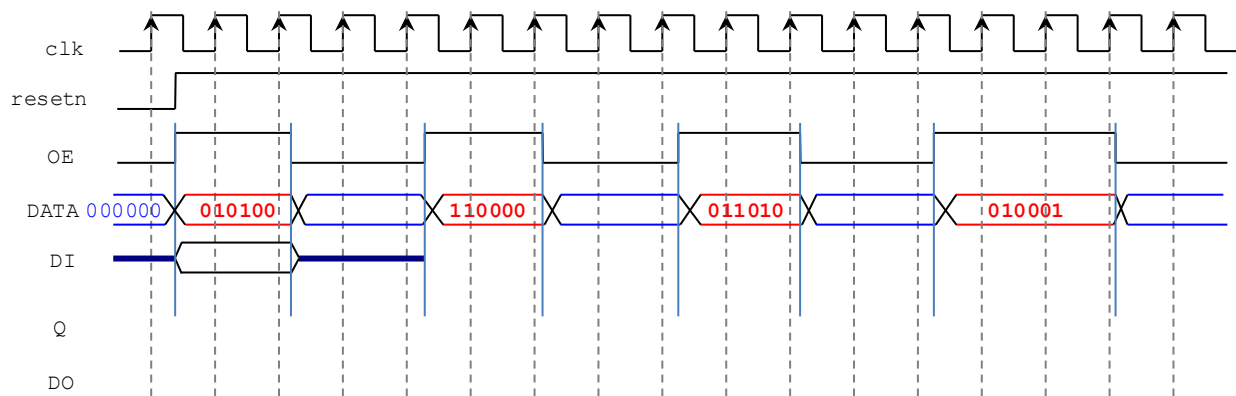 
PROBLEM 4 (18 PTS)

- Given the following circuit, complete the timing diagram (signals DO , Q and $DATA$).
The LUT 6-to-6 implements the following function: $OLUT = [ILUT^{0.5}]$, where $ILUT$ is an unsigned number.
For example: $ILUT = 35$ (100011_2) $\rightarrow OLUT = [35^{0.5}] = 6$ (000110_2)



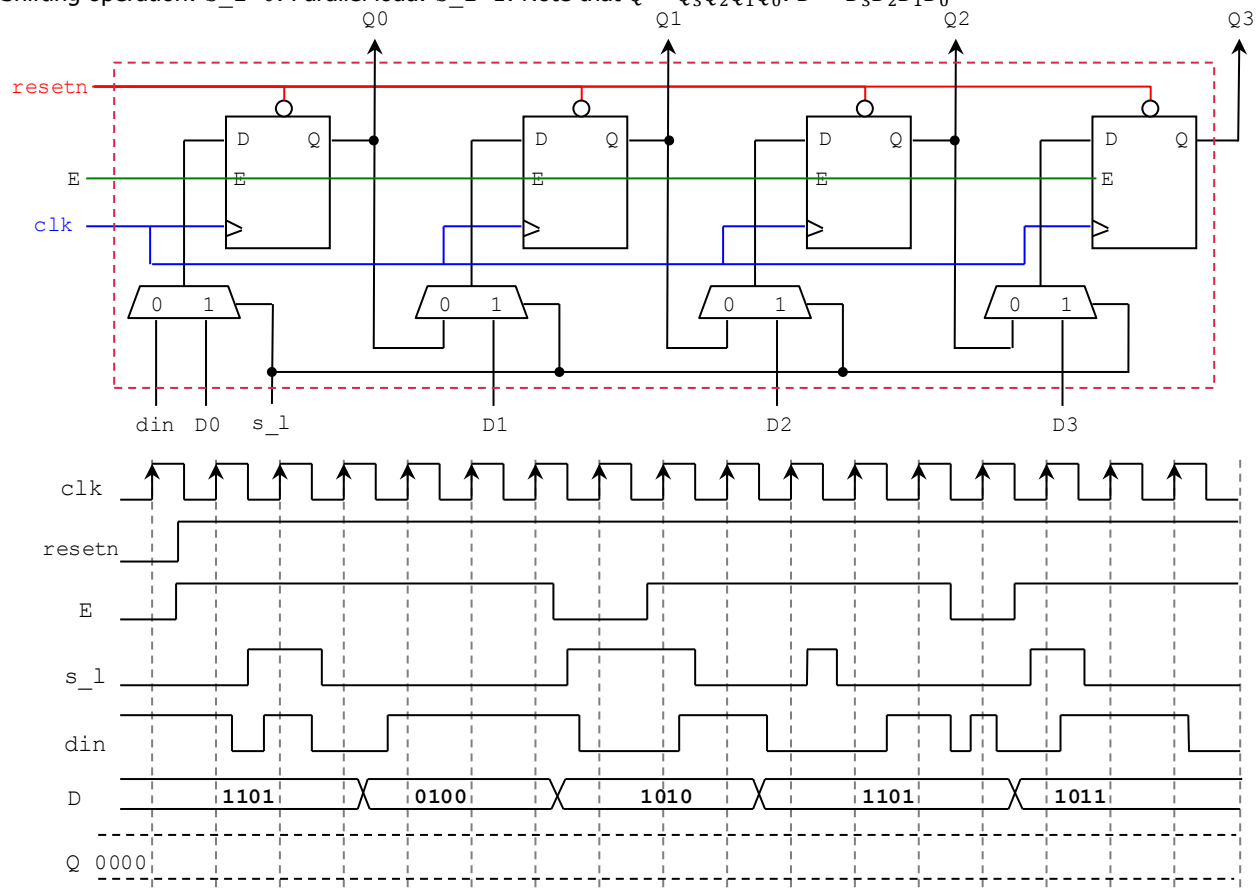PROBLEM 5 (12 PTS)

- Complete the timing diagram of the following 4-bit parallel access shift register with enable input. Shifting operation: $s_1=0$. Parallel load: $s_1=1$. Note that $Q = Q_3Q_2Q_1Q_0$. $D = D_3D_2D_1D_0$



PROBLEM 6 (25 PTS)

- For the following circuit, we have $R = R_3R_2R_1R_0$. $G = G_3G_2G_1G_0$
 - ✓ Write **structural** VHDL code. Create two files: i) flip flop, ii) top file (where you will interconnect the flip flops and the logic gates). Provide a printout. (10 pts)
 - ✓ Write a VHDL testbench according to the timing diagram shown below. Complete the timing diagram by simulating your circuit (Behavioral Simulation). The clock frequency must be 100 MHz with 50% duty cycle. Provide a printout. (15 pts)

