


Homework 4

(Due date: March 26th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

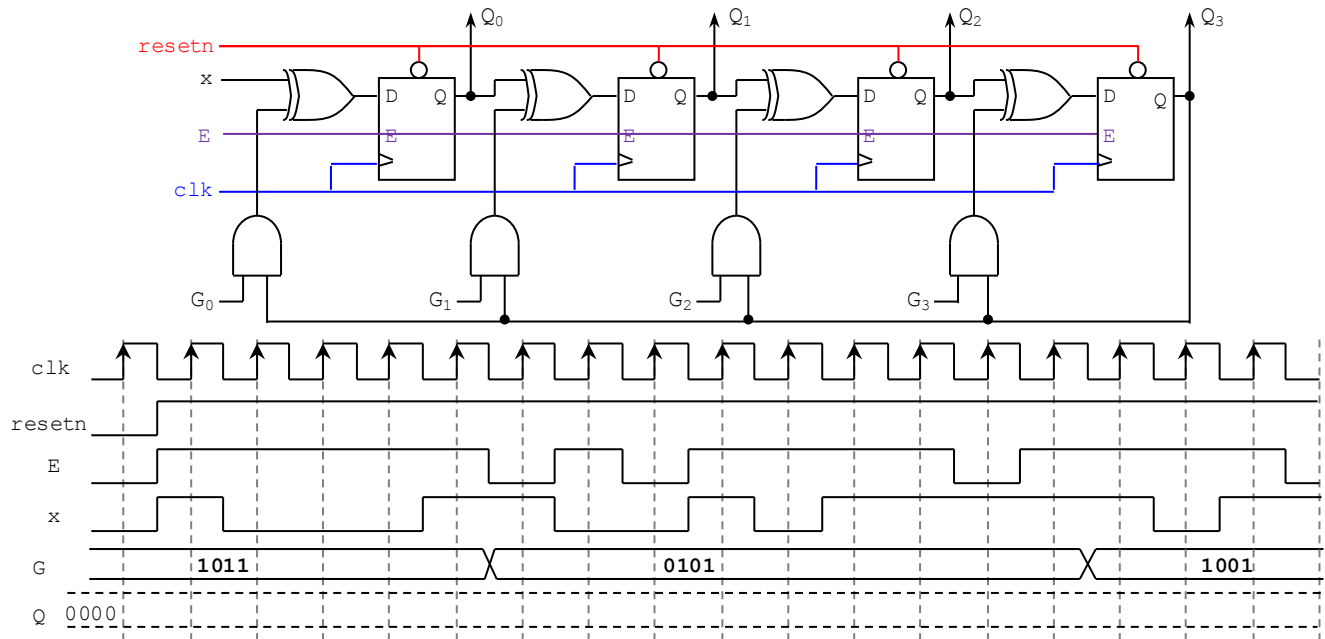
PROBLEM 1 (14 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0$, $Q = Q_3Q_2Q_1Q_0$



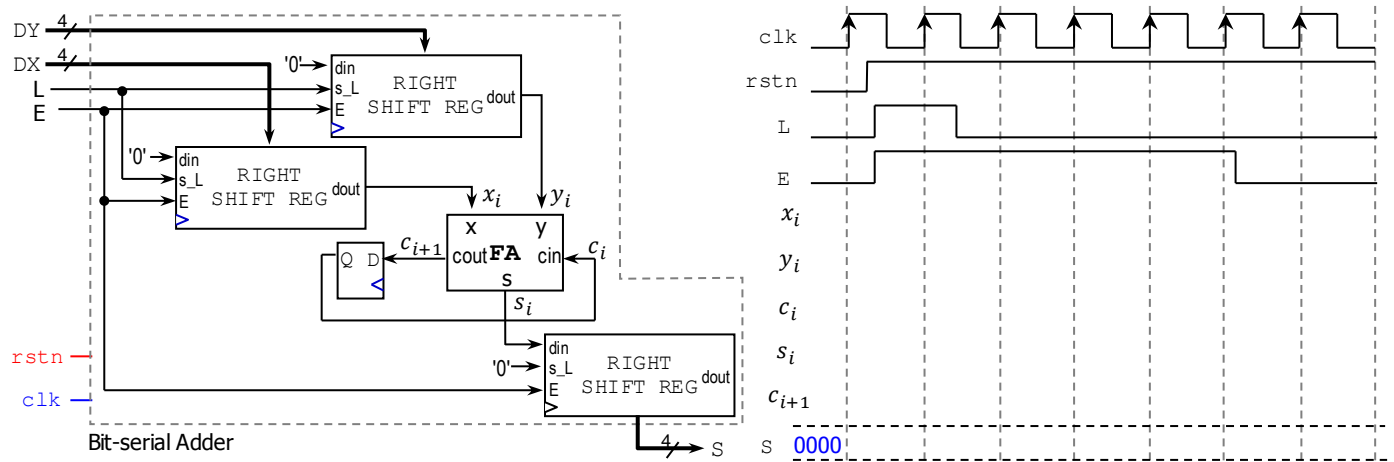
PROBLEM 2 (18 PTS)

- Complete the timing diagram of the following bit-serial adder. $DX=0101$, $DY=1001$. (8 pts)




- Given the following State Machine Diagram (10 pts).

 - Is this a Mealy or Moore Machine? Why?
- Get the excitation equations and the Boolean equation for z. (6 pts)
Use S0 (Q=00), S1 (Q=01), S2 (Q=10), S4 (Q=11) to encode the states.
- Sketch the circuit for this Finite State Machine. (3 pts)



 PROBLEM 3 (21 PTS)

- Sequence detector: The machine generates $z = 1$ when it detects the sequence 1011. Once the sequence is detected, the circuit looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E = 1$, x is valid, otherwise x is not valid.



- Draw the State Diagram (any representation), State Table, and the Excitation Table of this circuit. (14 pts)
- Provide the excitation equations and the Boolean equation for z (simplify your circuit: K-maps or Quine-McCluskey) (4 pts)
- Sketch the circuit. Is this a Mealy or a Moore machine? Why? (3 pts)

PROBLEM 4 (15 PTS)


- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or a Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;


entity myfsm is
  port ( clk, resetn: in std_logic;
        z, E, co: in std_logic;
        ER, LR, EC, EA: out std_logic);
end myfsm;
```

```
architecture behavior of myfsm is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (resetn, clk, z, E, co)
  begin
    if resetn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if E = '1' then y <= S2; else y <= S1; end if;
        when S2 =>
          if z = '1' then y <= S3; else y <= S2; end if;
        when S3 =>
          if E = '1' then y <= S3; else y <= S1; end if;
      end case;
    end if;
  end process;

   Outputs: process (y, z, E, co)
  begin
    ER <= '0'; LR <= '0'; EC <= '0'; EA <= '0';
    case y is
      when S1 => ER <= '1'; EC <= '1';
        if E = '1' then EA <= '1'; end if;
      when S2 => ER <= '1'; EA <= '1';
        if co = '1' then LR <= '1'; end if;
        if z = '0' then EC <= '1'; end if;
      when S3 =>
      end case;
    end process;
  end behavior;
```



- Complete the following timing diagram (A and P are specified as hexadecimals) of the following Iterative unsigned multiplier. The circuit includes an FSM (in ASM form) and a datapath circuit.
Register (for P): *sclr*: synchronous clear. Here, if *sclr* = $E = 1$, the register contents are initialized to 0.
- Parallel access shift registers (for A and B): If $E = 1$: $s_l = 1 \rightarrow \text{Load}$, $s_l = 0 \rightarrow \text{Shift}$

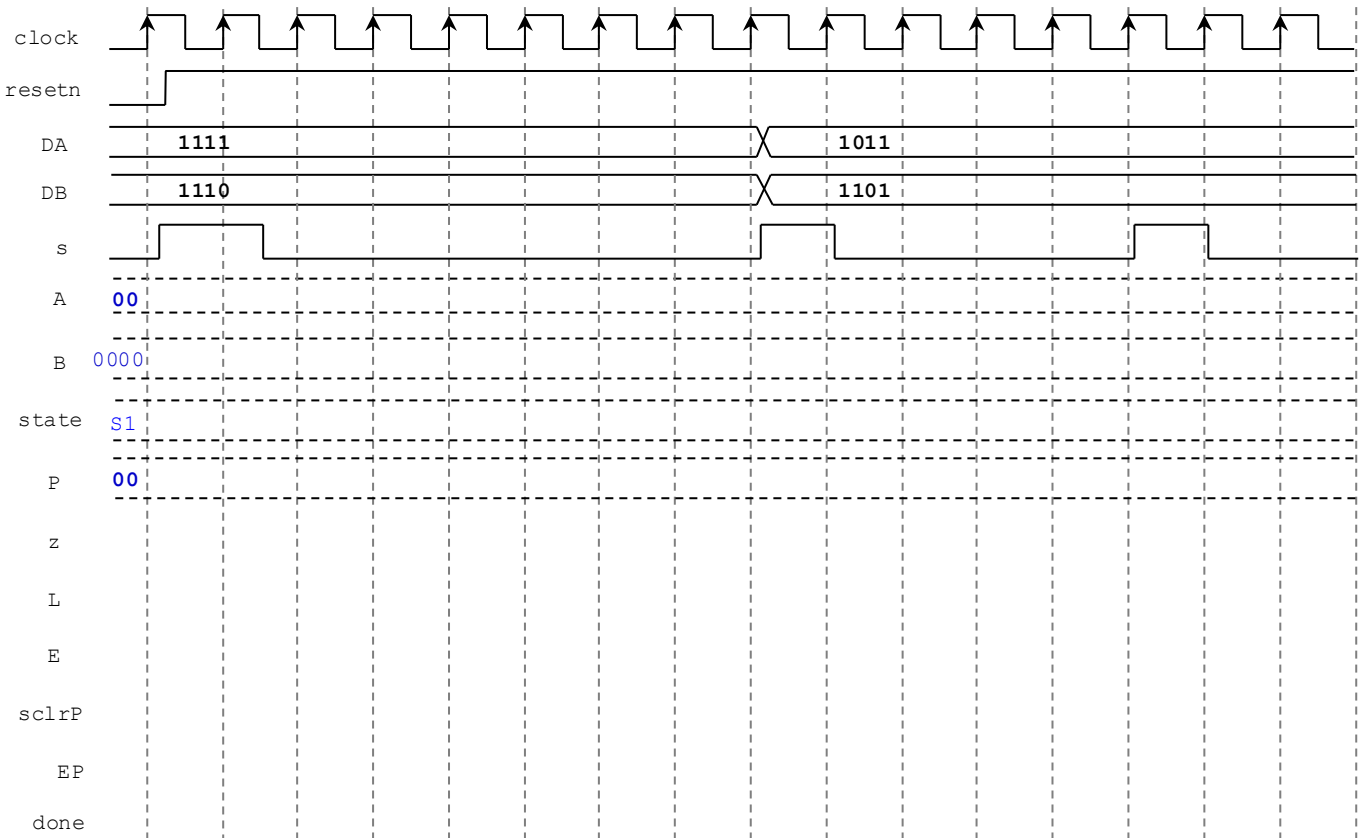

- Attach a printout of your Project Status Report (no more than a page). This report should contain the current status of the project, including a block diagram of your system. You **MUST** use the provided template (Final Project - Report Template.docx).