### BANNER ON A SEVEN SEGMENT DISPLAY WITH VARIOUS SCROLLING SPEEDS



BY GRANT TOOLEY, ADAM SNITGEN, CHRISTOPHER MARINELLO, STAVROS HABIB

### PROJECT DESCRIPTION

- Using VHDL code on the Nexys A7-50T FPGA Trainer Board to display a pre-coded message onto eight seven segment displays.
- We will show the message "ECE2700" on the seven segment displays with various scrolling speeds, shifting the letters from right to the left.

# USES IN THE REAL WORLD

- Digital Clocks, Clock Radios, Basic Calculators
- Odometers, Gas Pumps, and Electronic Billboard
- Alarm Clocks



#### COMPONENTS


Four counters

4-to-1 multiplexor

Shift Reg Finite State Machine


RAM shift register

7-segment serializer

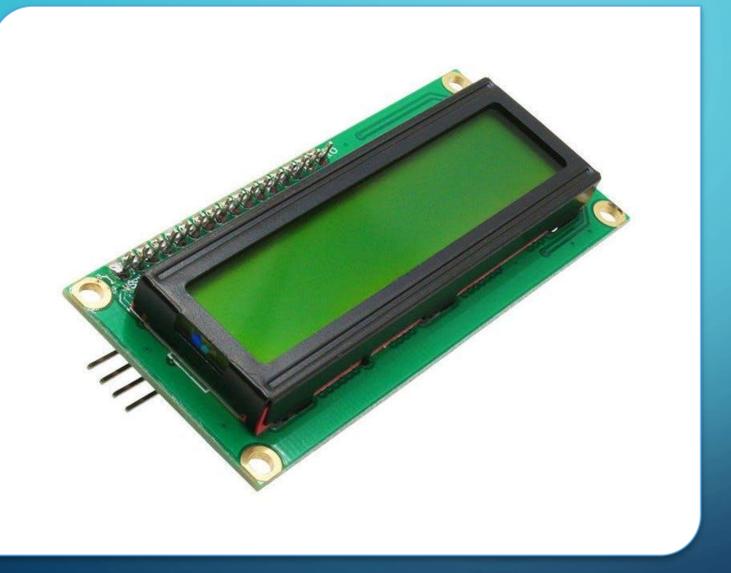

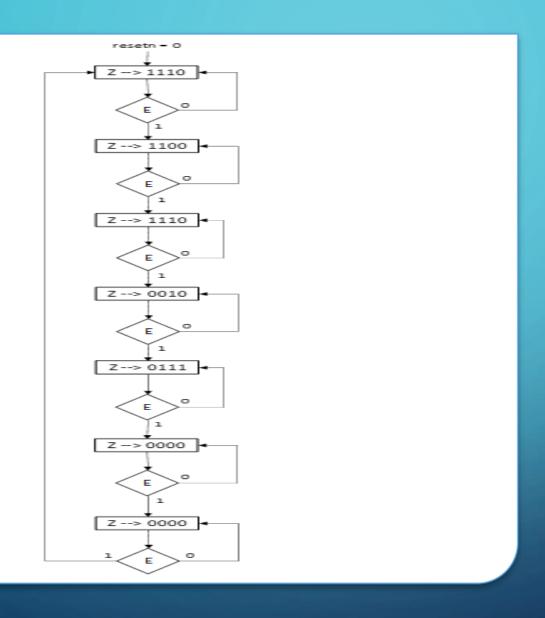
## IMPROVEMENTS FOR OUR PROJECT

- Code could have included a longer message using more displays
- Use an LCD display for a more modern day approach




FSM DIAGRAM

# TOP BLOCK DIAGRAM

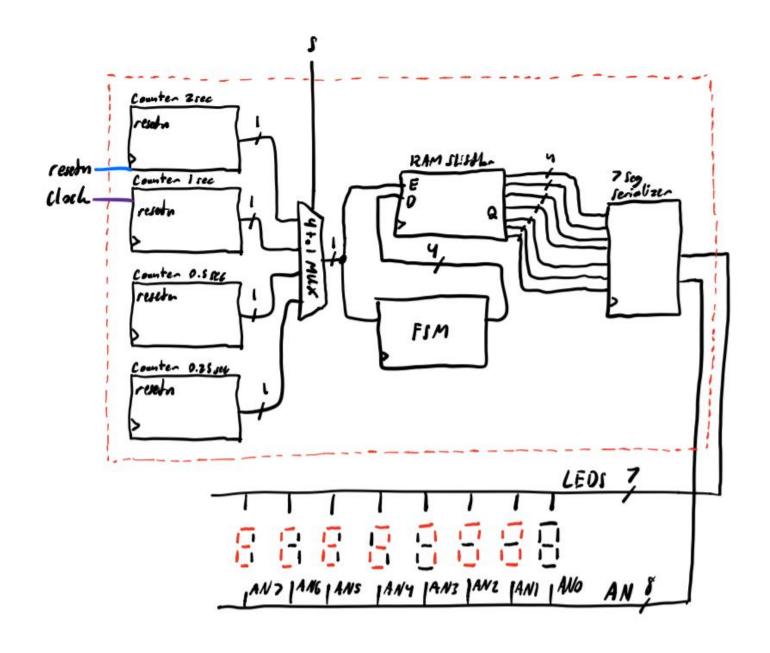

### SEVEN SEGMENT SERIALIZER SIMULATION

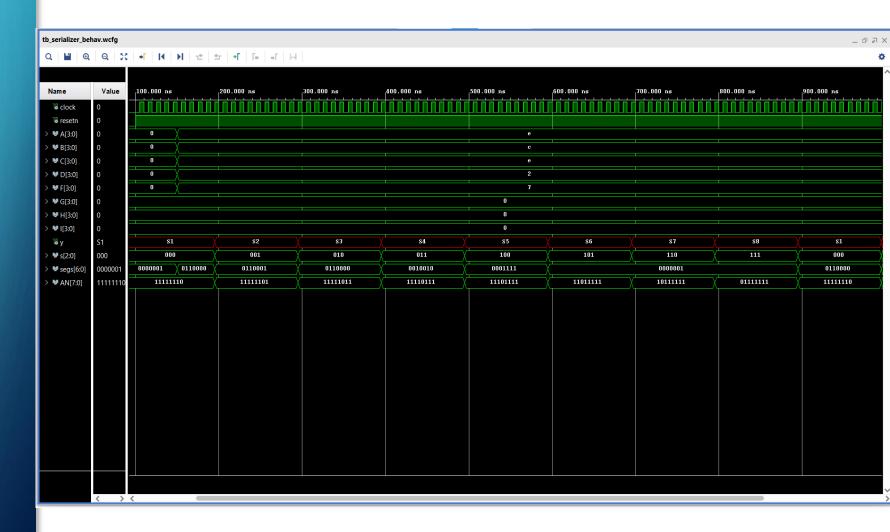

### **DEMONSTRATION**

 https://drive.google.com/file/d/12f6Shp4s4T\_r0BulWSHDLQ8QxJRTbm-G/view?ts=607245b1