

Student Honor Pledge:

All work submitted is completed by me directly without the use of any unauthorized resources or assistance

Initials: _____

Midterm Exam

(February 16th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

PROBLEM 1 (24 PTS)

- a) Complete the following table. The decimal numbers are unsigned: (5 pts.)

Decimal	BCD	Binary	Reflective Gray Code
31			
			110001
	001001000111		

- b) Complete the following table. The decimal numbers are signed. Use the fewest number of bits in each case: (15 pts.)

REPRESENTATION			
Decimal	Sign-and-magnitude	1's complement	2's complement
			10110
		10000	
			01101
	11011		
-31			
		100110	

- c) Convert the following decimal numbers to their 2's complement representations. (4 pts)


✓ -31.5

✓ 25.25

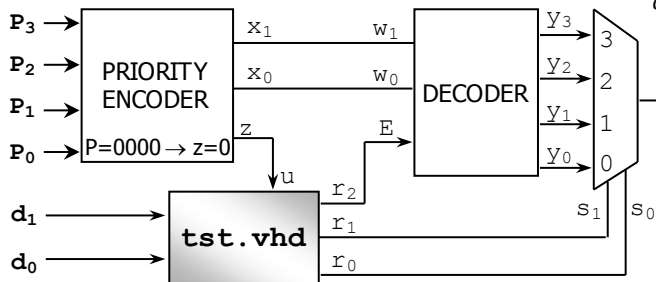PROBLEM 2 (18 PTS)

- Complete the timing diagram of the following circuit. The VHDL code (tst.vhd) corresponds to the shaded circuit.

$$d = d_1d_0, w = w_1w_0, r = r_2r_1r_0, y = y_3y_2y_1y_0$$



```

library ieee;
use ieee.std_logic_1164.all;
entity tst is
  port (d: in std_logic_vector(1 downto 0);
        r: out std_logic_vector(2 downto 0);
        u: in std_logic);
end tst;

```

architecture bhv of tst is

begin

process (d, u)

begin

r <= "11"&d(0);


if u = '0' then

r <= d&'0';

end if;


end process;

end bhv;

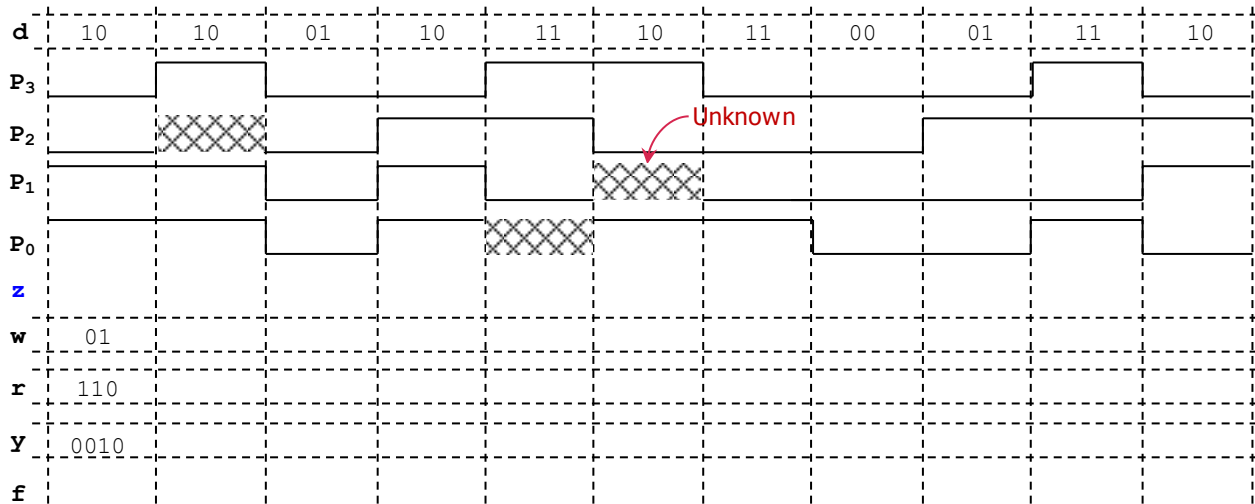

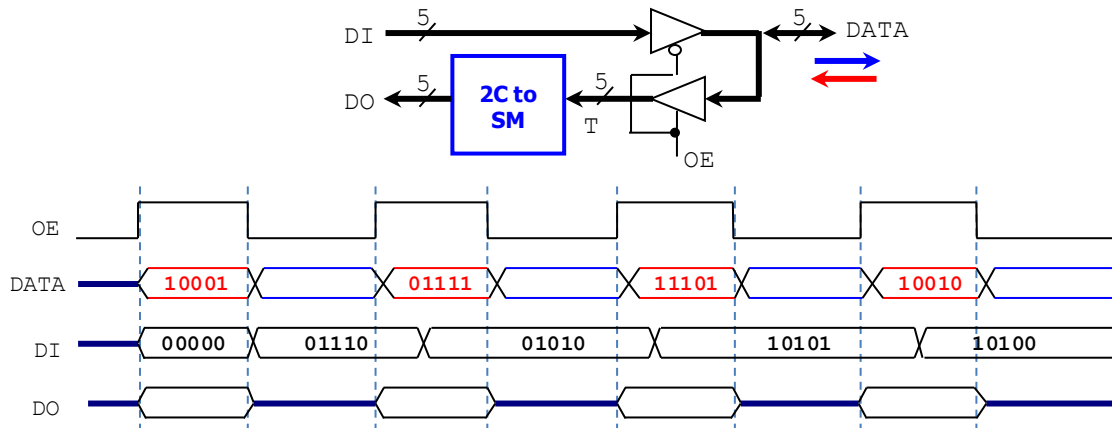
PROBLEM 3 (12 PTS)

- Complete the timing diagram (signals *DO* and *DATA*) of the following circuit. The circuit in the blue box treats the input *T* as a 5-bit signed (2C) number and converts it to the sign-and-magnitude representation with 5 bits.
✓ Example: if *T* = 10110, then *DO* = 11010.



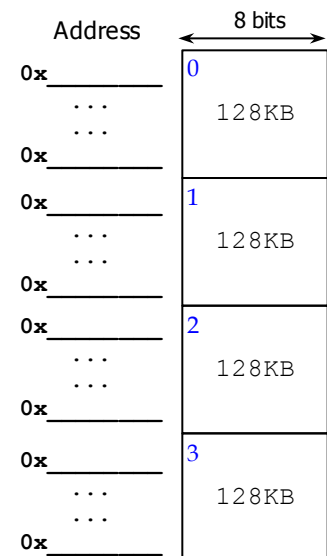PROBLEM 4 (11 PTS)

- A microprocessor has a memory space of 512 KB. Each memory address occupies one byte.
 - What is the address bus size (number of bits of the address) of this microprocessor?
 - What is the range (lowest to highest, in hexadecimal) of the memory space for this microprocessor?
 - The figure to the right shows four memory chips that are placed in the given positions:
 - ✓ Complete the address ranges (lowest to highest, in hexadecimal) for each of the memory chips.



PROBLEM 5 (18 PTS)

- Perform the binary unsigned subtraction of these unsigned integers. Use the fewest number of bits n to represent both operators. Indicate every borrow from b_0 to b_n . Determine whether we need to keep borrowing from a higher byte. (6 pts)
✓ $31 - 37$
- Perform the binary operation of these numbers, where numbers are represented in 2's complement. Indicate every carry from c_0 to c_n . Use the fewest number of bits to represent the summands and the result so that overflow is avoided. (8 pts)
✓ $31 - 37$
- Perform binary multiplication of the following numbers that are represented in 2's complement arithmetic. (4 pts)
✓ -11×7

PROBLEM 6 (17 PTS)

- A 3-input majority gate has an output value f that is 1 if there are more 1's than 0's on its inputs. The output f is 0 otherwise.
 - Provide the simplified expression for f and sketch this circuit using logic gates. (5 pts)
 - Implement the previous circuit using ONLY 2-to-1 MUXs (AND, OR, NOT, XOR gates are not allowed). (12 pts)

