

FPGA Sound Synthesizer

Armela Gjokaj | Forrest Mason | Mehvi Mehvi | Tyler Waddell
e-mails: armelagjokaj@oakland.edu, forrestmason@oakland.edu,
mehvi@oakland.edu, waddell@oakland.edu



Introduction

The project is about the implementation through VHDL of a Sound Synthesizer. It involves the connection of an external device, which is a buzzer, to the FPGA board through the PMOD ports. The user can use SW[0] to hold the system in its current state.

Notes ascend from C4 to C5, no sharps



Methodology


The process of building the circuit consists of two systems which are presented in diagrams. The state diagram describes the desired output based on the user input.

Math determined number constants


Clock Rate	Note	Note Frequency	TPWM Count	DC
100MHz	C	261	383142	191571
	D	293	341297	170648
	E	329	303951	151976
	F	349	286533	143266
	G	392	255102	127551
	A	440	227273	113636
	B	493	202840	101420
	C	523	191205	95602



Block Diagram

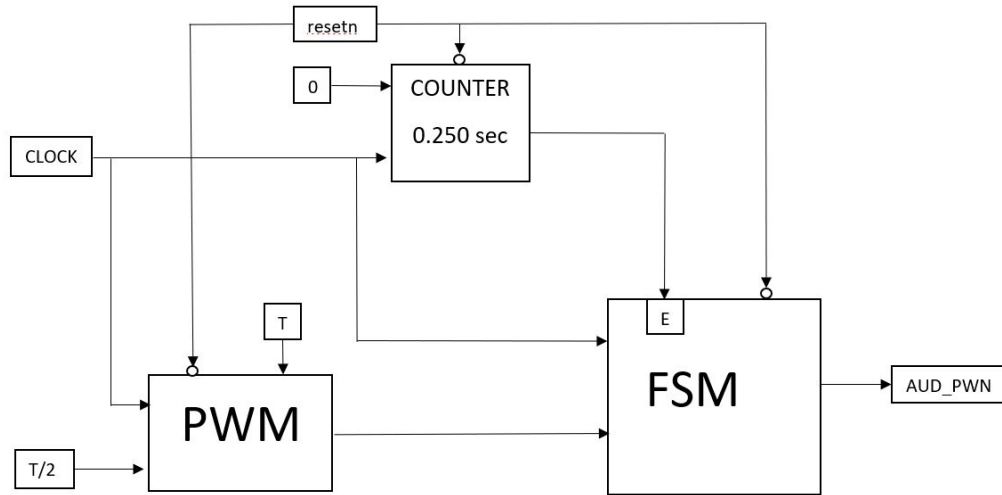

Counter counts to 25,000,000

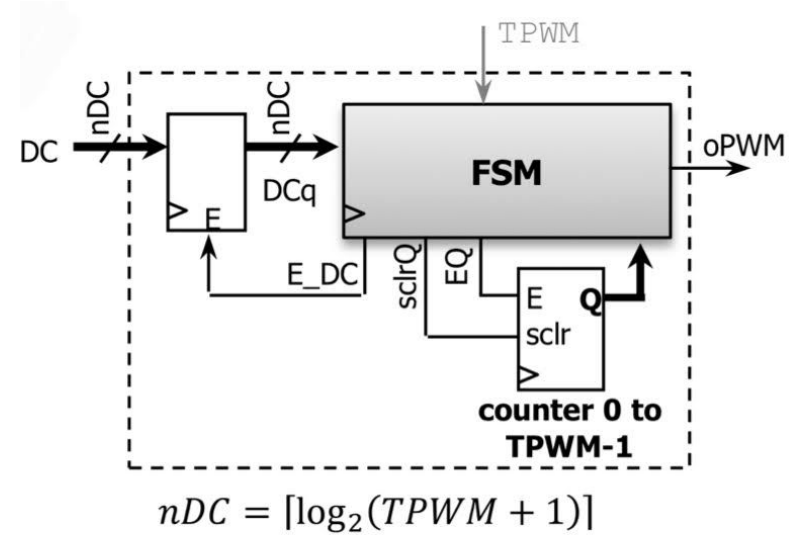



If $DC = 0 \rightarrow oPWM = 0$

If $DC = TPWM \rightarrow oPWM = 1$



System State Diagram

Each non-PWM state (S1-S8) sets the output to a unique frequency

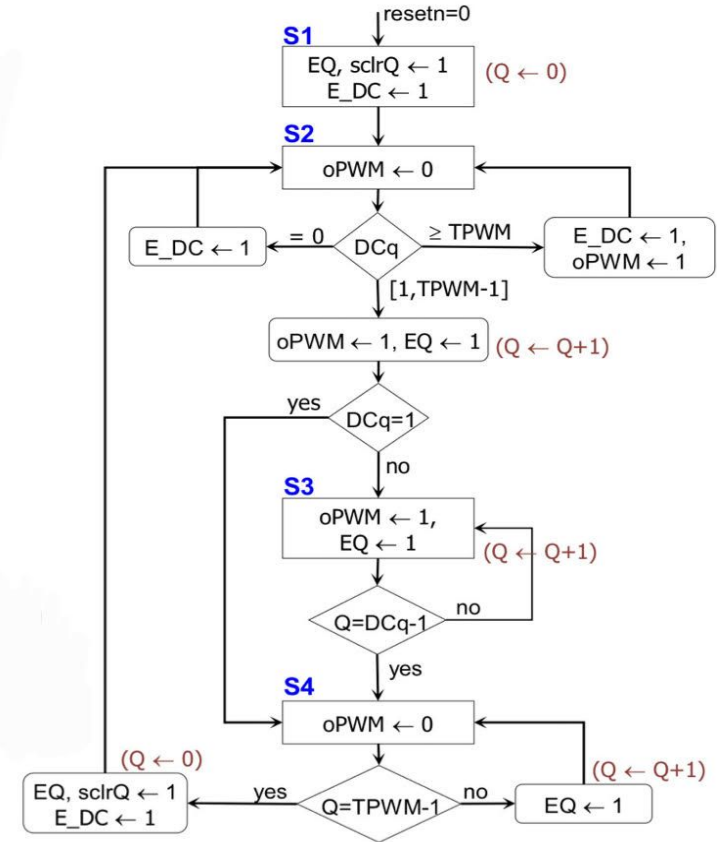 A enable-type input 'Q' acts as a hold on the current state and prevents progression



Demo

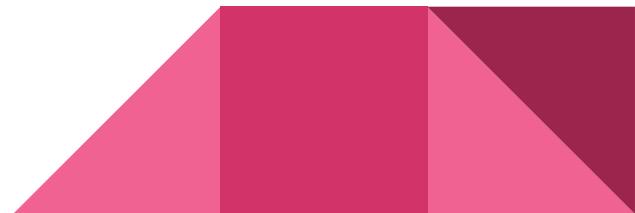 

Future Improvement and Conclusions

States can be expanded to accommodate a larger musical register

Current thought process on implementing measures involves a counter to determine which note is played next/for what duration

