

# Quiz 4

(April 5<sup>th</sup> @ 5:30 pm)

## PROBLEM 1 (35 PTS)

- Draw the state diagram (in ASM form) of the FSM whose VHDL description is listed below:

```
library ieee;
use ieee.std_logic_1164.all;

entity circ is
  port ( clk, rstn: in std_logic;
        r, p, q: in std_logic;
        x, w, z: out std_logic);
end circ;
```

```
architecture behavioral of circ is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (rstn, clk, r, p, q)
  begin
    if rstn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if r = '1' then y <= S2;
          else if p = '1' then y <= S3; else y <= S1; end if;
          end if;

        when S2 =>
          if p = '1' then y <= S1; else y <= S3; end if;

        when S3 =>
          if q = '1' then y <= S3; else y <= S2; end if;


      end case;
    end if;
  end process;

  Outputs: process (y, r, p, q)
  begin
    x <= '0'; w <= '0'; z <= '0';
    case y is
      when S1 => if r = '0' then x <= '1'; end if;
      when S2 => if q = '0' then w <= '1'; end if;
                   if p = '0' then z <= '1'; end if;
      when S3 => if q = '0' then w <= '1'; end if;
    end case;
  end process;
end behavioral;
```

- Circle or mark the correct FSM type:  
(Mealy)                      (Moore)
 
## PROBLEM 2 (35 PTS)

- Given the following FSM circuit:
  - Provide the Excitation Table and the Excitation equations (including the Boolean equation for z).



- Is this a Mealy or a Moore FSM? Why? (5 pts)

## PROBLEM 3 (30 PTS)

- Sequence detector: Draw the state diagram (any representation) of an FSM with input  $x$  and output  $z$ . The detector asserts  $z = 1$  when the sequence 0110 is detected. Right after the sequence is detected, the circuit looks for a new sequence.