


Overview

- This project is designed to allow a user to create a melody or short beat
- It includes a Nexys 4 DDR board and a connected speaker
- The user selects switches and uses buttons to choose how many and what kind of notes are played in a given melody
- The melody is then played in a loop through the speaker

Play and Pause Button FSM

 Designed to toggle between two states; play and pause

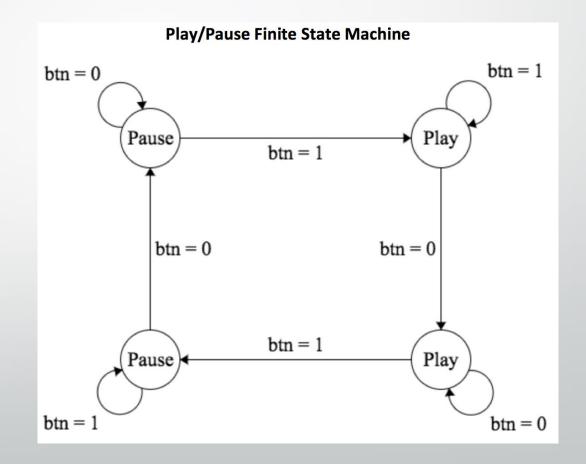 Used to ensure proper transitions between states



Clock Divider

 Used to convert the base clock MHz frequency of the Nexys board to a smaller frequency so a user has time to hear that sound

This sets the tempo of the melody generator

Counters


• Two main counters are used; one three bit and one four bit

Three bit counter is used to cycle between possible notes

Four bit counter is used to play through the 16 switches on the Nexys board

 Flip-flops are used to cycle through numbers to output either a three bit or four bit number

Button Debouncer

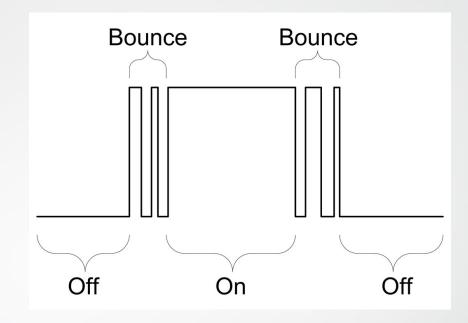

Button Debouncing is necessary for the buttons on the Nexys board

 Debouncer is used to prevent unwanted switches between states when a button is pressed (Play/Pause or Increment)

Frequency Increase Previous State Check

Used to increment a counter exactly once with a button press

Converts input to a pulse with a duration of one clock cycle

 When the input of the pulse generator goes high, its output goes high for exactly one clock cycle

PWM Frequency Generator

Note	Frequency	7-Segment Number
G# ₄	405Hz	1
A# ₄	473Hz	2
C ₅	526Hz	3
D ₅	588Hz	4
F ₅	684Hz	5
F# ₅	746Hz	6
A ₅	862Hz	7

- Generates a wave based on a 4 bit input
- Generates Sound using the PWM on the PMOD outputs
- This is done by dividing the input clock signal by a specific number to achieve the desired frequency
- The frequencies range from 405 Hz to 862 Hz to represent notes on a musical scale


Issues Overcome and Original Idea

Speaker too quiet

Would not play through switches in correct order

Original Idea was a Keyboard with Preset Melodies

How to Use

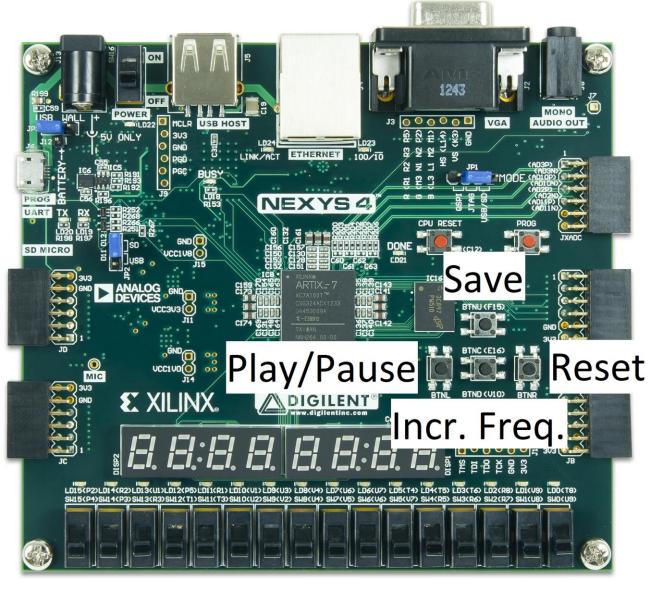

Switches for Notes

Project Demo

