

ECE-4710 Final Project

Professor Daniel Llamocca

Submitted by:
Connor Goetz
Ethan Postma
Matthew Hait

Introduction

- 16-bit machine code, multicycle microprocessor circuit via FPGA implementation
- 31 accessible registers
 - 2 utilized for specific purposes
 - 1 indexed (Register 1 address 0x01)
- Included program and data memories (using blockRAM)
- Four basic machine code categories

OP CODE	Offset Bits 7 to 2	Source B	Offset Bits 1 to 0	Function
1 0	_____	_____	__	__

Function	Outcome
0 0	PC = PC + Offset (Signed)
1 0	PC = PC + Offset (Signed) if Source B = 0
1 1	PC = PC + Offset (Signed) if Source B < 0

1 1 0	A = A xor B (Bitwise)
-------	-----------------------

OP CODE	Unused	Source B	Stack OP	Function
1 0	X X X X X	_____	__	0 1

Stack OP	Outcome
0 0	SP = SP + 1
0 1	SP = SP - 1
1 0	Store B on Stack, SP + 1
1 1	Pull data from stack onto B, SP - 1


0 0 1 1	B = B - 1
---------	-----------

OP CODE	Signed 14-bit Immediate Value
1 1	_____

1 DIR N	A = A shifted by N in DIR Direction, '0' = right, '1' = left (Signed)
---------	--

Block Overview

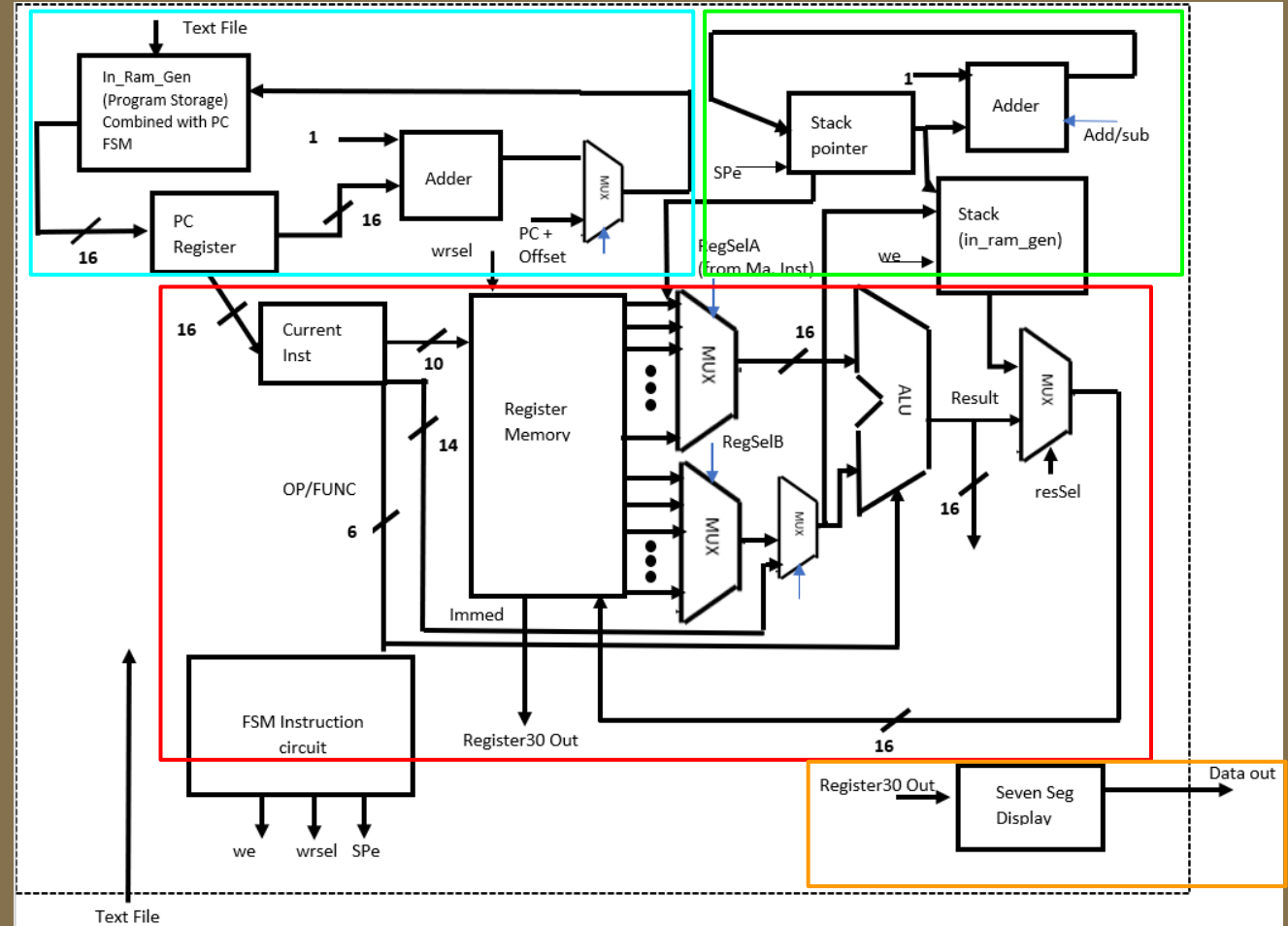- 4 Basic Blocks:
 - Data Path
 - Program Counter
 - Data Memory
 - Serializer
- 2 Finite State Machines
 - Program Counter
 - Data Path
- Inherent FSM and blockRAM reads cause delays
 - Multi-cycle Processor as a result
- User input is machine code .txt file
- Output is displayed on seven segment displays
 - Register 30 (Address 0x1E) reserved for output data



Data Path

Register Memory:



- 31 Registers, my_rege

ALU:

- Takes instructions directly from machine code
- Ability to perform arithmetic, logic, and branch checking operations
 - Emits asynchronous “branch_check” signal based upon current instruction (check for negative or zero)
 - Made up of adders, logic statements, and a bit-shifter
 - Purely combinatorial circuit, i.e. all possible outcomes calculated each cycle
 - Calculations asynchronous at cost of extra hardware


Finite State Machine:

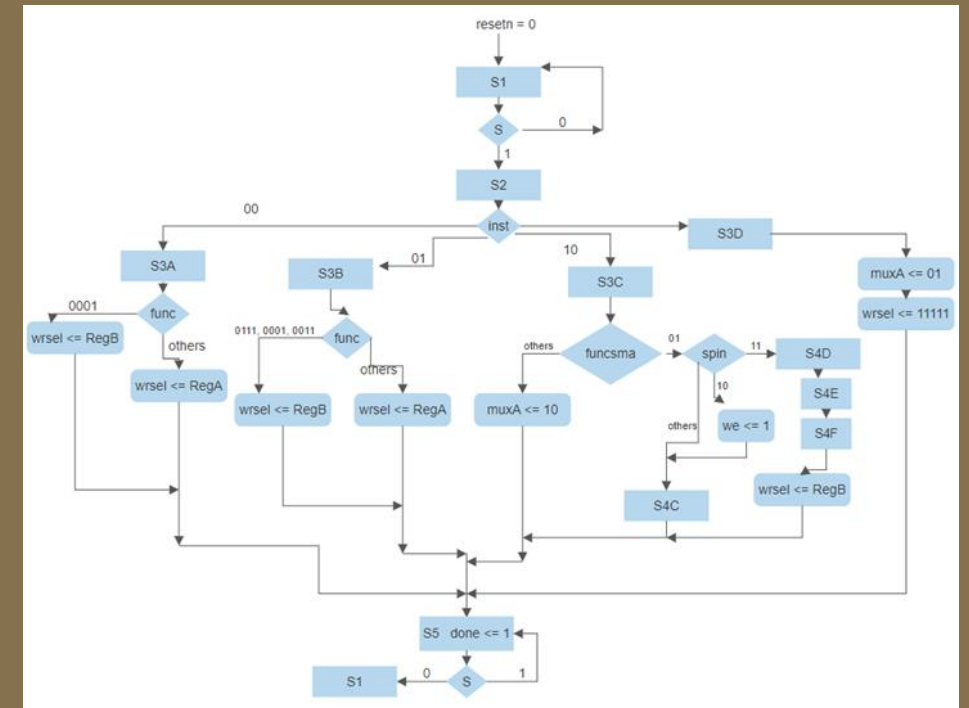 - Controls register enables and write signals
- Controls stack data memory signals
- Multicycle, but simplifies instruction decoding



Data Path - Data Memory

- “Stack” like system
 - User can pull data, push data, increment or decrement pointer
 - Unlike traditional stack, fills top up
 - 16-bit width, same as onboard registers
- Utilizing the onboard blockRAM
 - Creates a time delay as reading takes extra cycles
 - Very large space relative to what can be accomplished with a ram emulator
 - Shares blockRAM with the program file
 - To prevent data overwrites, begins at address 0x2000

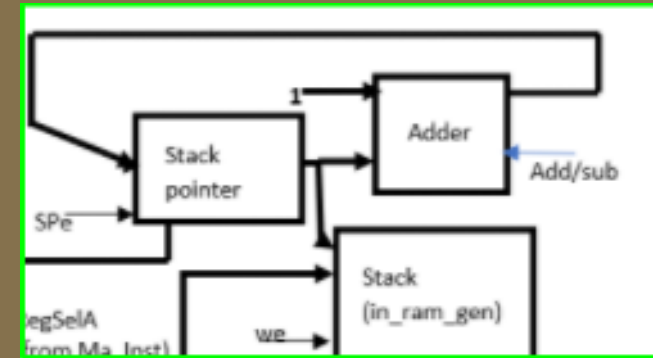


Stack OP	Outcome
0 0	SP = SP + 1
0 1	SP = SP - 1
1 0	Store B on Stack, SP + 1
1 1	Pull data from stack onto B, SP - 1

```
--RAM
stack: in_RAMgen generic map(nrows => 65536, ncols => 1, FILE_IMG => "myinival.txt", INIT_VALU
port map(clock => clock, inRam_idata => ALU_B,
         inRam_add => SP, inRam_we => we, inRam_en => '1',
         inRAM_odata => outram);
```

Program Counter

Block Diagram

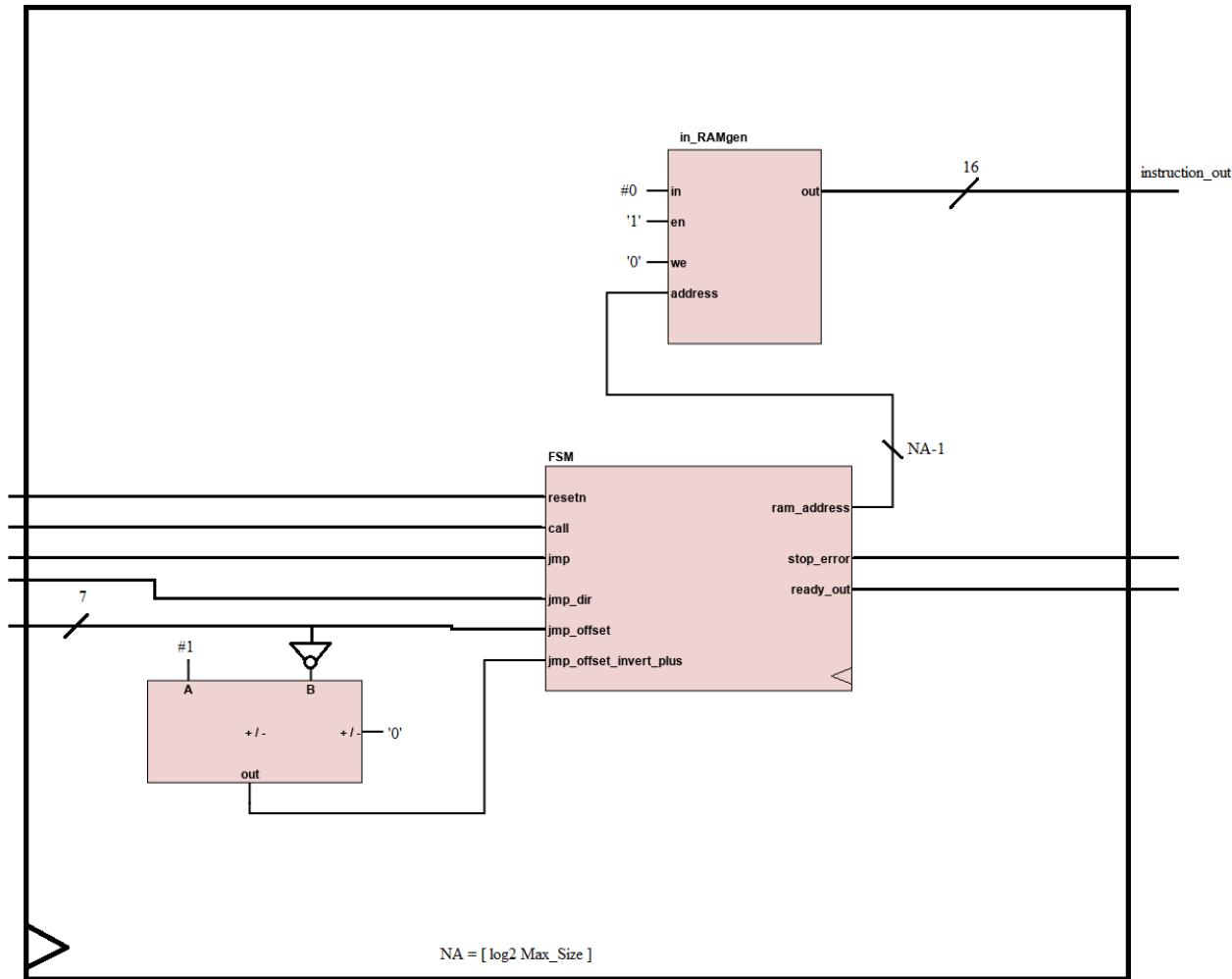
- “Max_Size” is number of stored instruction
- Utilizes blockRAM
- Block *grows* to fit instructions
 - Max_Size changes NA width
 - NA affects RAM allocation
 - NA affects ram_address width




Program Counter

Finite State Machine

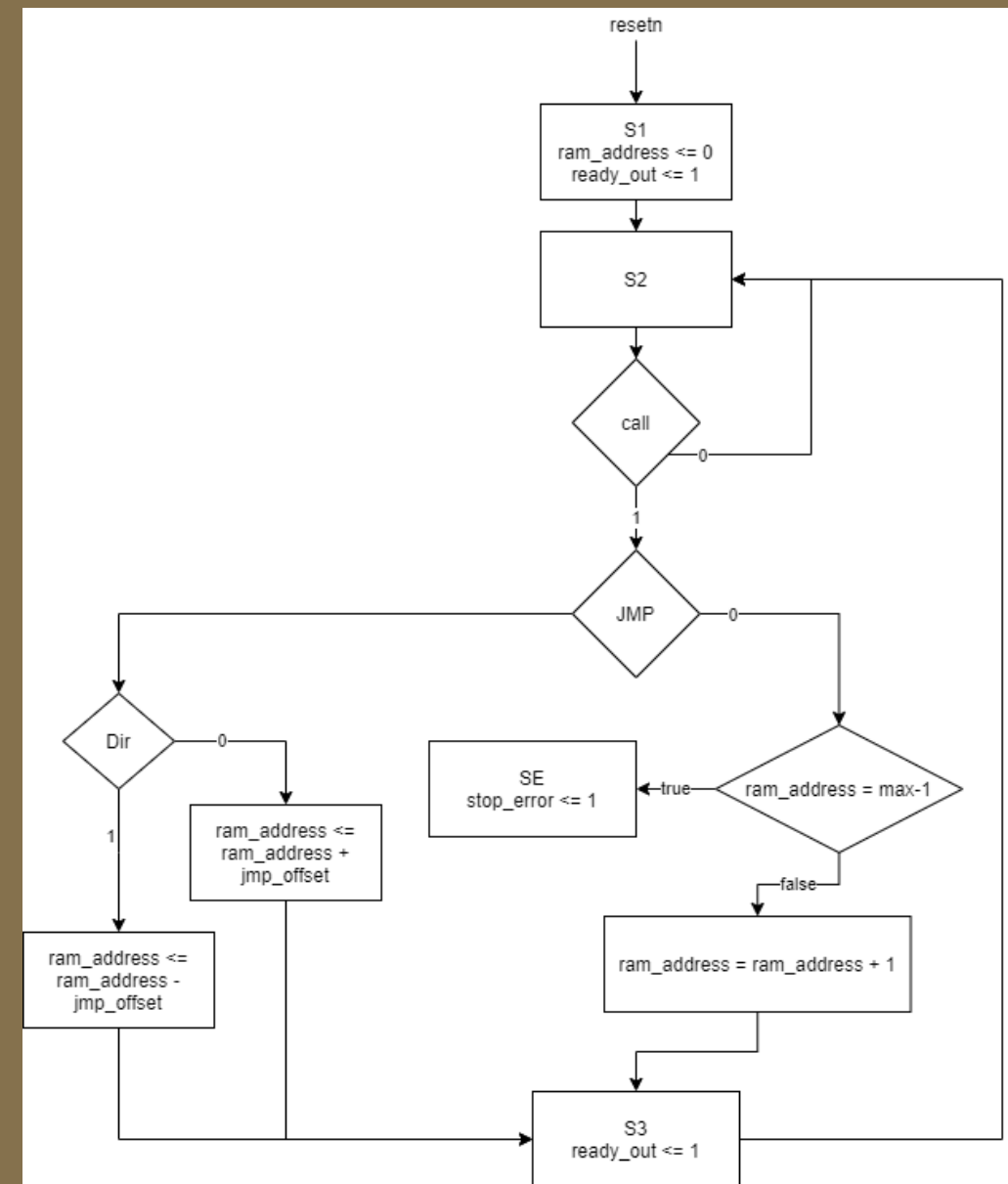- “stop_error” end of instruction indicator
- S3 initializes processor




 


```

jmp_check: process (op, funcma, branch_check)
begin
    sig_jump <= '0';
    if op = "10" then
        if funcma = "00" then
            sig_jump <= '1';
        end if;
        if branch_check = '1' then
            sig_jump <= '0'; --problem here
        end if;
    end if;
end process;


```

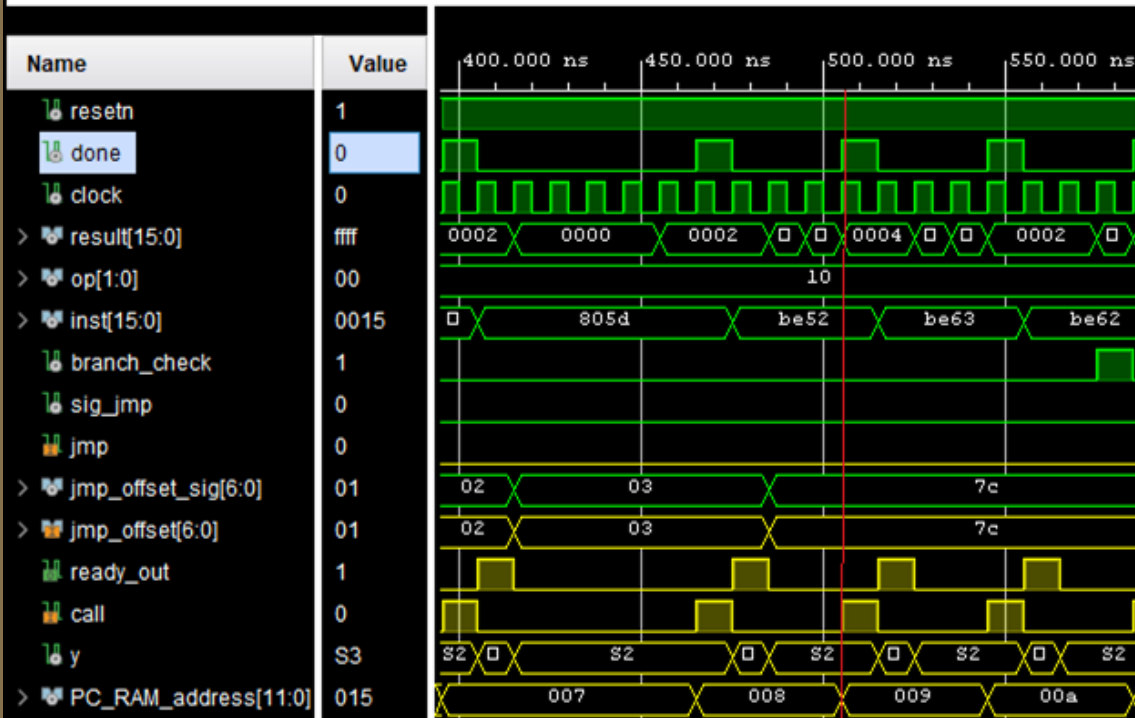

```

jmp_check: process (op, funcma, branch_check)
begin
    sig_jump <= '0';
    if op = "10" then
        if funcma = "00" then
            sig_jump <= '1';
        end if;
        if branch_check = '1' then
            sig_jump <= '1'; --problem here
        end if;
    end if;
end process;

```

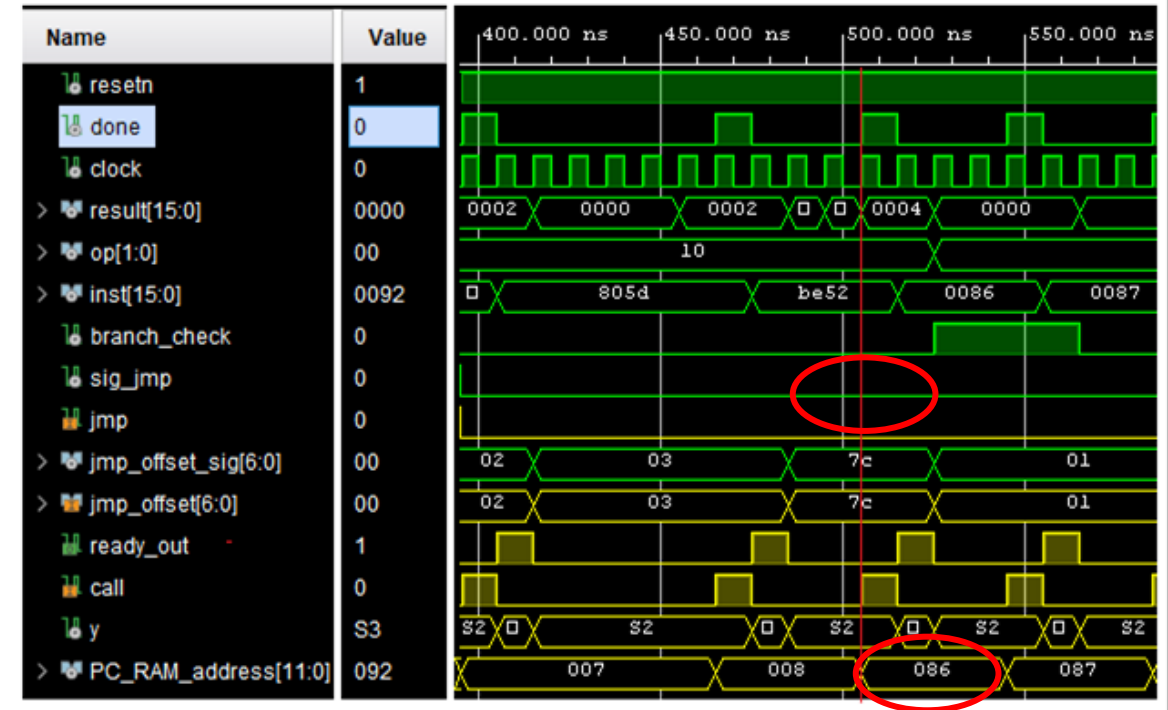


Aside: An extremely small timing error

- “branch_check” flips once after 520 ns
- Flip last for infinitely short period of time
- Resolved by adding clock event check


```
when S2 =>
  -- Added clock check to stop simulation error
  if (clock'event and clock = '1') then
    if call = '1' then
      if jmp = '1' then
        -- Jump Ram Address
        if jmp_dir = '1' then
          -- Negative
          PC_RAM_address <= PC_RAM_address - conv_std_logic_vector (unsigned(jmp_offset_invert_plus),NA-1);
        else
          -- Positive
          PC_RAM_address <= PC_RAM_address + conv_std_logic_vector (unsigned(jmp_offset),NA-1);
        end if;
      else
        -- No Jump, index by 1
        PC_RAM_address <= PC_RAM_address + conv_std_logic_vector (1,NA-1);
      end if;
    end if;
  end if;
```

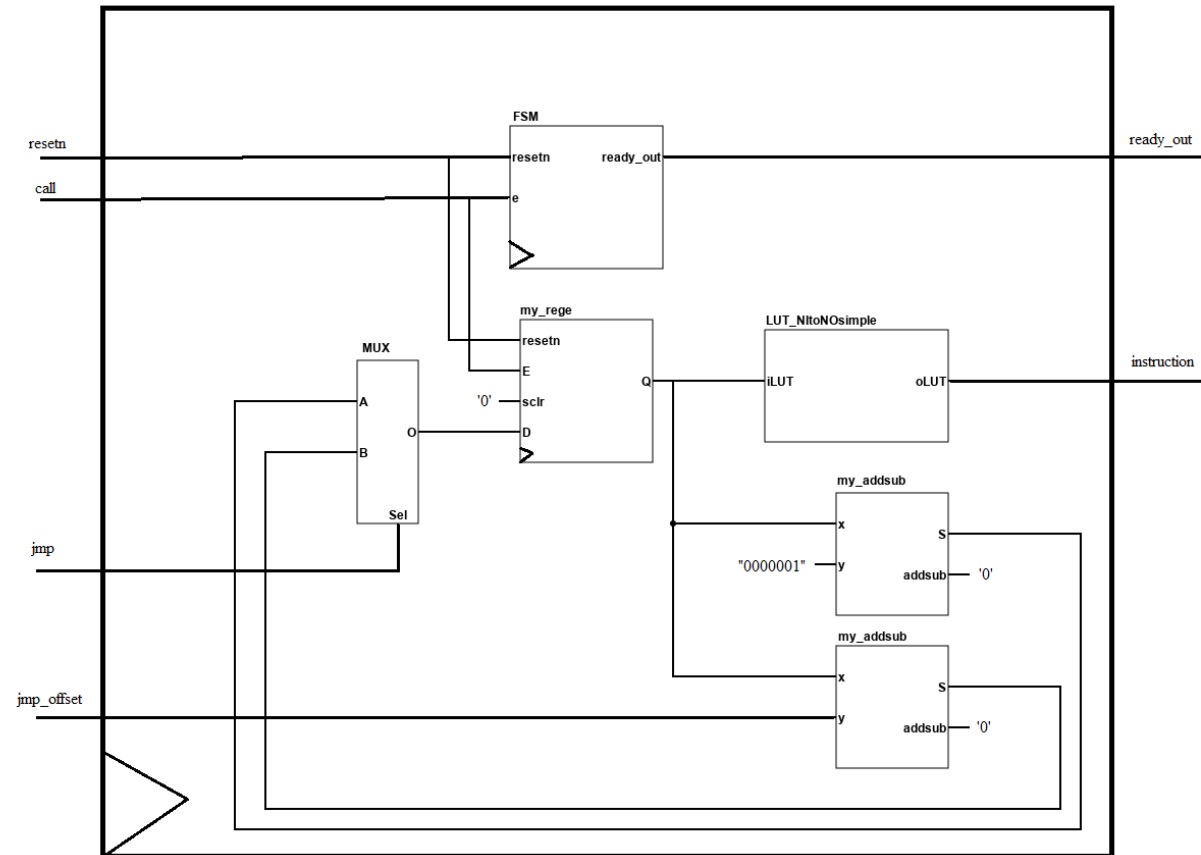- Original program counter failed in post-synthesis timing
 - Unmapped synthesized ram signals
 - Possibly result of using two in_RAMgen
- Revised PC uses LUT
 - Loads from text file



Serializer

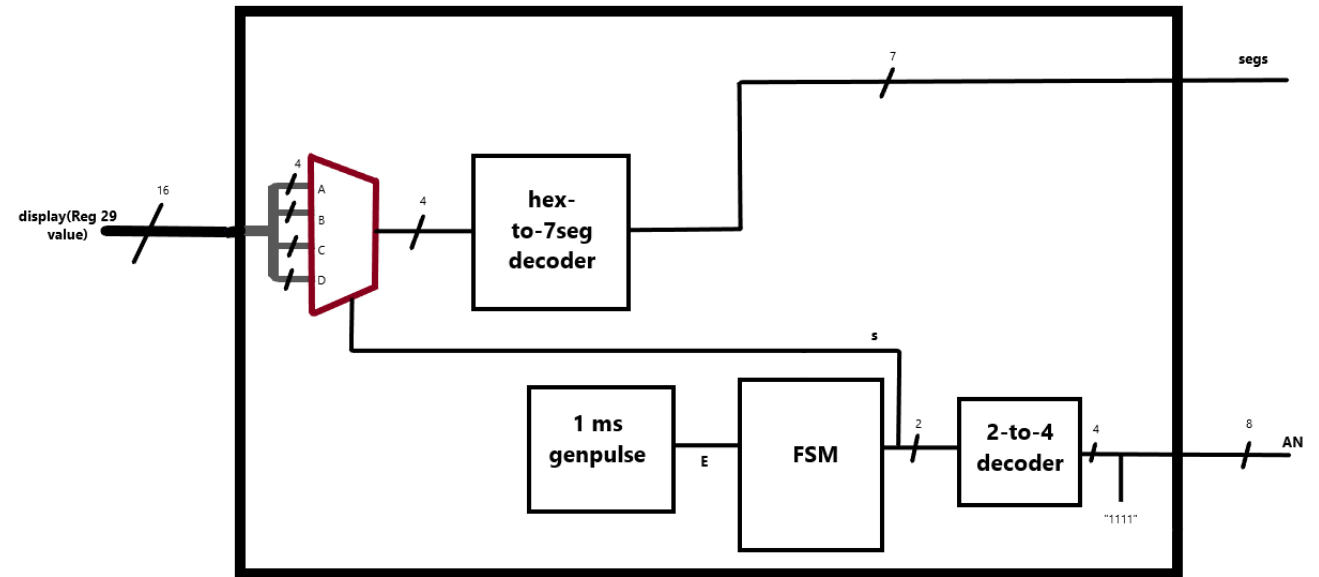Takes constant output from register 29, the “output” register




Basic parametric code, important to the real life applications of our microprocessor

Machine Code Instructions

Table shows the different machine code inputs for the functions in our microprocessor

Bit:	15	14	13	12	11	10	9	8	7	6	5	4	3	2	1	0	Instruction
Logic:	0	0	Destination Register/ Register A					Register B					Function Op Code				
	0	0											x	0	0	0	A = Not A
	0	0											x	0	0	1	B = Not B
	0	0											x	0	1	0	A = A and B
	0	0											x	0	1	1	A = A or B
	0	0											x	1	0	0	A = A nand B
	0	0											x	1	0	1	A = A nor B
	0	0											x	1	1	0	A = A xor B
	0	0											x	1	1	1	A = A xnor B
	0	0															
Arithmetic:	0	1	Destination Register/ Register A					Register B					Function Op Code				
	0	1											0	0	0	0	A = A + 1
	0	1											0	0	0	1	B = B + 1
	0	1											0	0	1	0	A = A - 1
	0	1											0	0	1	1	B = B - 1
	0	1											0	1	0	0	A = A + B
	0	1											0	1	0	1	A = A - B
	0	1											0	1	1	1	B = A
	0	1															
	0	1															
Move/Stack:	1	0	Offset High Bits										Offset Low		OP		
	1	0	dir	off(5)	off(4)	off(3)	off(2)						off(1)	off(0)	0	0	JMP
	1	0	dir	off(5)	off(4)	off(3)	off(2)						off(1)	off(0)	1	0	BRN if B = 0
	1	0	dir	off(5)	off(4)	off(3)	off(2)						off(1)	off(0)	1	1	BRN if B is -
	1	0	x	x	x	x	x						0	0	0	1	SP = SP + 1
	1	0	x	x	x	x	x						0	1	0	1	SP = SP - 1
	1	0	x	x	x	x	x						1	0	0	1	Push to stack
	1	0	x	x	x	x	x						1	1	0	1	Pull from stack
	1	0															
Load IM(R30)	1	1	Load Value														

Test Program

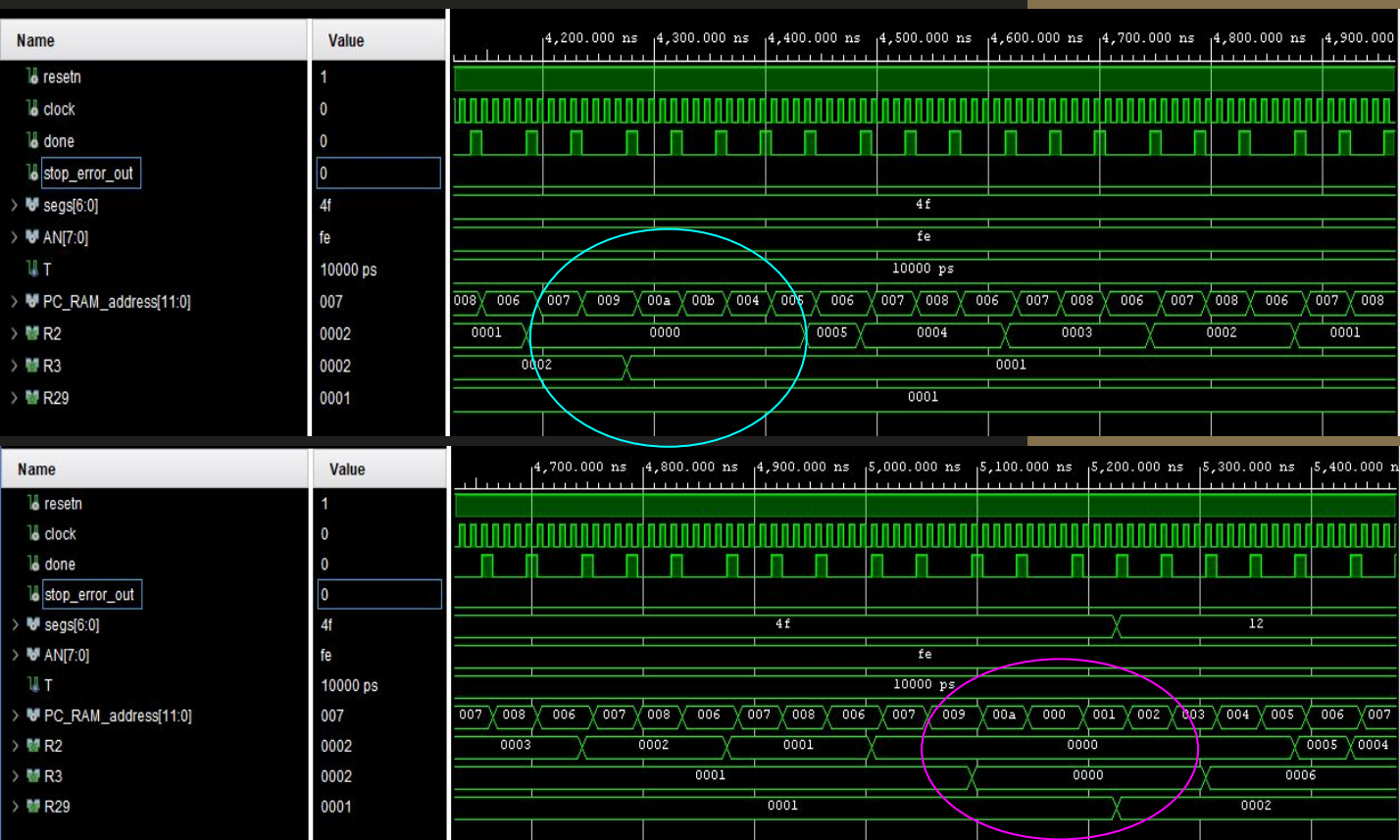

4200; R1 = R1 + 1 PC:
000
43E7; R29(output) = R1 PC: 001
C006; IM = 6 PC: 002
7E37; R3 = IM PC:
003
C005; IM = 5 PC:
004
7E27; R2 = IM PC:
005
4402; R2 = R2 - 1 PC:
006
802A; Branch to 009 if R2 = 0 PC: 007
BE38; JMP to 006 PC:
008
4602; R3 = R3 - 1 PC:
009 In order to demonstrate this counter working on the
BA3A board, the values 0001 to Reg-2 and Reg-3 have to be
BC34 changed to create a 1 second delay. Since each PC:
00B instruction takes about 40 ns, FFFF is loaded into R2
and 007F is loaded into R3 to create approximately a 1
second delay, incrementing the value of the output
register every 1 second. This calculation takes the timing
for the jump instructions into consideration.

Block
Overview


Data Path

Program
Counter

7- Seg
Serializer

Program

Demo

 

<https://www.youtube.com/watch?v=DOc6HEfDoSk>

Block
Overview

Data Path

Program
Counter

7- Seg
Serializer

Program

Demo