

# Laboratory 4

(Due date: **005**: March 20<sup>th</sup>, **006**: March 21<sup>st</sup>)

## OBJECTIVES

- ✓ Implement a Digital System: Control Unit and Datapath.
- ✓ Learn about reading PDM-coded input audio and playback PDM-coded output audio.
- ✓ Learn interfacing with MEMS microphones (that generate PDM signals) and using BlockRAMs in FPGAs.



## VHDL CODING

- ✓ Refer to the [Tutorial: VHDL for FPGAs](#) for a tutorial and a list of examples.

## FIRST ACTIVITY: AUDIO RETRIEVAL AND PLAYBACK: DESIGN AND SIMULATION (60/100)

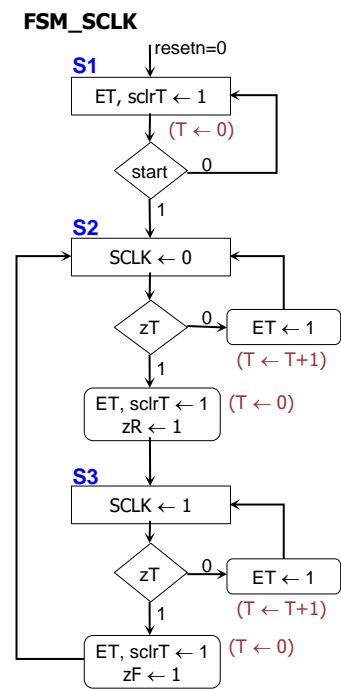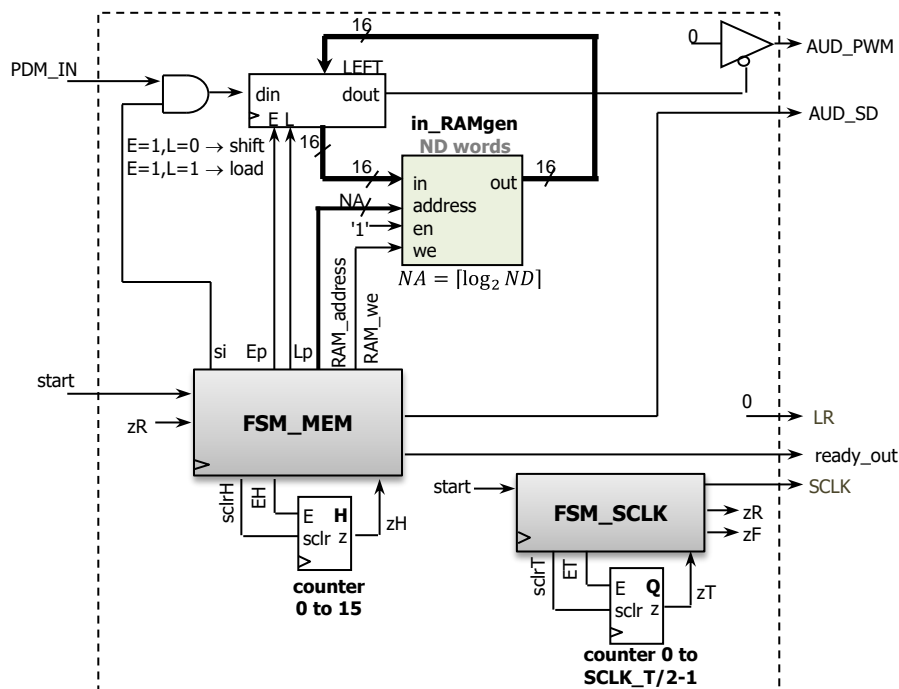
### DESIGN PROBLEM

- **MICROPHONE AND MONO AUDIO OUTPUT:** Implement the following circuit that reads data from the ADMP421 MEMS microphone, stores data in memory and plays data back on a mono audio output.



- **MEMS MICROPHONE (ADMP421):**
  - ✓ SCLK: 1 – 3 MHz. We use 1.2 MHz.
  - ✓ PDM\_IN: PDM signal generated by the ADMP421.
  - ✓ LR: Left right control for stereo mode. We use LR = 0 (Data is captured on CLK rising edge).
- **MONO AUDIO OUTPUT:**
  - ✓ The on-board audio jack of the board (Nexys-A7-50T/A7-100T, Nexys 4-DDR) does not support stereo output. Thus, we only retrieve a mono audio input from the ADMP42 microphone (e.g. L/R = 0). Keep this in mind when testing (as only one speaker or earphone side will work).
  - ✓ The on-board audio jack is driven by a low-pass filter with 12 KHz cut-off frequency. We need to feed a PDM signal (AUD\_PWM: open-drain output) into the low-pass filter. Note that AUD\_PWM is the output of a tri-state buffer:
    - If we want to transmit a '0', AUD\_PWM = '0'.
    - If we want to transmit a '1', AUD\_PWM = 'Z'.
- **FSM\_SCLK:**
  - ✓ This circuit generates a free running clock (SCLK). It also generates a pulse on zR when a rising edge on SCLK occurs, and a pulse on zF when a falling edge on SCLK occurs. We want to use a frequency of 1.2 MHz. This requires SCLK\_T=84.


- To set up  $SCLK\_T=84$ , you need to use the VHDL code `fsm_sclk.vhd` (along with `my_genpulse_sclr.vhd`) and set up its parameter `COUNT_SCKLHP = SCLK_T/2=42`.
- **MEMORY:** Implemented with the on-chip memory (BlockRAMs) inside the Artix-7 FPGA.
  - ✓ Data requested or to be written is available on the next clock cycle. Use the given VHDL code in `RAMgen.vhd`. This is a 2D memory of `nrows×ncols`. Word length: 16 bits. We can use it as a 1D memory by making `ncols=1`. Use the following parameters `nrows`=(this depends on the board), `ncols=1`, `INIT_VALUES="NO"`, `FILE_IMG="myinival.txt"`.
    - For Nexys A7-100T/Nexys-4 DDR, use: `nrows=512*512`
    - For Nexys A7-50T, use `nrows=512*256` (there is less memory in the FPGA inside this board)
- **FSM\_MEM:** This is the main controller. This FSM embeds the counter `RAM_address`. Make sure to use the correct ND:
  - ✓  $ND = 512 \times 512 = 2^{18}$  for Nexys A7-100T/Nexys-4 DDR. Sequence duration:  $2^{18} \times 16 \times 84 \times 10ns = 3.52$  seconds.
  - ✓  $ND = 512 \times 256 = 2^{17}$  for Nexys A7-50T.

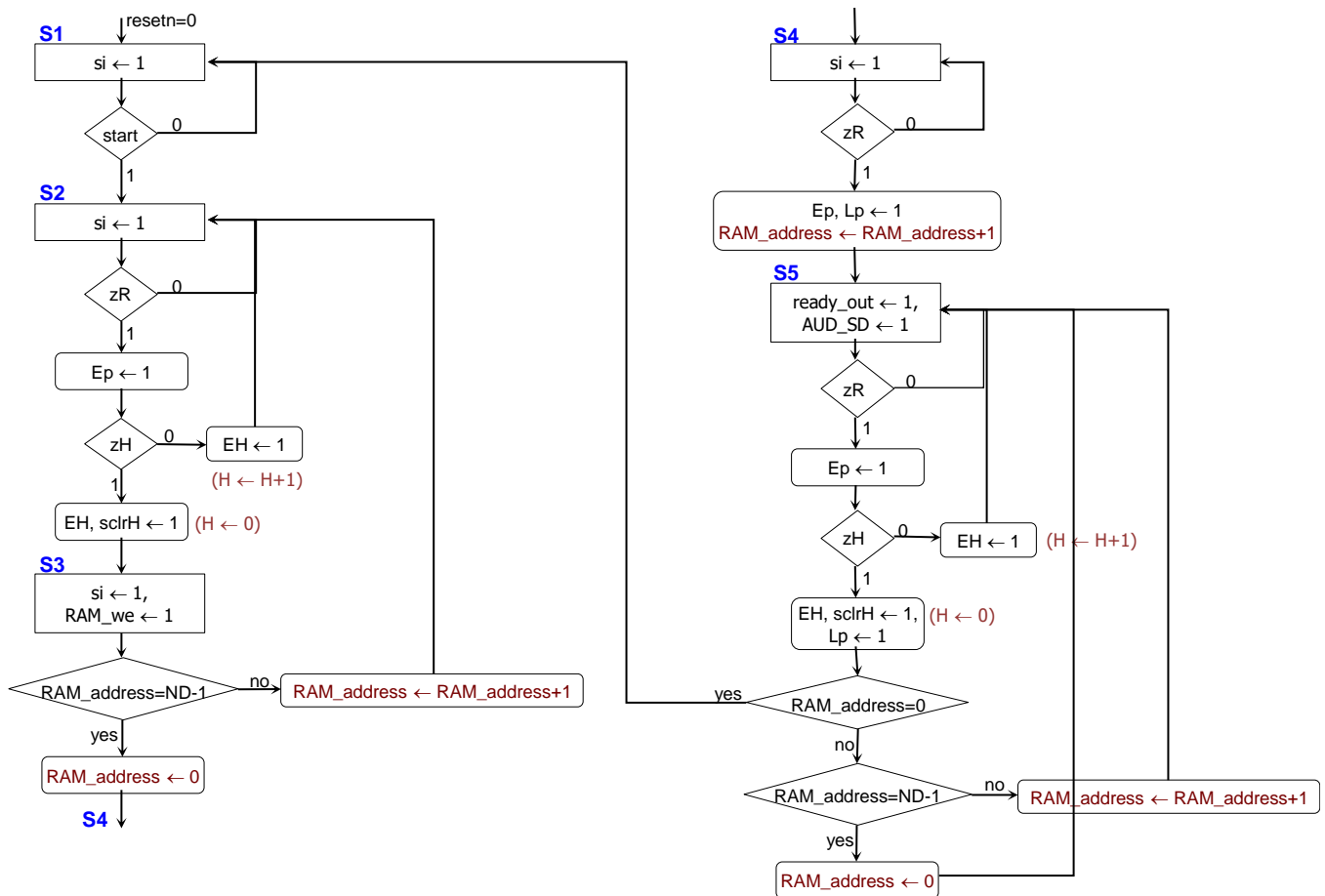
 
## PROCEDURE

- **Vivado: Complete the following steps:**
  - ✓ Create a new Vivado Project. Select the corresponding Artix-7 FPGA device (e.g.: the XC7A100T-1CSG324 FPGA device for the Nexys A7-100T board).
  - ✓ Write the VHDL for the given circuit. Synthesize your circuit. (Run Synthesis).
    - Use the **Structural description**: Create (or re-use) a separate `.vhd` file for i) parallel access shift register, ii) `inRAM_gen`, iii) `FSM_MEM`, iv) `FSM_SCLK`, and v) top file (where you will interconnect them all).
      - Use the proper parameters and I/O connections. Note that `FSM_SCLK` is made from two `.vhd` files.
  - ✓ Write the VHDL testbench (generate a 100 MHz input clock for your simulations).
    - To avoid long simulation times, only for simulation purposes use these parameters in the following blocks:
      - Memory: `nrows=4x4, ncols=1`.
      - `FSM_SCLK`: `COUNT_SCKLHP = SCLK_T/2 = 2`.

- PDM\_IN: Generate the following serial input stream (4x4 16-bit words), where each bit is to be captured at the rising edge of SCLK: 1110 1100 1110 1011 0100 0111 0001 0000 1010 1100 1110 1101 1110 1010 0101 0001 and then just 1's. These bits are stored in memory (inRAM\_gen) as 16-bit values: ECEB 4710 ACED EA51 FFFF ... FFFF.
- The timing diagram depicts how to set up the input signals.



- ✓ Perform Behavioral Simulation (Run Simulation → Run Behavioral Simulation). **Demonstrate this to your TA.**
  - To help debug your circuit, add internal signals to the waveform (e.g.: FSM\_MEM/state, RAM\_address, SCLK, inRAM\_gen/in, inRAM\_gen/out, etc).
  - Run the simulation for 21 us (remember to use `nrows=4x4, ncols=1, COUNT_SCLKHP = SCLK_T/2 = 2`).
    - Verify that the hexadecimal values (see testbench directions) appear on inRAM\_gen/out (memory output) during state S5 in FSM\_MEM.
    - Verify that the serial stream (see testbench directions) appears on dout (parallel access left shift register output)

## SECOND ACTIVITY: TESTING (40/100)

### ▪ Vivado: complete the following steps:

- ✓ I/O Assignment: Create the XDC file associated with your board.
  - Suggestion (Nexys A7-50T/A7-100T, Nexys 4/DDR):

Board pin names	CLK100MHZ	CPU_RESET	BTNC	M_DATA	M_CLK	M_LRSEL	AUD_PWM	AUD_SD	LED0
Signal names in code	clock	resetn	start	PDM_IN	SCLK	LR	AUD_PWM	AUD_SD	ready_out
- ✓ Implement your design (Run Implementation).
  - Ensure that the correct parameters values are set up in the Memory (`nrows`, `ncols`) and in FSM\_CLK (`COUNT_SCLKHP`). Do not use the same parameter values you used for simulation.
- ✓ Generate and download the bitstream on the FPGA. Test the circuit. **Demonstrate this to your TA.**
  - Press start and record an audio sequence for 3.52 seconds (this is for the Nexys A7-100T/Nexys-4 DDR). After that, the audio sequence is played back (use a headphone/speaker).

## SUBMISSION

- Submit to Moodle (an assignment will be created):
  - ✓ This lab sheet ([as a .pdf](#)) completed (if applicable) and signed off by the TA (or instructor).
    - Note: *The lab assignment has two activities. You get full points of the 1<sup>st</sup> activity if you demo it by the due date. You can demo the 2<sup>nd</sup> activity by the due date or late (here, we apply a penalty towards the points of the 2<sup>nd</sup> activity).*
  - ✓ ([As a .zip file](#)) All the generated files: VHDL code, VHDL testbench, and XDC file. **DO NOT submit the whole Vivado Project.**
    - Your .zip file should only include one folder. Do not include subdirectories.
    - It is strongly recommended that all your design files, testbench, and constraints file be located in a single directory. This will allow for a smooth experience with Vivado.
    - You should only submit your source files AFTER you have demoed your work. Submission of work files without demoing will be assigned NO CREDIT.

TA signature: \_\_\_\_\_

Date: \_\_\_\_\_