

Solutions - Homework 1

(Due date: January 30th @ 11:59 pm)

Presentation and clarity are very important! Show your procedure!



PROBLEM 1 (15 PTS)

- Greatest Common Divisor (GCD):** This circuit processes two n -bit unsigned numbers (A, B) and generates the GCD of A and B. For example:
 - ✓ If $A = 132, B = 72 \rightarrow \text{GCD} = 12$.
 - ✓ If $A = 216, B = 192 \rightarrow \text{GCD} = 24$.
 - ✓ If $A = 169, B = 63 \rightarrow \text{GCD} = 1$.
- The digital system (based on a sequential algorithm) is depicted in the figure below, and includes an FSM (in ASM) and a datapath circuit.
- Complete the timing diagram of the digital system (DA, DB, a_i , b_i are decimal values)

Sequential Algorithm

```

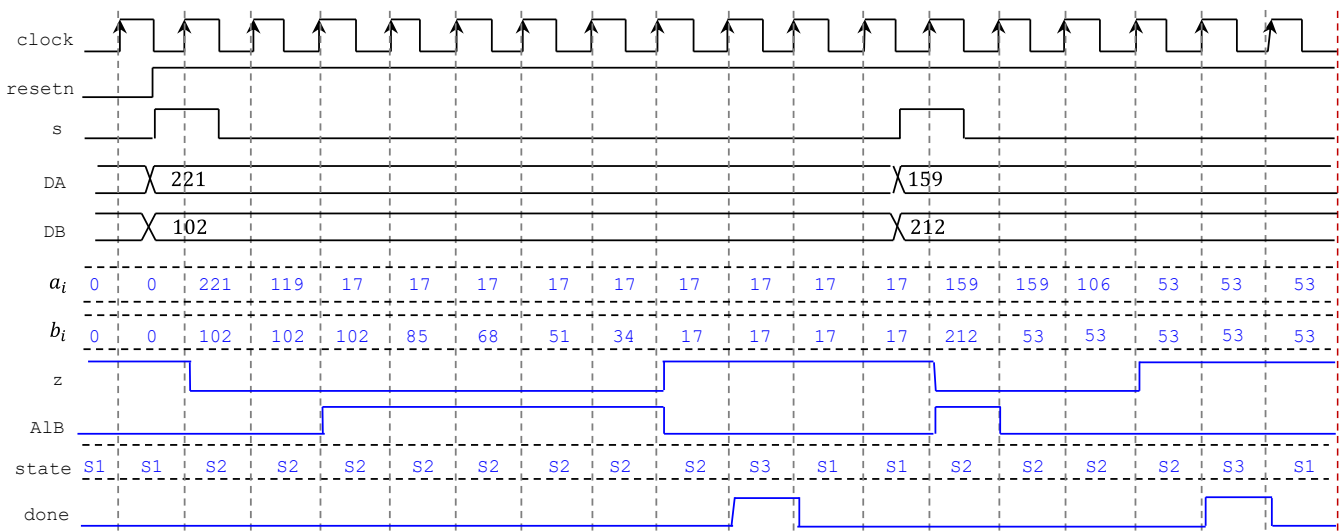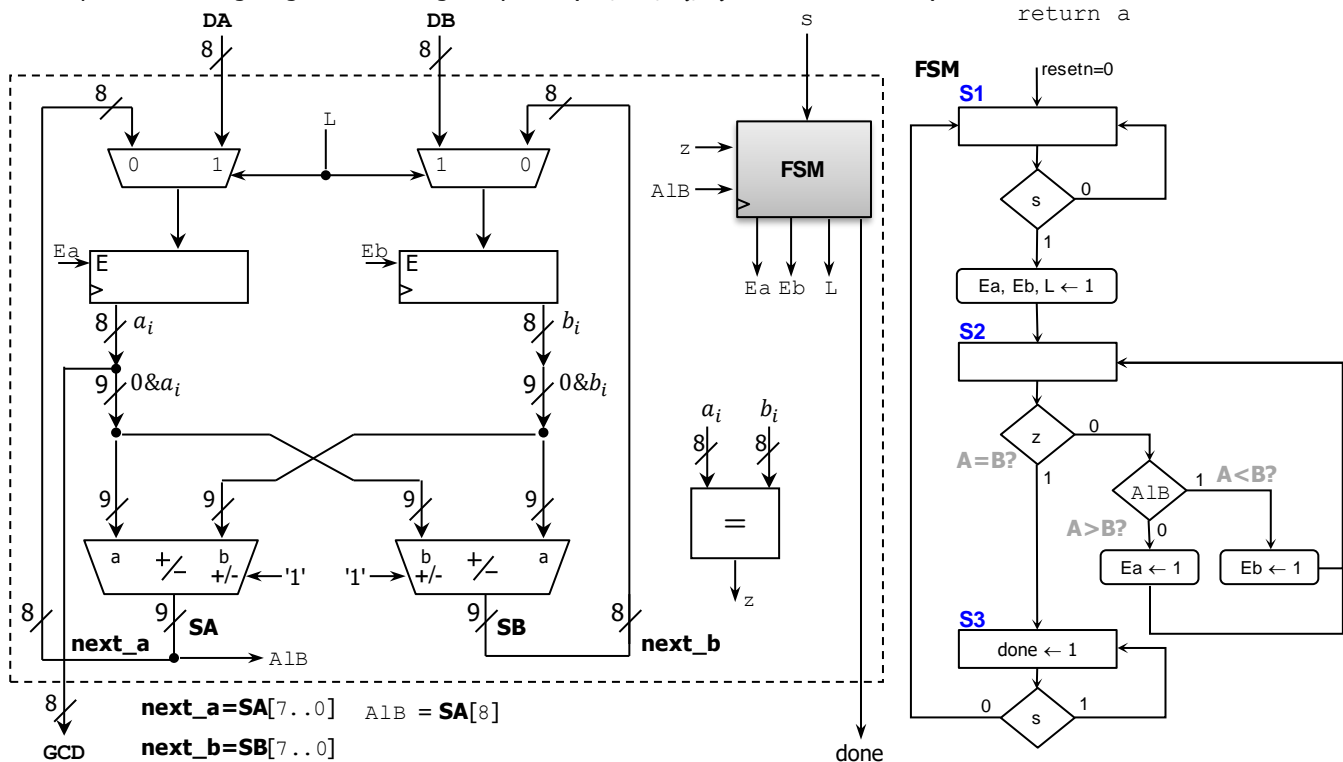a,b: unsigned integers
while a ≠ b
    if a > b
        a ← a-b
    else
        b ← b-a
end while
return a
    
```



PROBLEM 2 (45 PTS)

- **Leading Zero Detector (LZD):** This iterative circuit processes a 15-bit input (MSB first) and generates the number of leading 0's. before the first 1. Example:
 - ✓ If the sequence is: 0000 0001 1000 001 $\rightarrow R = 7$
 - ✓ If the sequence is: 0000 0000 0011 010 $\rightarrow R = 10$
 - ✓ If the sequence is: 0001 0000 0011 010 $\rightarrow R = 3$
- **Iterative architecture:** The figure depicts the FSM (in ASM form) and a datapath circuit.
 - ✓ Inputs: X (serial data, MSB first), start.
 - ✓ Outputs: z (leading 1 detected), done (N bits processed), and R (number of 0's before the first 1).
 - ✓ Processing begins when start is asserted. When the first '1' is detected on X, then $z=1$ (for 1 clock cycle) and R is frozen.
 - ✓ When all the bits of the sequence have been processed, done=1. We can re-start the process after this.
 - Note: if X is just 0's, z is never '1'.
 - ✓ Counters R and Q: modulo-(N+1): count from 0 to N. (N=15).

Generic component - counter (my_genpulse_sclr):
Behavior on the clock tick:


Counter modulo-N (0 to N+1): If E=0, the count stays.

```


if E = 1 then
  if sclr = 1 then
    Q ← 0
  else
    Q ← Q+1
  end if;
end if;
* z=1 if Q = N-1 (max. count)
  
```




- **Procedure:**

- ✓ Complete the timing diagram of the digital circuit (next page). Note that 3 sequences are evaluated.
- ✓ Write a structural VHDL code. You MUST create a file for i) modulo-16 counter, ii) flip-flop, iii) Finite State Machine, and v) Top file (where you will interconnect all the components).
- ✓ Write a testbench according to the timing diagram shown (next page). Perform Behavioral Simulation. Verify that the simulation is correct by comparing it with the timing diagram you completed manually.
 - R and Q are specified as decimals.
- ✓ Upload (as a .zip file) the following files to Moodle (an assignment will be created):
 - VHDL design source files
 - VHDL testbench
 - A simulation screenshot, showing the processing of the first data input (000000100100101).

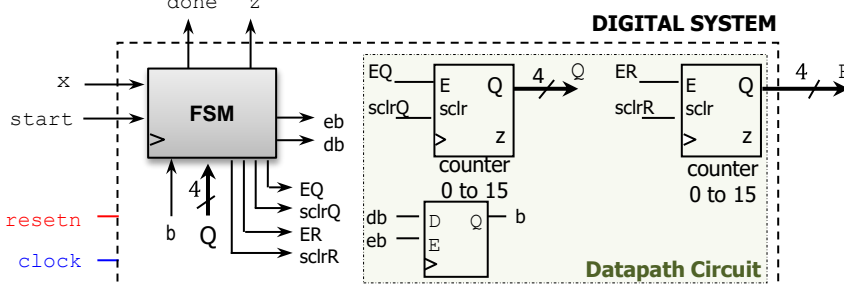

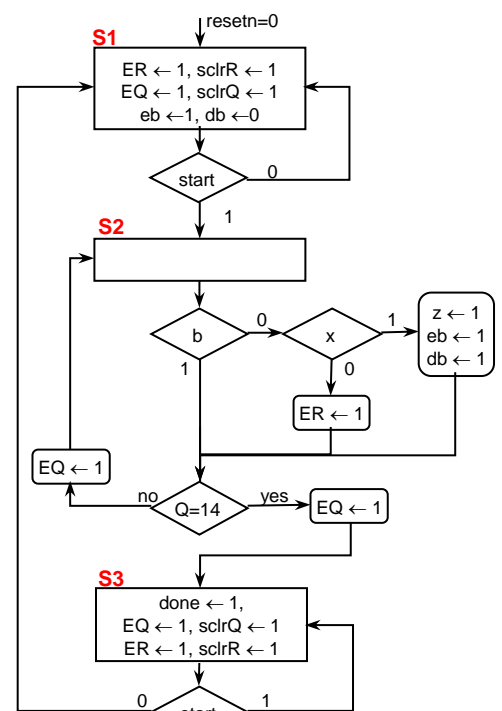See attached .zip file: SolutionsHW1p2.zip



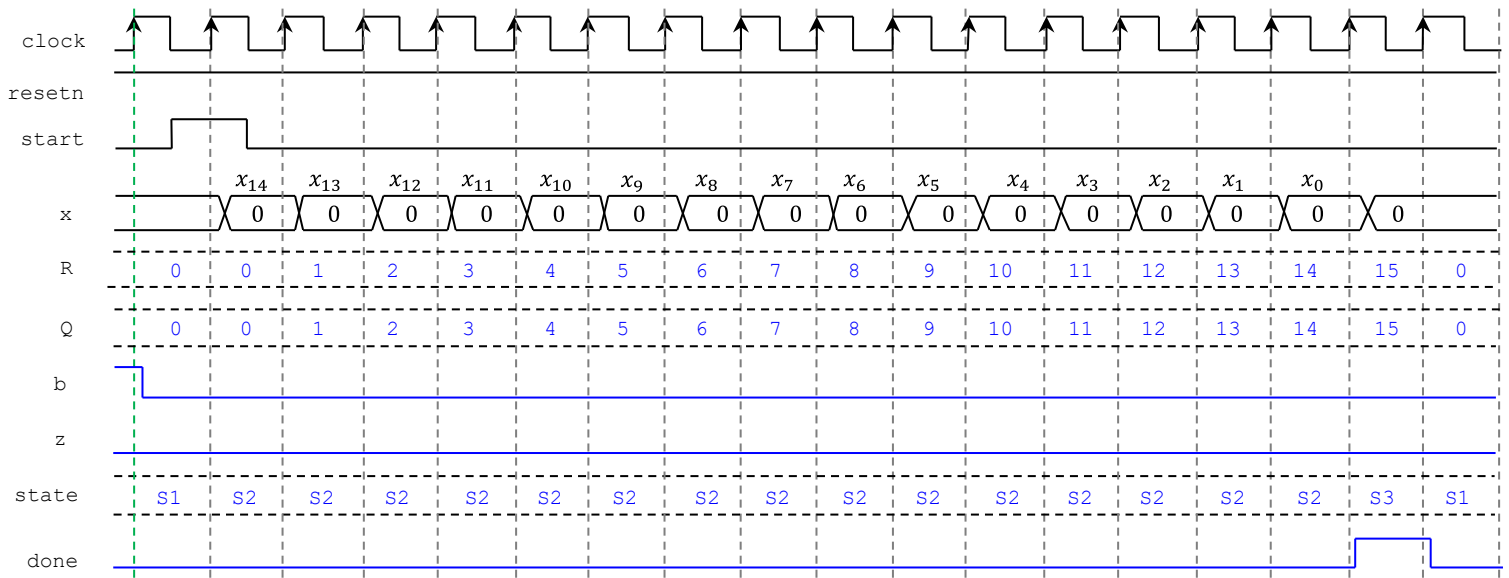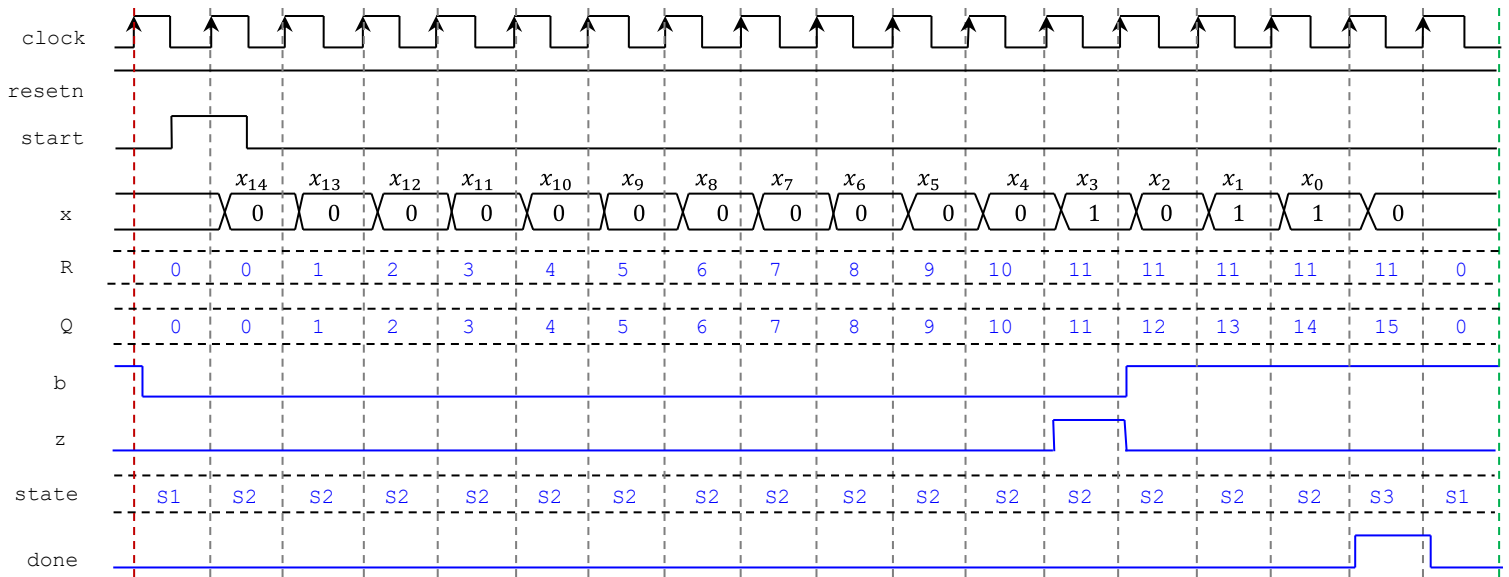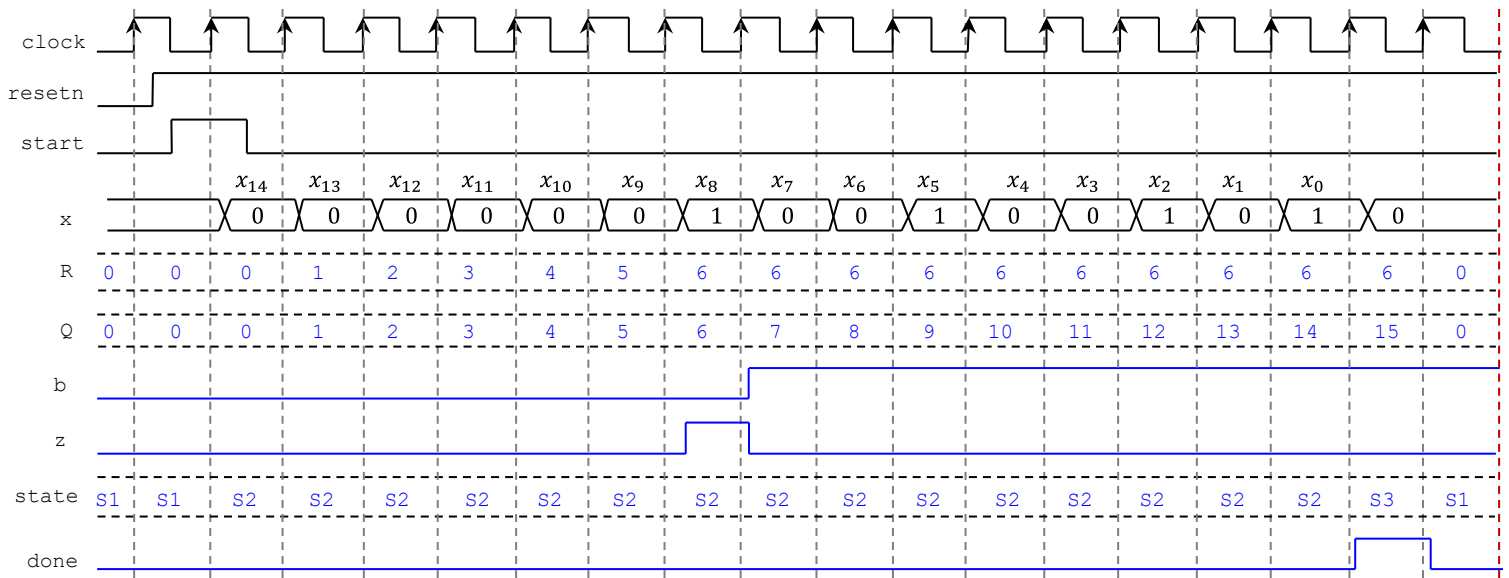

PROBLEM 3 (25 PTS)

- **Fibonacci numbers Computation:** We want to design a circuit that reads an unsigned number ($n > 1$) and generates F_n :

$$F_n = F_{n-1} + F_{n-2}, F_0 = 0, F_1 = 1$$

- ✓ To compute F_n in an iterative fashion, we can use:



```

n: unsigned integer
F0=0, F1=1
if n > 1
  for i = 2 to n
    Fi = Fi-1 + Fi-2
  end
end
return Fn

```




- Operation: The circuit reads n when the s signal (usually a one-clock cycle) is asserted. When the result (F_n) is ready, the signal $done$ is asserted.
 - ✓ Input: s (start signal), n (input data)
 - ✓ Outputs: F_n (result), $done$.
 - ✓ Clock frequency: 100 MHz.
 - ✓ We restrict the bitwidth of F_n to 16 bits. As a result, the largest n would be 24 ($F_{24} = 46368$).
- Sketch the circuit: FSM (in ASM form) + Datapath components. Specify all the I/Os of the FSM, as well as the signals connecting the FSM and the Datapath components (as in Problem 2).
 - ✓ Suggestion: Use two registers (for F_{i-1} and F_{i-2}), initialized with $F_1 = 1$ and $F_0 = 0$ (iterations start at $i = 2$). At every iteration ($i = 2, \dots, n$), F_i is computed, and then the registers (parametric register with enable: my_rege) are updated:
 - Register F_{i-1} : It captures the computed F_i .
 - Register F_{i-2} : It captures F_{i-1} .
 - ✓ Feel free to use any other standard component (e.g.: register, counter, comparator, adder, busmux).
 - ✓ The iteration index i can be implemented with a standard counter ($my_genpulse_sclr$). Here, you can only initialize the count to 0. To ensure that iterations start at $i = 2$, you can include more states (to increase the count).
 - ✓ To simplify the design, you can assume that $n > 1$.

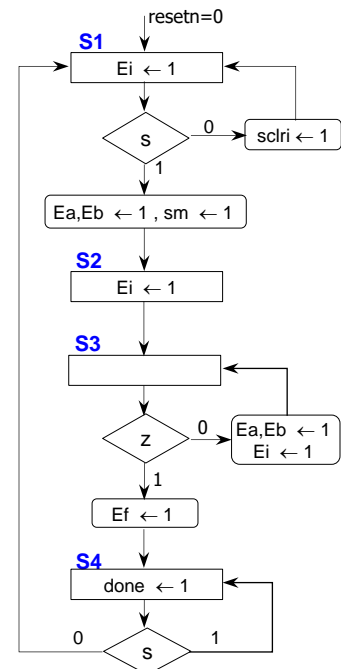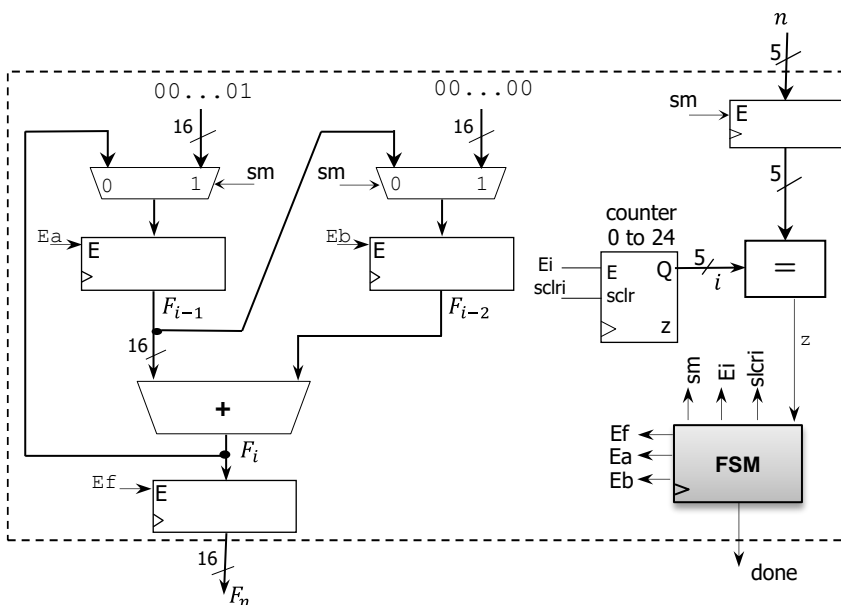

PROBLEM 4 (15 PTS)

- Calculate the result of the following operations, where the operands are signed integers. For the division, calculate both the quotient and the residue. **No procedure = zero points.**

01011 × 10010	10010 × 11011	10101 ÷ 1011	1010011 ÷ 0110	011101 ÷ 1101
------------------	------------------	-----------------	-------------------	------------------

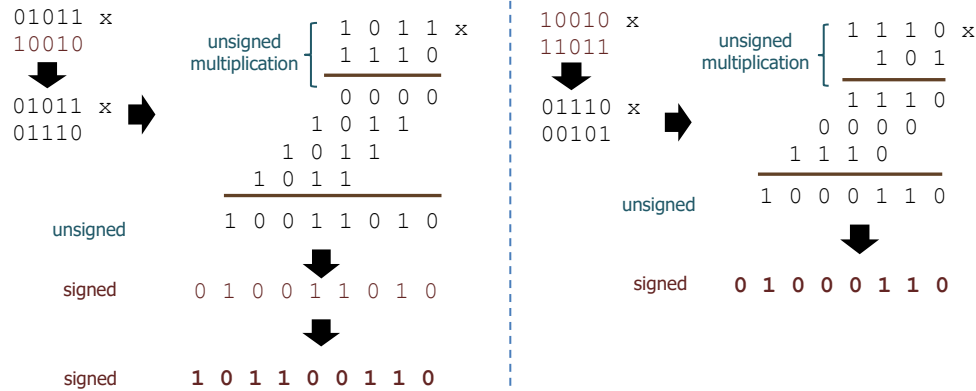

$$\checkmark \frac{10101}{1011} = \frac{-11}{-5}$$

$$\begin{array}{r} 0010 \\ 101 \overline{) 1011} \\ \underline{101} \\ 01 \end{array}$$

$$\text{To unsigned: } \frac{01011}{0101}$$

$$\text{Unsigned Integer Division: } Q' = 10, R' = 1$$

$$\rightarrow Q = Q' = 010, \rightarrow R = -R' = 2C(01) = 1$$

$$\text{Verification: } -11 = (-5 \times 2) - 1$$

$$\checkmark \frac{1010011}{0110} = \frac{-45}{6}$$

$$\begin{array}{r} 000111 \\ 110 \overline{) 101101} \\ \underline{1010} \\ 1010 \\ \underline{110} \\ 1001 \\ \underline{110} \\ 011 \end{array}$$

$$\text{To unsigned: } \frac{0101101}{0110}$$

$$\text{Unsigned Integer Division: } Q' = 111, R' = 11$$

$$\rightarrow Q = -Q' = 2C(0111) = 1001, \rightarrow R = -R' = 2C(011) = 101$$

$$\text{Verification: } -45 = (-7 \times 6) - 3$$

$$\checkmark \frac{011101}{1101} = \frac{29}{-3}$$

$$\begin{array}{r} 01001 \\ 11 \overline{) 11101} \\ \underline{11} \\ 0101 \\ \underline{11} \\ 10 \end{array}$$

$$\text{To unsigned: } \frac{011101}{0011}$$

$$\text{Unsigned Integer Division: } Q' = 1001, R' = 10$$

$$\rightarrow Q = -Q' = 2C(01001) = 10111, \rightarrow R = 010$$

$$\text{Verification: } 29 = (-9 \times -3) + 2$$