



Solutions - Homework 3


(Due date: November 7th @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

 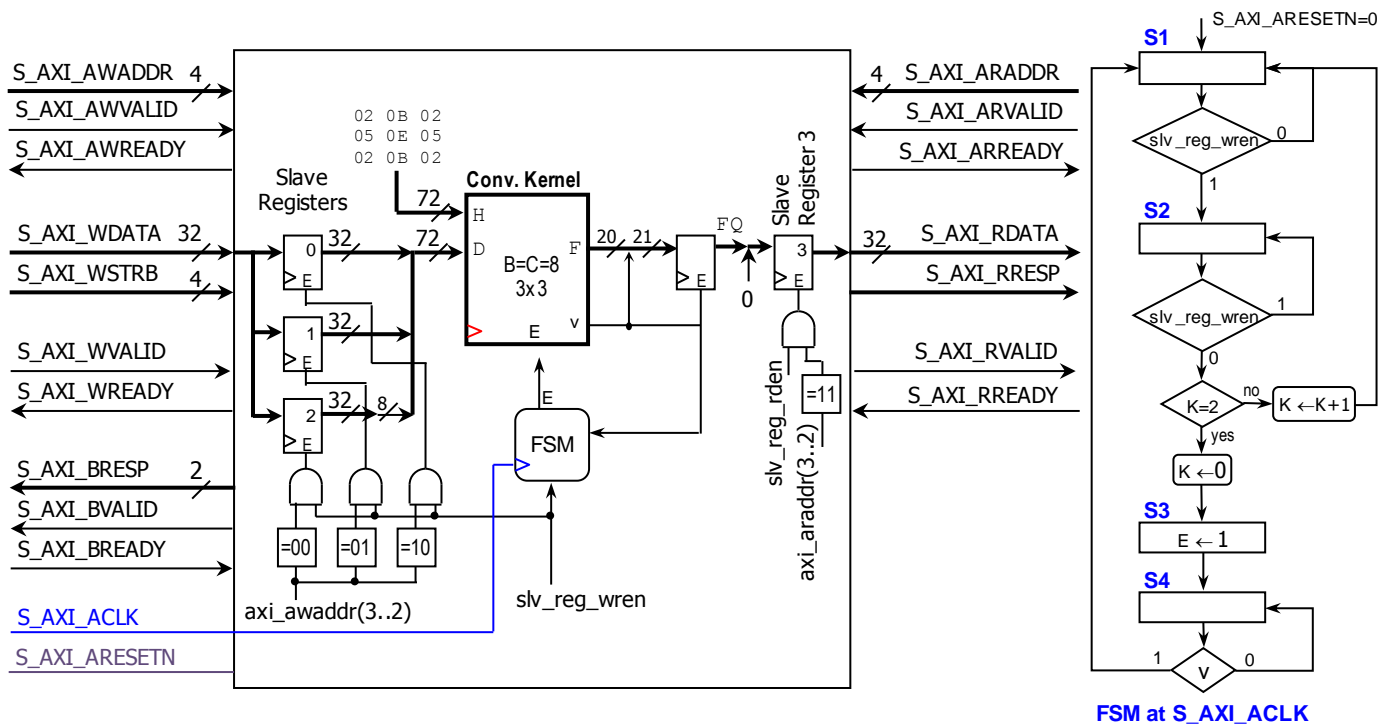PROBLEM 1 (15 PTS)


- AXI4-Lite interface: The following is the interface for the pipelined 2D convolution kernel. The input/output timing diagram of the pipelined 2D convolutional kernel is shown below. For the input data (0xA1B2C3D4F0E1D2C3B3), the result is 0x2B82 and it appears 6 clock cycles after E is asserted.
- Given the AXI signals, complete the timing diagram of the signals corresponding to the 2D Convolution Kernel block (E , v , y , F , FQ signals) on the next page.



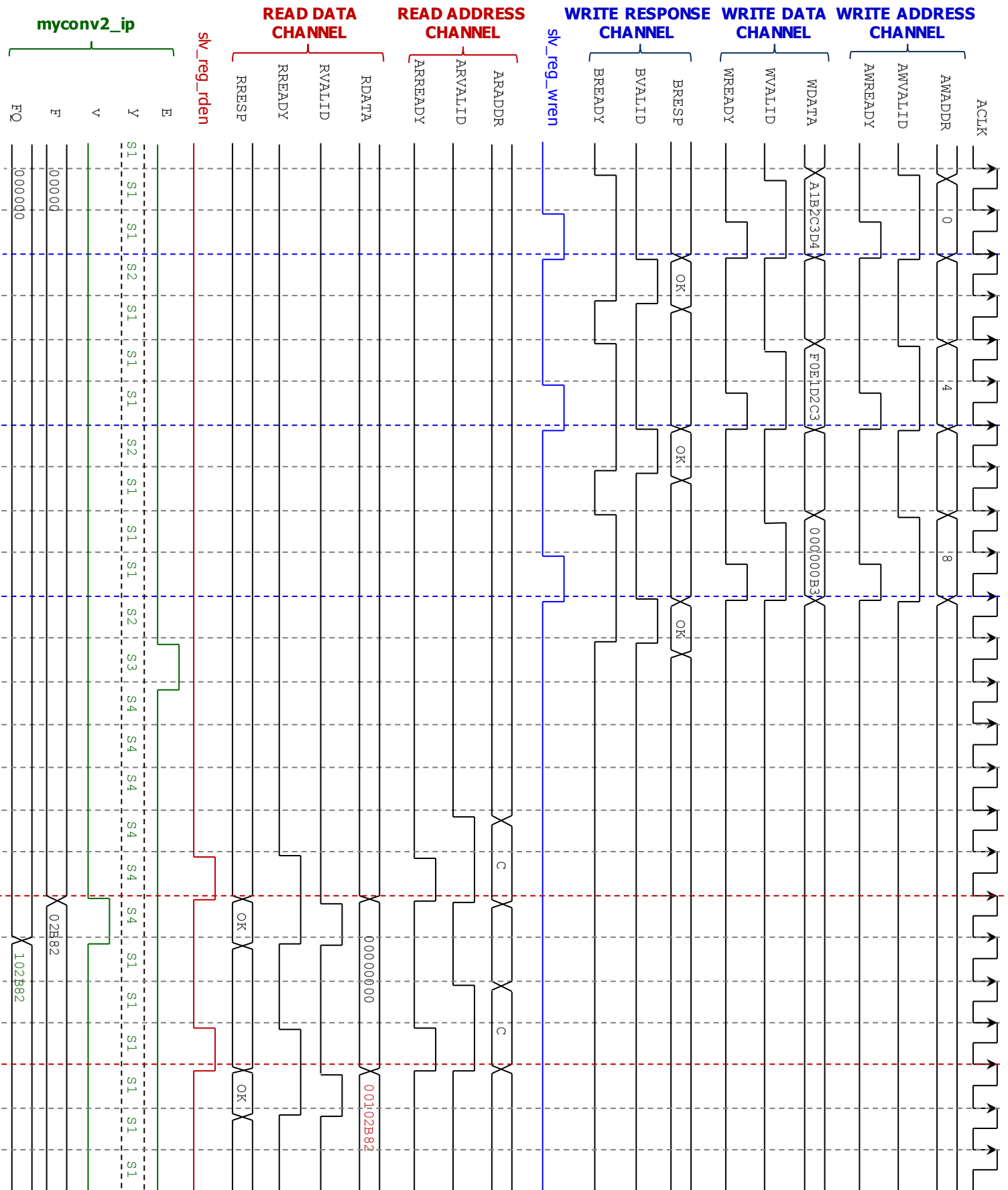


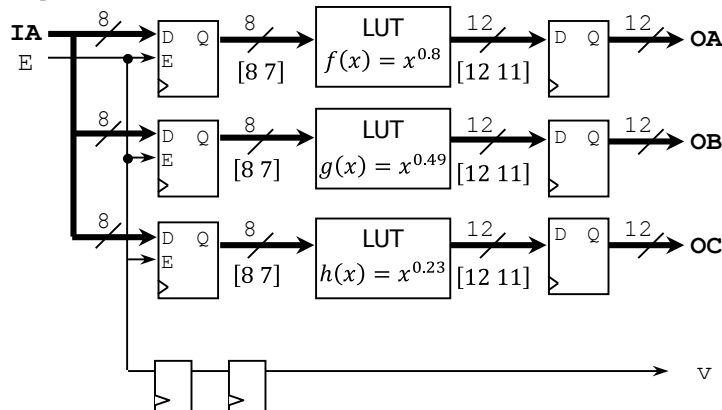PROBLEM 2 (85 PTS)

- Implement the following circuit using the LUT approach.
 - Input format: [8 7] (unsigned)
 - Output format: [12 11] (unsigned)



 - Pre-compute the LUT values and store them as binary numbers in a text file. You can use the MATLAB script `LUTvalGen8to12.m` to do this. Your VHDL code should read the text file.
- The text file should be divided as follows: the first 256 entries for the first function, the second 256 entries for the second function, and the third 256 entries for the third function:



SIMULATION

- Create a testbench to test your circuit. The testbench must generate all the possible input cases (from 00000000 to 11111111) and write the output results in a text file. For simplicity's sake, it is suggested that you write three 12-bit words per line (256 lines), where each 12-bit word represents the output of a different function.
- To verify the correct operation of your circuit, compare the text file you are generating on the Simulation with the input text file you created for Synthesis.
- Upload the following files to Moodle (an assignment will be created):
 - VHDL code
 - VHDL testbench
 - Input and output text files.

See attached .zip file: `Solutions_hw3_p2.zip`.