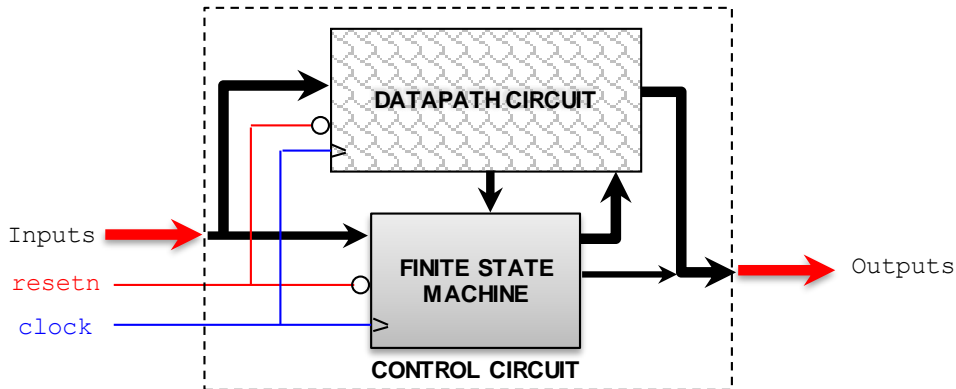





# Unit 2 - Digital System Design

## COMPONENTS: FSM (CONTROL) + DATAPATH CIRCUIT


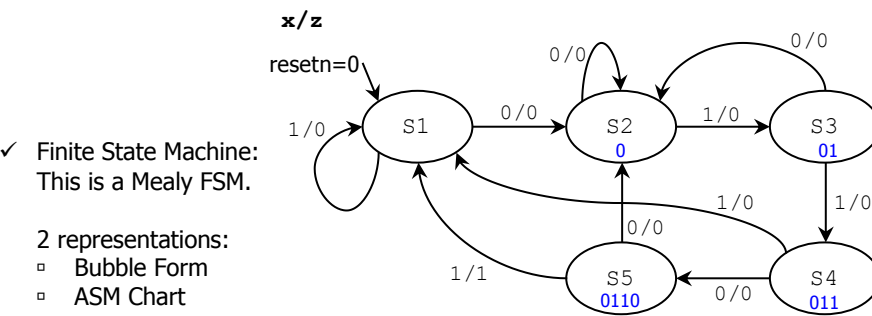  
### FINITE STATE MACHINES (FSMs)

- For a review of this topic in detail, please refer to [ECE2700 – Synchronous Sequential Circuits](#).
- State Machine representation: we will use the Algorithmic State Machine (ASM) Charts.
- Example:** Sequence detector. It generates  $z=1$  when it detects the sequence 01101. Once the sequence is detected, it looks for a new sequence.




- ✓ Finite State Machine: This is a Mealy FSM.


2 representations:

- Bubble Form
- ASM Chart

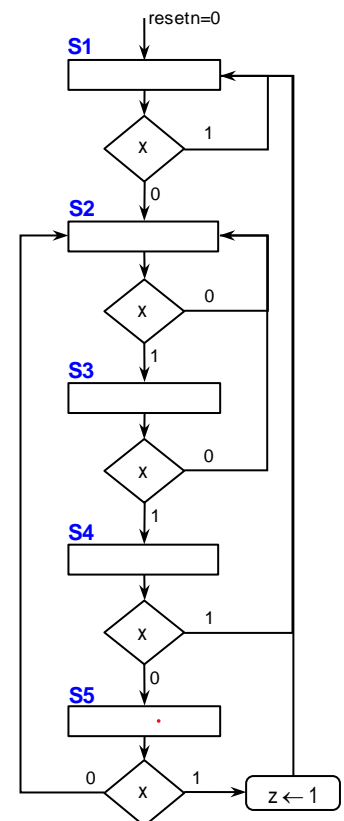- ✓ [Video](#): convert bubble form into ASM (also: VHDL coding of ASM).



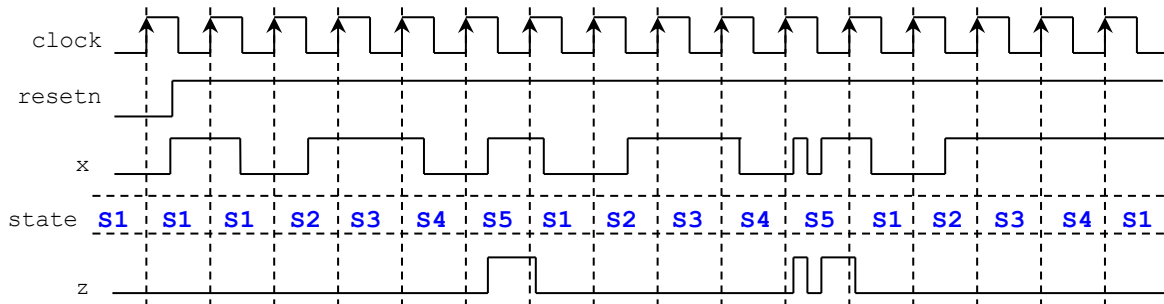✓ Timing diagram: Sequence detector – 01101.



Note: The output z can change as soon as the input x changes.


▪ **Example:** This is a more complex FSM (Mealy-type). Given the VHDL code, we complete the FSM diagram, the timing diagram and provide the state table, excitation table, excitation table, and circuit implementation.

```
library ieee;
use ieee.std_logic_1164.all;


entity myfsm is
    port ( clk, resetn: in std_logic;
          r, p: in std_logic;
          x, w, z: out std_logic);
end myfsm;
```

```
architecture behavioral of myfsm is
    type state is (S1, S2, S3);
    signal y: state;
begin
    Transitions: process (resetn, clk, r, p)
    begin
        if resetn = '0' then y <= S1;
        elsif (clk'event and clk = '1') then
            case y is
                when S1 =>
                    if r = '1' then y <= S2;
                    else
                        if p = '1' then y <= S3; else y <= S1; end if;
                    end if;
                when S2 =>
                    if p = '1' then y <= S1; else y <= S3; end if;
                when S3 =>
                    if p = '1' then y <= S3; else y <= S2; end if;
            end case;
        end if;
    end process;

    Outputs: process (y, r, p)
    begin
        x <= '0'; w <= '0'; z <= '0';
        case y is
            when S1 => if r = '0' then
                if p = '0' then z <= '1'; end if;
            end if;
            when S2 => if r = '0' then x <= '1'; end if;
                if p = '0' then w <= '1'; end if;
            when S3 => if p = '0' then x <= '1'; end if;
        end case;
    end process;
end behavioral;
```

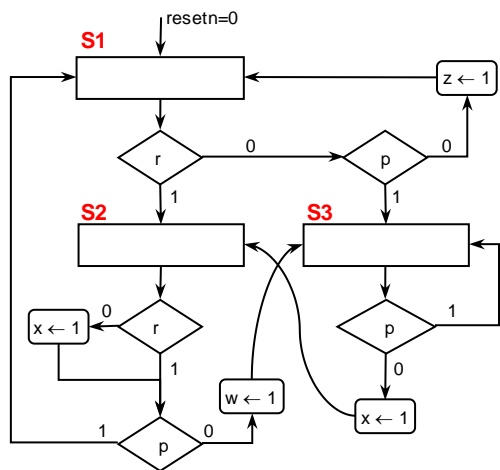

 ✓ Timing Diagram: Note that the outputs x, w, z can change as soon as the input x changes.



✓ State Table and Excitation Table:

*State Assignment:*

S1: Q=00, S2: Q=01, S3: Q=10

PRESENT STATE		NEXT STATE		
r	p	x	w	z
0	0	S1	S1	0 0 1
0	0	S2	S3	1 1 0
0	0	S3	S2	1 0 0
0	1	S1	S3	0 0 0
0	1	S2	S1	1 0 0
0	1	S3	S3	0 0 0
1	0	S1	S2	0 0 0
1	0	S2	S3	0 1 0
1	0	S3	S2	1 0 0
1	1	S1	S2	0 0 0
1	1	S2	S1	0 0 0
1	1	S3	S3	0 0 0



r	p	Q <sub>1</sub> Q <sub>0</sub> (t)	Q <sub>1</sub> Q <sub>0</sub> (t+1)	x	w	z
0	0	0 0	0 0	0	0	1
0	0	0 1	1 0	1	1	0
0	0	1 0	0 1	1	0	0
0	0	1 1	X X	X	X	X
0	1	0 0	1 0	0	0	0
0	1	0 1	0 0	1	0	0
0	1	1 0	1 0	0	0	0
0	1	1 1	X X	X	X	X
1	0	0 0	0 1	0	0	0
1	0	0 1	1 0	0	1	0
1	0	1 0	0 1	1	0	0
1	0	1 1	X X	X	X	X
1	1	0 0	0 1	0	0	0
1	1	0 1	0 0	0	0	0
1	1	1 0	1 0	0	0	0
1	1	1 1	X X	X	X	X

✓ Excitation equations and Boolean output equations:

$$Q_1(t+1) \leftarrow \bar{r}p\bar{Q}_0(t) + pQ_1(t) + \bar{p}Q_0(t)$$


$$Q_0(t+1) \leftarrow rQ_1(t)\bar{Q}_0(t) + \bar{p}Q_1(t)$$

$$x = \bar{p}Q_1(t) + \bar{r}Q_0(t) \quad w = \bar{p}Q_0(t) \quad z = \bar{r}\bar{p}Q_1(t)\bar{Q}_0(t)$$

✓ Circuit implementation:

Note that we highlight the components of the FSM model.

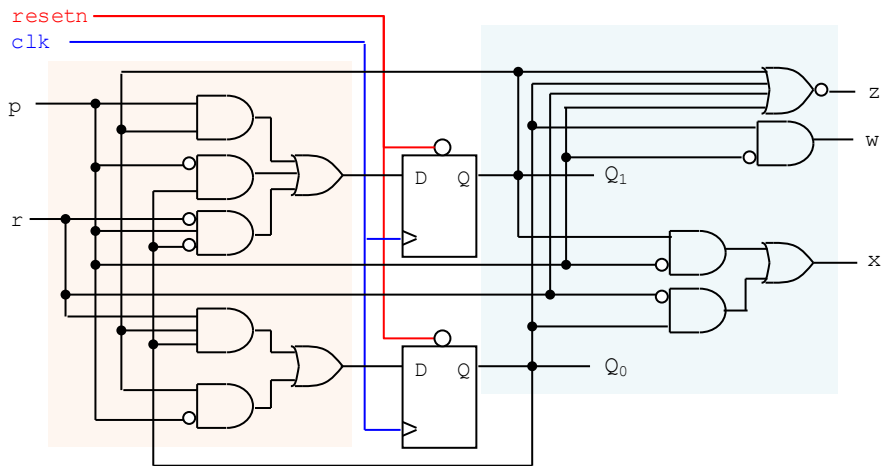Also, refer to the VHDL for FPGAs tutorial – Unit 6 on how the VHDL code maps into the circuit components.



DATAPATH CIRCUIT

- The components required here vary widely and depend on your specific application. Typical components found include arithmetic circuits, special encoders/decoders, counters, registers, shift registers, etc.

DIGITAL SYSTEM DESIGN

- Usually, you start with the specifications of your circuit. Then, you define the I/Os. After this, it is up to you to decide on what components to use, how to interconnect them, and how to control it via a FSM.

VHDL CODING

Refer to [VHDL for FPGAs Tutorial](#) for a complete tutorial on VHDL design that includes slides and examples (VHDL code). For the description of digital systems in VHDL, the following concepts are of utmost importance:

- **FSM Description:** VHDL coding of ASMs:
  - ✓ [VHDL on FPGA Tutorial – Unit 6 slides](#): How to write VHDL code for FSMs.
  - ✓ [Video](#): VHDL description for ASM chart (sequence detector 01101), synthesis and simulation in Vivado.
- **Interconnection of components:** hierarchical design (port map): [VHDL for FPGA Tutorial – Unit 4 slides](#).
- **Testbench generation:** Refer to [VHDL for FPGAs Tutorial – Unit 5 slides](#) for detailed explanation. Also, look at the examples in Unit 6 and Unit 7 of this VHDL for FPGAs Tutorial.
- **Use of generic components:** These components are ubiquitous in digital system design: counters, registers, shift registers. To optimize design time, we recommend using parameterized components (VHDL for FPGAs Tutorial – Unit 5 examples):
  - ✓ *n*-bit register with enable and synchronous clear: my\_rege
  - ✓ Counter modulo-N with enable and synchronous clear: my\_genpulse\_sclr
  - ✓ *n*-bit parallel access (right/left) register with enable and synchronous clear: my\_pashiftreg\_sclr

Usually, we want to use these components with different variations: bit-width, direction (shift registers), modulus (counters). To properly use parametric components, refer to [VHDL for FPGAs Tutorial – Unit 7 slides](#) (generic map).

- **Digital System Design:** Refer to the following material:
  - ✓ [VHDL for FPGAs Tutorial – Unit 7 slides](#): Detailed step-by-step example (stopwatch design).
  - ✓ [VHDL for FPGAs Tutorial – Unit 7](#): VHDL code for a variety of digital systems (e.g.: bit-counting, sequential multiplier).
  - ✓ [Video](#): Bit-counting circuit ( $n = 8$ ): step-by-step VHDL coding, synthesis and simulation in Vivado.
  - ✓ [Video](#): 4x4 Sequential Multiplier: step-by-step VHDL coding, synthesis and simulation in Vivado.
  - ✓ [Video](#): 2x2 Sequential Multiplier: VHDL coding, synthesis, simulation, implementation, and testing on ZYBO Board.

## DESIGN EXAMPLES

### BIT-COUNTING CIRCUIT (COUNTING 1'S) ([Parametric VHDL Code](#)) ([Video](#): VHDL coding in Vivado, $n=8$ )

- This circuit counts the number of bits in register A whose value is '1'. Example ( $n=8$ ):  $A = 00110111 \rightarrow C = 0101$ .
- The sequential algorithm (pseudo-code) is shown. Here, we can follow this procedure to design a digital system:
  - ✓ Sketch the block diagram: We need start and done signals to indicate when the process starts and finishes. We also include input (Data for the Register A) and output data (Count).
  - ✓ Sketch the high-level control mechanism (state machine) for the Bit-counting circuit. Here, you can include combinational blocks as well as common synchronous blocks (registers, shift registers, counters).
  - ✓ With the block diagram and high-level state machine, we can draft the components and their signals in the datapath. From the high-level state machine, we can design the actual FSM that includes actual signals controlling the components.


#### Sequential Algorithm

```



C ← 0
while A ≠ 0
  if a0 = 1 then
    C ← C + 1
  end if
  right shift A
end while
    
```



#### High-level FSM

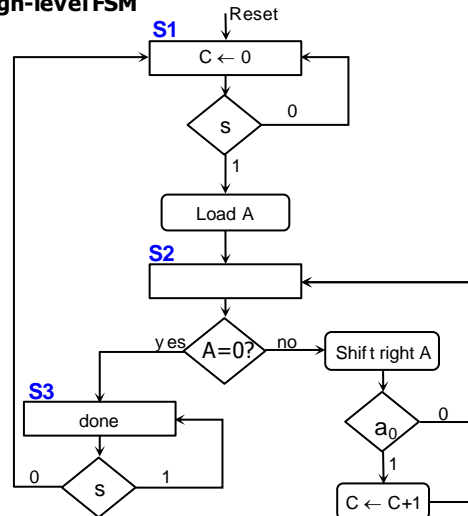
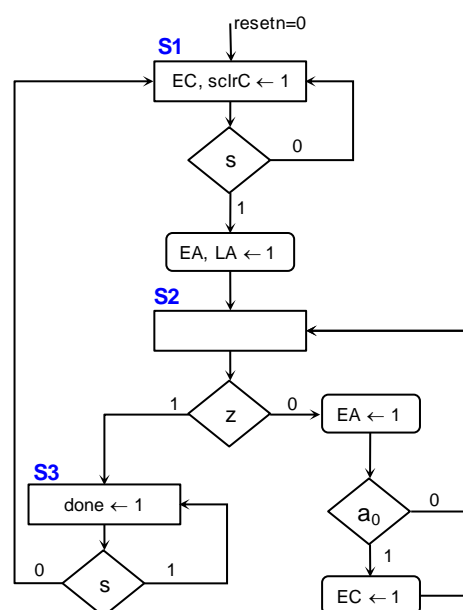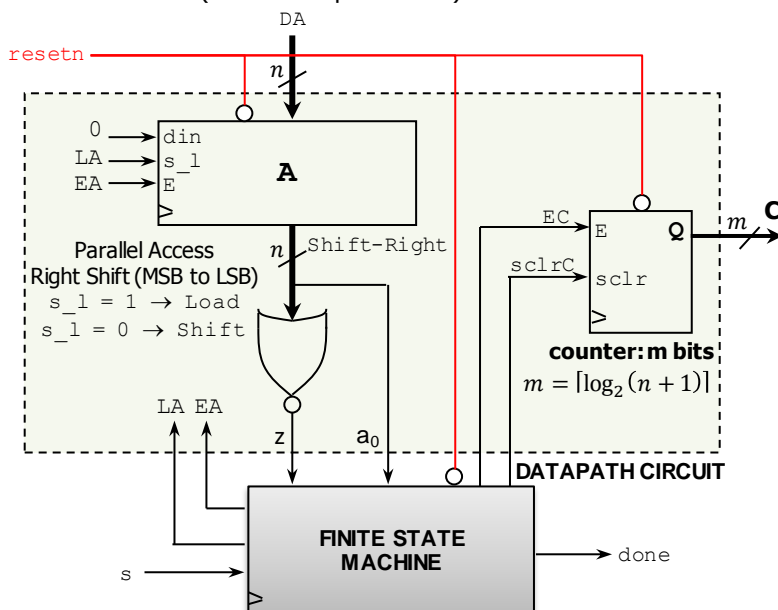
### DIGITAL SYSTEM (FSM + Datapath circuit)



- Components: Behavior on the clock tick.

*m*-bit counter (modulo-*n*+1): If *E*=0, the count stays.

```

if E = 1 then
  if sclr = 1 then
    Q ← 0
  else
    Q ← Q+1
  end if;
end if;
    
```

*n*-bit Parallel access shift register: If *E*=0, the output is kept.

```

if E = 1 then
  if s_l = '1' then
    Q ← D
  else
    Q ← shift in 'din' (to the right)
  end if;
end if;
    
```

- Timing diagram (*n*=8, *m*=4):

✓ Examples shown in figure:


- If *A* = 00110110, then *C* = 0100.
- If *A* = 00001110, then *C* = 0011.

✓ [Video](#): Bit-counting circuit (*n*=8): Completing timing diagrams (For DA=10110110 and 00000011)

✓ To complete timing diagrams for digital systems, the following procedure can be followed:

For every clock cycle:

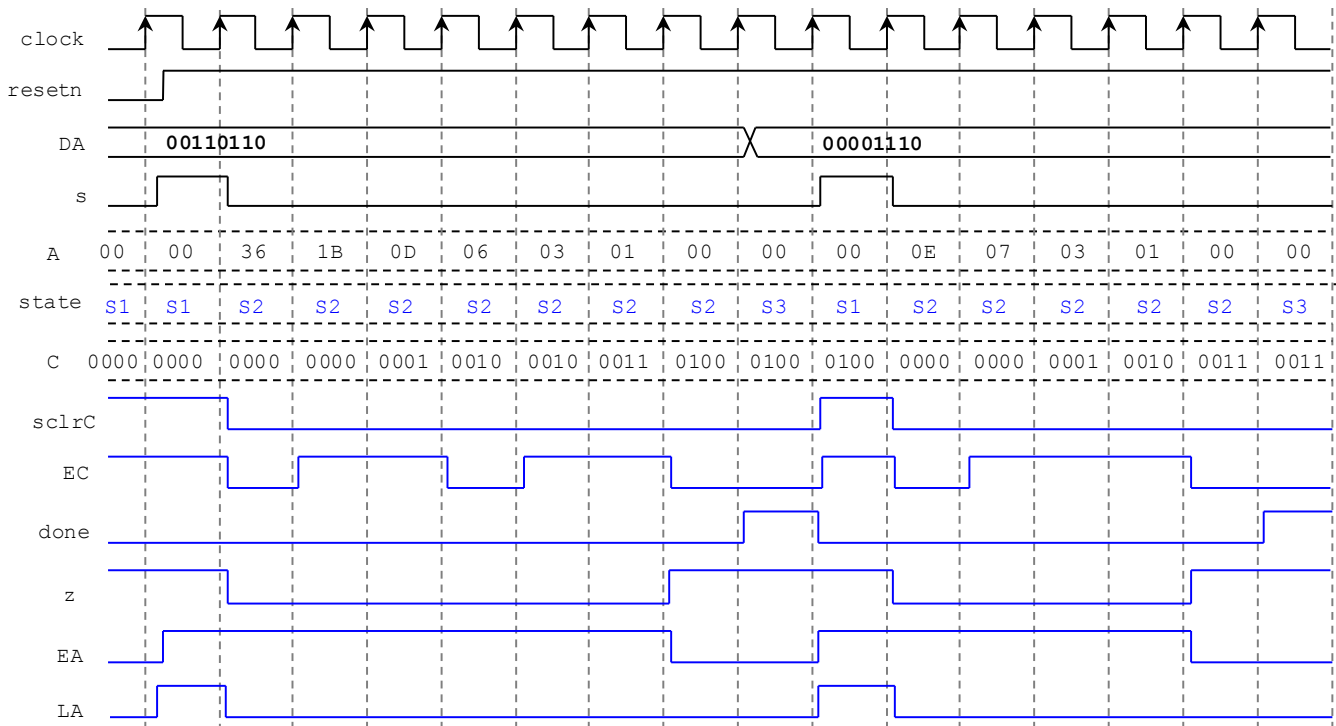
- Complete the registered signals (i.e.: *A*, state, *C*). These signals are kept constant during a clock cycle.
- Complete the signals that are not outputs of the FSM, but that are inputs of the FSM (*z*).
- Complete the FSM outputs. Note they might change at any moment during the clock cycle.
- For the next clock cycle, go to 'a.'



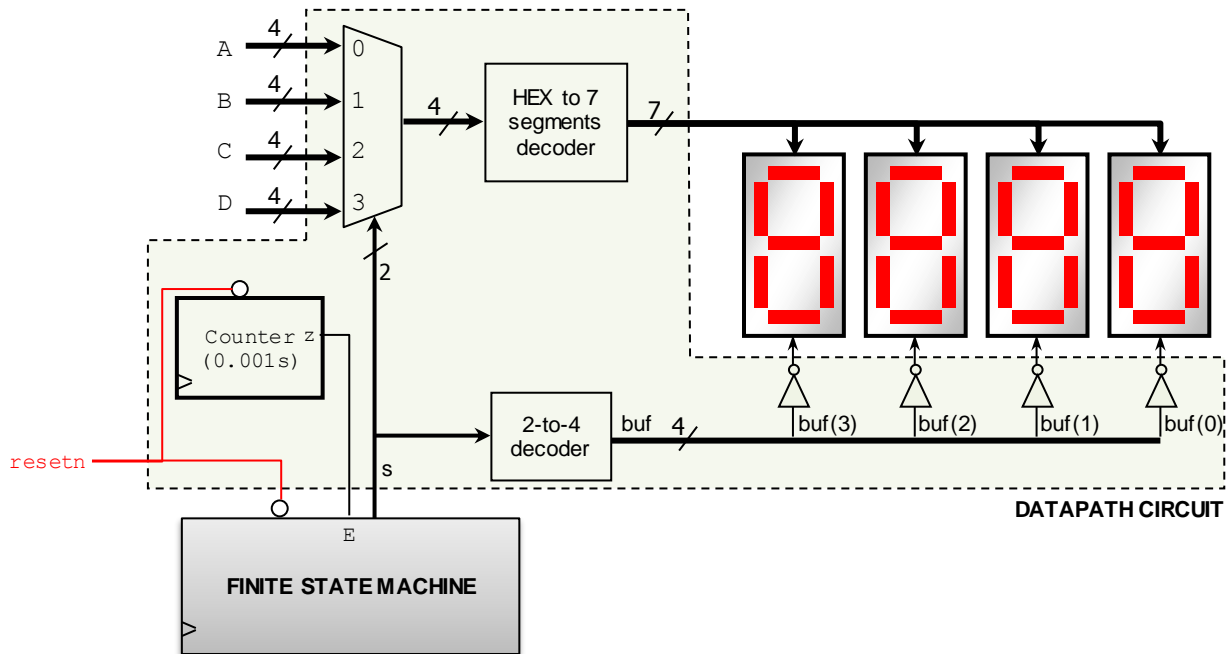EXAMPLE: 7-SEGMENT SERIALIZER (VHDL code)

**DIGITAL SYSTEM** (FSM + Datapath circuit)

- Most FPGA Development boards have a number of 7-segment displays (e.g., 4, 8). However, only one can be used at a time.
- If we want to display four digits (inputs A, B, C, D), we can design a serializer that will only show one digit at a time on the 7-segment displays.
- Since only one 7-segment display can be used at a time, we need to serialize the four BCD outputs. In order for each digit to appear bright and continuously illuminated, each digit is illuminated for 1 ms every 4 ms (i.e. a digit is un-illuminated for 3 ms and illuminated for 1 ms). This is taken care of by feeding the output *z* of the 'counter to 0.001s' to the enable input of the FSM. This way, state transitions only occur each 0.001 s.
- In the figure, the enable signals for the four 7-segment displays are active low (this is usually the case).



- Component: Behavior on the clock tick.


0.001 s counter (modulo-10<sup>5</sup>): Free running counter

```

if Q = 105 - 1 then
    Q ← 0
else
    Q ← Q+1
end if;
end if;

* z = 1 if Q = 105-1
    
```

 - Algorithmic State Machine (ASM) chart:** This is a Moore-type FSM.



EXAMPLE: SEQUENTIAL MULTIPLIER ([Parametric VHDL Code](#)) ([Video](#): VHDL coding in Vivado, n=4)

UNSIGNED MULTIPLICATION: SEQUENTIAL ALGORITHM

```


Example:
    1 1 1 1 x
    1 1 0 1
    -----
    1 1 1 1 → P ← 0 + 1111
    0 0 0 0 → P ← 1111
    1 1 1 1 → P ← 1111 + 111100 = 1001011
    1 1 1 1 → P ← 1001011 + 1111000 = 11000011
    -----
    1 1 0 0 0 0 1 1
    
```

$P \leftarrow 0$ , Load A,B  
 while  $B \neq 0$   
   if  $b_0 = 1$  then  
      $P \leftarrow P + A$   
   end if  
   left shift A  
   right shift B  
 end while


$P \leftarrow 0, A \leftarrow 1111, B \leftarrow 1101$   
 $b_0=1 \Rightarrow P \leftarrow P + A = 1111. \quad A \leftarrow 11110, B \leftarrow 110$   
 $b_0=0 \Rightarrow P \leftarrow P = 1111. \quad A \leftarrow 111100, B \leftarrow 11$   
 $b_0=1 \Rightarrow P \leftarrow P + A = 1111 + 111100 = 1001011. \quad A \leftarrow 1111000, B \leftarrow 1$   
 $b_0=1 \Rightarrow P \leftarrow P + A = 1001011 + 1111000 = \mathbf{11000011}. \quad A \leftarrow 11110000, B \leftarrow 0$

DIGITAL SYSTEM (FSM + Datapath circuit)

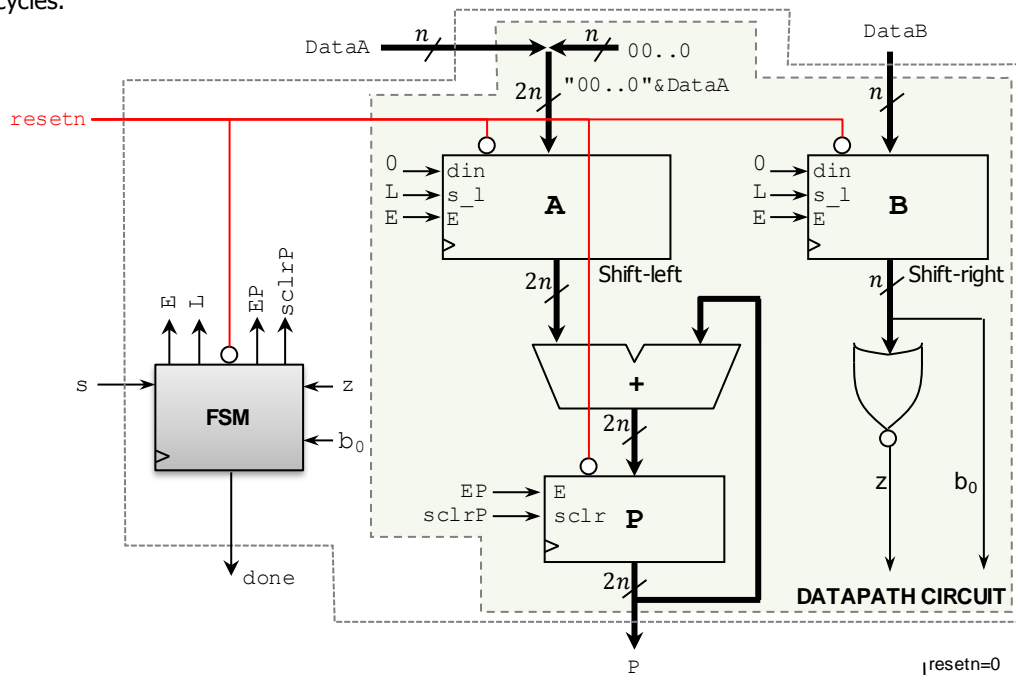- Iterative Multiplier Architecture. Register P: *sclr*: synchronous clear. Here, if  $E = sclr = 1$ , the register contents are initialized to 0. Parallel Access Shift Registers A and B: If  $E = 1: s_l = 1 \rightarrow$  Load,  $s_l = 0 \rightarrow$  Shift. The result is computed in at most  $n + 1$  cycles.



Algorithmic State Machine (ASM) chart:

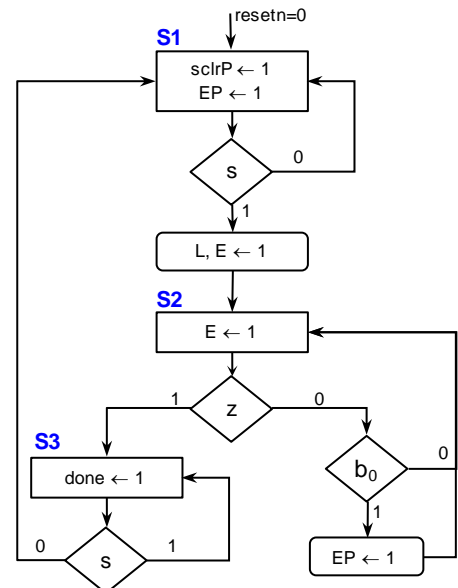

- Components: Behavior on the clock tick:

2n-bit register: If E=0, the output is kept.

```

if E = 1 then
  if sclr = 1 then
    Q ← 0
  else
    Q ← D
  end if;
end if;
    
```

Parallel access shift register: If E=0, the output is kept.

A (2n bits, left shift), B (n bits, right shift)

```

if E = 1 then
  if s_l = '1' then
    Q ← D
  else
    Q ← shift in 'din' (to the left (A) or right (B))
  end if;
end if;
    
```

- Timing Diagram: n = 4.

