


Solutions - Final Exam

(April 21st @ 7:00 pm)

Presentation and clarity are very important! Show your procedure!

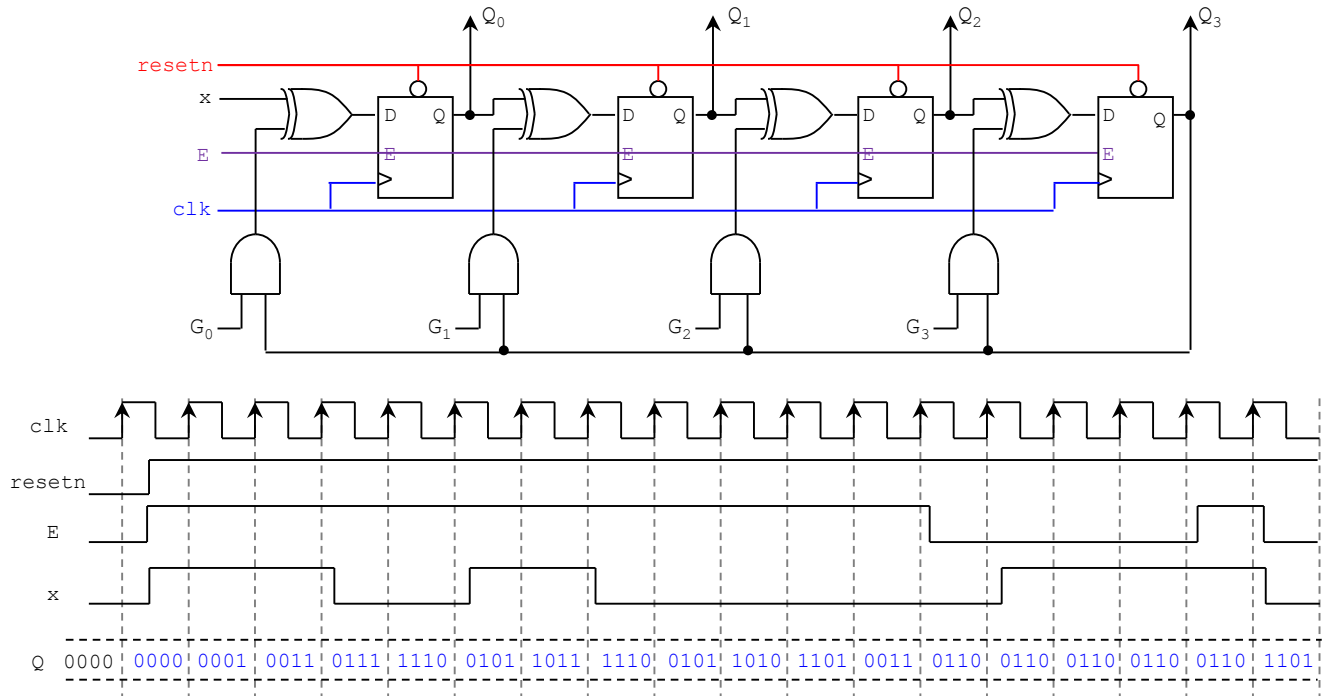PROBLEM 1 (12 PTS)

- Complete the timing diagram of the following circuit. $G = G_3G_2G_1G_0 = 1001$, $Q = Q_3Q_2Q_1Q_0$



PROBLEM 2 (20 PTS)

- Provide the State Diagram (any representation), the Excitation Table, and the Excitation equations of the following Finite State Machine: (12 pts)


$$Q_1(t+1) = (Q_1 + Q_0)w$$

$$Q_0(t+1) = (\overline{Q_1}Q_0) \oplus w$$

$$z = Q_1 + Q_0$$

- State Assignment:

 
- ✓ S1: $Q = 00$
- ✓ S2: $Q = 01$
- ✓ S3: $Q = 10$
- ✓ S4: $Q = 11$




PRESENT STATE		NEXT STATE	
w	$Q_1Q_0(t)$	$Q_1Q_0(t+1)$	z
0	0 0	0 0	0
0	0 1	0 1	1
0	1 0	0 0	1
0	1 1	0 0	1
1	0 0	0 1	0
1	0 1	1 0	1
1	1 0	1 1	1
1	1 1	1 1	1



w	PRESENT STATE	NEXT STATE	z
0	S1	S1	0
0	S2	S2	1
0	S3	S1	1
0	S4	S1	1
1	S1	S2	0
1	S2	S3	1
1	S3	S4	1
1	S4	S4	1

 

 - Complete the timing diagram of the circuit shown below: (8 pts)




PROBLEM 5 (18 PTS)

- Design a counter using a Finite State Machine (FSM):


Counter features:

 - ✓ Count: **00**, 11, 01, 10, **00**, 11, 01, ...
- ✓ *resetn*: Asynchronous active-low input signal. It initializes the count to "00"
- ✓ Input *E*: Synchronous input that increases the count when it is set to '1'.
- ✓ output *z*: It becomes '1' when the count is 10.



- Provide the State Diagram (any representation), State Table, and the Excitation Table. Is this a Mealy or a Moore machine? Why? (10 pts)
- Provide the excitation equations (simplify your circuit using K-maps or the Quine-McCluskey algorithm) (5 pts)
- Sketch the circuit. (3 pts)

 - State Diagram, State Table, and Excitation Table:*



	PRESENT STATE	NEXT STATE	z
E	STATE	STATE	
0	S1	S1	0
0	S2	S2	0
0	S3	S3	0
0	S4	S4	1
1	S1	S2	0
1	S2	S3	0
1	S3	S4	0
1	S4	S1	1

PRESENT STATE			NEXTSTATE	
E	$Q_1Q_0(t)$		$Q_1Q_0(t+1)$	z
0	0	0	0 0	0
0	1	1	1 1	0
0	0	1	0 1	0
0	1	0	1 0	1
1	0	0	1 1	0
1	1	1	0 1	0
1	0	1	1 0	0
1	1	0	0 0	1

- State Assignment:*

S1: Q = 00 S3: Q = 01
S2: Q = 11 S4: Q = 10


The output 'z' only depends on the present state \Rightarrow Moore FSM.

- Excitation equations, minimization and circuit implementation:*

$$Q_1(t+1) = \bar{E}Q_1 + E\bar{Q}_1 = E \oplus Q_1$$


$$Q_0(t+1) = E\bar{Q}_1\bar{Q}_0 + \bar{E}Q_0 + Q_1Q_0$$

$$z = \bar{Q}_0Q_1$$

 


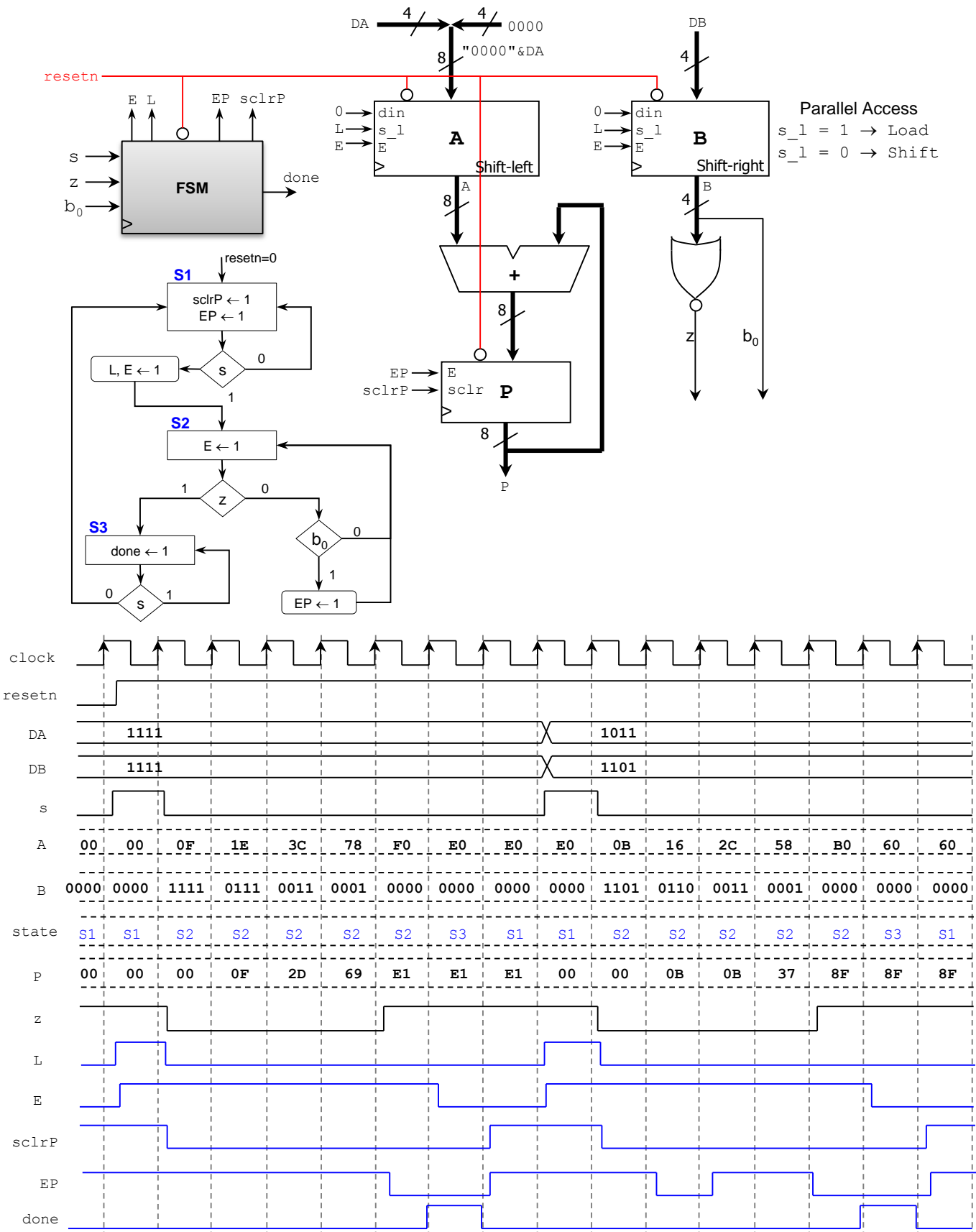
PROBLEM 3 (20 PTS)

- Iterative unsigned multiplier: Complete the following timing diagram of the following digital circuit that includes an FSM (in ASM form) and a datapath circuit.
Register (for P): *sclr*: synchronous clear. Here, if *sclr* = *E* = 1, the register contents are initialized to 0.
Parallel access shift register (for A and B): If *E* = 1: *s_l* = 1 → Load, *s_l* = 0 → Shift



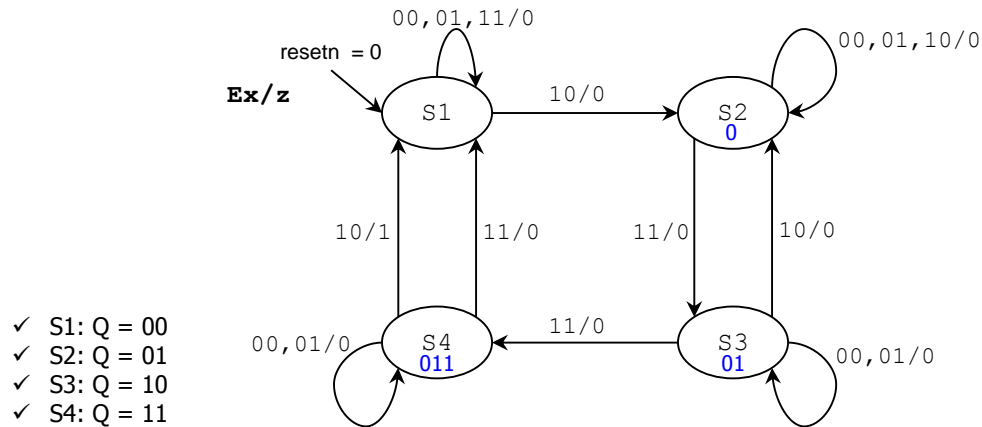 PROBLEM 4 (15 PTS)

- Sequence detector: Draw the State Diagram (any representation) and the Excitation Table of a circuit with an input x and output z . The machine has to generate $z = 1$ when it detects the sequence 0110. Once the sequence is detected, the circuits looks for a new sequence.
- The signal E is an input enable: It validates the input x , i.e., if $E = 1$, x is valid, otherwise x is not valid.



PRESENT STATE			NEXT STATE	z
E	x	STATE	STATE	
0	0	S1	S1	0
0	0	S2	S2	0
0	0	S3	S3	0
0	0	S4	S4	0
0	1	S1	S1	0
0	1	S2	S2	0
0	1	S3	S3	0
0	1	S4	S4	0
1	0	S1	S2	0
1	0	S2	S2	0
1	0	S3	S2	0
1	0	S4	S1	1
1	1	S1	S1	0
1	1	S2	S3	0
1	1	S3	S4	0
1	1	S4	S1	0


PRESENT STATE				NEXTSTATE		
E	x	Q ₁ Q ₀ (t)		Q ₁ Q ₀ (t+1)		z
0	0	0	0	0	0	0
0	0	0	1	0	1	0
0	0	1	0	1	0	0
0	0	1	1	1	1	0
0	1	0	0	0	0	0
0	1	0	1	0	1	0
0	1	1	0	1	0	0
0	1	1	1	1	1	0
1	0	0	0	0	1	0
1	0	0	1	0	1	0
1	0	1	0	0	1	0
1	0	1	1	0	0	1
1	1	0	0	0	0	0
1	1	0	1	1	0	0
1	1	1	0	1	1	0
1	1	1	1	0	0	0

PROBLEM 6 (15 PTS)

- Draw the State Diagram (in ASM form) of the FSM whose VHDL description is shown below. Is it a Mealy or Moore FSM?
- Complete the Timing Diagram.

```
library ieee;
use ieee.std_logic_1164.all;

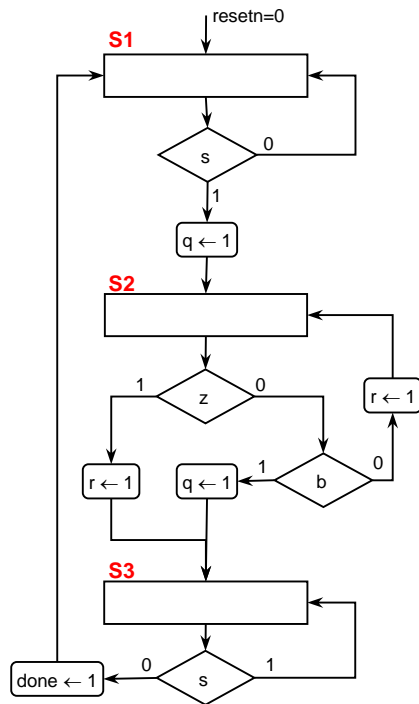entity circ is
  port ( clk, resetn: in std_logic;
        s, b, z: in std_logic;
        done, r, q: out std_logic);
end circ;
```




```
architecture behavioral of circ is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (resetn, clk, s, b, z)
  begin
    if resetn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if s = '1' then y <= S2; else y <= S1; end if;

        when S2 =>
          if z = '1' then
            y <= S3;
          else
            if b = '0' then y <= S2; else y <= S3; end if;
          end if;

        when S3 =>
          if s = '1' then y <= S3; else y <= S1; end if;
      end case;
    end if;
  end process;

  Outputs: process (y, z, b)
  begin
    done <= '0'; q <= '0'; r <= '0';
    case y is
      when S1 => if s = '1' then q <= '1'; end if;
      when S2 => if z = '0' then
        if b = '1' then
          q <= '1';
        else
          r <= '1';
        end if;
      else
        r <= '1';
      end if;
      when S3 => if s = '0' then done <= '1'; end if;
    end case;
  end process;
end behavioral;
```

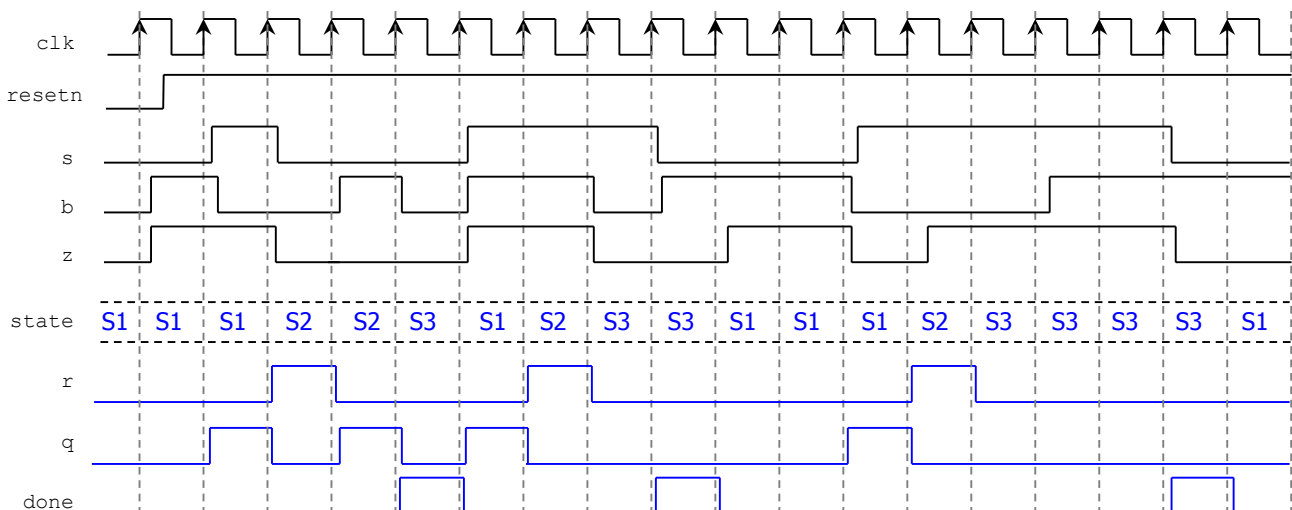

The outputs 'done', 'q', 'r' depend on the present state as well as on the inputs \Rightarrow Mealy FSM.