


# Solutions - Homework 3

(Due date: March 16<sup>th</sup> @ 5:30 pm)

Presentation and clarity are very important! Show your procedure!

## PROBLEM 1 (25 PTS)

 a) Complete the timing diagram of the circuit shown below. (5 pts)




b) Complete the timing diagram of the circuit whose VHDL description is shown below: (5 pts)

```
library ieee;
use ieee.std_logic_1164.all;


entity circ is
  port ( clrn, x, clk: in std_logic;
        q: out std_logic);
end circ;

architecture a of circ is
  signal qt: std_logic;

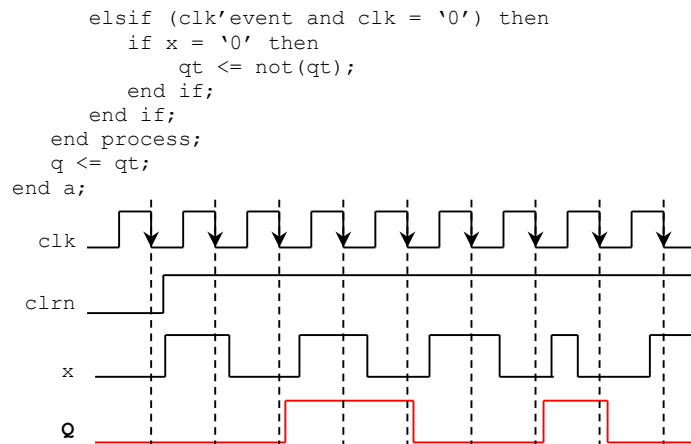begin
  process (clrn, clk, x)
  begin
    if clrn = '0' then
      qt <= '0';
    else
      if (clk'event and clk = '1') then
        qt <= not(qt);
      end if;
    end if;
    q <= qt;
  end process;
end a;
```




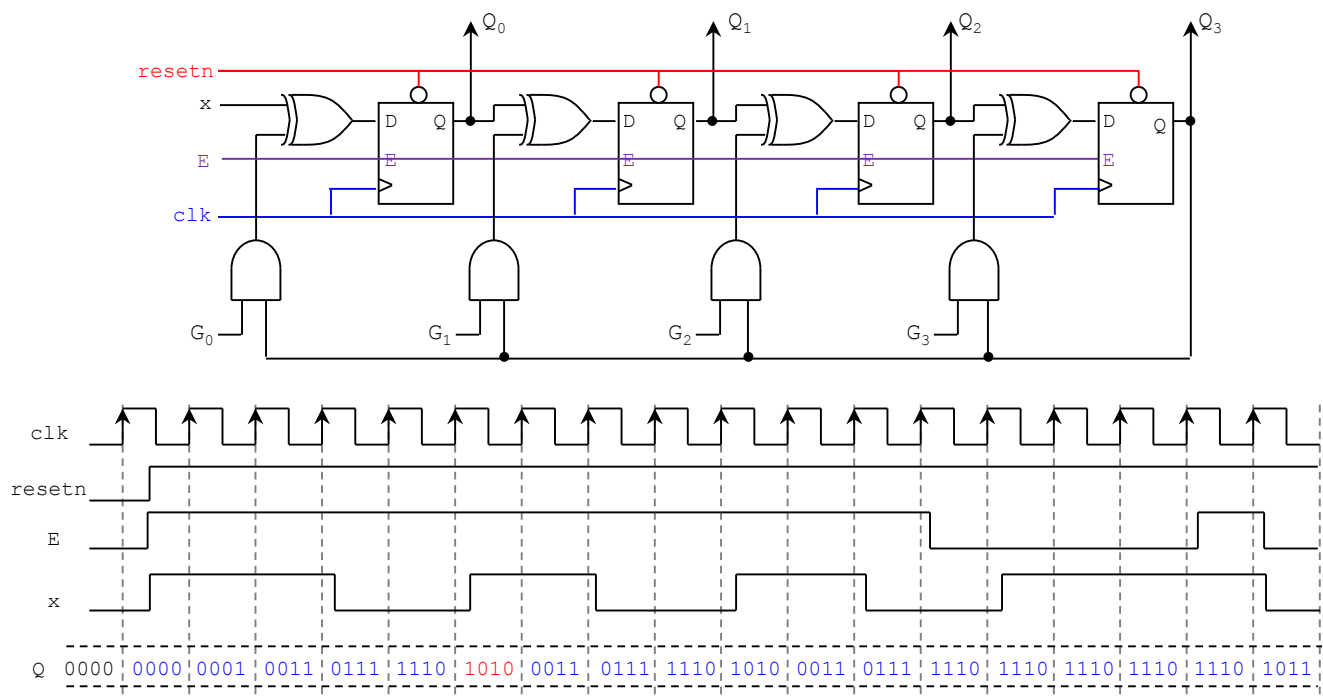c) Complete the timing diagram of the following circuit.  $G = G_3G_2G_1G_0 = 0110$ ,  $Q = Q_3Q_2Q_1Q_0$  (15 pts)



 
## PROBLEM 2 (28 PTS)

- Sequence detector: The machine generates  $z = 1$  when it detects the sequence 00110101. Once the sequence is detected, the circuit looks for a new sequence.
  - ✓ Draw the state diagram (any representation), State Table, and the Excitation Table of this circuit with input  $x$  and output  $z$ . Is this a Mealy or a Moore Machine? Why? (17 pts)
  - ✓ Provide the excitation equations (simplify your circuit using K-maps). (6 pts)
  - ✓ Sketch the circuit. (5 pts)



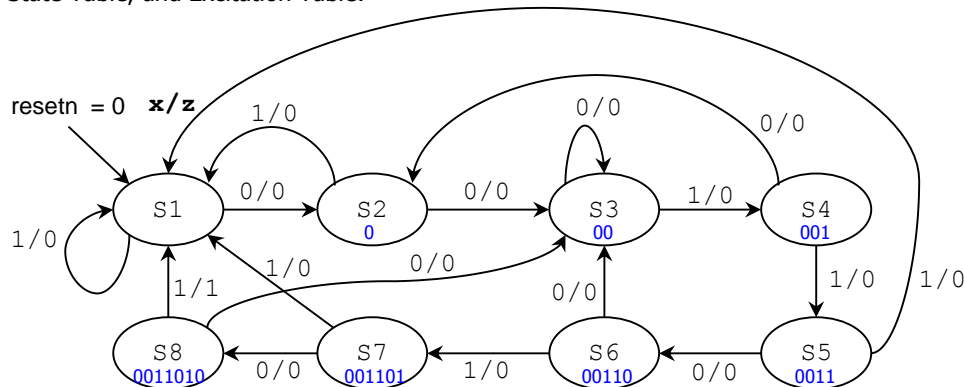- State Diagram, State Table, and Excitation Table:



PRESENT STATE				NEXT STATE			
x	STATE	NEXT STATE	z	x	Q <sub>2</sub> Q <sub>1</sub> Q <sub>0</sub> (t)	Q <sub>2</sub> Q <sub>1</sub> Q <sub>0</sub> (t+1)	z
0	S1	S2	0	0	0 0 0 0	0 0 1	0
0	S2	S3	0	0	0 0 0 1	0 1 0	0
0	S3	S3	0	0	0 0 1 0	0 1 0	0
0	S4	S2	0	0	0 0 1 1	0 0 1	0
0	S5	S6	0	0	0 1 0 0	1 0 1	0
0	S6	S3	0	0	0 1 0 1	0 1 0	0
0	S7	S8	0	0	0 1 1 0	1 1 1	0
0	S8	S3	0	0	0 1 1 1	0 1 0	0
1	S1	S1	0	1	1 0 0 0	0 0 0	0
1	S2	S1	0	1	1 0 0 1	0 0 0	0
1	S3	S4	0	1	1 0 1 0	0 1 1	0
1	S4	S5	0	1	1 0 1 1	1 0 0	0
1	S5	S1	0	1	1 1 0 0	0 0 0	0
1	S6	S7	0	1	1 1 0 1	1 1 0	0
1	S7	S1	0	1	1 1 1 0	0 0 0	0
1	S8	S1	1	1	1 1 1 1	0 0 0	1

State Assignment:

S1: Q = 000 S2: Q = 001 S3: Q = 010 S4: Q = 011

S5: Q = 100 S6: Q = 101 S7: Q = 110 S8: Q = 111

This is a Mealy Machine. The output 'z' depends on the input as well as the present state.

- Minimization, Excitation equations, and circuit implementation:

$$Q_2(t+1) = \bar{x}Q_2\bar{Q}_0 + xQ_2\bar{Q}_1Q_0 + x\bar{Q}_2Q_1Q_0 = \bar{x}Q_2\bar{Q}_0 + xQ_0(Q_2 \oplus Q_1)$$

$$Q_1(t+1) = \bar{Q}_2Q_1\bar{Q}_0 + \bar{x}Q_2Q_1 + \bar{x}\bar{Q}_1Q_0 + Q_2Q_1Q_0 = \bar{Q}_2Q_1\bar{Q}_0 + \bar{x}Q_2Q_1 + \bar{Q}_1Q_0(\bar{x} + Q_2)$$

$$Q_0(t+1) = \bar{x}\bar{Q}_1\bar{Q}_0 + \bar{x}Q_2\bar{Q}_0 + \bar{x}\bar{Q}_2Q_1Q_0 + x\bar{Q}_2Q_1\bar{Q}_0 = \bar{x}\bar{Q}_0(\bar{Q}_1 + Q_2) + \bar{Q}_2Q_1(x \oplus Q_0)$$

$$z = xQ_2Q_1Q_0$$

**$Q_2(t+1)$**

$xQ_2$	$Q_1Q_0$	00	01	11	10
00	00	0	1	0	0
01	01	0	0	1	0
11	11	0	0	0	1
10	10	0	1	0	0

**$Q_1(t+1)$**


$xQ_2$	$Q_1Q_0$	00	01	11	10
00	00	0	0	0	0
01	01	1	1	1	0
11	11	0	1	0	0
10	10	1	1	0	1

**$Q_0(t+1)$**

$xQ_2$	$Q_1Q_0$	00	01	11	10
00	00	1	1	0	0
01	01	0	0	0	0
11	11	1	0	0	0
10	10	0	1	0	1


**$z$**

$xQ_2$	$Q_1Q_0$	00	01	11	10
00	00	0	0	0	0
01	01	0	0	0	0
11	11	0	0	1	0
10	10	0	0	0	0

 

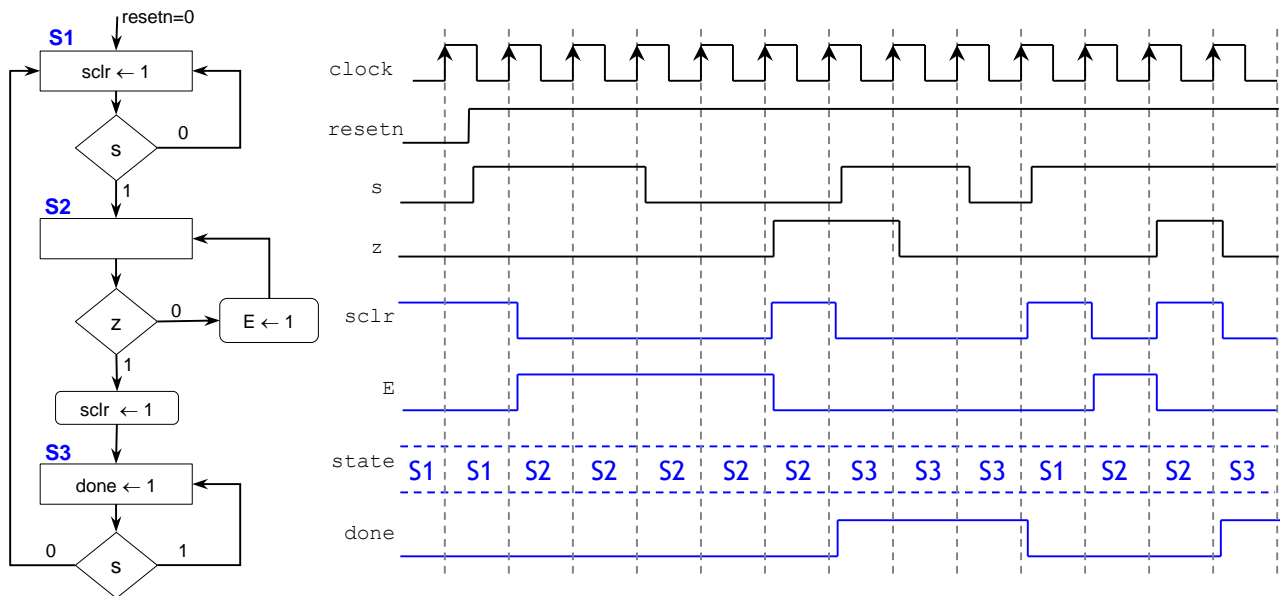
### PROBLEM 3 (37 PTS)


- Complete the timing diagram of the following FSM (represented as an ASM chart). (10 pts)



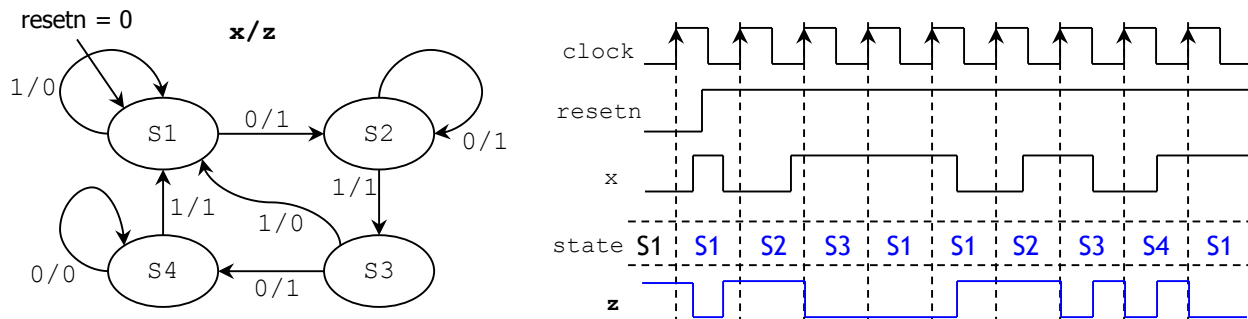- Complete the timing diagram of the following FSMs. Are these Mealy or Moore machines? Why? (10 pts)



 This is a Mealy Machine. The output 'z' depends on the input as well as the present state.




This is a Moore Machine. The output 'z' only depends on the present state.

- Provide the state diagram (in ASM form) and complete the timing diagram of the FSM whose VHDL description is listed below. (17 pts)

```
library ieee;
use ieee.std_logic_1164.all;

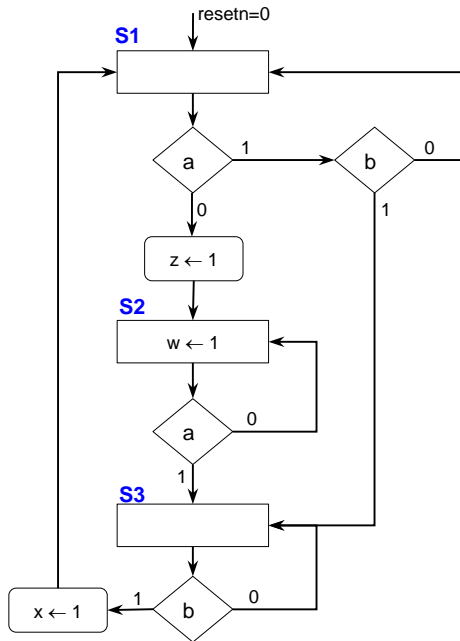entity myfsm is
  port ( clk, resetn: in std_logic;
        a, b: in std_logic;
        x,w,z: out std_logic);
end myfsm;
```



```
architecture behavioral of myfsm is
  type state is (S1, S2, S3);
  signal y: state;
begin
  Transitions: process (resetn, clk, a, b)
  begin
    if resetn = '0' then y <= S1;
    elsif (clk'event and clk = '1') then
      case y is
        when S1 =>
          if a = '1' then
            if b = '1' then y <= S3; else y <= S1; end if;
          else
            y <= S2;
          end if;
        when S2 =>
          if a = '0' then y <= S1; else y <= S3; end if;
        when S3 =>
          if b = '1' then y <= S1; else y <= S3; end if;
      end case;
    end if;
  end process;

  Outputs: process (y, a, b)
  begin
    x <= '0'; w <= '0'; z <= '0';
    case y is
      when S1 => if a = '0' then z <= '1'; end if;
      when S2 => w <= '1';
      when S3 => if b = '1' then x <= '1'; end if;
    end case;
  end process;
end behavioral;
```

